

USN

--	--	--	--	--	--	--	--	--	--

CS33

Third Semester B.E. Degree Examination, June 2012

Logic Design

Time: 3 hrs.

Max. Marks:100

Note: Answer any FIVE full questions

1. a. Define Boolean algebra. State and prove absorption law. (06 Marks)
 b. Describe the Shannon's reduction theorem. Simplify the following expression using Shannon's reduction theorem

$$f(w, x, y, z) = x + \overline{w} \overline{x} (y + wx) + \overline{x} y + \overline{w} z$$
 (06 Marks)
 c. Perform the following operations on the Boolean expression

$$x \overline{y} + wx (\overline{y} + \overline{w} \overline{x}) + wxz$$
 - i) Expand into the form

$$(x + g_1(w, y, z))(\overline{x} + g_2(x, y, z))$$
 - ii) Convert into the minterm canonical form. (08 Marks)
2. a. Simplify the following Boolean functions, using algebraic manipulation
 - i) $f(x, y, z) = \overline{x} \overline{y} \overline{z} + \overline{x} y + xyz$
 - ii) $f(w, x, y, z) = \overline{w} \overline{y} \overline{z} + wz + \overline{y} z + xyz$ (08 Marks)
 b. Realize the following function, using (no simplification)
 - i) NAND gates only
 - ii) NOR gates only
$$f(x, y, z) = x \overline{z} + x \overline{y} z + \overline{x} + y$$
 (08 Marks)
 c. Show the steps in the graphical procedure for the realization of Boolean function, using NAND gates only. (04 Marks)
3. a. Define the prime implicate and the irredundant conjunctive normal form. (04 Marks)
 b. Using K-map obtain the minimal sum of products for the following Boolean function show the essential prime implicants on the map

$$f(w, x, y, z) = \sum m(0, 2, 6, 7, 8, 10, 12) + dc(3, 15)$$
 (08 Marks)
 c. Draw the K-map and simplify the following expression using z as the map-entered variable and x and y as map variables.

$$f(x, y, z) = \overline{x} \overline{y} + \overline{x} y \overline{z} + x \overline{y} z$$
 (08 Marks)
4. a. Use Quine – McCluskey method to obtain the prime implicants for the following function. Identify the essential prime implicants, if any. Also obtain the minimal sum of products.

$$f(w, x, y, z) = \sum m(1, 3, 4, 6, 7, 9, 11, 13, 15)$$
 (10 Marks)
 b. Briefly discuss the row and column reduction technique used for the simplification of Boolean functions. (04 Marks)
 c. Using decimal method obtain the minimal product of sums for the following function

$$f(x, y, z) = \pi m(0, 1, 4, 6)$$
 (06 Marks)
5. a. Discuss the following performance parameters of logic gates.
 - i) Noise margin
 - ii) Propagation delay
 - iii) Power dissipation. (06 Marks)
 b. With the help of the circuit diagram, explain the working of a two input TTL NAND gate. (10 Marks)
 c. Write short note on Schottky TTL. (04 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg. 42+8 = 50, will be treated as malpractice.

- 6 a. Realize the following function, using 4 to 1 MUX and external gates if w and x are applied to the select lines.
 $f(w, x, y, z) = \Sigma m(0, 1, 3, 5, 7, 8, 10, 14) + dc(4, 6, 12).$ (10 Marks)
- b. Illustrate how PLA can be used to realize the following functions, using $3 \times 4 \times 2$ PLA
 $f_1(x, y, z) = \Sigma m(0, 1, 6, 7)$
 $f_2(x, y, z) = \Sigma m(0, 3, 4, 6, 7).$ (10 Marks)
- 7 a. Show the circuit diagram, for a J-K flip-flop using NAND gates and explain its working. Also derive the expression for the Q output. (10 Marks)
- b. Design a mod – 6 synchronous counter, using SR flip-flops. (10 Marks)
- 8 a. Differentiate between Moore model and mealy model of clocked synchronous sequential network. (08 Marks)
- b. For the clocked synchronous sequential circuit whose excitation equations for T-flip-flop are $T_1 = \bar{x} Q_2$ and $T_2 = \bar{x} Q_2 \bar{Q}_1 + x \bar{Q}_1 \bar{Q}_2$
 And output equation
 $Z = Q_1 Q_2$
 Prepare the excitation table, transition table, state table and state diagram where x is 1 the external input to the circuit. (12 Marks)

* * * * *