

(1)

Measurement of Resistance

- * Depending on the value of the resistance are classified as i) low resistance ii) medium resistance iii) High resistance
- * Any resistance of the order 1- Ω & less is considered as low resistance.
- * The resistance whose value lie in b/w 1- Ω to 1,00,000- Ω is considered as medium resistance
- * The resistance whose value is more than 1,00,000- Ω is considered as high resistance

The resistance of armature windings of electrical machines, the resistance of series field winding of a DC machine, resistance of shunts and lead wires are examples of low resistance.

- * The insulation resistance of cables and wires are examples of high resistance.

* Measurement of Medium Resistance

The different methods used for the measurement of medium resistance are →

- 1) Ammeter - voltmeter method
- 2) Substitution method
- 3) Wheatstone bridge method
- 4) Ohmmeter method.

* Wheatstone bridge method

* Above fig shows Wheatstone bridge circuit, which is used for the measurement of medium resistance.

* As shown above it consists of four resistive arms together with a source of emf E & galvanometer.

* Galvanometer is used as null detector, the current through the galvanometer depends on the potential difference between the points b & d.

* However the bridge is said to be balanced, when the current through the galvanometer is zero or when the potential difference between the points b and d is zero. When the bridge is balanced, there is no current flowing through the galvanometer.

$$\text{At balance } V_{ab} = V_{ad} \quad I_1 P = I_2 R \quad \text{or} \quad \frac{I_1}{I_2} = \frac{R}{P} \quad \text{--- (1)}$$

$$\text{also, } V_{bc} = V_{cd} \quad I_3 Q = I_4 S \quad \text{but } I_1 = I_3 \quad \text{and } I_2 = I_4.$$

$$\therefore I_1 Q = I_2 S.$$

$$\Rightarrow \frac{I_1}{I_2} = \frac{S}{Q} \quad \text{--- (2)}$$

equating the equations (1) & (2) $\frac{R}{P} = \frac{S}{Q}$.

$$\Rightarrow R = P \frac{S}{Q}$$

Where P & Q are the resistances of ratio arm
S = resistance of standard arm. R = unknown resistance

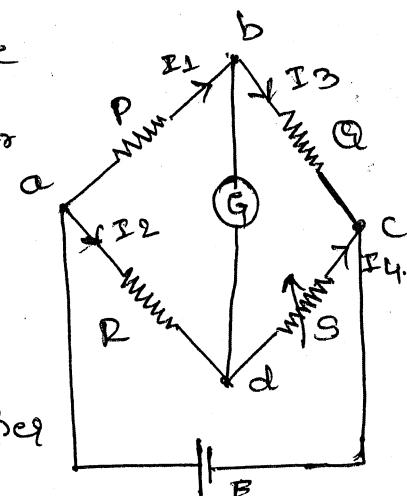


fig-a) WheatStone bridge

* Sensitivity of Wheatstone Bridge (SB) (2)

The sensitivity of the Wheatstone bridge is defined by the deflection of the galvanometer per unit fractional change in the value of ^{unknown} resistance.

$$\text{ie } S_B = \frac{\Theta}{(\Delta R/R)} \quad \text{--- (1)}$$

Where Θ = deflection of the galvanometer


ΔR = change in the value of R .

The sensitivity to the unbalance may be computed by solving the bridge circuit for a small unbalance.

$$\text{When the bridge is balanced} = P/Q = R/S \text{ or } \frac{P}{P+Q} = \frac{R}{R+S} \quad \text{--- (2)}$$

Let R be changed to $(R+\Delta R)$, so that there is an unbalance, which will cause an emf e to appear across the galvanometer.

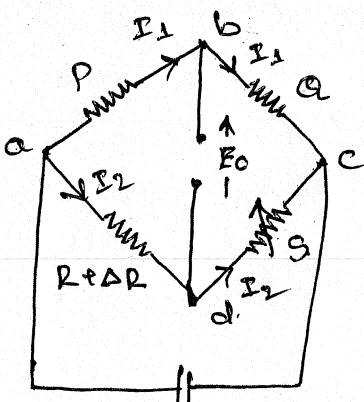Let the galvanometer is removed and the voltage across the galvanometer is represented by the Thevenin's voltage E_0 . as shown below.



B fig.

from the fig

$$V_{ab} = I_1 P = E \cdot \frac{P}{P+Q}$$

$$V_{ad} = I_2 (R + \Delta R) = E \cdot \frac{(R + \Delta R)}{(S + R + \Delta R)}$$

$$\text{Now } V_{db} = E_0 = V_{ad} - V_{ab}$$

$$\therefore V_{db} = E_0 = E \left[\frac{R + \Delta R}{(R + \Delta R + S)} - \frac{P}{P+Q} \right] \quad \text{We know } \frac{P}{P+Q} = \frac{R}{R+S}$$

$$\therefore V_{db} = E_0 = E \left[\frac{R + \Delta R}{R + \Delta R + S} - \frac{R}{R+S} \right]$$

$$= E \left[\frac{(R + \Delta R)(R + S) - R(R + \Delta R + S)}{(R + \Delta R + S)(R + S)} \right]$$

$$= E \left[\frac{R^2 + RS + R\Delta R + S\Delta R - R^2 - R\Delta R - RS}{(R + \Delta R + S)(R + S)} \right]$$

$$= \frac{ES\Delta R}{(R + \Delta R + S)(R + S)} \quad \begin{array}{l} \text{as } \Delta R \text{ is very small} \\ \text{compared to } R + S \end{array}$$

$$\therefore (R + \Delta R + S) \cong (R + S)$$

$$\therefore V_{db} = E_0 = \frac{ES\Delta R}{(R + S)(R + S)}$$

$$E_0 = \frac{ES\Delta R}{(R + S)^2}$$

if $S_V = \frac{\Theta}{E_0}$ is the voltage sensitivity of the galvanometer then

$$\Theta \cdot S_V E_0 = \frac{S_V E S \Delta R}{(R + S)^2} \quad \text{--- 3}$$

But we have bridge sensitivity.

$$S_B = \frac{\Theta}{(\Delta R / R)}$$

$$\therefore S_B = \cancel{S_V} \frac{S_V E S \Delta R}{(R + S)^2 (\Delta R / R)}$$

$$S_B = \frac{S_v ESR}{(R+S)^2} = \frac{S_v ESR}{R^2 + S^2 + 2RS}$$

divide N & D by RS

$$\therefore S_B = \frac{S_v E}{\left(\frac{R}{S} + S/R + 2\right)} = \frac{S_v E}{\left(P/Q + Q/P + 2\right)} \quad \text{--- (4)}$$

from the above equation it is clear that, the bridge sensitivity S_B is maximum when $P/S = 1$

* Galvanometer current

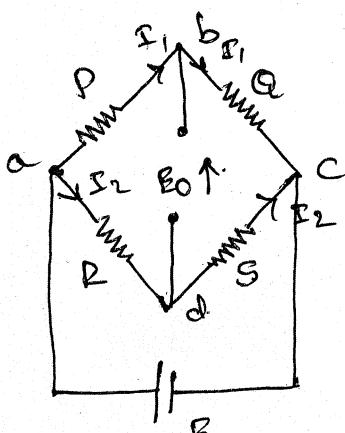


fig-a)

The current through the galva-

nometer is found by finding the thevenin's equivalent circuit of the bridge. as shown below.

The open circuit voltage


is obtained in the points b & d by

$$E_0 = V_{ad} - V_{ab} = E_0 = R_2 R - I_1 R$$


$$\therefore E_0 = \frac{E R}{(R+S)} - \frac{E P}{(P+Q)} = E \left[\frac{R}{R+S} - \frac{P}{P+Q} \right]$$

Now thevenin's equivalent resistance is found by short circuiting the voltage source E & finding the equivalent resistance b in the points b & d which is given by.
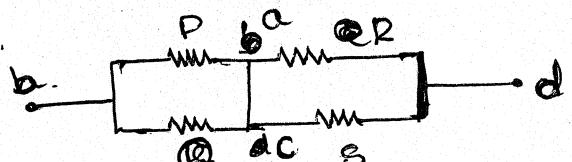
$$R_0 = \frac{PQ}{P+Q} + \frac{RS}{R+S} \quad \text{if } P=Q=R=S, \text{ then } R_0 = R$$



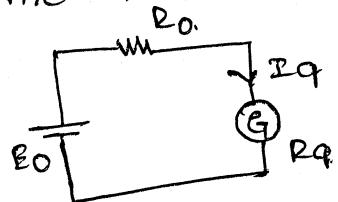The thevenin's equivalent circuit is as shown below
the current through the galvanometer is given by



$$I_g = \frac{E_0}{(R_0 + R_g)}$$

fig - b

We know that, the deflection of the galvanometer for a small change R' is ΔR .

$$\Theta = \frac{S_v E S \Delta R}{(R + S)^2}$$

$$\text{But } S_v = S_i / (R_0 + R_g)$$

$$\therefore \Theta = \frac{S_i E S \Delta R}{(R_0 + R_g)(R + S)^2} \quad \text{But } S_B = \Theta / \Delta R / R$$

$$\therefore S_B = \frac{S_i E S \Delta R}{(R_0 + R_g)(R + S)^2 \times \cancel{\Delta R}}$$

$$= \frac{S_i E S R}{(R_0 + R_g)(R + S)^2} //$$

$$S_{BX} \neq S_{B4} \quad \text{If } P = Q = R = S$$

Then $S_B = \frac{S_i E S R}{(R_0 + R_g)(R^2 + S^2 + 2RS)}$

~~$= S_i E S R$~~

* Limitations of Wheatstone Bridge.

(4)

Wheatstone bridge is used for the measurement of medium resistance, the errors are introduced when it is used for the measurement of low or high resistance. The limitations of Wheatstone bridge are as follows.

1) Resistance of lead :-

When the low resistances are measured, the resistance of the lead wire must be deducted to get the correct value of the resistance which is to be measured.

for example → A lead of 22 SWG wire having a length of 25cm has a resistance of about 0.012Ω & it will introduce error when small resistances are measured.

2) Contact Resistance → errors are introduced due to a contact resistance of switches


3) Thermo-electric effect :- Thermo electric emfs are often present in the measuring circuit & they affect the galvanometer deflection. However these effects may be eliminated by reversing the battery connections to the bridge.

4) Temperature effects :- The errors are caused due to the change of charge, & change of resistance is due to temperature, specially in the case of resistances.

having large value of temperature co-efficiency

- 5) When high resistances are measured using the Wheatstone bridge the sensitivity of the bridge is decreased & errors are introduced.

* Measurement of Low Resistance *

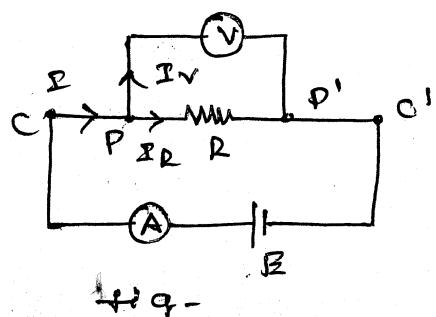


The construction for the measurement of low resistance is as shown above

- * It has four terminals, the pair of terminals cc' are called as current terminals they are used to lead the current to and from the resistor.
- * The pair of terminals pp' are used to measure the voltage drop across the resistance.
- * The voltage drop measured across the resistance does not include any contact resistance drop which may be present at the current terminals cc' .
- * The contact resistance is a part of potential circuit whose resistance is usually very high and the contact resistance of the potential terminals is negligible as compared to that of the potential circuit.

* Method of Measurement of low resistance

- 1) Ammeter - voltmeter method
- 2) Kelvin's double bridge method
- 3) potentiometer method
- 4) duster ohmmeter method.

* Kelvin's double bridge

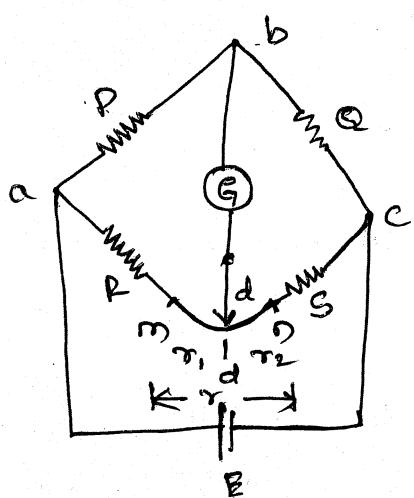

KDB is the modification of the Wheatstone bridge & it accurately measures low resistance.

fig - Kelvin's double bridge

Let us consider KDB as shown above where r represents the resistance of lead that connects unknown resistance R & standard resistance S b/w the terminals m & n . There is a sliding contact which can be moved from m to n .

The sliding contact is varied & the bridge is balanced when it is at point d . Then

$$R + r_1 = P / Q (S + r_2)$$

the value of r is such that $r_1/r_2 = P/Q$.

$$\frac{\tau_1}{\tau_1 + \tau_2} = P/P+Q$$

$$\tau_1 = \frac{P}{P+Q} \cdot (\tau_1 + \tau_2) = P \cdot \tau$$

Similarly $\tau_2 = Q/P+Q \cdot \tau$


$$\therefore \left[R + P \cdot \tau \right] = P/Q \left[S + \frac{Q \cdot \tau}{P+Q} \right]$$

$$\text{i.e. } \frac{P}{Q} = R/S.$$

\therefore the bridge is balanced at point d, & τ will not affect the result.

* But however it is difficult to set the pointer exactly at point d, in order to keep bridge in a balanced condition.

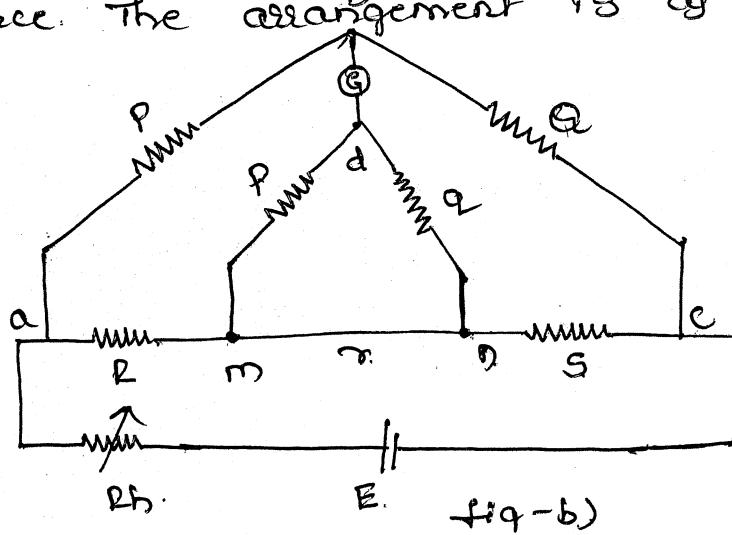
* However Kelvin's double bridge is modified in order to eliminate the effect of resistance of the leads during the measurement of unknown resistance. The arrangement is as shown below.



The KDB has two ratio arms i) P and Q

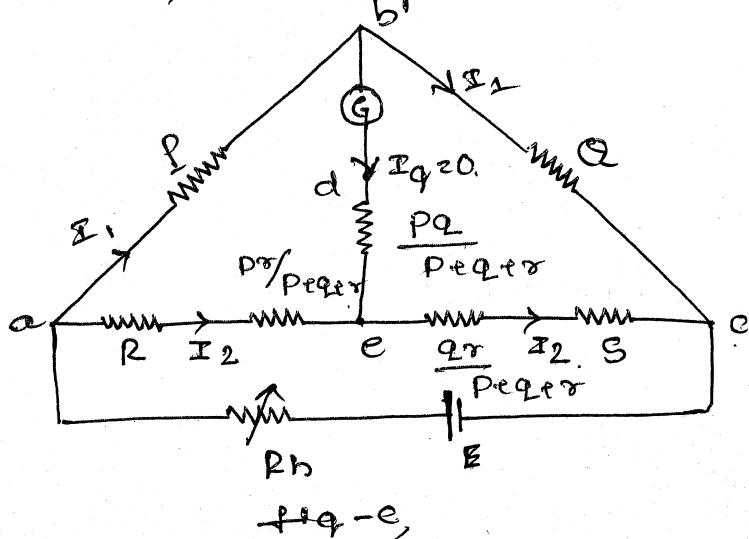ii) p and q such that $P/Q = P/q$, Hence it is called as Kelvin's double bridge.

* converting the resistances P, q and r connected in Δ into Y, the bridge is redrawn as shown below.



at balanced condition, there is no flow of current through the galvanometer.

$$\therefore v_{ab} = v_{ae}$$

$$\text{ie } PI_1 = \left(R + \frac{Pr}{P+Q+r} \right) I_2 \quad \text{--- (1)}$$

$$\& v_{cb} = v_{ce}$$

$$QI_1 = \left[S + \frac{qr}{P+Q+r} \right] I_2 \quad \text{--- (2)}$$

divide equation (1) by (2)

$$\frac{P}{Q} = \frac{\left[R + \frac{Pr}{P+Q+r} \right]}{\left[S + \frac{qr}{P+Q+r} \right]} = \frac{R(P+Q+r) + Pr}{S(P+Q+r) + qr}$$

$$\frac{P}{Q} = \frac{R(P+qr) + Pr}{S(P+qr) + qr}$$

$$\frac{P}{Q} \cdot S(P+qr) + qr = R(P+qr) + Pr$$

~~P/Q~~, $\frac{P}{Q} \left(S + \frac{qr}{P+qr} \right) = R + \frac{Pr}{P+qr}$

$$\therefore R = \frac{P}{Q} \cdot S + \frac{P}{Q} \cdot \frac{qr}{P+qr} - \frac{Pr}{P+qr}$$

$$= \frac{P}{Q} \cdot S + \frac{qr}{P+qr} \left[\frac{P}{Q} - \frac{Pr}{P+qr} \right]$$

If $P/Q = P/q$, then the above equation becomes

$R = \frac{P}{Q} \cdot S$

\therefore the above equation shows that, the resistance of the connecting leads has no effect on the measurement of R , with $P/Q = P/q$ if there is small difference b/w P/q & P/Q then error is introduced.

The resistance measured with the help of EDB is usually b/w 0.1 to 1.0 Ω.

* In a Wheatstone bridge, the resistances of various arms are, $P = 1000\Omega$, $Q = 100\Omega$, $R = 2005\Omega$ and $S = 200\Omega$. The battery has an emf of 5V. and negligible internal resistance. The galvanometer has a d.c. sensitivity of $10\text{mm}/\text{mA}$ and an internal resistance of 100Ω . Calculate the deflection of the galvanometer and the sensitivity of the bridge in terms of deflection per unit change of resistance.

$$\Rightarrow \text{Given } P = 1000\Omega, Q = 100\Omega, R = 2005\Omega, S = 200\Omega \\ \text{emf} = 5V, \text{ d.c. sensitivity of galvanometer} = 10\text{mm}/\text{mA} \\ R_Q = 100\Omega, \underline{\underline{Q = ?}}$$

We know that at balanced condition

$$R = \frac{P}{Q} \cdot S = \frac{1000}{100} \times 200 = 2000\Omega$$

In actual bridge the unknown resistance is 2005Ω . \therefore Actual resistance $= 2005 - 2000 = 5\Omega$

$$E_0 = E \left[\frac{R}{R+S} - \frac{P}{P+Q} \right] = 5 \left[\frac{\frac{2005}{2005+200}}{\frac{2005+200}{1000+100}} - \frac{\frac{1000}{1000+100}}{\frac{1000+100}{1000+100}} \right] = 1.0308 \times 10^{-3}$$

$$R_0 = \frac{RS}{R+S} + \frac{PQ}{P+Q} = \frac{2005 \times 200}{2005+200} + \frac{1000 \times 100}{1000+100} = 272.77\Omega$$

$$I_g = \frac{E_0}{R_0 + R_Q} = \frac{1.0308 \times 10^{-3}}{272.77 + 100} = 2.7744A$$

$$\theta = S : I_g = 10 \times 2.77 = 27.7 \text{ mm}$$

$$S_B = \frac{27.7}{\frac{\text{Actual Resistance}}{5}} = \frac{27.7}{5} = 5.54 \text{ mm}/\Omega$$

* A Wheatstone bridge has ratio arms of 1000Ω and 100Ω and is used to measure a resistance of 50Ω . Two galvanometers are available to be used as detectors. Galvanometer A has a resistance of 100Ω and a sensitivity of 400 mm/ma . Galvanometer B has a resistance of 1000Ω & a sensitivity of 800 mm/ma . Find out which of the two galvanometers is more sensitive to a small imbalance in the above bridge.

\Rightarrow

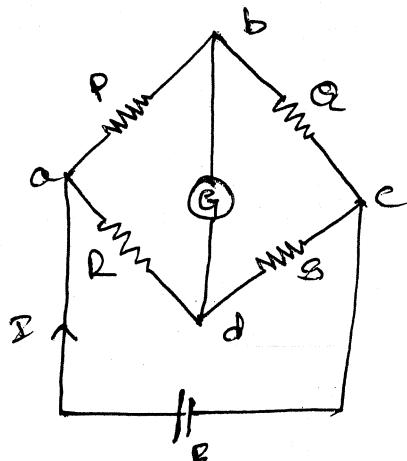


Fig - Wheatstone
bridge

$$\text{Given } P = 1000 \quad Q = 100$$

$$R = 50\Omega$$

$$Rg_A = 100 \quad \textcircled{S} \quad (Si)_A = 400 \text{ mm/ma}$$

less

$$Rg_B = 1000 \quad (Si)_B = 800 \text{ mm/ma}$$

more

$$\therefore R = \frac{P \cdot S}{Q}$$

$$\Rightarrow S = \frac{Q \cdot R}{P} = \frac{100}{1000} \times 50$$

$$= \underline{\underline{5\Omega}}$$

$$\begin{aligned} \text{Now } R_0 &= \frac{Rg}{R+S} + \frac{PQ}{P+Q} \\ &= \frac{50 \times 5}{50+5} + \frac{1000 \times 100}{1000+100} \\ &= \underline{\underline{95.46\Omega}} \end{aligned}$$

We have the deflection in the galvanometer for a small change in resistance is given

$$\text{by } \Theta = \frac{S_i E S D R}{(R_0 + R_g)(R + S)^2}$$

$$\begin{aligned} \therefore \frac{\Theta_A}{\Theta_B} &= \frac{(S_i)_A E S D R}{(R_0 + R_{gA})(R + S)^2} / \frac{(S_i)_B E S D R}{(R_0 + R_{gB})(R + S)^2} \\ &= \frac{(S_i)_A (R_0 + R_{gB})}{(S_i)_B (R_0 + R_{gA})} \\ &= \frac{400}{800} \times \frac{95.46 + 1000}{(95.46 + 100)} = 2.8 \end{aligned}$$

$$\boxed{\frac{\Theta_A}{\Theta_B} = 2.8}$$

from the equation it is clear
that galvanometer A is 2.8
times more sensitive than galvanometer B.

* Thevenin's equivalent voltage of a Wheatstone bridge is 25mV & the galvanometer current is 20mA.
The resistance of the galvanometer is 50Ω , the ratio arms have resistances of 1000Ω & 5000Ω respectively. Find the value of standard resistance for which the above conditions are satisfied.
The value of the resistance to be measured is 600Ω .

$$\Rightarrow \text{We have } I_g = \frac{E_0}{(R_0 + R_g)} \Rightarrow 20 \times 10^{-6} = \frac{25 \times 10^{-3}}{R_0 + 50}$$

$$\therefore R_0 = 1950\Omega$$

$$R_0 = \frac{R_g}{R+S} + \frac{R_g}{P+Q} \Rightarrow 1950 = \frac{600 \times S}{600 + S} + \frac{1000}{(1000 + 5000)} \\ S = 1363.67\Omega$$

* Earth resistance measurement

All the electrical equipments are earthed through the electrode to avoid the shock to the person who touches the body of the equipment. Earthing provides bypass of leakage current. The various factors which affect the earth resistance are ⇒

- i) shape and material of the earth electrodes.
- ii) depth of the electrode at which they are buried in soil
- iii) Specific resistance of the soil surrounding the electrode.

The specific resistance of the soil varies from one type of soil to another

* The amount of moisture present in the soil affects the specific resistance.

* Depending on the moisture content, the specific resistance of the soil varies from $80 \times 10^3 \Omega \cdot m$ to $80 \times 10^6 \Omega \cdot m$.

* Method of measuring earth resistance

There are two methods of measurement

of earth resistance

- i) Fall of potential method
- ii) By using an earth tester.

* Fall of potential method


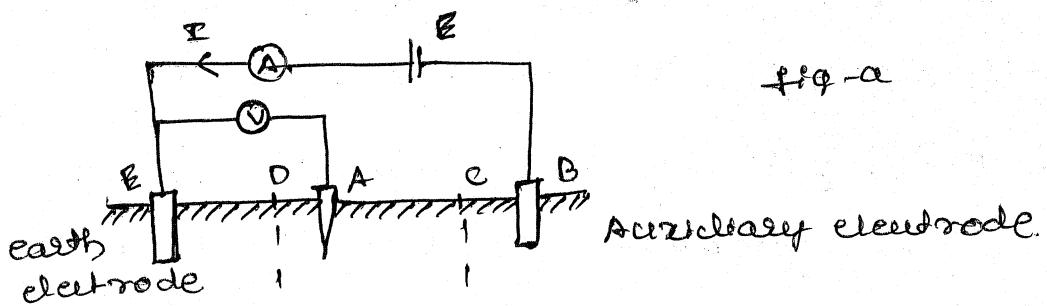


fig-a

Auxiliary electrode.

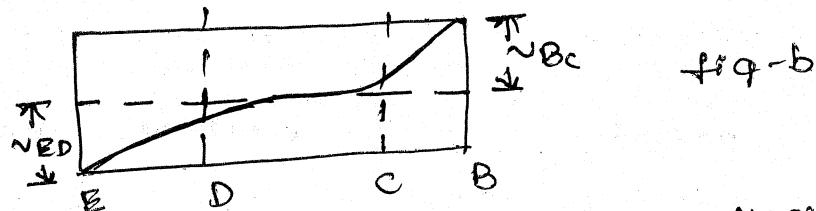

diagram

Above fig shows the circuit for the measurement of earth resistance using fall of potential method.

* A current I is passed through earth electrode E to an auxiliary electrode B , which is usually an iron spike, inserted in the earth at a certain distance away from the earth electrode.

* A second auxiliary electrode A is inserted in the earth b/w E and B .
 * The potential difference b/w E and A is V , which is measured using a voltmeter.

The way in which the ground is filled b/w the electrodes E and B are as shown below:

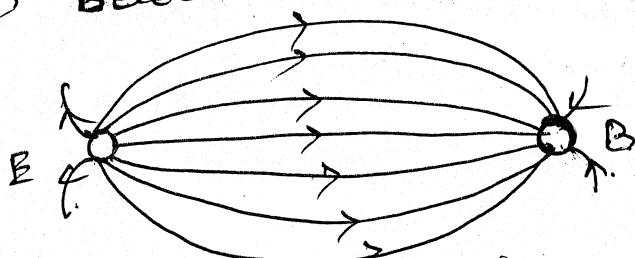


fig-c.


As shown above air at E diverge and converge at B. The potential distribution b/w the electrodes E and B are as shown above.

* from the fig it is clear that the potential rises in the proximity of electrode E & B & it is constant along the middle section.

The resistance of the earth is given by $R_E = \frac{V_E}{I}$

* However the position of the electrode E & B are fixed & position of the electrode A is changed & R_E is calculated for the various positions of electrode A.

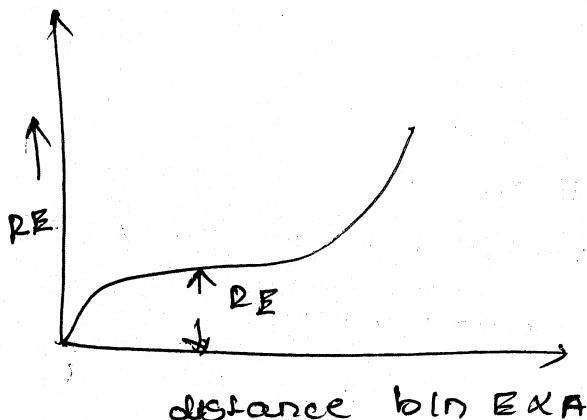* A graph is plotted b/w R_E and distance b/w the electrodes E & A.



from the graph
it is clear that
the R_E depends on the

position of the auxiliary electrode A

* R_E rises rapidly remains constant & rises again. as electrode moved from E to B

* Megger

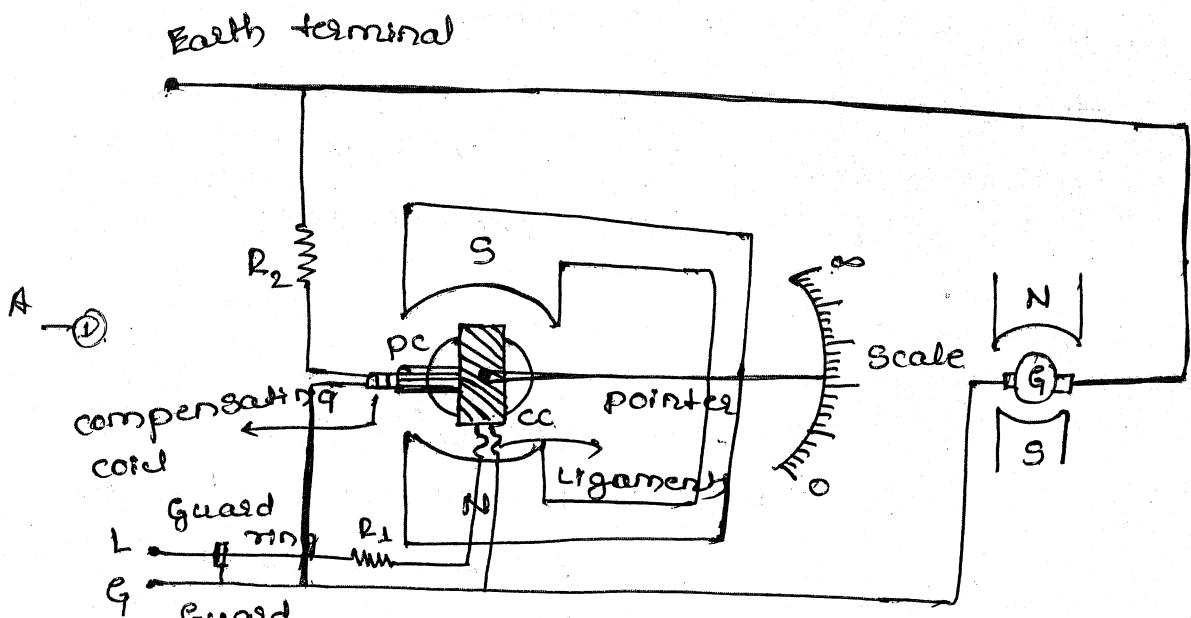


fig - Megger

Megger is an instrument which is used for the measurement of very high resistance of the order of mega ohms such as insulation resistance.

- * Construction :- The construction of a ~~hand driven~~ ~~dc~~ ~~generator~~ Megger is as shown below in the above fig.
 - 1) It consisting of hand driven dc generator and a direct reading ohm meter, there is a potential coil PC and current coil CC, which are fixed to the spindle and which are free to rotate about a vertical axis between the poles N & S of a permanent magnet.
 - 2) The coils are connected through flexible leads known as ligaments. The current coil is connected in series with a resistance R_1 .
 - 3) The potential coil is connected in series with an

compensating coil and resistance R_2 and across the generator terminals.

* The terminal G is known as Guard terminal, which is used to connect the guard ring to the insulation under test, the test voltage generated by an generator is usually 500V to 1000V.

* Working principle

The high resistance which is to be measured is connected b/w the test terminals L and G. The generator handle is rotated slowly at a uniform speed till the pointer give steady reading, this reading give the value of the resistance.

* The test terminals satisfactory working of Megger is tested as follows, The test terminals L & G are kept open, Now the resistance across L & G is infinite the generator is slowly rotated due to which c/w flows through the potential coil and there is no c/w through the current coil. \therefore the pointer rotates in such a direction that pointer deflected & comes to rest at point marked as on the scale.

* Next the test terminals are short circuited & generator handle is rotated, Now very large c/w flows through the CC & small c/w flows through the PC. The resultant torque produced deflects the pointer in opposite direction showing 0 reading on scale.

* after checking above two extreme condition on scale, high resistance which is to be measured

is connected b/w the test terminals. the generator handle is rotated, now reasonable amount of induced current is both p.c & c.c & torque deflects the pointer the pointer on calibrated scale which gives the value of resistance to be measured.

* Sources and detectors


usually for ac circuit, a low voltage high frequency supply is required. Electronic oscillators are universally used as sources for ac bridge as their frequency is constant.

- * A typical ^{electronic} oscillator has a frequency range of 40Hz to 125kHz with power output of 4W.
- * The detectors commonly used for ac bridge are i) vibration galvanometer
ii) Head phone
iii) Tunable amplifier circuits.

- The vibration galvanometers are used for power & low audio frequency range
→ They can be used for frequency range of 5Hz to 100Hz.
- * Head phones are used for frequency range 250Hz to 4kHz as they are very sensitive to these frequency ranges.
- * The tunable amplifier detectors used for the frequency range of 10Hz to 100kHz. CRO can also be used as detector.

- * Ac bridge — Ac bridge are used for the measurment of L & C and some related quantity such as loss factor, Q factor etc.
- * The arms of ac bridge are impedance consisting of individual elements of R, L & C or their combinations.

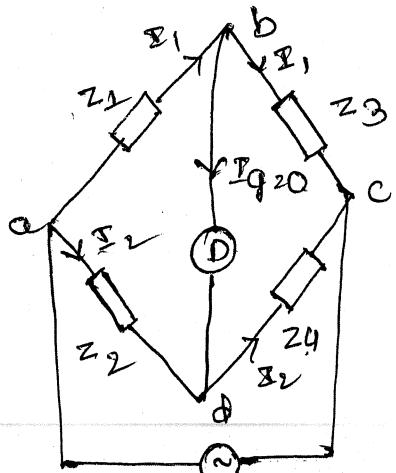* General equilibrium equations for ac bridge



A general ac bridge also is as shown above

When the bridge is balanced there is no current through galvanometer i.e $I_q = 0$

$$\therefore v_{ab} = v_{ad}$$

$$I_1 z_1 = I_2 z_2 \quad \text{--- (1)}$$

$$\& v_{bc} = v_{dc}$$

$$I_1 z_3 = I_2 z_4 \quad \text{--- (2)}$$

from equation (1) \times (2) we get

$$z_1/z_3 = z_2/z_4$$

or $z_1 z_4 = z_2 z_3$ or $y_1 y_4 = y_2 y_3$ this is the balancing equation of ac bridge.

The product of the impedance of one pair of opposite arms must be equal to the product of the impedance of the other pair of opposite

across:

$$\text{i.e } |z_1| \angle \theta_1 \times |z_4| \angle \theta_4 = |z_2| \angle \theta_2 \times |z_3| \angle \theta_3$$

$$\text{i.e } |z_1||z_4| (\theta_1 + \theta_4) = |z_2||z_3| (\theta_2 + \theta_3)$$

Hence the two balancing equations of a bridge are $|z_1||z_4| = |z_2||z_3|$ & $\theta_1 + \theta_4 = \theta_2 + \theta_3$
even the above equation can also be written as

$$(R_1 + jx_1)(R_4 + jx_4) = (R_2 + jx_2)(R_3 + jx_3)$$

$$\text{or } R_1R_4 + j(R_1R_4 + R_1x_4) - x_1x_4 = R_2R_3 + j(R_2x_3 + x_2R_3)$$

$$R_1R_4 - x_1x_4 = R_2R_3 - jR_2x_3 - x_2R_3$$


$$\& (R_1R_4 + R_1x_4) = x_2R_3 + x_3R_2.$$

* Measurement of Self inductance.

There are various bridges can be used to measure the self inductance of a coil they are

- 1) Maxwell's inductance bridge
- 2) Maxwell's inductance - capacitance bridge
- 3) Hay's bridge
- 4) Anderson bridge.

* Anderson Bridge.

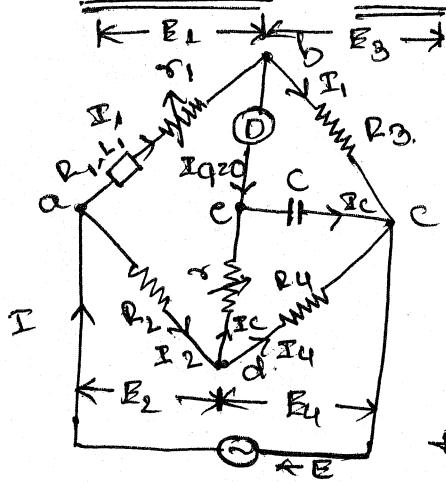

The above fig shows Anderson's bridge, in which the self inductance is measured in terms of a standard capacitor.

fig - Anderson bridge

& self inductance can be measured over a wide range of values.

as shown above

L_1 = Self - inductance of the inductor to be measured.

R_s = resistance of self inductor

r_1 = resistance connected in series with self inductor.

R_2, R_3, R_4 = known non-inductive resistances
C = fixed standard capacitor.

* vector diagram \Rightarrow The vector diagram for Anderson's bridge is as shown below.

at balance

$$V_{BC} = V_{EC} \Rightarrow I_1 R_3 = I_C (\gamma - jx_C)$$

$$I_1 R_3 = \frac{I_C}{j\omega C} \quad \therefore I_C = j\omega C R_3 I_1 \quad \textcircled{1}$$

$V_{AB} = V_{ADE}$

$$I_1 (R_1 + \gamma_1 + j\omega L_1) = I_2 R_2 + I_C \gamma$$

$$I_1 R_1 + I_1 \gamma_1 + I_1 j\omega L_1 = I_2 R_2 + I_C \gamma \quad | \text{ we have } I_C = j\omega C R_3 I_1$$

$$\therefore I_1 R_1 + I_1 \gamma_1 + I_1 j\omega L_1 = I_2 R_2 + j\omega C R_3 I_1 \quad \textcircled{2}$$

$$I_1 (R_1 + \gamma_1 + j\omega L_1 - j\omega C R_3 \gamma) = I_2 R_2$$

& $V_{CD} = V_{CCD}$

$$I_4 R_4 = I_C (\gamma - jx_C)$$

$$= I_C (\gamma + \frac{1}{j\omega C}) \quad | \text{ we have } I_C = j\omega C R_3 I_1$$

$$(I_2 - I_C) R_4 = (j\omega C R_3 I_1) (\gamma + \frac{1}{j\omega C})$$

$$(I_2 - j\omega C R_3 I_1) R_4 = j\omega C R_3 I_1 \gamma + \frac{j\omega C R_3 I_1}{j\omega C}$$

$$I_2 R_4 - j\omega C R_3 R_4 I_1 - j\omega C R_3 \gamma - j\omega C R_3 \gamma = 0.$$

$$I_2 R_4 = j\omega C R_3 R_4 \gamma + j\omega C R_3 \gamma + j\omega C R_3 \gamma \quad \frac{j\omega C}{j\omega C}$$

$$\gamma_2 R_4 = I_1 (j\omega C R_3 R_4 + j\omega C R_3 \gamma + R_3) \quad \textcircled{3}$$

from equations $\textcircled{2} \times \textcircled{3}$ divide equation $\textcircled{2}$ by $\textcircled{3}$

$$\frac{R_2}{R_4} = \frac{R_1 + \gamma_1 + j\omega L_1 - j\omega C R_3 \gamma}{j\omega C R_3 R_4 + R_3 + j\omega C R_3 R_4}$$

$$R_1 R_4 + \gamma_1 R_4 + j\omega L_1 R_4 - j\omega C R_3 R_4 \gamma = j\omega C R_2 R_3 R_4 + R_2 R_3 + j\omega C R_2 R_3 R_4.$$

equating real & imaginary parts.

$$R_1 R_4 + \gamma_1 R_4 = R_2 R_3 \quad \text{or} \quad R_1 = \frac{R_2 R_3 - \gamma_1}{R_4}$$


$$L_1 R_4 - C R_3 R_4 \gamma = C R_2 R_3 \gamma + C R_2 R_3 R_4.$$

$$\gamma = 1363.67 \Omega$$

* Maxwell's Inductance bridge

$$\begin{aligned}L_1 &= CR_3R_4\tau + CR_2R_3\tau + CR_2R_3R_4 \\&= CR_3\tau + CR_2\frac{R_3}{R_4}\tau + CR_2R_3 \\&= \frac{CR_3}{R_4} [R_4 + R_2\tau + R_2R_4] \\&= CR_3/R_4 [R(R_2 + R_4) + R_2R_4]\end{aligned}$$

* Maxwell's Inductance bridge.

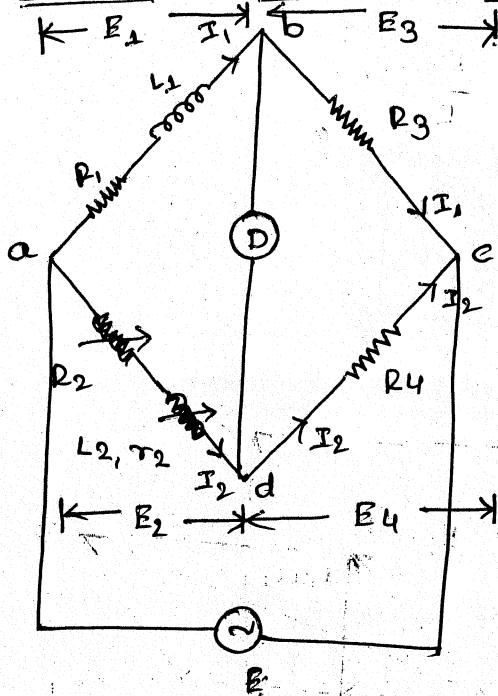

①

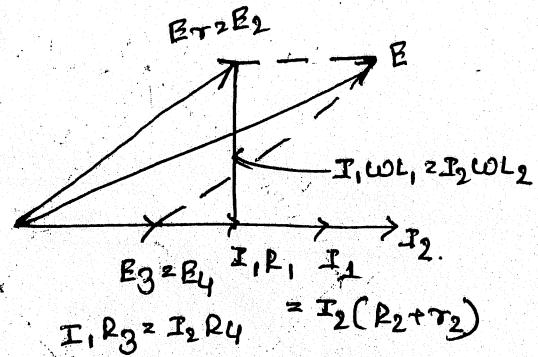


fig-b) phasor diagram

fig-a) Maxwell's Inductance bridge

The above fig shows Maxwell's Inductance bridge & its phasor diagram. The bridge circuit measures an Inductance by comparison with standard self inductance.

Let L_1 = unknown inductance of resistance R_1 ,

L_2 = variable inductance of fixed resistance r_2

R_2 = variable resistance connected in series with inductor L_2 .

R_3, R_4 = known non-inductive resistances.

When bridge is balanced we know $Z_1 Z_4 = Z_2 Z_3$.

$$\text{i.e. } (R_1 + j\omega L_1) R_4 = (R_2 + r_2 + j\omega L_2) R_3$$

$$R_1 R_4 + R_4 j\omega L_1 = R_2 R_3 + R_3 r_2 + j\omega L_2 R_3$$

Equating real & imaginary parts

$$R_1 R_4 = R_2 R_3 + R_3 r_2$$

$$R_1 = \frac{R_3}{R_4} (R_2 + r_2) //$$

Imaginary part $j\omega L_1 R_4 = j\omega L_2 R_3$

$$L_1 = \frac{R_3}{R_4} \cdot L_2$$

* Maxwell's Inductance - Capacitance bridge.

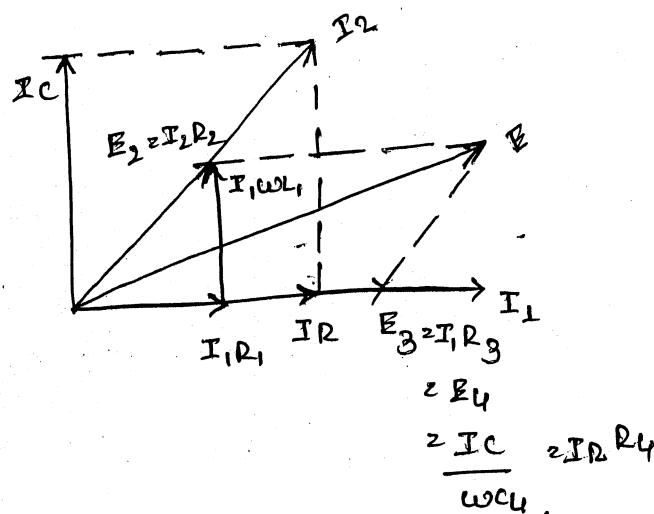
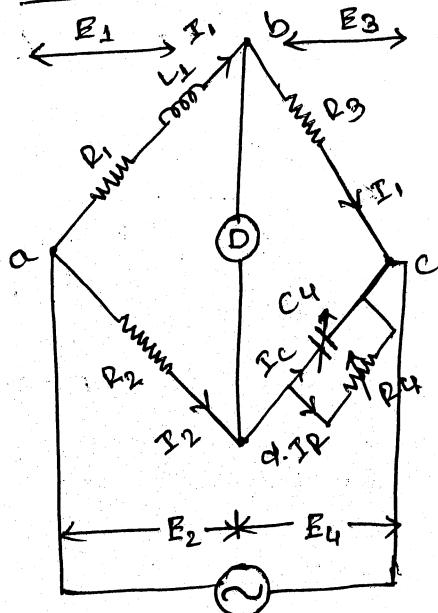


fig - Maxwell's inductance capacitance bridge.

In Maxwell's inductance capacitance bridge, an inductance is measured by comparison with a standard variable capacitance. The bridge connection & phasor diagram is as shown above

Where L_1 = unknown inductance

R_1 = effective resistance of inductor

R_2, R_3, R_4 = known non-inductive resistances

C_4 = variable standard capacitor.

at the balanced condition.

$$Z_1 Z_4 = Z_2 Z_3$$

$$(R_1 + j\omega L_1) \left(\frac{R_4}{1 + j\omega C_4 R_4} \right) = R_2 R_3 \quad (2)$$

$$R_1 R_4 + j\omega L_1 R_4 = R_2 R_3 + j\omega C_4 R_4 R_2 R_3$$

Separating real and imaginary part

$$R_1 R_4 = R_2 R_3$$

$$\therefore R_1 = \frac{R_2 R_3}{R_4}$$

\therefore

$$L_1 R_4 = C_4 R_4 R_2 R_3$$

&

$$L_1 = C_4 R_2 R_3 //$$

$$\text{The expression for Q factor is } Q = \frac{\omega L_1}{R_1}$$

$$= \frac{\omega C_4 R_2 R_3 R_4}{R_2 R_3}$$

$$Q = \omega C_4 R_4 //$$

* Advantages.

- 1) The two balance equations are independent if we choose R_4 and C_4 as variable elements.
- 2) The frequency does not appear in any of the two equations.
- 3) L_1 & R_1 is calculated in simple way.

* disadvantage

- 1) The bridge requires variable capacitor which is expensive.

* Hay's Bridge

The Hay's bridge is a modification of Maxwell's bridge. The connection diagram for the bridge is as shown below

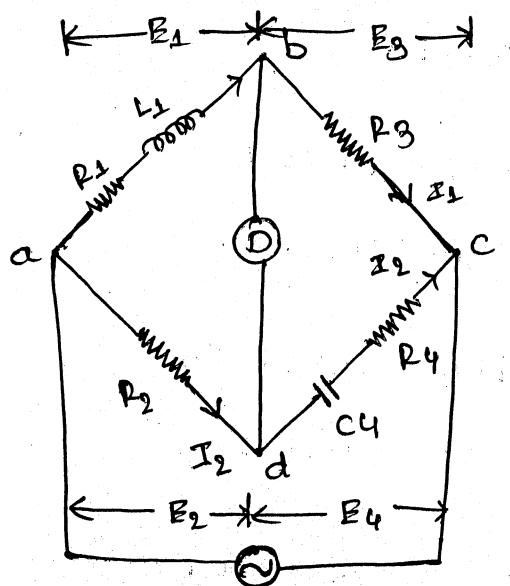


fig - Hays bridge

Let L_1 = unknown inductance having a resistance R_1

R_2, R_3, R_4 = known non-inductive resistance

C_4 = standard capacitor

at balanced condition. $Z_1 Z_4 = Z_2 Z_3$

$$(R_1 + j\omega L_1) \left(R_4 + j\frac{1}{\omega C_4} \right) = R_2 R_3$$

$$R_1 R_4 + \frac{jR_1}{\omega C_4} + j\omega L_1 R_4 + \frac{L_1}{C_4} = R_2 R_3$$

separating real & imaginary parts.

$$R_1 R_4 + \frac{L_1}{C_4} = R_2 R_3 \quad \text{--- (1)} \qquad j\omega L_1 R_4 = \frac{jR_1}{\omega C_4}$$

$$\omega^2 L_1 R_4 C_4 = R_1$$

put the value of L_1 in equation (1)

$$L_1 = \frac{R_1}{\omega^2 R_4 C_4} \quad \text{--- (2)}$$

$$\therefore R_1 + \frac{R_1}{\omega^2 R_4 C_4^2} = R_2 R_3$$

$$R_1 \left(R_4 + \frac{1}{\omega^2 R_4 C_4^2} \right) = R_2 R_3$$

$$\Rightarrow R_1 \left(\frac{\omega^2 R_4^2 C_4 + 1}{\omega^2 R_4 C_4^2} \right) = R_2 R_3 \quad (3)$$

$$\therefore R_1 = \frac{\omega^2 R_4 C_4^2 R_2 R_3}{\omega^2 R_4^2 C_4 + 1} \quad (3)$$

$$\therefore R_1 = \frac{R_2 R_3 C_4}{\omega^2 R_4 C_4} \quad \text{put eqn (3) in below L_1}$$

$$\text{Now } L_1 = \frac{R_1}{\omega^2 R_4 C_4}$$

$$\therefore L_1 = \frac{\omega^2 R_4 C_4^2 R_2 R_3}{(\omega^2 R_4^2 C_4 + 1)(\omega^2 R_4 C_4)}$$

$$L_1 = \frac{R_2 R_3 C_4}{(1 + \omega^2 R_4^2 C_4)} \parallel$$

Now Q factor is

$$Q = \frac{\omega L_1}{R_1} = \omega \times \frac{\frac{R_2 R_3 C_4}{(1 + \omega^2 R_4^2 C_4)}}{\frac{\omega^2 R_4 C_4^2 R_2 R_3}{(1 + \omega^2 R_4^2 C_4)}} = \frac{\omega R_2 R_3 C_4}{(\omega^2 R_4 C_4^2 R_2 R_3)}$$

$$\therefore Q = \frac{1}{\omega C_4 R_4}$$

* Advantages

- 1) It provides simple expression for unknown inductance for high Q coils,
- 2) It gives simple expression for Q factor.

* Disadvantage :-

- 1) The Hays bridge is suitable for the measurement of high Q inductors, whose Q factor is more than 10.

* Measurement of capacitance

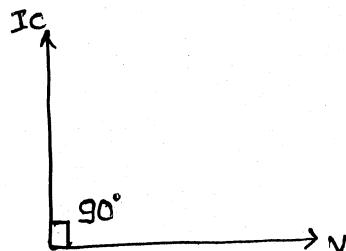


fig-a)

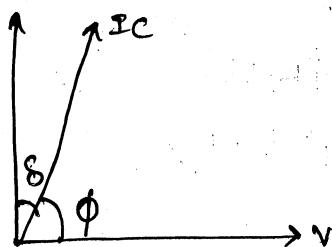


fig-b)

A pure capacitance does not consume power i.e. the dielectric loss is zero. The current I_c leads voltage by 90° as shown below in fig.

In practice there will be some dielectric loss in the capacitor due to resistance component, during this case I_c leads V by an angle slightly less than 90° as shown in fig b. for which ϕ is known as p.f. angle & S is known as loss angle or dissipation angle.

The power consumed by the capacitor is given by $P = VI_c \cos\phi = VI_c \cos(90-S) = VI_c \sin S$.

* A practical capacitor with if resistance in series is as shown below.

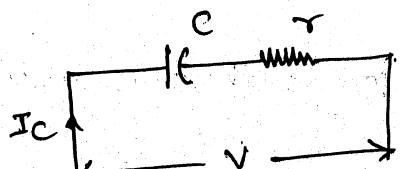


fig-c

$$V = I_c - j \frac{I_c}{\omega C}$$

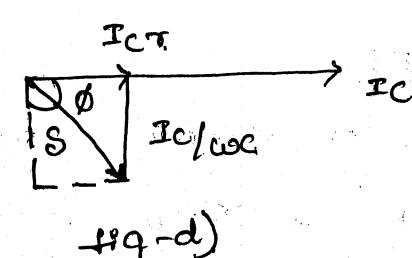


fig-d)

$$\tan S = \frac{I_c r}{I_c / \omega C} = \omega C r = \omega C \tau = \text{loss factor}$$

factor or dissipation factor.

* A practical capacitor is ~~ll~~⁴ with resistance R as shown below.

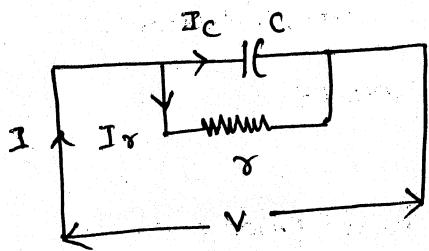


Fig - e)

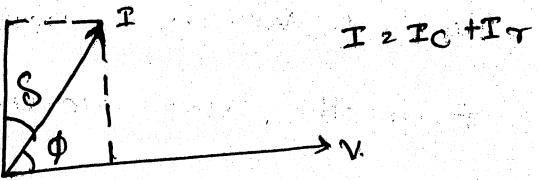


Fig - f

$$\text{Loss factor} = \tan \delta = \frac{I_R}{I_C} = \frac{V/R}{V/\omega C} = \frac{1}{\omega CR}$$


The pf of the capacitor is given by $\cos \phi = \cos(90^\circ - \delta)$

* There are two bridges that can measure capacitance.

- 1) Schering bridge
- 2) DeSauty's bridge

* The Schering bridge is widely used for the measurement of capacitance, dielectric loss and pf of the capacitor. The best advantage of Schering bridge is it can be used for both low voltage & high voltage.

* Low voltage Schering Bridge.

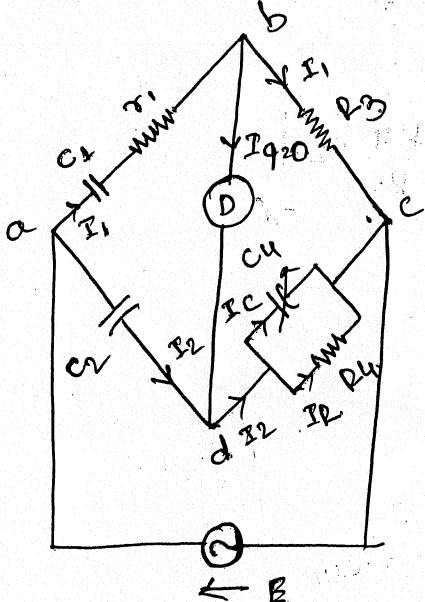

The connection diagram for Low voltage Schering Bridge is as shown above.

Where: C_x = The unknown capacitance

R_1 = Resistance representing if loss component

C_2 = Standard loss free air capacitor.

Fig - Low voltage Schering Bridge.

R_3 = non-inductive resistance

C_4 = A variable capacitor

R_4 = A variable, non-inductive resistance

E is the loop voltage at source.

The detector may be headphones or a vibration galvanometer.

When the bridge is balanced,

$$Z_1 Z_4 = Z_2 Z_3$$

$$\left(r_1 + \frac{1}{j\omega C_1} \right) \left(\frac{R_4}{1 + j\omega C_4 R_4} \right) = \frac{1}{j\omega C_2} R_3$$

$$(r_1 + 1/j\omega C_1) R_4 = (1/j\omega C_4 R_4) \frac{R_3}{j\omega C_2}$$

$$r_1 R_4 + \frac{R_4}{j\omega C_1} = \frac{R_3}{j\omega C_2} + \frac{R_3 R_4 C_4}{C_2}$$


equating real & imaginary parts we get

$$r_1 R_4 = \frac{R_3 R_4 C_4}{C_2}$$

$$\therefore r_1 = \frac{R_3 C_4}{C_2}$$

$$\& \quad \frac{R_4}{C_1} = \frac{R_3}{C_2}$$

$$\therefore C_1 = \frac{R_4}{R_3} C_2$$

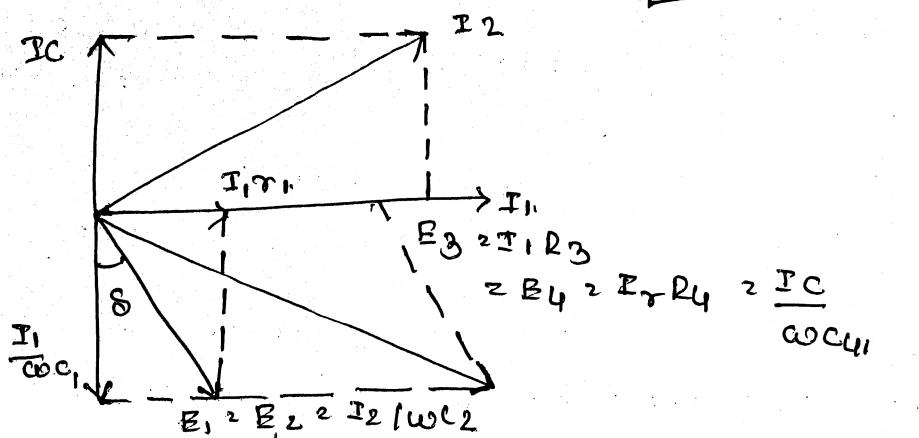


Now the dissipation factor is obtained as

$$\tan \delta = \omega C_1 T_1 = \omega \frac{R_4}{C_2} \cdot \frac{C_4}{C_2} \frac{R_3}{C_2} = \omega C_4 R_4.$$

However the values of C_4 and R_4 are alternatively varied to obtain balance, as each one of them appear in the two balancing equations separately.

* High voltage Schering Bridge

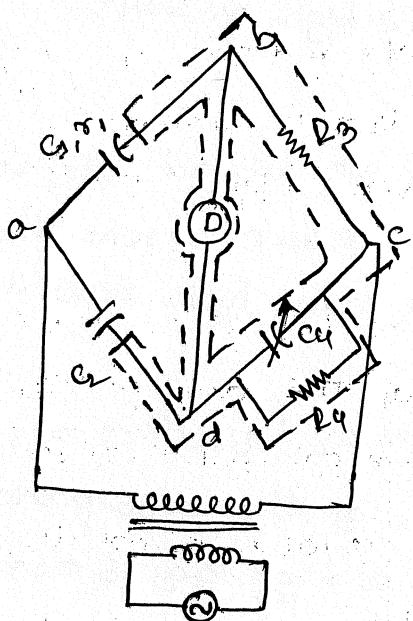

The Schering bridge is generally used for the measurement of capacitance & their dissipation factors, but in particular it is used to measure the properties of insulators, condenser bushings, insulating oil & other insulating material.

Fig - b) High voltage * High voltage Schering bridge
Schering Bridge. is used for the measurement of small capacitances.

* Special features of High voltage Schering Bridge

1) The high voltage supply is obtained from a transformer usually at 50Hz. The detector used is vibration galvanometer.

2). Arm ab and ad contain only capacitors. These capacitors are designed for high voltage work. The impedances of these arms are very high.

compared to those of arms bc & cd. The point c is earthed. Even when voltage of 100 kV is applied the voltage across bc & cd are ~~also~~
~~very~~ ^{are} above earth.

- 3) Spark gaps are provided across arms bc & cd to prevent very high voltage appearing across these arms, when either of the high voltage capacitors breaking down.
- 4) The impedances of the arms ab and ad are very large and hence the current drawn from the source is very small. Hence, a very high sensitive detector has to be used.
- 5) The fixed standard capacitor C_2 has either air or compressed gas as dielectric as the dissipation factor of dry and clear air or gas is zero.
- 6) Earthed screens are used to avoid errors due to inter capacitance b/w high and low voltage arms of the bridge.

Instead of earthing one point of the circuit the earth capacitance effect on the galvanometer ready are eliminated by means of "Wagner earthing device".

* Sources of errors in Bridge circuits

The various factors which cause errors in the bridge measurement are as follows \Rightarrow

- i) Electrostatic coupling b/w the impedance of ratio arms.
- ii) Electromagnetic coupling b/w the impedance of ratio arms.
- iii) Stray capacitance effects.
- iv) Resistance not being fully non-inductive.
- v) Incorrect frequency and waveform of supply voltage

The errors which are introduced due to above effects they are considerably at high voltage & high frequency. Hence remedial measures have to be taken to reduce these effects.

① Errors due to electrostatic coupling :- If the adjacent branches of a bridge are at different potentials, there will be inter-capacitance effect due to which the electric field of the branches may interact they introduce errors.

This error can be reduced by covering the impedances by metal shields.

② Errors due to electromagnetic field coupling :-

When the adjacent arms of bridge contain inductive coils, there is mutual coupling b/w them and the effect of mutual inductance b/w the coils is not taken into consideration while deriving the balance equations, ∴ the errors are introduced in the measurement.

③ errors caused due to stray electric fields.

When the junction points of a bridge also are at different potentials, stray capacitance exist

between these points and the earth due to which errors are introduced in the bridge measrt.

The error due to this can be minimized by using special device known as "Wagner earthing device".

4) Errors due to resistance being non-inductive :-

If the resistances used in the bridge include small inductance & the inductance values are not included during measrt then errors are introduced during measrt.

5) Errors due to Incorrect frequency and waveform of Supply voltage.

If the supply frequency is not constant & changes from its value, as the magnitude of the impedance of the various arms depends on frequency, errors are introduced in the measrt.

In order to minimize the errors due to this effect, frequency has to be checked frequently during the measurement.

If the waveform of the supply is not sinusoidal, then it may not be possible to obtain balance, as the bridge can't be simultaneously balanced both for the fundamental & harmonics. This difficulty may be overcome by using wave filters which will eliminate harmonics.

* Shielding of Bridge elements

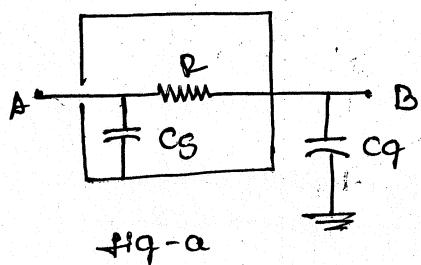


fig-a

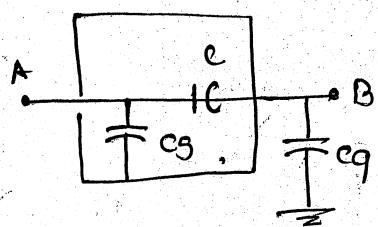


fig-b.

capacitance b/w the bridge elements and b/w the elements and earth affect the accuracy of a bridge measurements.

* An effective way of reducing the effect of these capacitances is to enclose the elements in earthed metallic shield.

* The shielding of the elements shift these capacitances where they do not harm.

* As shown in fig a resistance is shielded, a capacitance c_g exists b/w the resistor & the shield.

* Capacitor c_q exists b/w the shield and ground. By shielding, all the stray capacitances are concentrated at point B , shielding of resistor makes its value definite & bridge can be balanced without any problem.

* As shown in fig b a capacitance is shielded, after a capacitance c_g exists b/w the capacitor & shield & c_q exists b/w the shield and ground.

* By shielding of all the capacitances are concentrated at point B & their values are definite.
∴ bridge is balanced without any problem

* Dekarty's bridge.

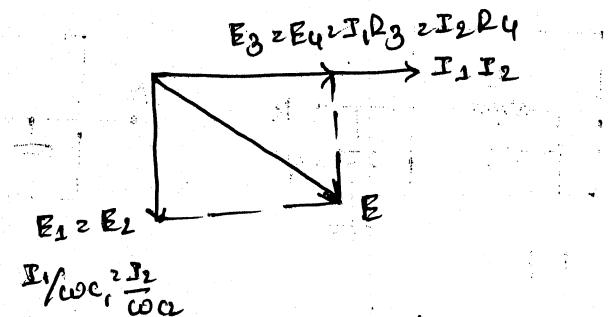
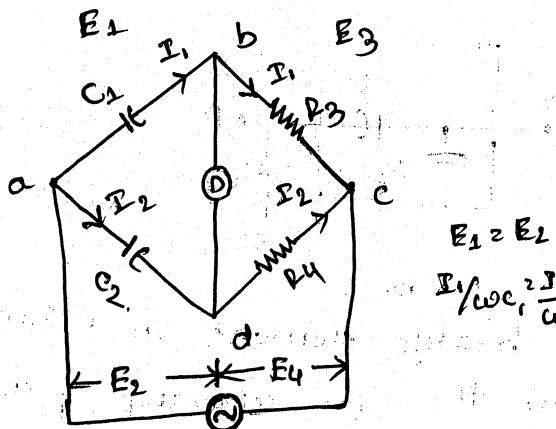


fig-b) phasor diagram

fig-a) dekarty bridge.

Above fig shows dekarty's bridge & phasordiagram of dekarty's bridge.

Let C_x = capacitor whose capacitance is to be measured.

C_2 = a standard capacitor.

R_3, R_4 = non inductive resistors

When bridge is balanced condition. $Z_1Z_4 = Z_2Z_3$

$$(\frac{1}{j\omega C_1})R_4 = (\frac{1}{j\omega C_2})R_3$$

$$\frac{R_4}{R_3} = \frac{j\omega C_1}{j\omega C_2}$$

$$\frac{R_4}{R_3} = \frac{C_1}{C_2} \quad \textcircled{1}$$

The balance of bridge is obtained by varying either R_3 or R_4 . With this method only lossless capacitors like air capacitors can be compared.

In order to make measurement on imperfect capacitors, the bridge is modified as shown below.

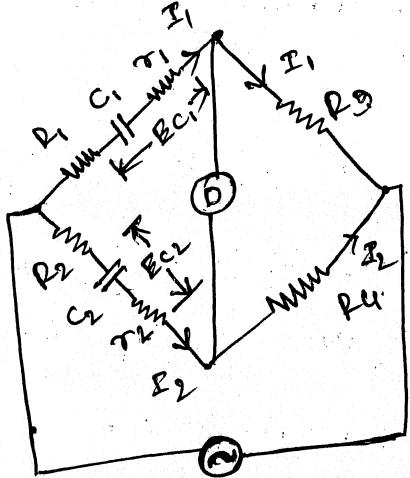


fig-c) modified de Sauty bridge

The modified de Sauty bridge & corresponding phasor diagram is as shown in fig c & fig d respectively.

Registers R_1 and R_2 are connected in series with C_1 and C_2 , r_1 and r_2 are resistance representing the loss component of two capacitors connected in series with

c_1 & c_2 .

At balanced condition of bridge

$$z_1 z_4 = z_2 z_3$$

$$(R_1 + r_1 + \frac{1}{j\omega C_1}) R_4 = (R_2 + r_2 + \frac{1}{j\omega C_2}) R_3$$

$$\frac{R_1 R_4 + r_1 R_4 + \frac{1}{j\omega C_1}}{\frac{1}{j\omega C_1}} = R_2 R_3 + r_2 R_3 + \frac{1}{j\omega C_2}$$

$$\frac{R_4}{R_3} = \frac{R_2 + r_2 + \frac{1}{j\omega C_2}}{\frac{R_1 + r_1 + \frac{1}{j\omega C_1}}{\frac{1}{j\omega C_1}}}$$

By solving the above equation we get

$$\frac{R_4}{R_3} = \frac{R_2 + r_2}{R_1 + r_1} = \frac{C_1}{C_2} \quad \text{--- (2)}$$

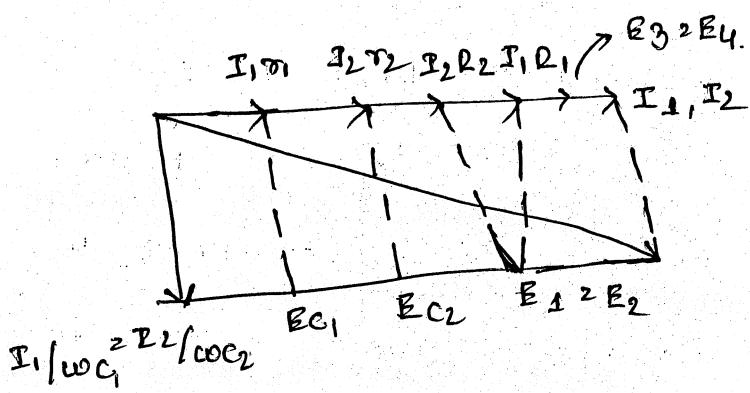


fig-d) phasor diagram

The balance of the bridge is obtained by the variation of R_1, R_2, R_3, R_4

figd, shows the phasor diagram of the bridge under balance conditions. The angles δ_1 and δ_2 are the phase angles of capacitors C_1 and C_2 respectively

dissipation factor for the capacitors are

$$D_1 = \tan \delta_1 = \omega C_1 r_1 \quad \text{and} \quad D_2 = \tan \delta_2 = \omega C_2 r_2$$

the equation ② can also be written as

$$C_1(R_1 + r_1) = C_2(R_2 + r_2)$$

$$C_1 R_1 + C_1 r_1 = C_2 R_2 + C_2 r_2$$

$$C_2 r_2 - C_1 r_1 = C_1 R_1 - C_2 R_2$$

$$\begin{aligned} & D_2 / D_1 \\ & \omega C_2 r_2 - \omega C_1 r_1 = \omega C_1 R_1 - \omega C_2 R_2 \\ & \qquad\qquad\qquad = \omega [C_1 R_1 - C_2 R_2] \quad \left| \begin{array}{l} D_2 = \omega C_2 r_2 \\ D_1 = \omega C_1 r_1 \end{array} \right. \end{aligned}$$

But we know that $C_1/C_2 = R_4/R_3$

$$\text{or } C_1 = C_2 R_4 / R_3$$

$$\therefore D_2 - D_1 = \omega \left[C_2 R_4 / R_3 \cdot R_1 - C_2 R_2 \right]$$

$$D_2 - D_1 = \omega C_2 \left[\frac{R_1 R_4 - R_2}{R_3} \right] //$$

from the above equation it is clear if the dissipation factor of one capacitor is known we can obtain the dissipation factor of second one

* An ac bridge has the following branches

Arm ab : an unknown impedance (R_3, L_3) in series with a non-inductive variable resistor r_1

Arm bc = a non inductive resistor $R_3 \approx 100\Omega$


Arm cd = " " " $R_4 \approx 200\Omega$

Arm da = " " " $R_2 \approx 250\Omega$

Arm de = a non inductive variable resistor r

Arm ec = logarithmic capacitor $C \approx 1\text{MF}$ and

Arm be = a detector.

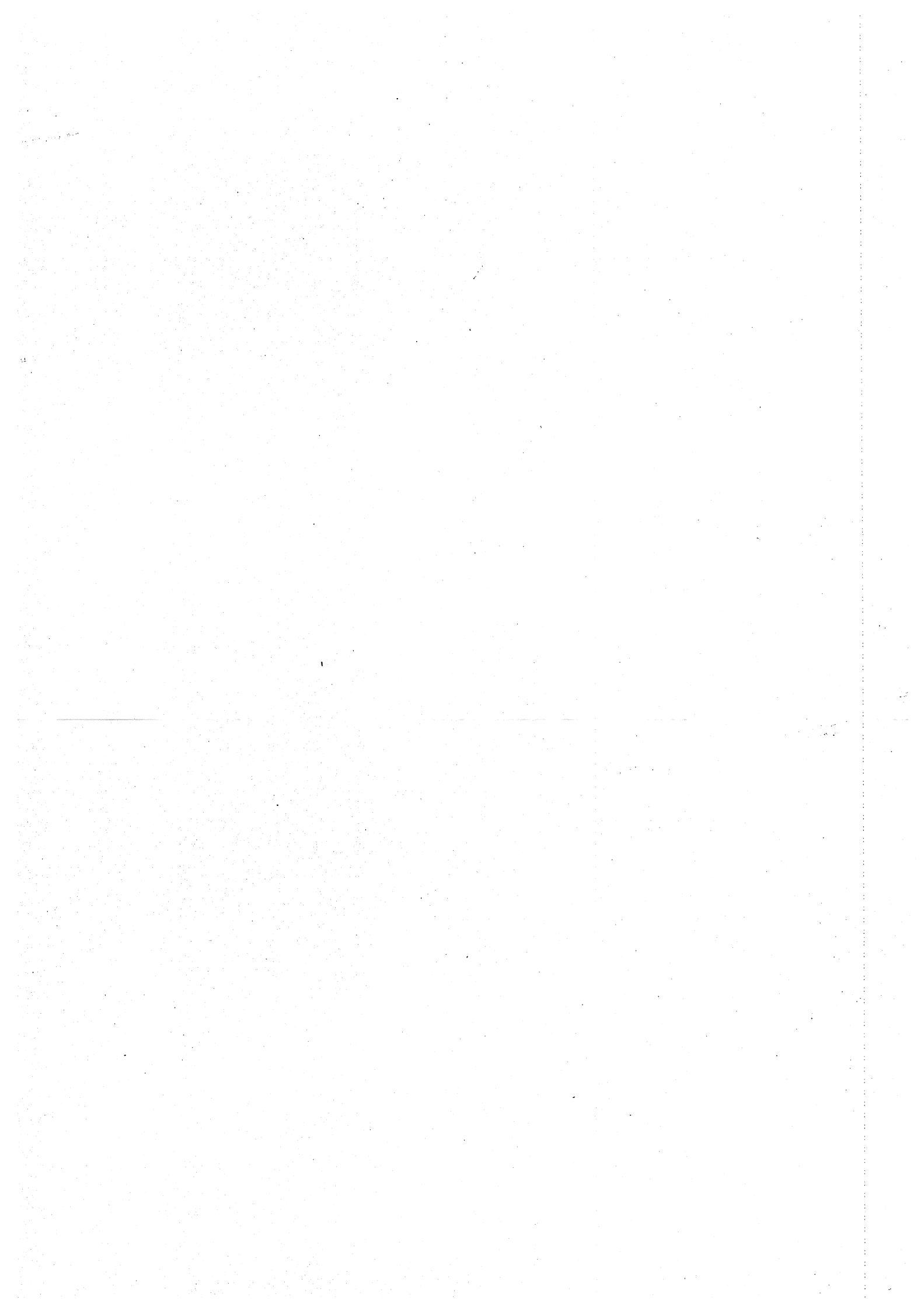

chapter - 4.



Measurement of power & Related parameters

29

power is the rate at which energy is consumed, its unit is watt. In dc the power is given by the product of voltage across the current. i.e. $P = VI$ watts for dc, while in ac it's the power given by product of voltage, current & power factor. $P = V I \cos \phi$ watts in ac.

However the wattmeter are universally used for the measurement of power.

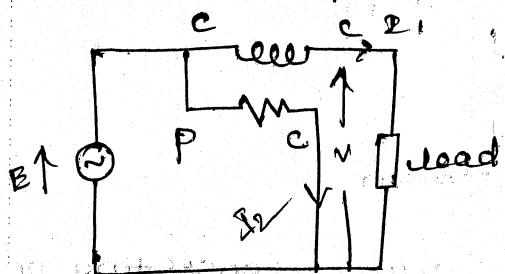


fig-a) wattmeter

as shown in the above fig a wattmeter consisting of ac type current coil is connected in series with the load while the potential coil is connected across the supply. Here wattmeter directly reads

the power consumed.

There are different type of wattmeter but the universally used wattmeter is the dynamometer type wattmeter.

* Dynamometer type wattmeter

The below fig shows the dynamometer type of wattmeter which is universally used for the measurement of dc as well as ac power.

30

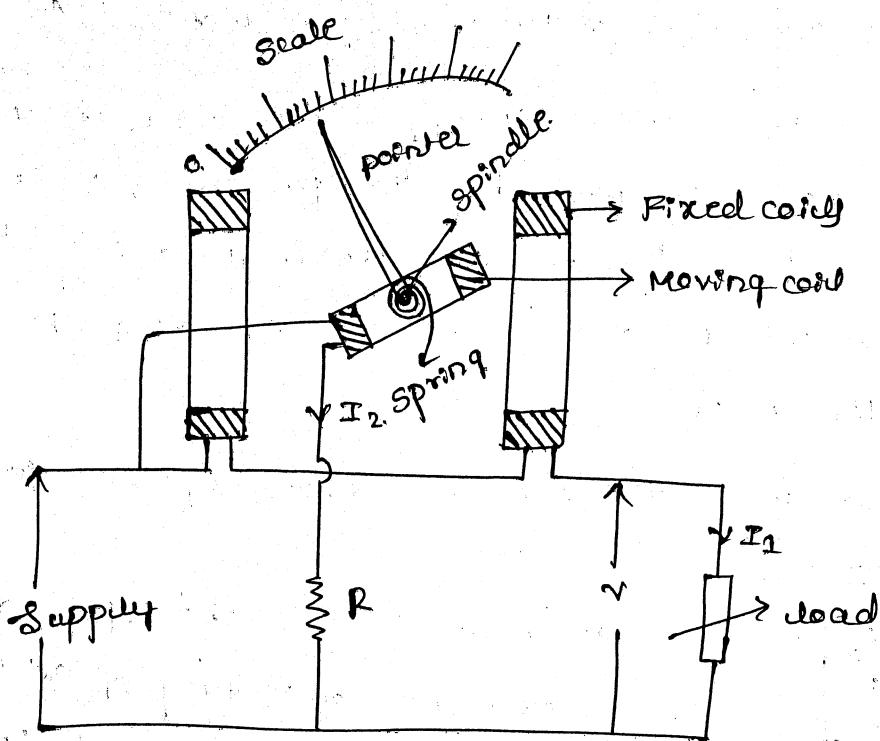


fig - dynamometer Type wattmeter

Construction :- As shown in the above fig it consisting of fixed pearl which forms the ce & it consisting of moving coil which forms the potential coil & pc. The fixed coil is split into two equal parts & placed at a distance in parallel with each other & they are air cored to avoid hysteresis loss when used for the measurement of Ac power.

Fixed coils are connected in series with the load to carry the current I_1 , whereas the moving coil is ^{Spindle} ~~in two fixed coils~~, & a pointer is attached to the placed on the spindle, which move over a graduated scale, in the two fixed coils,

The moving coil is connected across the supply & it carries a current of I_2 , which is proportional to the applied voltage.

However a high resistance R is connected in series with the moving coil, to limit the current flowing through the coil.

Working principle :-

① When the coil carrying moving coil is placed in the fixed magnetic field, which is produced by another current carrying moving coil, a force is produced on the coil sides of the moving coil, due to which a deflection torque is produced & the moving coil deflects.

[deflection torque \rightarrow

controlling torque \rightarrow

② Now the deflection torque is controlled by the controlling torque which is produced by the springs.

③ When the direction of coil is reversed in both the coils during the -ve half cycle, while measuring the AC power the direction of deflection torque remains same & hence the dynamometer type of wattmeter is used for the measurement for both AC & DC power.

④ When the moving coil deflects, the pointer attached to the spindle moves over a graduated scale & comes to rest & it comes to rest when deflection torque is equal to controlling torque.

DC power meas.

Let V = voltage across the load

I_1 = load current

I_2 = current through the moving coil

$$I_2 \propto V$$

Since the fixed coil is air-cored, hence the flux density produced in the fixed coil is directly proportional to the current $\therefore B \propto I_2 \quad \text{--- (1)}$

The deflection torque produced is given by

$$T_d \propto BI_2$$

$$\propto I_1 I_2$$

$$\propto I_1 V$$

& power consumed by the load

\therefore the deflection of the pointer due to the deflection torque T_d is proportional to power consumed by the load.

* AC power measurement

Let $v =$ instantaneous voltage across the load

Let $i_1 =$ current through the load

Let $i_2 =$ current through moving coil

$V =$ rms value of the voltage across the load

$I_1 =$ current through the load.

$\cos\phi = \text{pf of the load}$

If $v = V_m \sin \omega t$, & $i_1 = I_m \sin(\omega t - \phi)$,

assuming the load is inductive

due to the inertia of the moving coil, the deflection is proportional to the average torque.

\therefore Avg deflection torque \propto average value of $(i_1 \times i_2)$

\propto

$\therefore v i_1 = V_m \sin \omega t \times I_m \sin(\omega t - \phi)$

$$v_i = V_m I_m \cdot \frac{1}{2} [\cos \phi - \cos(2\omega t - \phi)]$$

$$i = \frac{1}{2} V_m I_m [\cos \phi - \cos(2\omega t - \phi)]$$

power is a scalar quantity hence only its average value must be considered.

The above ~~term~~ equation containing the two terms

$$i) \frac{1}{2} V_m I_m \cos \phi$$

$$ii) -\frac{1}{2} V_m I_m \cos(2\omega t - \phi)$$

The second term is periodically varying term & hence its average value over a period of time is zero.

$$\therefore \text{Average value of } (v_i i_1) = \frac{1}{2} V_m I_m \cos \phi$$

$$\Rightarrow \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi = VI \cos \phi \quad \text{--- (2)}$$

$$\therefore T_d \propto VI \cos \phi$$

However $VI \cos \phi$ gives average power consumed by the load,

$$\therefore T_d \propto VI \cos \phi \quad \text{--- (3)}$$

$$\text{At steady deflection } T_d = TC$$

From the equation (3) it is clear that the deflection of the pointer is proportional to the power consumed by the load.

* Advantages

- i) Dynamometer type of wattmeter is used to measure both ac & dc power.

- ② They have a uniform scale
- ③ They are accurate & reliable.

* Disadvantages


- ① At low power factor, the inductance of the potential coil causes the second error.
- ② The reading of the meter is affected by stray magnetic field acting on the moving coil.

* Attenuation — 1, 16, 22, 23, 32, 33

* Errors in dynamometer wattmeter

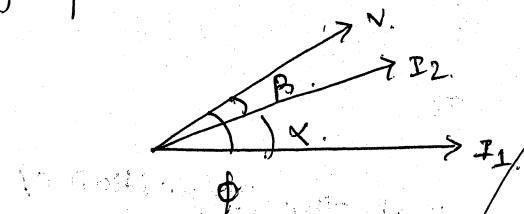- i) Due to the inductance of the pressure coil.
In an ideal wattmeter it is assumed that the pressure coil is purely resistive and the current through it is I_2 , in phase with the applied voltage V .

However the pressure coil will have a small inductance due to which it lags the applied voltage V by a small angle β as shown in the below fig.




Where $R_2 = r_2 + R$ = total resistance of the pc coil.

r_2 = resistance of the pressure coil.

R = resistance in series with the pc.

I_1 = dead coil current through the coil.

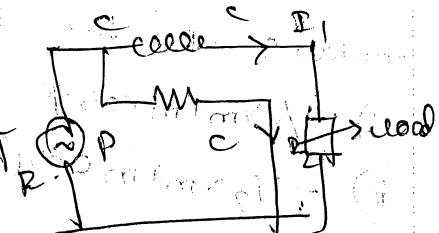In such case, the actual wattmeter reading is given by:



$$\text{where } \beta = \tan^{-1} \frac{r_2}{R}$$

Laws during
measuring
current
and test
book value


20 sec from
no

A

Errors in dynamometer type of wattmeter - cePR

i) due to the insulation of the pressure coil :-

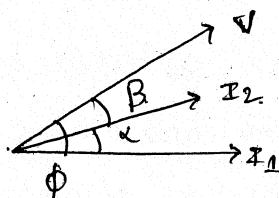3) due to In an ideal wattmeter, it is assumed that the p.e. is purely resistive, & the current through it is I_2 . which is in phase with applied voltage. But however the p.e. & self, have small inductance L due to which the ch. I_2 lags the applied voltage V by a small angle β . as shown.



$$\beta = \tan^{-1} \frac{wL}{R_2} \quad \text{Where } R_2 = R + r_2 = \text{total resistance of the p.c. cell}$$

r_2 = resistance of procedure cont.

R = registrator or server with PC

read current or flow through the eddy currents.

In such a case wattmeter reading is given by
 $W_a = V_1 I_1 \cos \beta \cos(\phi - \beta)$. — ① The true power is given by

divide eqn ② by ①.

$$\text{True power} = \frac{VI_1 \cos \phi}{VI_1 \cos \beta \cdot \cos(\phi - \beta)} = \frac{\cos \phi}{\cos \beta \cdot \cos(\phi - \beta)} = \text{correction factor}$$

$$\therefore \text{True power} = \frac{\cos \phi}{\cos \beta \cdot \cos(\phi - \beta)} \times \text{actual wattmeter reading.}$$


$$\therefore \text{true power} = \text{correction factor} \times \text{actual wattmeter reading}$$

for reading power factor

$$\text{correction factor} = \frac{\cos \phi}{\cos \beta \cdot \cos(\phi + \beta)}$$

The errors due to small inductance of pressure coil can be reduced by connecting a suitable capacitor in parallel with a portion of resistance R .

38

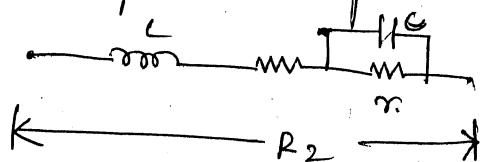

i) due to the capacitance of the pressure coil

\Rightarrow The pressure coil of the circuit may have capacitance in addition to the inductance. The effect of this capacitance ~~may affect on~~ wattmeter is opposite to that of the inductance here due to capacitance against wattmeter reads more lagging p.f. of the load.

ii) due to the mutual inductance.

Errors are introduced in the ~~wattmeter due to~~ ^{so less loss} ~~losses due to~~ the mutual inductance b/w the current coil & pressure coil of the wattmeter. These errors are very small at power frequency but at the ^{high} power frequencies they are more.

But nowadays the arrangements of both coils are done in such way that, they have zero mutual inductance & hence reduction in the error.

iii). due to the method of connection of CC & PC.

There are two methods of connecting a wattmeter in a.c.c. as shown below:

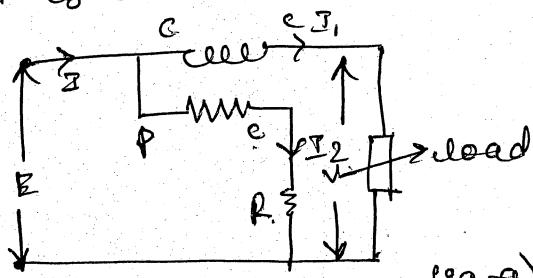


fig-a).

As shown in the above fig the primary coil is connected on the supply side. ∴ The voltage applied to the primary coil is the sum of the voltage across the load + the voltage drop across the current coil. 39

Thus the wattmeter reads the sum of power consumed by the load & the power loss in the curr coil.

$$\therefore \text{power indicated by the wattmeter} = \text{power consumed by the load} + \text{power loss in the curr coil}$$

$$= \text{power consumed by the load} + I_1^2 R_1$$

where R_1 = resistance of the curr coil.

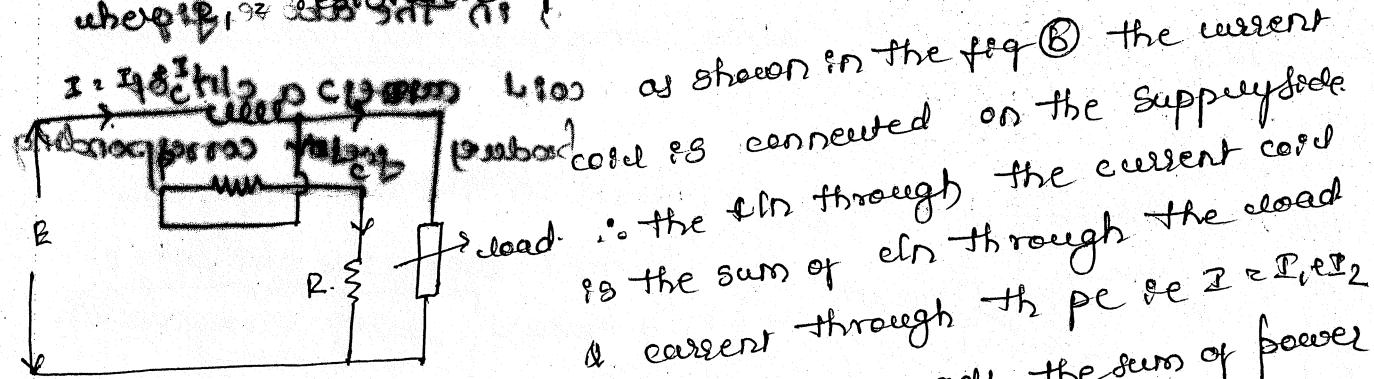


fig-b. Hence the Wattmeter reads the sum of power consumed by the load & power loss in primary coil.

∴ power indicated by the wattmeter = power consumed by the load + power loss in pc


$$= \text{load} + \frac{V^2}{R_2}$$

$$V_2 = \text{voltage across load}$$

& R_2 = resistance of pc

Note -> If the load current is small then voltage drop in the current coil is small & it gives small error in the wattmeter reading hence fig A is considered for the 40 coil connection.

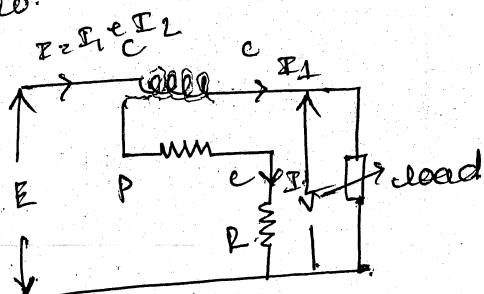2) If the load ch is large the ch in the pc ie I_2 is very small compared to load ch I_1 hence power loss in the primary coil is reduced hence fig B is taken finally instead of these two connection one more connection is preferred along compensating coil as shown below.



① as shown in the above figure the ch coil carries a current I_2 & produces a field corresponding to the ch.

② The compensating coil is exactly similar to the ch which is connected in series with the pc but carries a current of I_2 . In such direction ie if shunt coil produce the field which is exactly opposite to the field produced by I_2 through current coil.

③ i.e. the field produced by I_2 through current coil is compensated by the ch I_2 flowing through the compensating coil therefore the resultant field is produced just with the help of I_1 .

④ now the error caused is just by primary coil ch I_2 which is flowing through the current coil & wattmeter directly reads power consumed by load.

Eddy current error.

(3)

34. Eddy currents are ~~not~~ induced in the solid metal parts & within the thickness of the conductors of the ctr coil. When the wattmeter is used for the measurement of power in ac circuit.

These eddy currents will produce the field of their own & alter the magnitude & phase of ctr through the current coil & they cause error.

Due to these errors the wattmeter reads less for lagging power factor & high for leading power factor.

In order to reduce these errors care must be taken while construction of wattmeter such that no metal parts are to be used & grounded conductors are used for the ctr coil.

* Stray magnetic effects

The dynamometer wattmeter has a relatively a weak operating field which is affected by the stray magnetic effects. Hence the wattmeter must be shielded to avoid stray magnetic effects.

* error due to the vibration of moving sys.

The torque on the moving system of a wattmeter varies with the natural frequency which is two times the frequency of supply voltage. Again if the pointer spring or any other moving part sys have a natural frequency

which is equal to the frequency of the torque of the moving arm, due to which the pointer vibrates & we may not read the deflection on scale properly that's why errors are introduced.

This can be avoided just by selecting the natural frequency just away to the supply frequency.

* Temperature effect. \Rightarrow The wattmeter reading is affected due to the change in temperature. Any change in temp changes the resistance of precise coil & the stiffness of the springs. The errors caused by these two effects are opposite to one another & nearly neutralise each other.

How power factor wattmeter

As we know there are certain errors while measuring the power from dynamometer type of wattmeter such as

- ① at the low power factor the resistance of the precise coil introduces the errors.
- ② the deflecting torque on the moving arm is low even though when both current coil & precise coil are fully excited.

Hence special features are introduced in the dynamometer type of wattmeters when they are used to measure the power in circuit at low power factor. They are as follows \rightarrow

Chapter - 4

Measurement of power and Related parameters

Power is a rate at which energy is consumed, its unit is watt. In dc circuit the power is given by the product of voltage & current i.e $P = VI$ watts for dc, while in ac circuit the power is given by product of voltage, current & power factor i.e $P = VI\cos\phi$ watts in ac. However the wattmeters are universally used for the measurement of power.

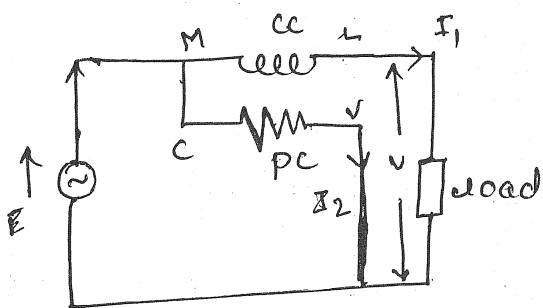


fig-a) Wattmeter

as shown in a fig wattmeter consisting of cc & pc, current coil is connected in series with load & potential coil pc is connected across the supply. Here wattmeter directly

measures the power consumed. There are different types of wattmeters are there but the universally used wattmeter is the dynamometer type of wattmeter.

* Dynamometer type of Wattmeter

The below fig shows the dynamometer type of wattmeter which is universally used for the most of ac as well as dc power.

* Construction

As shown in the above fig it consisting of fixed coil which forms the current coil & it consisting of moving coil which forms the potential

i.e PC.

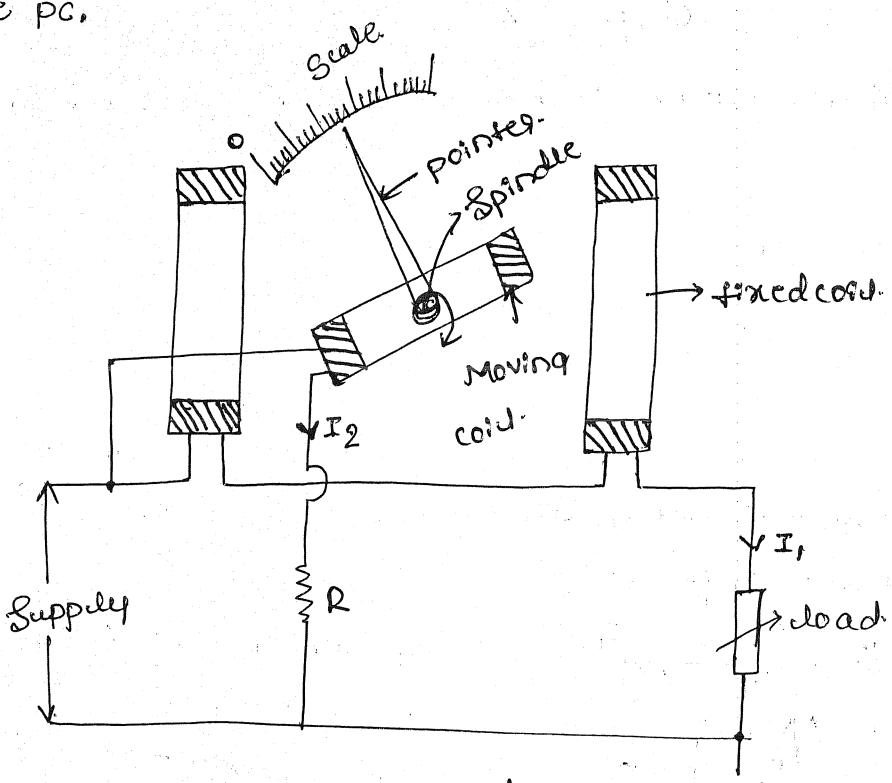


fig - Dynamometer type of Wattmeter.

As shown above the fixed coil is split into two equal parts & placed at a certain distance in parallel with each other. & they are aircored to avoid hysteresis loss, when used for the measurement of AC power.

Fixed coils are connected in series with the load to carry the current I_1 , where as moving coil is placed on spindle, b/w two fixed coils. A pointer is attached to the placed on the spindle, which moves over a graduated scale, b/w the two fixed coils.

The moving coil is connected across the supply & it carries a current I_2 , which is proportional to the applied voltage.

however a high resistance R is connected in series with the moving coil, to limit the current flowing through the coil.

Working principle :-

- ① When the coil carrying moving coil is placed in the magnetic field, which is produced by another current carrying fixed coil, a force is produced on the coil side of the moving coil, due to which a deflection torque is produced if the moving coil deflects.
deflection torque \rightarrow
controlling torque \rightarrow

- ② Now the deflection torque is controlled by the controlling torque which is produced by the springs.
③ When the direction of coil is reversed in both the coils during the -ve half cycle, while measuring the AC power the direction of deflection torque remains same & hence the dynamometer type of wattmeter is used for the measurement for both AC & DC power.
- ④ When the moving coil deflects, the pointer attached to the spindle moves over a graduated scale & comes to rest & it comes to rest when deflection produced equal to controlling torque.

DC power measrt.

Let V = voltage across the load

I_1 = load current

I_2 = current through the moving coil

$$I_2 \propto V$$

Since the fixed coil is air-cored, hence the flux density produced in the fixed coil is directly proportional to the current I_1 : $B \propto I_1 \quad \dots \text{--- } ①$

The deflection torque produced is given by

$$T_d \propto BI_2$$

$$\propto I_1, I_2$$

$$\propto I_1 V$$

& power consumed by the load

\therefore the deflection of the pointer due to the deflection torque T_d is proportional to power consumed by the load.

* AC power measurement.

Let $V =$ instantaneous voltage across the load

Let I_1 = current flowing through the load coil

I_2 = current flowing through moving coil

Let V_m = rms value of the voltage across the load

$I_1 =$ current flowing through the load

$\cos \phi =$ pf of the load

$$\cos \phi = \frac{P}{V_m I_m \sin \omega t} \quad \& \quad I_m = I_m \sin(\omega t - \phi)$$

$$\text{If } V = V_m \sin \omega t$$

assuming the load is resistive $\cos \phi = 1$

due to the inertia of the moving coil, the deflection is proportional to the average torque.

is proportional to the average value of $(I_1 \times I_2)$

\therefore Avg deflection torque \propto average value of $(I_1 \times I_2)$

$$\& \quad \propto V I_1 = V_m \sin \omega t \times I_m \sin(\omega t - \phi)$$

$$\therefore V I_1 = V_m \sin \omega t \times I_m \sin(\omega t - \phi)$$

$$v_i = V_m I_m \cdot \frac{1}{2} [\cos \phi - \cos(2\omega t - \phi)]$$

$$v_i = \frac{1}{2} V_m I_m [\cos \phi - \cos(2\omega t - \phi)]$$

power is a scalar quantity hence only its average value must be considered.

The above ~~term~~ equation containing the two terms

$$\text{i) } \frac{1}{2} V_m I_m \cos \phi$$

$$\text{ii) } -\frac{1}{2} V_m I_m \cos(2\omega t - \phi)$$

The second term is periodically varying term & hence its average value over a period of time is zero.

$$\therefore \text{Average value of } (v_i) = \frac{1}{2} V_m I_m \cos \phi$$

$$\Rightarrow \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cos \phi = V_i \cos \phi \quad \text{--- (2)}$$

$$\therefore T_d \propto V_i \cos \phi$$

However $V_i \cos \phi$ gives average power consumed by the load,

$$\therefore T_d \propto V_i \cos \phi \quad \text{--- (3)}$$

At steady deflection $T_d \propto C$

From the equation (3) it is clear that the deflection of the pointer is proportional to the power consumed by the load.

* Advantages

- i) Dynamometer type of wattmeter is used to measure both ac & dc power.

- ② They have a uniform scale
- ③ They are accurate & reliable.

* Disadvantages


- ① At low power factor, the inductance of the potential coil causes the serious error.
- ② The reading of the meter is affected by stray magnetic fields acting on the moving coil.

* Attenuation — 1, 16, 22, 23, 32, 33,

* Errors in dynamometer wattmeter

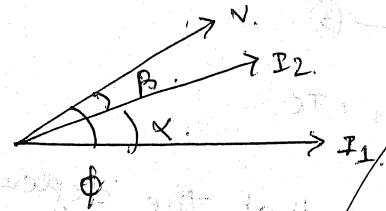- i) Due to the inductance of the pressure coil.
 \Rightarrow In an ideal wattmeter it is assumed that the pressure coil is purely resistive and the current through it is I_2 , in phase with the applied voltage V .

However the pressure coil will have a small inductance due to which current I_2 lags the applied voltage V by a small angle β as shown in the below fig.




Where $R_2 = r_2 + R$ total resistance of the pc coil.

r_2 = resistance of the pressure coil.

R = resistance in series with the pc.

I_1 = load current through the cl.

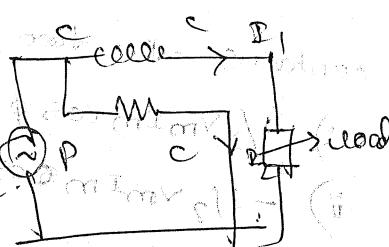In such case, the actual wattmeter reading is given by.



$$\text{where } \beta = \tan^{-1} \frac{r_2}{R} = \tan^{-1} \frac{r_2}{R_2} = \tan^{-1} \frac{r_2}{R_2 + r_2}$$

Let $R_2 = R$ for first test
 $r_2 = r$ for second test
 $R = R_2 + r$ book value

①.

Errors in dynamometer type of wattmeter - cepr

i) due to the inductance of the pressure coil :-

In an ideal wattmeter, it is assumed that the pc is barely resistive, & the current through it is I_2 . which is in phase with applied voltage. However the pc coil have small inductance L due to which the current I_2 lags the applied voltage V by a small angle β . as shown.

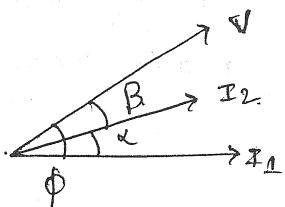


fig-a,

I_1 = load current or

I_2 = current through the coil

$$\beta = \tan^{-1} \frac{r_2}{R_2} \quad \text{where } R_2 = R + r_2 = \text{total resistance of the pc coil}$$

r_2 = resistance of pressure coil

R = resistance in series with pc

in true power is given by

$$W_a = VI_1 \cos\phi \cos(\phi - \beta) \quad \text{--- ①} \quad \text{The true power is given by}$$

$$W = VI_1 \cos\phi \quad \text{--- ②}$$

divide eqn ① by ②.

$$\frac{\text{True power}}{\text{Actual wattmeter reading}} = \frac{VI_1 \cos\phi}{VI_1 \cos\phi \cdot \cos(\phi - \beta)} = \frac{\cos\phi}{\cos\beta \cdot \cos(\phi - \beta)} = \frac{\cos\phi}{\cos\beta \cdot \cos(\phi - \beta)} = \text{correction factor}$$

$$\therefore \text{True power} = \frac{\cos\phi}{\cos\beta \cdot \cos(\phi - \beta)} \times \text{actual wattmeter reading}$$


$$\therefore \text{true power} = \frac{\cos\phi}{\cos\beta \cdot \cos(\phi - \beta)} \times \text{correction factor} \times \text{actual wattmeter reading}$$

for reading power factor

$$\text{correction factor} = \frac{\cos\phi}{\cos\beta \cdot \cos(\phi + \beta)}$$

The errors due to small inductance of pressure coil can be reduced by connecting a suitable capacitor in parallel with a portion of resistance R .

38

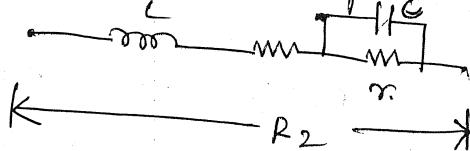

ii) due to the capacitance of the pressure coil.

\Rightarrow The pressure coil of the circuit may have capacitance in addition to the inductance. The effect of this capacitance may affect on wattmeter is opposite to that of the inductance here due to capacitance against wattmeter reads more lagging p.f. of the load.

iii) due to the mutual inductance.

Errors are introduced in the wattmeter due to the mutual inductance b/w the current coil & pressure coil of the wattmeter. These errors are very small at power frequency but at the ^{high} frequencies they are more.

But nowadays the arrangements of both c.c & p.c. are done in such way that, they have zero mutual inductance & hence reduction in the errors.

iv). due to the method of connection of CC & PC.

There are two methods of connecting a wattmeter in a.c. as shown below.

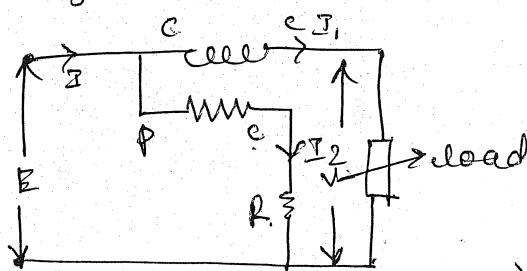


fig-a).

As shown in the above fig the pressure coil is connected on the supply side. ∴ The voltage applied to the pressure coil is the sum of the voltage across the load + the voltage drop across the current coil. 39

∴ the wattmeter reads the sum of power consumed by the load & the power loss in the cln coil.

$$\therefore \text{power indicated by the wattmeter} = \text{power consumed by the load} + \text{power loss in the current coil}$$

$$= \text{power consumed by the load} + I_1^2 R_1$$

where R_1 = resistance of the cln coil.

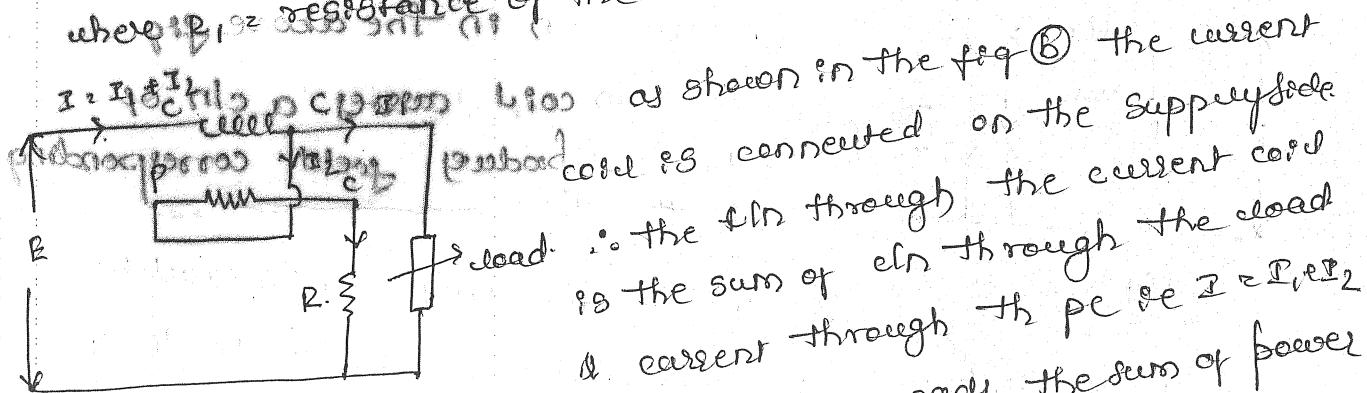



fig-b. Hence the wattmeter reads the sum of power consumed by the load & power loss in pressure coil.

∴ power indicated by the wattmeter = power consumed by the load + power loss in PC

$$= \text{load} + \frac{V^2}{R_2} \quad (\because R_2 = \text{resistance of PC})$$

Note - 1) If the load current is small then voltage drop in the current coil is small & it gives small error in the wattmeter reading hence fig-a is considered for the 40 coil connection.

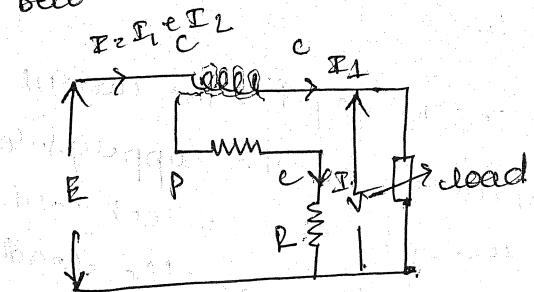2) If the load ch is large the ch in the pc ie I_2 is very small compared to load ch I_1 , hence power loss in the pressure coil is reduced & hence fig(B) is taken finally instead of these two connection one more connection is preferred along compensating coil as shown below.



① as shown in the above figure the ch coil carries a ch I_1 & I_2 & produce field corresponding to the ch.

fig-c ② The compensating coil is exactly similar to the ch which is connected in series with the pc but carries a current of I_2 in same direction ie if shunt coil produced the field which is exactly opposite to the field produced by I_2 through current coil.

∴ the field produced by I_2 through current coil is compensated by the ch I_2 flowing through the compensating coil therefore the resultant field is produced just with the help of I_1 .

③ now the error caused is just by pressure coil ch I_2 which is flowing through the current coil & wattmeter directly reads power consumed by load.

Eddy current error.

(3)

34 eddy currents are ~~not~~ induced in the solid metal parts & within the thickness of the conductors of the cln coil. When the wattmeter is used for the measurement of power in ac.

These eddy currents will produce the field of their own & alter the magnitude & phase of cln through the current coil & they cause error.

Due to these errors the wattmeter reads less for lagging power factor & high for leading power factor.

In order to reduce these errors care must be taken while construction of wattmeter such that no metal parts are to be used & guarded conductors are used for the cln coil.

* stray magnetic effect

The dynamometer wattmeter has a relatively a weak operating field which is affected by the stray magnetic effects. Hence the wattmeter must be shielded to avoid stray magnetic effects.

* error due to the vibration of moving sys.

The torque on the moving sys of a wattmeter varies with the natural frequency which is two times the frequency of supply voltage. Again if the pointer spring or any other moving part sys have a natural frequency

which is equal to the frequency of the torque of the moving coil, due to which the pointer vibrates & we may not read the deflection on scale properly that's why again the errors are introduced.

This can be avoided just by selecting the rated frequency just away to the supply frequency.

* Temperature effect. \Rightarrow The wattmeter reading is affected due to the change in temperature. Any change in temp changes the resistance of primary coil & the stiffness of the springs. The errors caused by these two effects are opposite to one another & nearly neutralise each other.

Low power factor wattmeter

As we know there are certain errors while measuring the power from dynamometer type of wattmeter when

- 1) at the low power factor the resistance of the primary coil introduces the errors.
- 2) The deflecting torque on the moving coil is low even though when both current coil & primary coil are fully excited.

Hence special features are introduced in the dynamometer type of wattmeter when they are used to measure the power in circuits at low power factor. They are as follows \rightarrow

Experiments.i) Theory of wattmeter.ii) Special features of LPF dynamometer wattmeter

27

i) precise coil circuit

The pc of the dt are designed in such a way that they must have low resistance & hence the current flowing through the pc is increased to produce an increased operating torque.

The resistance of the pc dt in LPF wattmeter

must be ~~less~~ 10 times less than that of in UPF wattmeter to produce reasonable deflating torque.


ii) compensation for precise coil current

The power measured in low power factor is small & the cts through the current coil is high hence the connection as shown in fig A can't be used, because due to high cts the power loss in the cts coil is higher & wattmeter gives error in reading.

Again in case of fig B, the power loss in the precise coil is also included the power loss in the cts coil in the wattmeter reading again shows error, hence it is necessary to compensate the effect of precise coil by compensating coil inserted with precise coil as shown in fig C.

1, 10, 10, 10, 10, 10, 10, 10, 10, 10, — Morning star

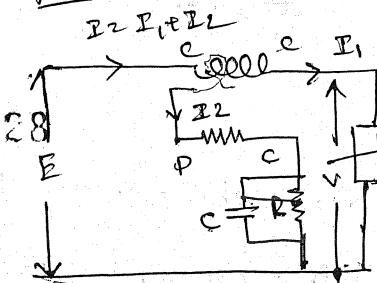iii) compensation for the inductance of PC




The error caused by pc inductance is given by $E \cdot \sin \phi$. If the pf is less, the value of ϕ becomes much more larger. & the error is more.

→ This error can be compensated just by connecting a capacitor of capacitance in parallel with the part of resistance.

iv) Small control torque:- Loop LPF wattmeters are designed to have a low control torque, hence they give fullscale deflection for $IPF = 0.1$.

* Given ohm of resistance $R_1 = 0.2 \Omega$

$$\text{& pc R is } R_2 = 5000 \Omega$$

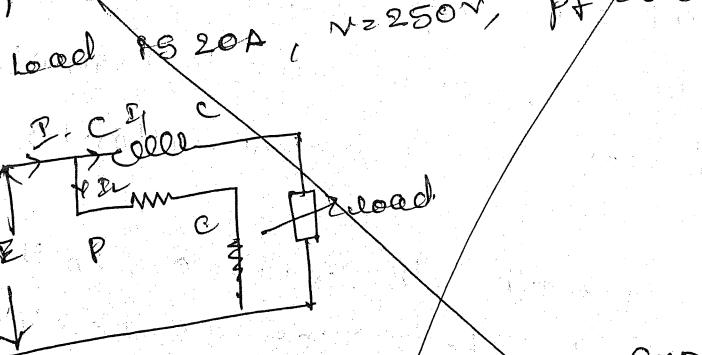

on supply side.

⇒ when pc is connected on supply side power consumed by the load $V I_1 \cos \phi = 280 \times 20 \times 0.8$

$$= 4000 \text{ Watts}$$

$$\text{power loss in coil} = I_1^2 R_1 \\ = 20^2 \times 0.2 = 80 \text{ watts}$$

$$\therefore \text{error} = \frac{80}{4000} \times 100 = 2\%$$

* A Wattmeter has a current coil of resistance 0.2Ω and a pressure coil of resistance 5000Ω is connected to measure the power consumed by the load. Calculate the % error in the reading of the wattmeter, when the load takes $20A$ at $250V$ with 0.8 pf, when i) the PC is connected on the supply side and ii) when the current coil is connected on the supply side iii) what load A would give equal errors with the two connections

\Rightarrow i) When the PC is connected on the Supply Side:

$$\text{power consumed by the load} = VI \cos\phi = 250 \times 20 \times 0.8 \\ = 4000 \text{ Watts.}$$

$$\text{power loss in the current coil} = I_1^2 R_1 = 20^2 \times 0.2 = 80 \text{ Watts}$$

$$\% \text{ error} = \frac{80}{4000} \times 100 = 2\%$$

ii) When the current coil is connected on the Supply side

$$\text{power loss in the PC} = V^2 / R_2 = \frac{250^2}{6000} = 12.5 \text{ W}$$

$$\% \text{ error} = \frac{12.5}{4000} \times 100 = 0.3125\%$$

iii) For equal errors with two ~~wattmeter~~ connections

$$I_1^2 R_1 = V^2 / R_2 \quad I_1 = \sqrt{\frac{V^2}{R_1 R_2}}$$

$$= \sqrt{\frac{250^2}{0.2 \times 5000}} = 7.906 \text{ A}$$

* A Wattmeter is connected to measure the power consumed by a load, which draws a current of $20A$ at $250V$. The pf of the load is 0.8 lagging. The cc has an impedance of $(0.08 + j0.04)\Omega$. The

resistance of the pc circuit is 6000Ω . Find the error in the reading of the wattmeter for if two possible connections to measure the power.

\Rightarrow Given load draws a current of $20A$ at $250V$
 $pf = 0.8$, cc resistance = 0.08Ω , The R_2 of PC = 6000Ω

i) When pressure coil is connected on Supply Side.

$$\therefore \text{power consumed by the load } P = VI\cos\phi \\ = 250 \times 20 \times 0.8 \\ = 4000W$$


$$\text{power loss in the current coil} \\ = I_1^2 R_1 = 20^2 \times 0.08 = 16 \text{ Watts}$$

$$\therefore \% \text{ error} = \frac{16}{4000} \times 100 =$$

$$\text{ii). power loss in the pressure coil} = V^2/R_2 = \frac{250^2}{6000} = 10.42$$

$$\% \text{ error} = \frac{10.42}{4000} \times 100 =$$

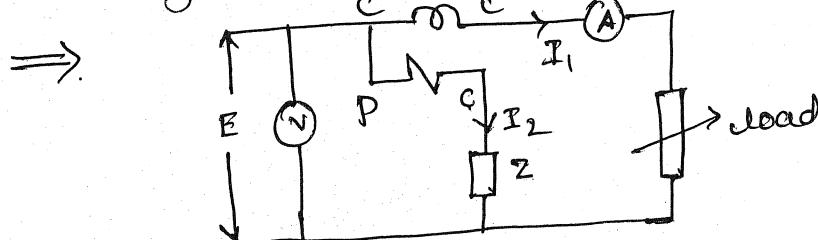* A Wattmeter is connected to read the power consumed by an inductive load ready $25W$. The voltmeter connected across the supply and the pc circuit ready $250V$. The ammeter connected in series with the cc and the load ready $5A$. The impedance of pc circuit is $(2000 + j6)\Omega$. The voltage drops across the ammeter and voltmeter are neglected. Find the % error in the wattmeter reading



phase angle of the pressure coil circuit is given by

$$\beta = \tan^{-1} X_2 / R_2 = \tan^{-1} 6 / 2000 = 0.172^\circ$$

$$\text{True power} = I_1^2 R_L = I_1^2 Z_L \cos \phi$$

Where Z_L = impedance of the inductive load

ϕ = pf angle of the load

$$Z_L = \frac{V}{I_2} = \frac{E}{I_1} = \frac{250}{5} = 50\Omega$$

$$\therefore \text{True power} = 5^2 \times 50 \times \cos \phi = 1250 \cos \phi.$$

$$\text{True power} = \frac{\cos \phi}{\cos \beta \cdot \cos(\phi - \beta)} \quad \text{x wattmeter reading}$$

$$\text{i.e. } 1250 \cos \phi = \frac{\cos \phi}{\cos \beta \cdot \cos(\phi - 0.172^\circ)} = 0.02.$$


$$\phi - 0.172^\circ = 88.854^\circ \quad \therefore \phi = 89.026^\circ \neq 21.248^\circ \text{ half}$$

$$\therefore \% \text{ error} = \frac{W_i - W_a}{W_a} \times 100$$

$$= \frac{25 - 21.248}{21.248} \times 100$$

$$= 17.658\%$$

✓

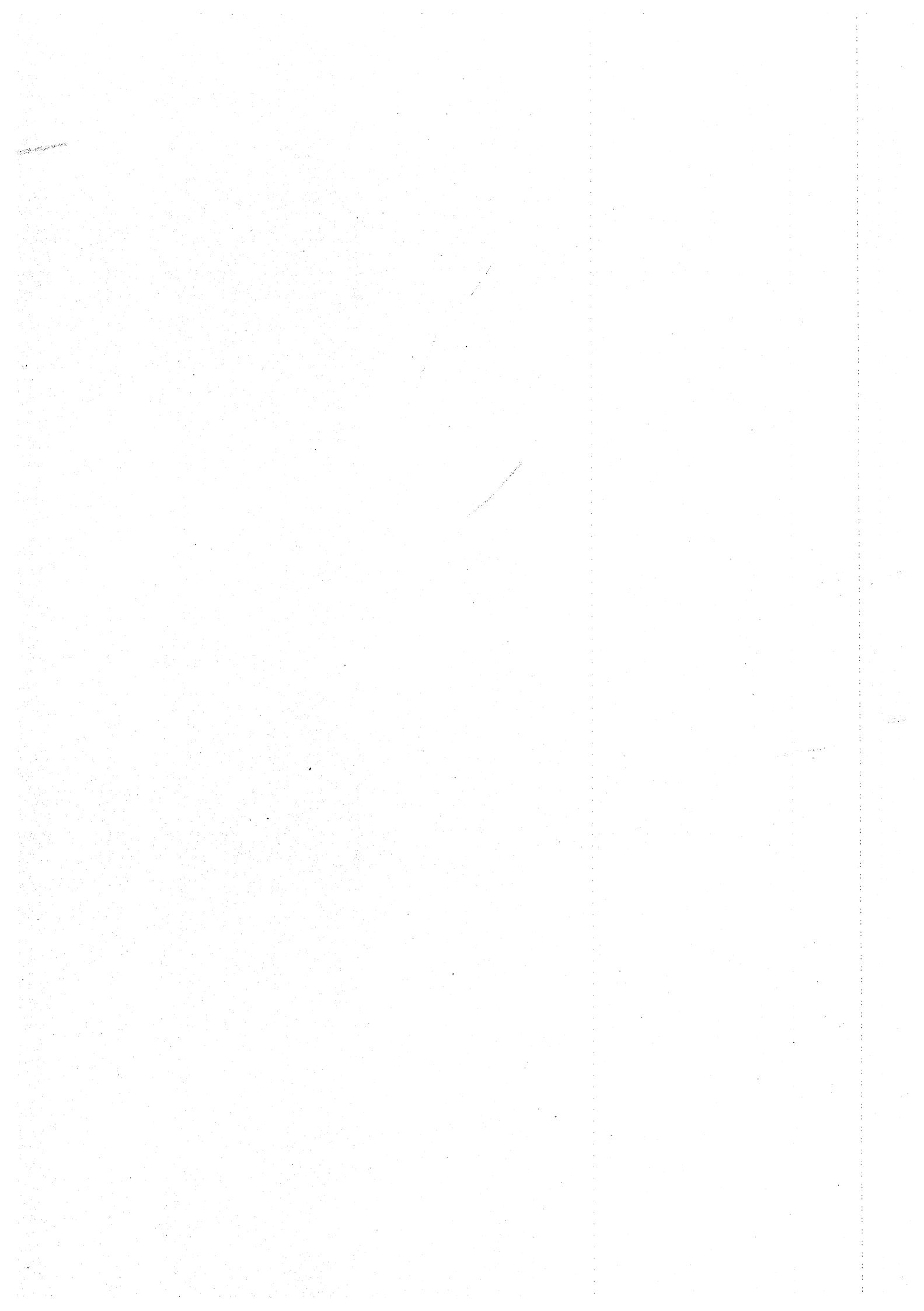

* Measurement of Real & reactive power in case of 3-Φ class

D) Three-phase Wattmeter method

[4th unit - PART A]

33

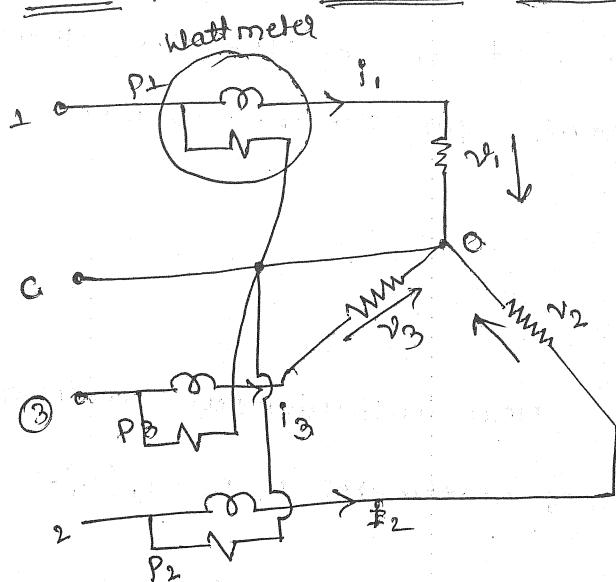


fig - three wattmeter method
for a meas of power in 3 phase
4 wire circuit.

The above fig shows 3 wattmeter method for the meas
of power in 3phase 4 wire circuit. in which the common
point C is of pressure coil & the neutral is O point
at which load coincide.

$$\therefore v = 0 \quad \& \quad v_1 = v'_1, \quad v_2 = v'_2, \quad v_3 = v'_3$$

Now sum of the instantaneous readings of watt-

$$\text{meters is } P = P_1 + P_2 + P_3 = v_1 i_1 + v_2 i_2 + v_3 i_3$$

$$\text{instantaneous power load} = v_1 i_1 + v_2 i_2 + v_3 i_3$$

\therefore Three wattmeter are used to measure the power of load.

* Two-wattmeter method :- In 3-phase system, 3 wire system

34 require three elements, but if we make the common path of the pressure coils coincide with one of the line then we require only $n-1 = 2$ elements for the measurement.

* Star-connection

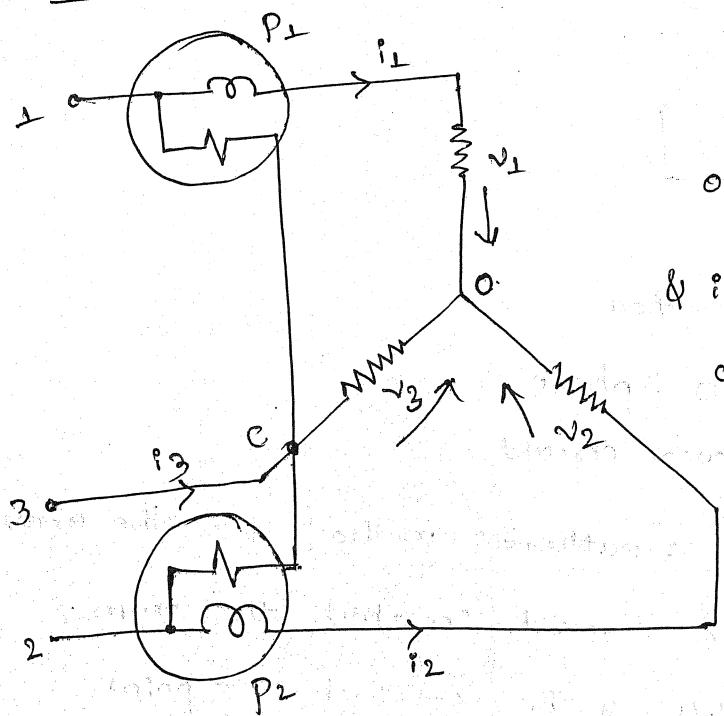


fig-a) two-wattmeter method
(Star-connection)

Now instantaneous reading of wattmeter 1, $P_1 = i_1(v_1 - v_3)$

& instantaneous reading of wattmeter 2 is
 $P_2 = i_2(v_2 - v_3)$.

Now sum of instantaneous reading of both the wattmeters is

$$\begin{aligned} P &= P_1 + P_2 \\ &= i_1(v_1 - v_3) + i_2(v_2 - v_3) \end{aligned}$$

Now from Kirchoff's current law (KCL)

$$i_1 + i_2 + i_3 = 0$$

$$i_1 + i_2 = -i_3$$

& sum of instantaneous power becomes

$$P = v_1 i_1 + v_2 i_2 - v_3 (-i_3) = v_1 i_1 + v_2 i_2 + v_3 i_3$$

$$= i_1 v_1 - v_3 i_1 + i_2 v_2 - i_2 v_3$$

$$= v_1 i_1 + v_2 i_2 - v_3 (i_1 + i_2)$$

i. Sum of instantaneous power two wattmeter reading is equal to the power consumed by the load & Here the load may be balanced or unbalanced. 35

* Two wattmeter method (Delta connection)

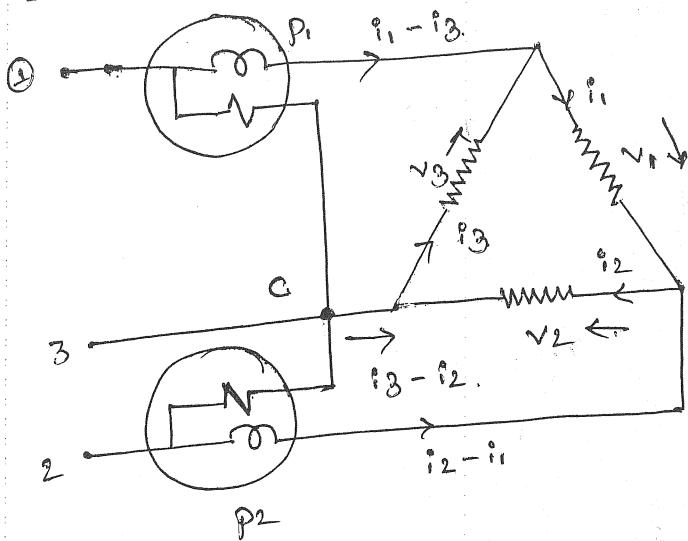


fig - two wattmeter method (Delta connection).

from the above fig, instantaneous reading of wattmeter

$$\text{for wattmeter } 1 \quad P_1 = V_3(i_1 - i_3)$$

$$\text{for wattmeter } 2 \quad P_2 = V_2(i_2 - i_1)$$

i. sum of the instantaneous readings of wattmeter P_1 & P_2

$$\therefore P_1 + P_2 = -V_3(i_1 - i_3) + V_2(i_2 - i_1)$$

$$= -V_3i_1 + V_3i_3 + V_2i_2 - V_2i_1 \quad \boxed{1}$$

$$= V_2i_2 + V_3i_3 - i_3(V_2 + V_3)$$

$$\text{From the Kirchhoff's voltage law} \quad V_1 + V_2 + V_3 = 0 \\ \therefore V_2 + V_3 = -V_1$$

$$\therefore \text{equation } \boxed{1} \text{ becomes } P_1 + P_2 = V_2i_2 + V_3i_3 + V_1i_1 \quad \boxed{2}$$

\therefore the sum of two wattmeter readings is equal to the $\sqrt{3}$ power consumed by the load. & this is irrespective of whether the load is balanced or unbalanced.

* Now let us consider the phasor diagram for a balanced Star connected load as shown below.

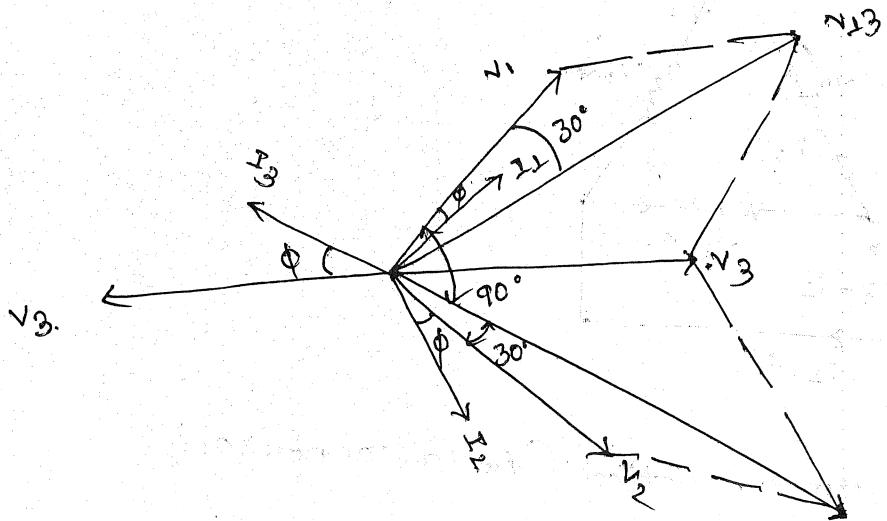


fig - phasor diagram for balanced
star connected load.

The above fig shows the phasor diagram for balanced star connected load.

The load is balanced

i.e. phase voltage

$$V_1 = V_2 = V_3 = V \quad \text{--- (1)}$$

Line voltage

$$V_{13} = V_{23} = V_{31} = \sqrt{3} V \quad \text{--- (2)}$$

phase current

$$I_1 = I_2 = I_3 = I \quad \text{--- (3)}$$

Line current

$$I_1 + I_2 + I_3 = I \quad \text{--- (4)}$$

power factor is $\cos \phi$.

The phase currents lag the corresponding phasor voltage by an angle ϕ . (37)

$$\text{Now reading of wattmeter } 1, P_1 = V_{13} I_1 \cos(30^\circ - \phi) \\ = \sqrt{3} VI \cos(30^\circ - \phi) \quad \text{--- (5)}$$

$$\text{reading of wattmeter } 2, P_2 = V_{23} I_2 \cos(30^\circ + \phi) \\ = \sqrt{3} VI \cos(30^\circ + \phi) \quad \text{--- (6)}$$

$$\begin{aligned} \text{sum of two wattmeters } P &= P_1 + P_2 \\ &= \sqrt{3} VI [\cos(30^\circ - \phi) + \cos(30^\circ + \phi)] \\ &= \sqrt{3} VI \cancel{\cos \phi} \cos \phi \end{aligned}$$

this is the power consumed by the load

$$P = P_1 + P_2$$

$$\text{P.f.} = \cos \phi = \cos \left[\tan^{-1} \frac{\sqrt{3} (P_1 + P_2)}{P_1 - P_2} \right]$$

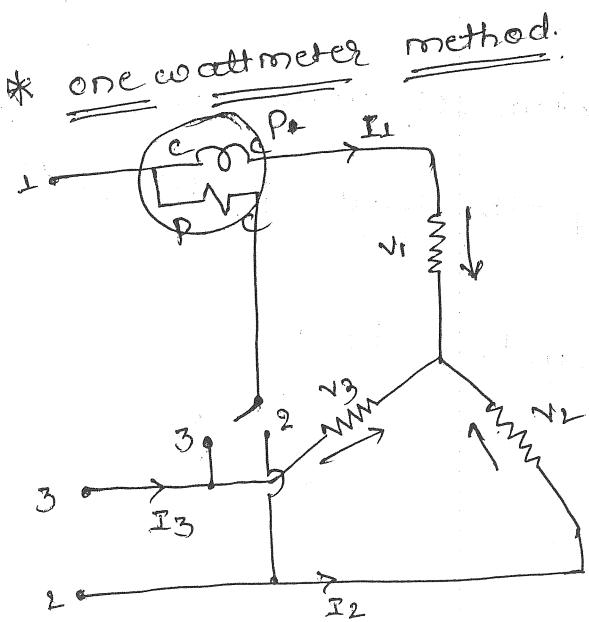


fig-a) one wattmeter method

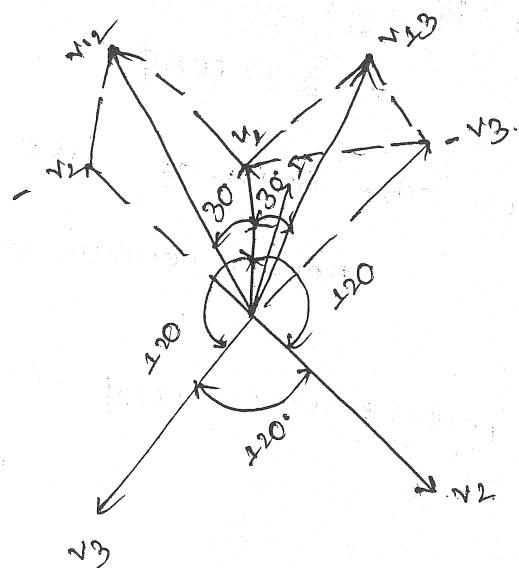


fig-b) phasor diagram of one wattmeter method.

This method is used only when the load is balanced.

38. In the above fig the current coil is connected as shown & one end of the pressure coil is connected in one of the line, & one end of the pressure coil is connected to the same line, & other end is connected alternately to the other two ~~two~~ lines.

We have $V_1 = V_2 = V_3 = V$ & $I_1 = I_2 = I_3 = I$.

$$\& V_{13} = V_{12} = \sqrt{3}V$$

Reading of wattmeter when switch at 3.

$$P_1 = V_{13} I_1 \cos(30^\circ - \phi) = \sqrt{3} V I \cos(30^\circ - \phi) \quad \text{--- (1)}$$

Now reading of wattmeter when switch is at 2

$$P_2 = V_{12} I_1 \cos(30^\circ + \phi) = \sqrt{3} V I \cos(30^\circ + \phi) \quad \text{--- (2)}$$

Sum of the two wattmeter readings

$$P_1 + P_2 = [\sqrt{3} V I \cos(30^\circ - \phi) + \sqrt{3} V I \cos(30^\circ + \phi)] \\ = 3 V I \cos \phi$$

Thus the sum of two wattmeter readings =

power consumed by the load $P = P_1 + P_2$

If power factor $\cos \phi = \cos \left[\tan^{-1} \sqrt{3} \frac{P_1 - P_2}{P_1 + P_2} \right]$

* Reactive power measurement in 3-φ circuit.

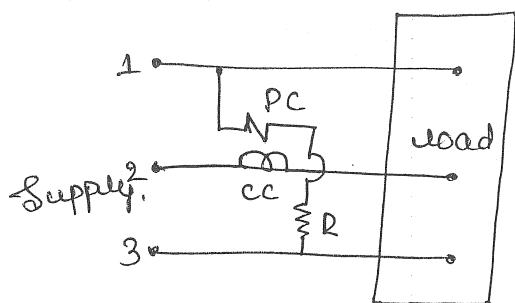


fig-a) Reactive power measurement with one wattmeter.

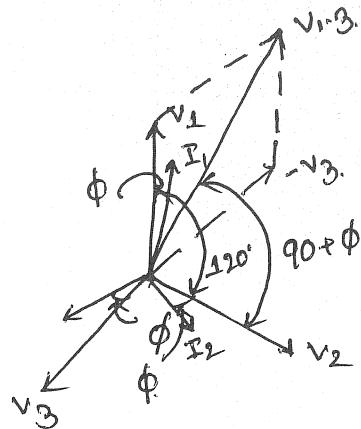


fig-b) phasor diagram

In case of balanced three phase circuit, it is simple to use a single wattmeter to read the reactive power.

→ as shown above the current coil of the wattmeter is connected in one line & the pressure coil is connected across two lines as shown above.

current through the current coil = I_2
voltage across the pressure coil = V_{13}

$$\therefore \text{Reading of Wattmeter} = V_{13} I_2 \cos(90^\circ + \phi)$$

$$= \sqrt{3} V I \cos(90^\circ + \phi)$$


$$= -\sqrt{3} V I \sin \phi,$$

Total reactive volt amperes of the circuit

$$Q = 3 V I \sin \phi$$

$$= (-\sqrt{3}) \times \text{Reading of wattmeter}$$
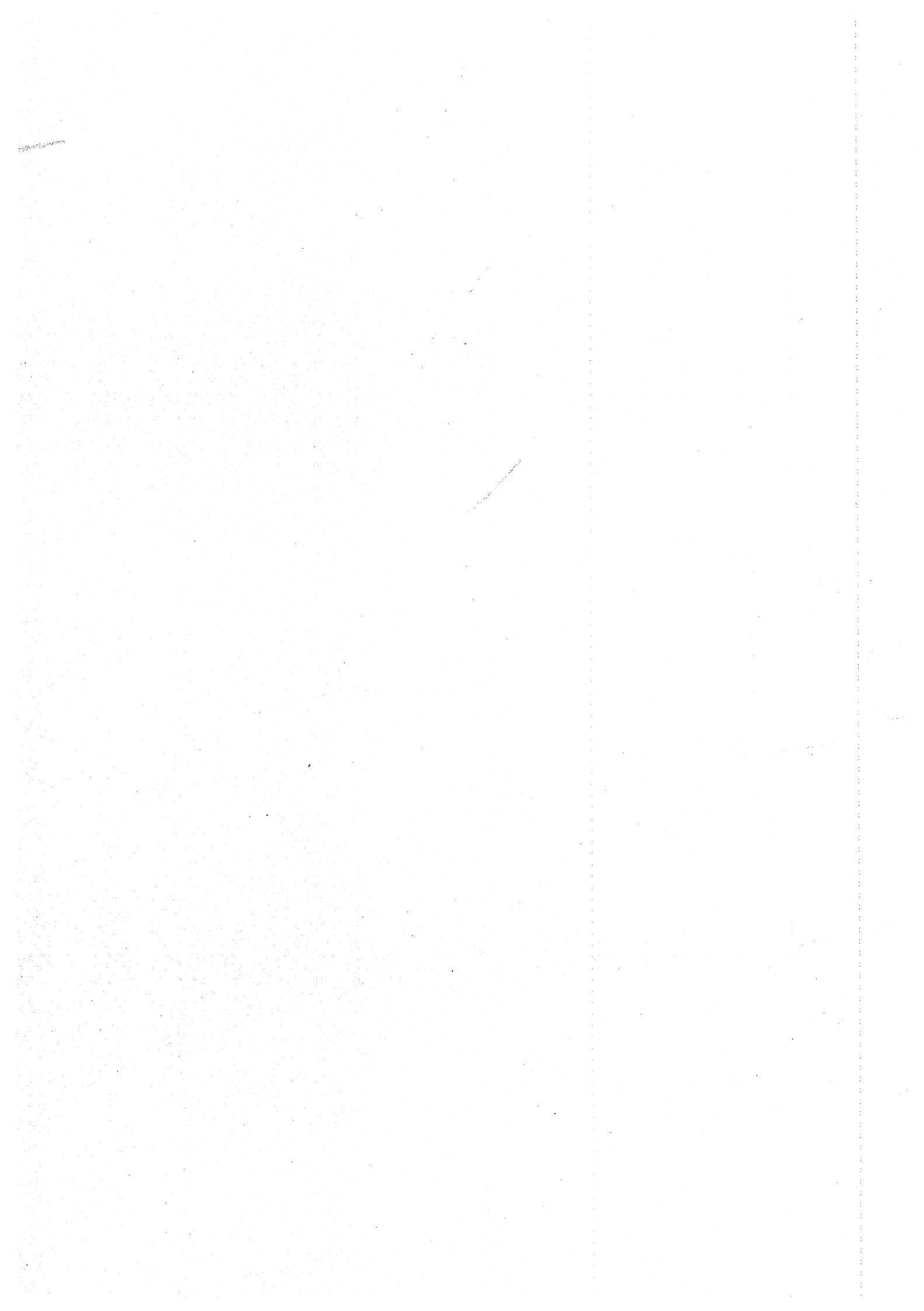
$$\text{phase angle } \phi = \tan^{-1} (\frac{Q}{P})$$



* Induction type of 1-φ energy meter.

31

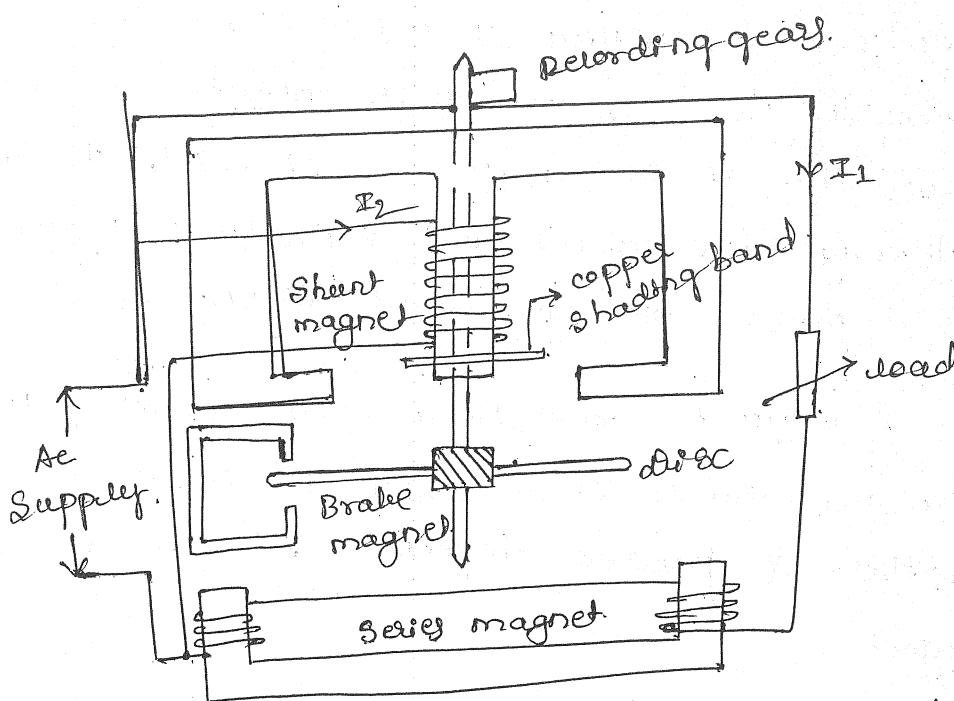


fig - Induction type of 1-φ energy meter.

- (④) The above fig shows the induction type 1-φ energymeter. Induction type of instruments are used to measure the only for Ac measurement, hence induction type 1-φ energy meter is used to measure energy consumed in Ac circuit.

* construction?

An Induction type of 1-φ energy meter mainly consisting of i) a driving system ii) a moving system iii) a braking system iv) a recording mechanism.

* A driving system.

A driving system mainly consists of two magnets, series magnet & shear magnet.

As shown in the above the series magnet contains

U shaped laminations of silicon steel, which are insulated from one another & pressed together to form a core.

32

* A coil of thick wire consisting of a few turns ~~are~~ \approx 8 is wound on both the legs of core & is connected in series with the load; this is known as current coil. The load current I_1 flows through the current coil & produces a flux of ϕ_1 which is in phase with the load current I_1 .

* Again a shunt magnet consisting of a number of M shaped silicon steel laminations which are insulated from one another & pressed together to form a core of shunt magnet.

* A coil of thin wire, having large number of turns is wound on the central limb of the shunt magnet. This is known as voltage coil or potential coil. If it is connected across supply, it is excited by $elm I_2$ which is proportional to the applied voltage.

In order to obtain the deflecting torque, the coil in the pole must lag the applied voltage by 90° ; to achieve this copper ring is provided on the central limb of shunt magnet.

The shunt magnet produces a flux of ϕ_2 due to the $elm I_2$, flowing through the coil & it is proportional to the applied voltage & in quadrature with the applied voltage.

ii) The moving system

The moving system contains eight aluminium disc, mounted on the spindle. The aluminium disc is placed in the airgap b/w the series magnet & shunt magnet.

* due to the absence of control torque the disc continuously rotates ^{under} ~~due to~~ the action of deflecting torque for which is produced due to the resultant magnetic field.

iii) Braking System

A permanent magnet, known as brake magnet is placed near to aluminium disc. When aluminium disc rotates under the influence of magnetic field produced by the brake magnet & induced emf in disc, the eddy currents will produce circulation in the disc in such a way that the torque produced will oppose the rotation of disc.

[* The eddy currents induced in the disc are proportional to the speed of disc, & hence the braking torque exerted on the disc is proportional to the speed]

* The position of brake magnet can be adjusted hence the braking torque is also adjusted.

iv) Recording mechanism

The main function of recording mechanism is to record the number of revolutions made by the disc.

* Working principle

34

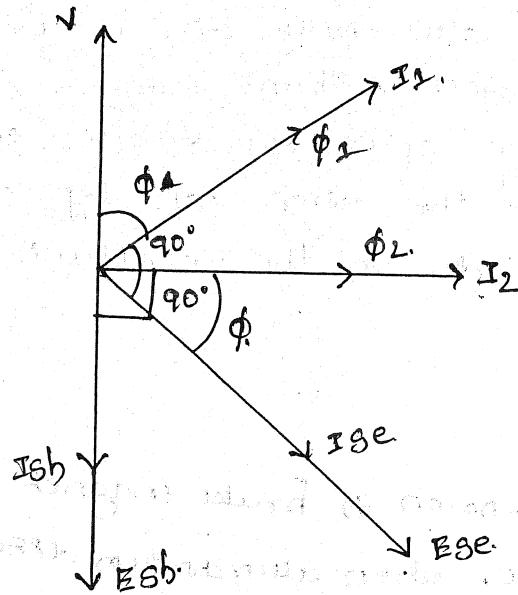


Fig - phasor diagram.

Suppose initially the energy meter is connected to a supply and voltage, due to supply current I_2 , flows to the pc

1) Initially the energy meter is connected to a supply and voltage, due to supply current I_2 , flows to the pc & produce a flux of Φ_2 .

2) As potential coil is inductive in nature current I_2 lags the supply voltage V by an angle of 90° .

3) When the energy meter is connected to a load, a load current I_1 flows through the coil due to which a flux Φ_1 is produced.

④ The phase angle θ in the voltage & load current I_1 depends on the nature of load. If the load is inductive in I_1 lags the voltage by an angle ϕ .

⑤ Due to sheet magnet flux Φ_2 & servo magnet flux Φ_1 the emf E_{sh} & E_{sc} are generated in the disc respectively.

The two emf's E_{sh} & E_{sc} lag the corresponding fluxes ϕ_2 & ϕ_1 by an angle of 90° . 35

The eddy currents I_{sh} & I_{sc} are set up by the induced emf's & they are assumed to be in phase with their respective emfs. Due to these eddy currents two opposite torques are produced, one due to flux ϕ_2 & E_{sc} & other torque due to flux ϕ_1 & I_{sh} etc. The difference b/w these two torque will drive the disc & disc shaft rotating.

* Theory → the torque produced is given by

$$T_d \propto \phi_2 I_{sc} \cos \phi - \phi_1 I_{sh} \cos(180 - \phi)$$

$$\propto \phi_2 I_{sc} \cos \phi + \phi_1 I_{sh} \cos \phi$$

$$\propto k_1 V I_1 \cos \phi + k_2 V I_2 \cos \phi$$

$$\propto V I_1 \cos \phi (k_1 + k_2)$$

$$\propto V I_1 \cos \phi$$

& power consumed by the load.

$$P = T_b N \quad \text{for steady speed} \quad T_d = T_b$$

$$\therefore P = N \times \text{power} \propto N \times k$$

power k represents the power consumed in & seconds & N — represents the number of revolutions

made by the disc.

Finally the speed of disc can be adjusted

by suitably varying the position of brake magnet such that, the energy consumed by the load is equal to the energy supplied, this is called celebration

of energy meter

* Errors in single phase Energy meter.

The errors are mainly caused due to i) driving slip
ii) braking system.

errors caused by the driving slip are

i) incorrect magnitude of fluxes

incorrect magnitude of fluxes are mainly due to abnormal current & voltage. The error in the shunt coil flux is due to the change in the resistance of pressure coil coil & due to abnormal frequency.

① incorrect phase angle :- incorrect phase angles are mainly due to improper lag adjustments, abnormal frequencies & due to the change in resistance due to temperature variation.

② lack of symmetry in magnetic ckt

If the magnetic ckt is not symmetrical then a driving torque causes the energy meter to creep [creeping \rightarrow in some energy meter the disc rotates even though there is no flow of current through the current coil is known as creeping]

* The errors caused by braking slip are

i) change in the strength of the brake magnet.

ii) change in disc resistance

iii) self-braking effect of series coil flux

iv) abnormal friction of parts, bearings, etc.

[friction is deflected by \rightarrow 27, 4, 14, 23, 22, 33, 36, 42, 64, 69].

37

* Adjustment in 1- ϕ energy meter

When the energy meter is used for the measurement of energy consumed in the circuit, then it is necessary to make the certain adjustment in the meter, \therefore the energy meter should give the energy consumed correctly & error must be within allowable limits $\pm 5\%$.

The adjustments made in the energy meter are \rightarrow

i) preliminary light load adjustment.

This type of adjustment is done on the energy meter to check whether the energy meter creeps or not. To check this the holes of disc are positioned in such way that, the holes are not under the influence of the field magnet. The rated voltage is applied across the pressure coil & there is no current flowing through the current coil. The light load device is adjusted till the device should stop the setting.

ii) full load up adjustment

In this case the pressure coil is connected across the rated supply voltage, where a rated current is passed through the current coil at 45° . The position of brake magnet is adjusted such that the light aluminum disc should rotate at correct speed within the required limits of error.


iii) Lpf adjustment :- Again here the pressure coil is connected across the ^{rated} supply voltage, & rated current is passed through the current coil at 0.5 pf lagging. However the lag device is adjusted till the disc rotates at correct speed.

iv) Light load adjustment :- in this case a rated supply voltage is applied across the pressure coil & a very small current about 5% of full load current is passed through the current coil at c.p.t., the light load is adjusted in such a way the disc rotates at correct speed.

v) Creep adjustment :-

To make the creep adjustment the pressure coil is excited by 110% of rated voltage with zero load current. If the light load adjustment is correct the meter will not creep.

* Calibration of 1-Φ Energy meter *

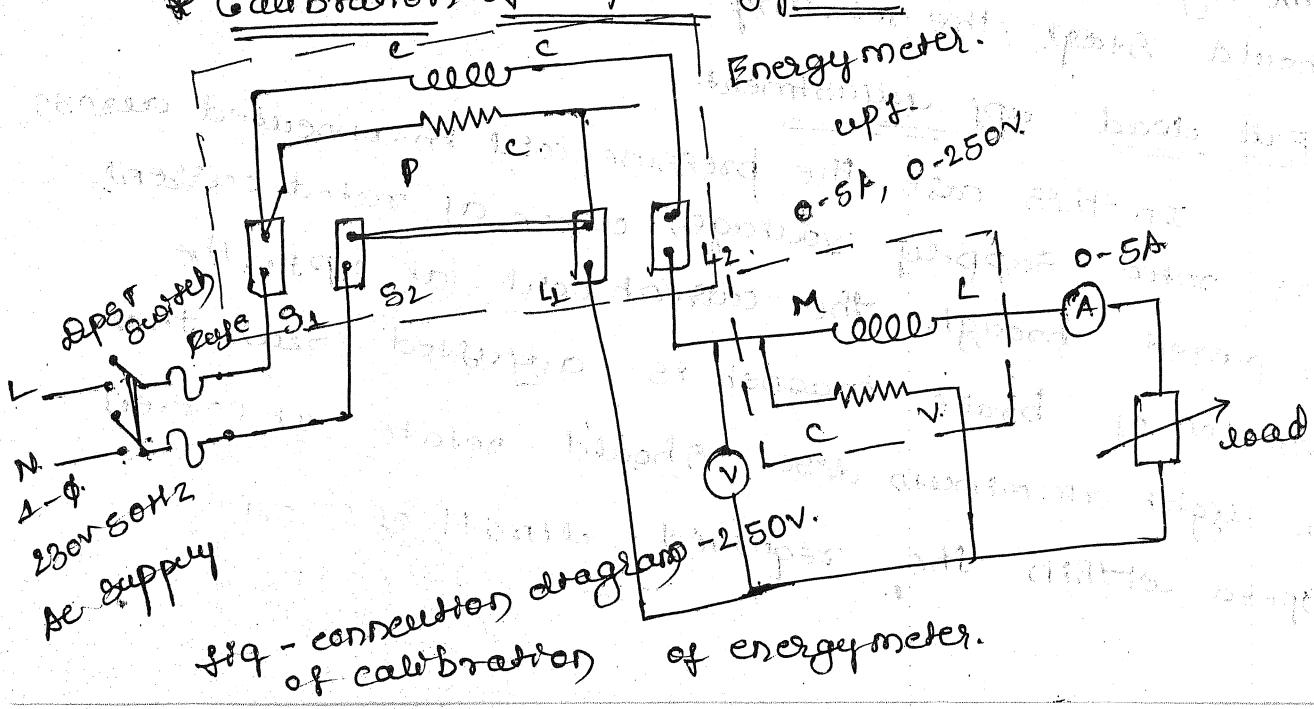

Be The above fig shows connection diagram for the calibration of energimeter. Before the energimeter is used for the measurement of energy in any circuit, it ^{is} to be calibrated (checked), so that the indicated energy E_i is approximately equal to the actual energy consumed E_a .

The procedure for calibrating the energimeter is as follows:

- ① The connections are made as per the above circuit diagram.
- ② keep the load switch open & supply switch is closed.
- ③ now the pc is energized & there is no current in the circuit. coil, observe the disc if disc is not rotating then the disc is creeping, or else if the disc is rotating then the load device is adjusted till the disc stops rotating.
- ④ now the load switch is closed & a small current ie 5% of the full load current is made to flow through the current coil.
- the load is considered as lamp load which is purely resistive, the pf of load is unity.
- the readings of ammeter, voltmeter, wattmeter & time taken by the disc to make the revolutions is noted.
- the wattmeter constant is calculated by using the formula.

$$\text{Wattmeter constant} = \frac{\text{range} \times \text{current range} \times \text{pf}}{\text{full scale deflection of Wattmeter}}$$

Now the actual energy consumed by the load is given by $E_a = W \times k \text{ A.U} / 3600000 \text{ kwh}$ — ①

The energy indicated by the energymeter is given by

$$40 \quad E = D / E_k \quad \text{--- (2)}$$

where E_k is the constant of energymeter in revolution/kwh which is mentioned on the name plate of energymeter.

[ie 700 rev/kwh, 1000 rev/kwh etc]

$$\% \text{ error} = \frac{E_1 - E_0}{E_0} \times 100 \quad \text{--- (3)}$$

If the error is less than $\pm 5\%$ no load pf adjustment is required.

If the error is more than $\pm 5\%$, is not required. If the % error is more than $\pm 5\%$, then the load adjustment is done until the error reducing to $\pm 5\%$.

Now, the load is gradually applied, till the load is flowing through the circuit again the % of error is calculated by using above steps. If the error is less than $\pm 5\%$ then no adjustment is required, if it is more than $\pm 5\%$ then the position of brake magnet is adjusted till the error reducing to less than $\pm 5\%$. Finally energymeter is calibrated & used for the measurement of energy consumption.

* Electronic energymeter

An electronic energymeter extensively uses integrated circuit for its operation.

The block diagram is shown below.

* Electrodynamometer type of 1-φ pf meter.

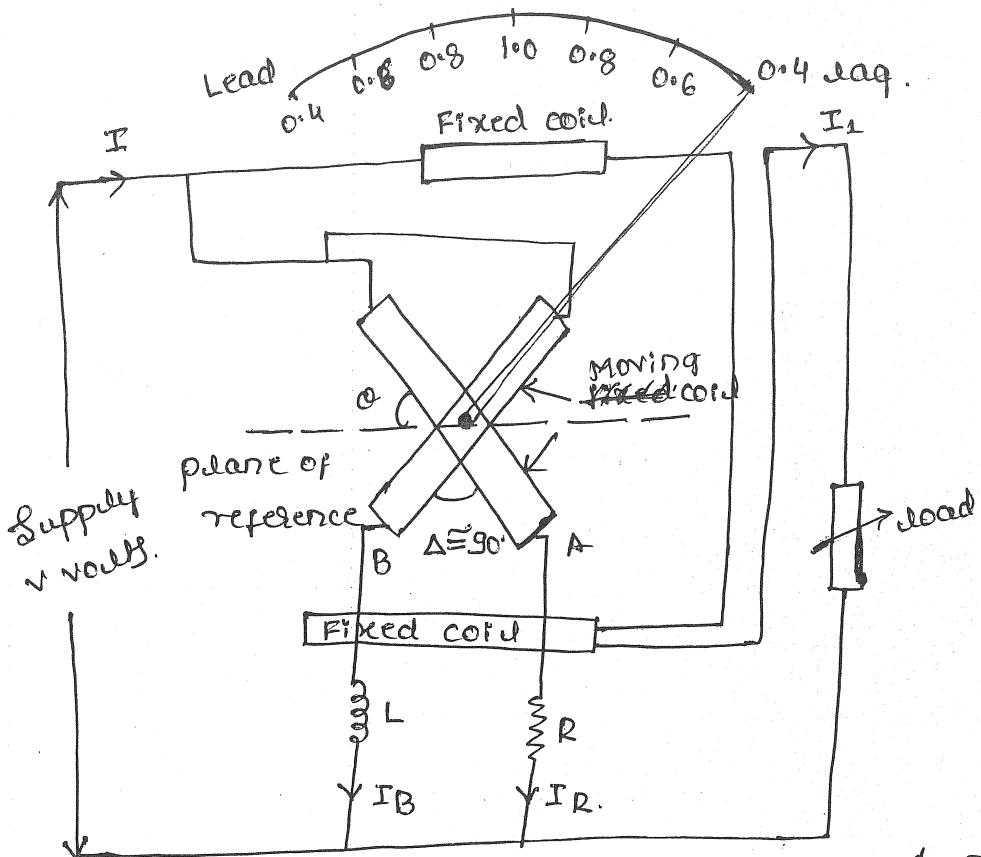


fig - Electrodynamometer type of 1-φ pf meter.

- ① The above fig shows the construction of electro-dynamometer type of 1-φ pf meter.
- ② It consisting of a current coil which is in the form of two fixed coils, which is connected in series with load & carry a current of 1 amp. However the magnetic field produced by the current coil is directly proportional to load current.
- ③ Again it consisting of two pressure coils A & B which are fixed to a spindle & they will form the moving system of pf meter.
- ④ As shown in the above fig A non inductive resistance R is connected in series with coil A

& a high inductive choke L_1 is connected in series with pressure coil. Both the pressure coils are connected across the supply voltage.

⑤ The values of R & L are adjusted in such a way that both the coils should carry a same current at normal frequency i.e. $R = \omega L$.

⑥ The current through the pressure coil A is I_A which is in phase with the applied voltage, while the current through the pressure coil B is I_B , which lags the applied voltage by an angle of α which is approximately equal to 90° .

⑦ However the angle between both the pressure coils A & B are also adjusted to an angle α , no controlling torque is required provided in the instrument.

⑧ The connections of moving coils are made with the help of silver or gold ligaments, which are flexible in nature. & they offer minimum controlling torque on the moving system.

* Working principle :- When the supply is given to the terminal of pf meter, two deflecting torques are produced, one is acting on coil A & other is acting on coil B. The windings of these two coils are arranged in such a way that torque acting on both the coils must have opposite direction. The moving system starts deflecting due to the difference b/w these two torques & it shows reading when both the torques become equal & at this

pointer indicates the pf of the circuit on calibrated scale.

39

Theory of operation

Let us assume that pf of the circuit is $\cos\phi$, which is lagging. The phasor diagram for the pf meter connection is as shown below.

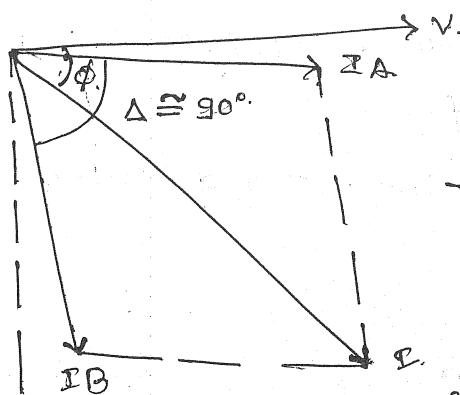


fig - phasor diagram

For the sake of simplicity, it is assumed that the angle $\delta \approx 90^\circ$ & the angle by the pressure coil is also $\Delta \approx 90^\circ$; The deflecting torque on coil A is assumed as 90° ; The deflecting torque on coil A is given by:

$$T_A = kV I_{A\max} \cos\phi \cdot \sin\theta \quad \text{--- (1)}$$

where k = constant V = applied voltage.

I = load current = Supply current

$I_{A\max}$ = maximum value of the mutual ordinate in the coils A & B.

θ = angular deflection of coil A from the plane of reference

ϕ = P.F angle.

Let us consider the torque T_A set in the clockwise direction. The deflecting torque on coil B is

$$\text{governed by } T_B = kV I_{B\max} \cos(90-\phi) \sin(90-\theta) \\ = kV I_{B\max} \sin\phi \cos\theta \quad \text{--- (2)}$$

Now the torque T_B acts in anticlockwise direction.
 Therefore due to the action of two oppositely directed torques, the moving coil comes to rest at position when both the torques are equal.
 Hence at equilibrium $T_A = T_B$.

$$\therefore kVI M_{max} \cos\theta \sin\theta = kVI M_{max} \sin\theta \cdot \cos\theta$$

$$\text{or } \cos\theta \cdot \sin\theta = \sin\theta \cdot \cos\theta$$


$$\text{or } \theta = \phi.$$

i. The deflection of the moving system gives the plane angle of the current.

* phase sequence indicator.

The phase sequence of a three phase supply is the order in which the maximum values of the phase voltages V_R, V_Y, V_B , occur during their operation. The phase sequence of 3-φ supply can be either RYB or RBG. During the synchronization of two different 3-φ AC supplies their phase sequences have to be same. ∴ a phase sequence indicator is used during synchronization. There are two types i) rotating type ii) static type.

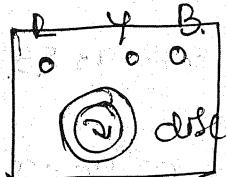* rotating type of phase sequence indicator.



The principle of working of these meters is same as 3-φ IM. The appearance of rotating type of phase sequence

indicator is as shown above. It consists of three coils which are mounted on 120° apart in space. The three ends of coils are brought out & connected to R Y B 39 terminal of the meter.

- ④ The three coils are connected in Star fashion & excited by the 3-φ supply, whose phase sequence is to be determined.
- ⑤ When the supply is given to the three coils, a rotating magnetic field is produced, due to which an emf is generated in the disc which circulates the eddy currents produced in the disc.
- ⑥ Finally the eddy currents interact with the rotating magnetic field & a torque is produced due to which disc starts rotating in a particular direction. The direction of rotation of the disc indicates the phase sequence of the supply.
- ⑦ An arrow is marked on the disc which indicates the direction of rotation. If the direction of rotation is same as mentioned on the disc then the phase sequence is as shown by the terminals of RYB. If the disc rotates in the opposite direction i.e. anti-clockwise direction, the phase sequence of supply must be RBY.

* Weston frequency meter *

- The above fig shows constructional details of weston frequency meter. It consists of two coils A & B which are mounted perpendicular to each other. Each coil is divided into two sections.

④ ⑤ ⑥ 20, 21, 22, 23, & 31, 35, 63, 70, → 220914

- ② A resistance R_A is connected in series with coil A & a inductance L_B is connected in series with coil B.
- ③ An inductance L_A is connected in parallel with coil A & a resistance R_B is connected in parallel with coil B. However the moving system is a soft iron needle.
- ④ There is no controlling force. L is a servo reactance coil which is used to suppress the hysteresis in the air, which is flowing through the meter, thereby reducing the error.

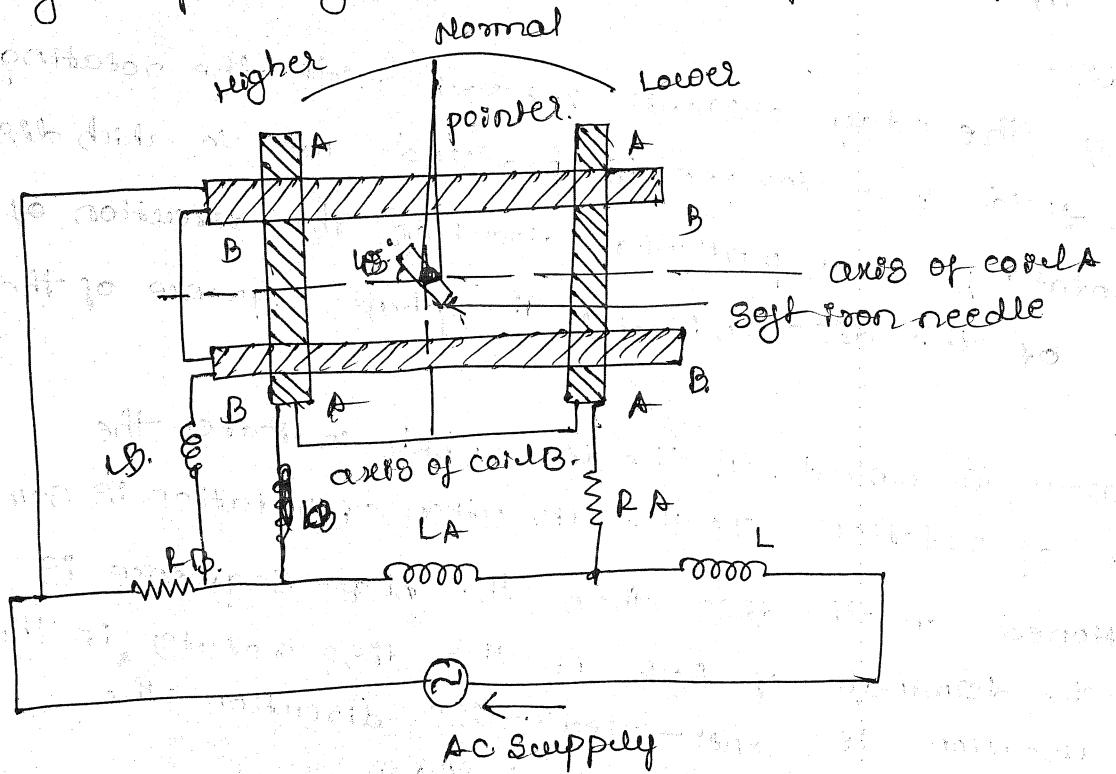


fig - Weston frequency meter.

* Working principle

- ① When the frequency meter is connected across the supply the current will flow in both the coils A & B respectively. & set up the two magnetic fields, which are right angle to each other.

- ② However the strength of magnetic field produced by both the coils depends on magnitude of current flowing through both the coils.
- ③ The values of resistance & inductance in the frequency meter are selected in such a way that, at the normal frequency the voltage drop across L_A & R_B must send equal currents through the coils A & B.
∴ the needle takes a position which is 45° to both the coils & pointer deflects to the centre of scale
- ④ If the frequency is more than a normal value, the reactance of L_A & L_B increases, while the values of R_A & R_B remains same ∴ the voltage impressed on coil A will be more than the voltage impressed on coil B, due to which current in coil A increases & current in coil B decreases
due to this the strength of field produced by coil A will be more than the field produced by coil B, ∴ the pointer deflects to left side where the higher frequency are marked
- ⑤ If the frequency is less than the normal frequency the pointer deflects to right side of the scale where lower frequency are marked By calibrating the scale the deflection of the pointer can be made directly to read the frequency of the supply on scale.

* phase Sequence indicator

ii) static type of phase sequence indicator

The circuit diagram of phase sequence indicator is as shown below

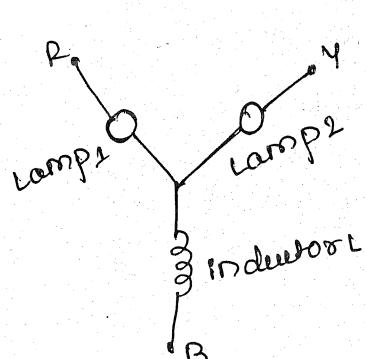


fig-a)

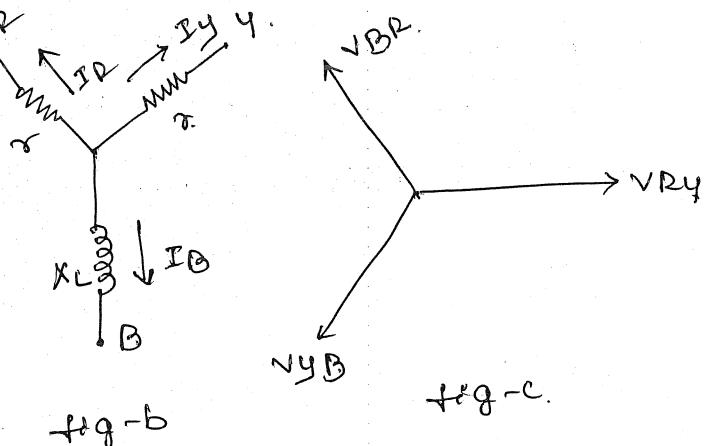


fig-b

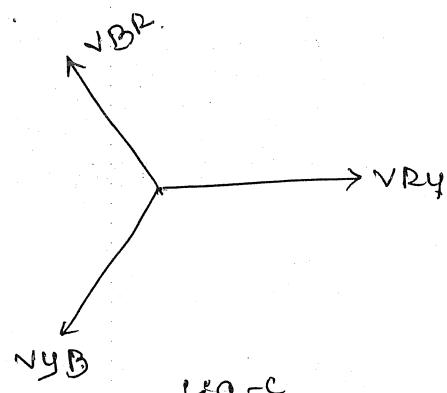


fig-c.

As shown in the above fig if consisting of two lamps & one inductor. When phase sequence is RYB the lamp 1 will glow dim while lamp 2 will glow brightly. When the phase sequence is RBY Lamp 1 will be bright & lamp 2 will glow dim. This phenomena can be analysed as follows

Initially assume that the phase sequence is RYB & the phasor relations of V_{RY} , V_{YB} & V_{BR} are

as shown in fig c

$$\therefore V_{RY} = \sqrt{1+j0} = \sqrt{1}^{\circ}$$

$$V_{YB} = \sqrt{[0.5 - j0.866]} = \sqrt{-120^{\circ}}$$

$$V_{BR} = \sqrt{[-0.5 + j0.866]} = \sqrt{120^{\circ}}$$

$$\begin{aligned} &\cos 0^{\circ} + j \sin 0^{\circ} \\ &\cos 120^{\circ} + j \sin 120^{\circ} \\ &\sin(120^{\circ}) \end{aligned}$$

Now let us assume the direction of current as shown in fig b.

as shown in fig b.

$$i.e. IR + I_y + I_B = 0 \quad \text{--- (1)}$$

from the fig(b) & fig(c) it is clear that

$$v_{RY} + I_y R - IR_y = 0 \quad \text{--- (2)}$$

$$v_{YB} + IR_j X_L - I_y R = 0 \quad \text{--- (3)}$$

By solving the equations (2) & (3) we get

$$\frac{IR}{I_y} = 1 + \frac{(1 + j2X_L/\pi)}{(v_{YB}/v_{RY}) - jX_L/\pi}$$

$$\text{But we have } \frac{v_{YB}}{v_{RY}} = -0.5 - j0.866$$

$$v_{RY}$$

\therefore If the inductor is designed such that $X_L = R$ at the line frequency we get $IR/I_y = 0.27$

\therefore the voltage drop across Lamp 1 is 27% that of across Lamp 2 \therefore if the phase sequence is RYB lamp ① glows dimly while lamp ② glows brightly

Now if the inductor is replaced by the capacitor the value is $IR/I_y = 3.7$ it means that lamp ① glow brightly & lamp ② glow dim if the phase sequence is RBY

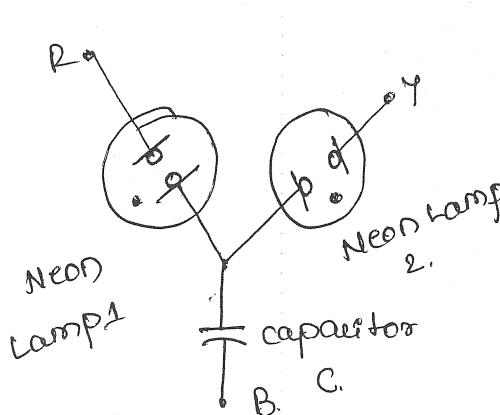


fig-a)


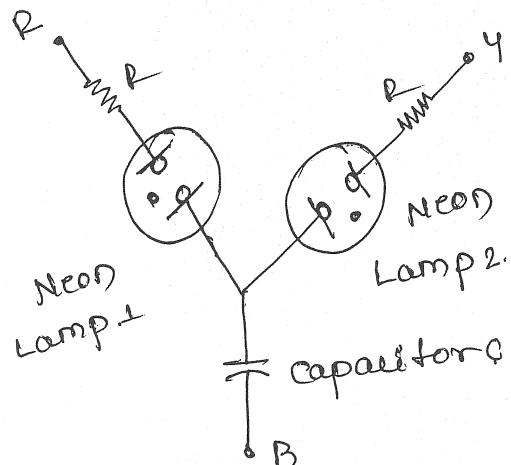


fig-b)

Another similar phase sequence indicator consists of two neon lamps & a capacitor as shown in fig (a). As shown in fig (b) a resistor is connected in series with neon lamp to limit the current.

When the phase sequence is RYB, lamp 1 will glow & lamp B will be dark, this is because when neon lamps are used as indicators, the lamp which has a lower voltage will not glow at all, as the voltage across it is lower than the breakdown voltage of the lamp.

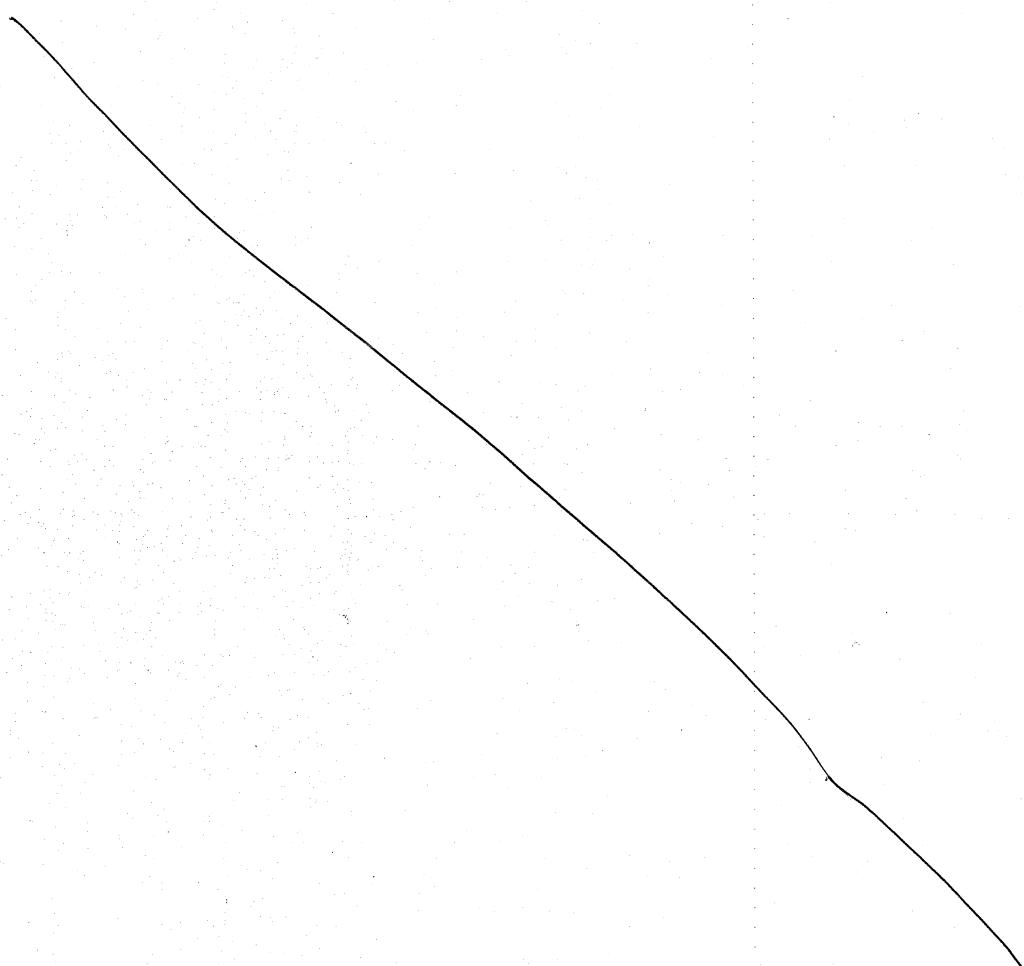

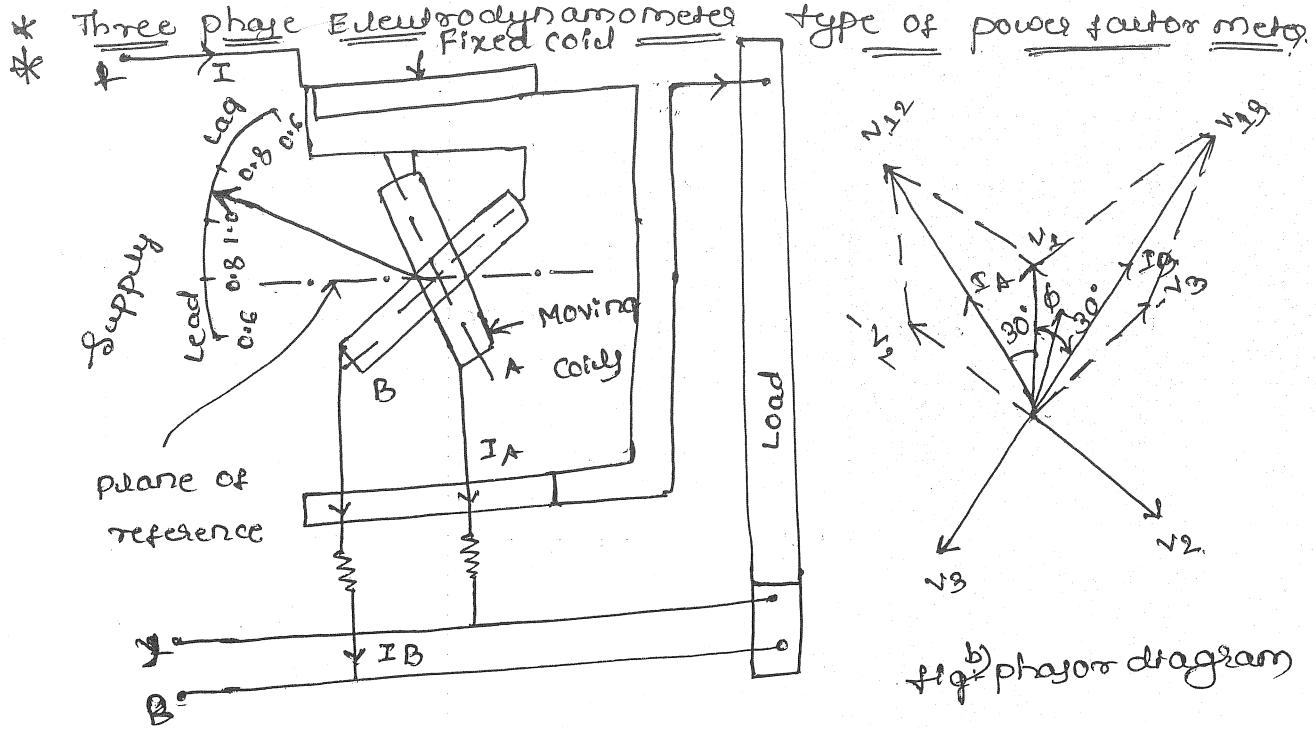


fig-a) 3 phase dynamometer type of power factor meter

fig-b) phasor diagram

of 3-φ pf meter


The above fig-a) shows construction of electrodynamic.

meter type 3-φ power factor meter, this meter is used for balanced loads

* As shown above the two moving coils are arranged in such a way that the angle between both moving coils is 120° , both the coils are connected across two different phases of supply.

* The coil A is connected between R and Y while coil B is connected by R and B phase as shown above.

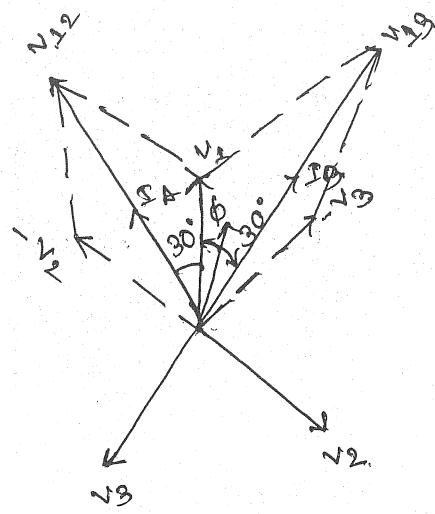* The phase difference between the currents through two moving coils is automatically created due to phase difference between the supply itself hence external R and L are not required as in case of single phase circuit.



- * the moving coils A and B are connected to the supply wires Y and B through series resistance.
- * the voltage across coil A is V_{12} and current I_A is in phase with V_{12} . & voltage across coil B is V_{13} & current I_B is in phase with V_{13} as coil circuit is resistive in nature.

Let ϕ = phase angle of circuit

Θ = angular deflection from the plane of reference.

$$V_1 = V_2 = V_3 = V$$

Torque acting on coil A is

$$\begin{aligned} T_A &= k V_{12} I M_{\max} \cos(30^\circ + \phi) \cdot \sin(60^\circ + \Theta) \\ &= \sqrt{3} k V I M_{\max} \cos(30^\circ + \phi) \sin(60^\circ + \Theta) \end{aligned}$$

Now torque acting on coil B is

$$\begin{aligned} T_B &= k V_{13} I M_{\max} \cos(30^\circ - \phi) \cdot \sin(120^\circ + \Theta) \\ &= \sqrt{3} V I M_{\max} \cos(30^\circ - \phi) \sin(120^\circ + \Theta) \end{aligned}$$

Torque T_A and T_B act in the opposite direction & moving coil come to rest when $T_A = T_B$

$$\therefore \cos(30^\circ + \phi) \sin(60^\circ + \Theta) = \cos(30^\circ - \phi) \sin(120^\circ + \Theta)$$

$$\therefore \Theta = \phi$$

\therefore the angular deflection of the pointer from the plane of reference is equal to the phase angle of the circuit to which meter is connected

* Three phase energy meter

In 3- ϕ , 4 wire system the measurement of energy is carried out by 3- ϕ energy meter.

- For 3- ϕ , 3 wire system the energy measurement is carried out by two element energy meter.
- 1) Three element energy meter
- 2) two element energy meter.

* Three Element Energy meter

Three Element Energy meter consists of three elements, The construction of an individual element is similar to that of a Single phase energy meter.

- The pressure coils are denoted as P_1, P_2, P_3 , the current coils are denoted as $C_1, C_2 \& C_3$
- The coils are arranged in such a manner that the net torque produced is sum of the torque due to all the three elements.
- The current coils are connected in series with the line and a neutral
- one unit of three ^{phase} element is always cheaper than three units of 1- ϕ energy meter. But due to the interaction of eddy currents produced by one element with the flux produced by another element, there may be errors in the measurement by 3- ϕ energy meter, Such errors are reduced by suitable adjustment

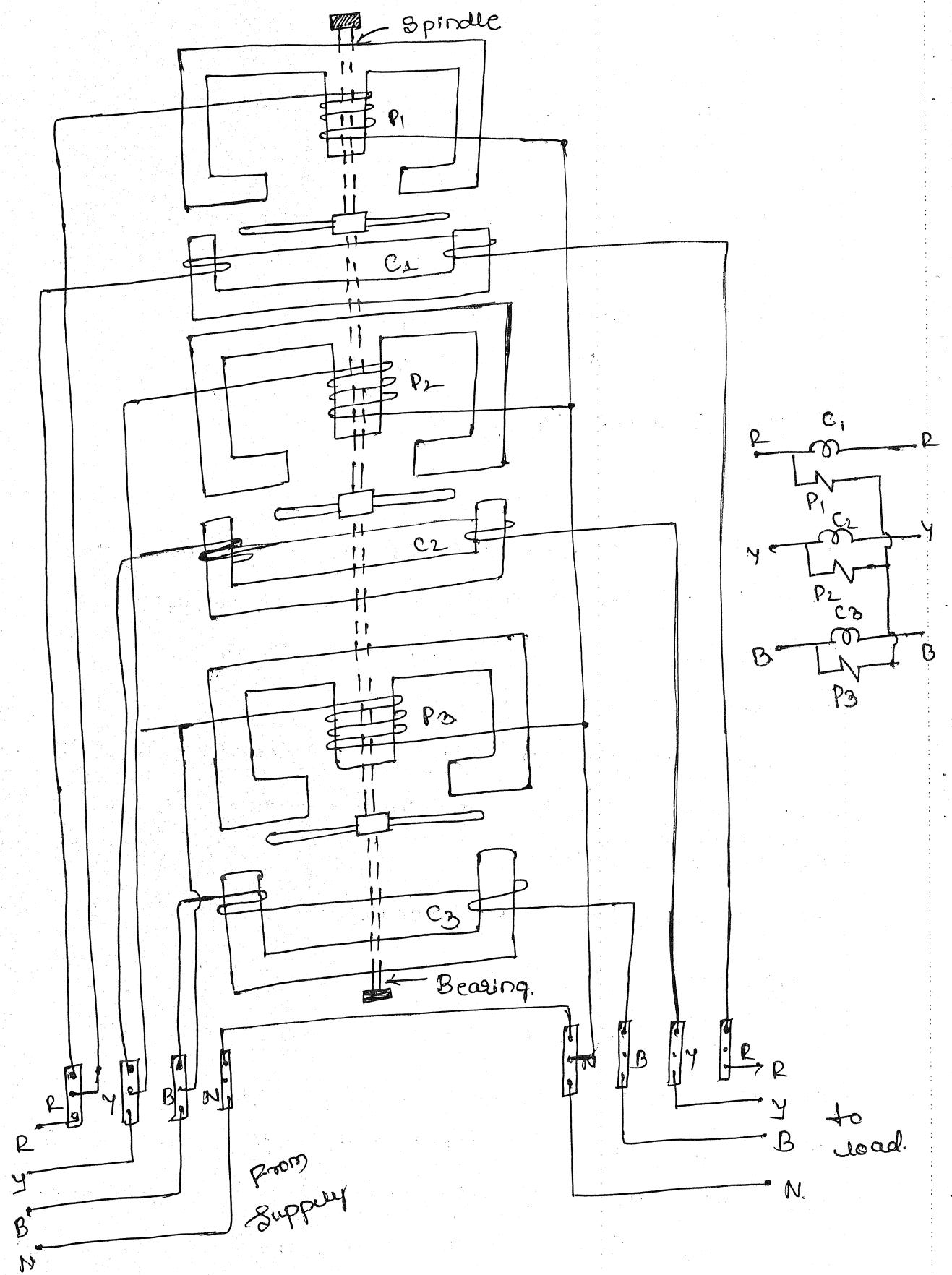


Fig- three element Energy meter.

* Two element Energy meter.

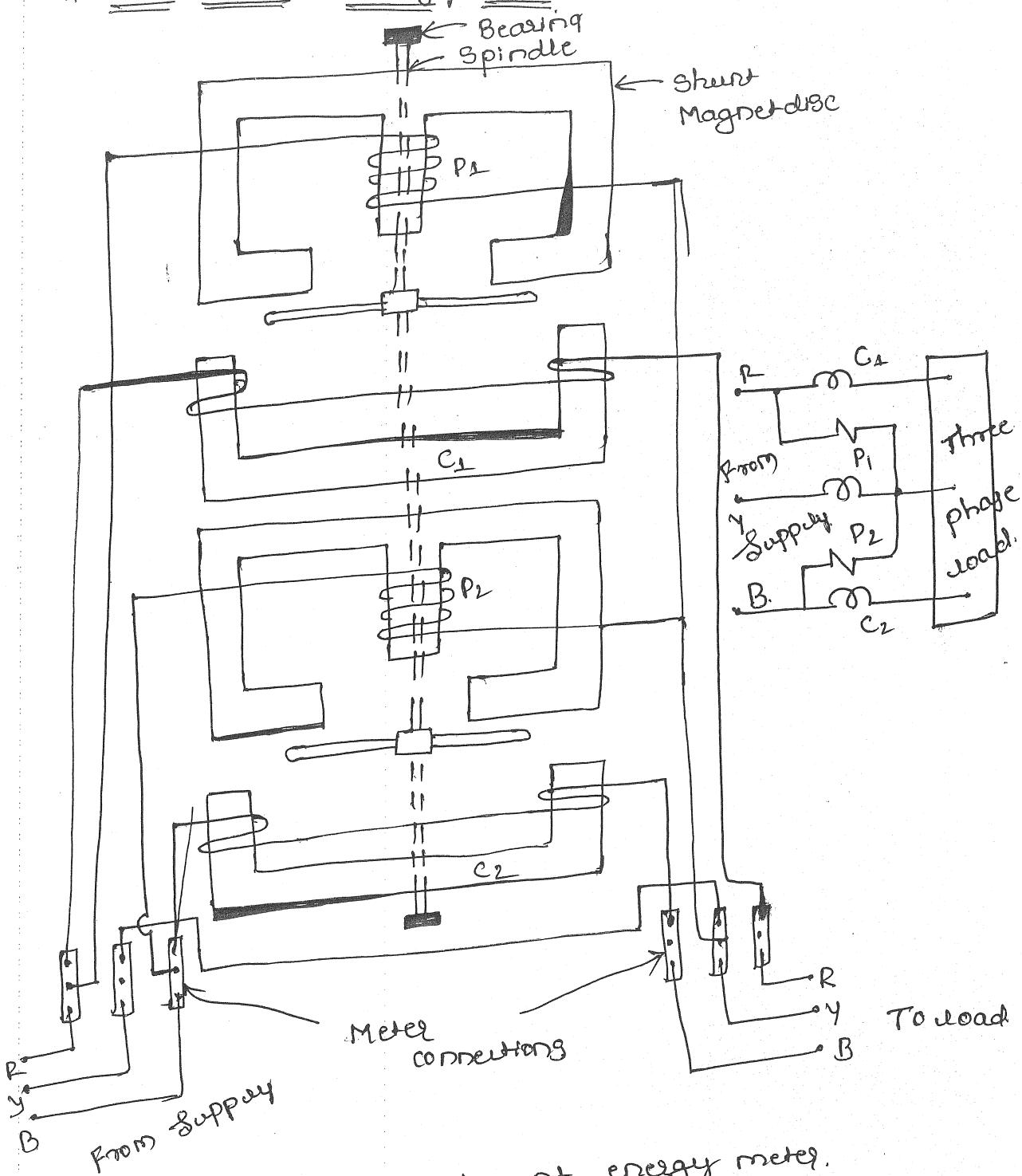


fig - Two element energy meter.

The above fig shows two element energy meter.

This energymeter is used for three phase, three wire systems. The shunt magnet forms the pressure coil & sleeve magnet forms current coil of meter.

- * The pc is connected in parallel and current coils are connected in series. The connections are similar to that of two wattmeter for measurement of power in 3phase 3wire System.
- * The total torque on the registering is applied to moving system, which is the torque of the individual elements.
- * The rotation of light aluminium disc gives the total power consumption for particular time.

Module - 3

* Extension of Instrument Range.

The range of any electrical instrument depends on how much current can be safely passed through the coil of instrument, which act as steady of current to the instrument.

* Normally the moving coil instruments such as ammeter & voltmeter are designed to carry a maximum current of 50mA & withstand a voltage of 50mV.

* However for the measurement of larger currents & voltages the ranges of these instruments are increased.

* Basically there are four methods for the extension of instrument ranges.

- i) By using shunts to increase the range of dc ammeter
- ii) By using multipliers to increase the range of dc voltmeter
- iii) By using current transformer to increase the range of ac ammeter.

- iv) By using potential transformer to increase the range of ac voltmeter.

* Shunts

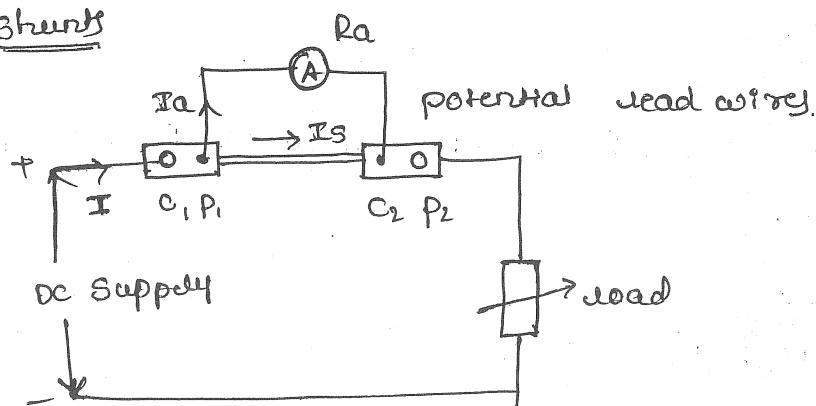


fig -

The connection diagram of shunt is fig with a low range ammeter to measure large current through the circuit is as shown in the above fig.

- * As shown in the above fig, a shunt is a very low resistance connected in parallel with the coil circuit of ammeter in order to extend its range.
- * By introducing a shunt, larger currents can also be measured using a low range ammeter.
- * A shunt has four terminals to coil terminals $C_1 \& C_2$, & two potential terminals $P_1 \& P_2$. The two coil terminals are connected in series with the main circuit & they have high coil carrying capacity.
- * The two potential terminals have low coil carrying capacity & across these terminals a low range ammeter is connected.

Let us consider an ammeter A of resistance R_A which includes the resistance of potential lead wires & it carries a current of I_a .

From the above fig, let I_g = current flowing through the shunt.

$$I_a R_A = I_g R_S$$

$$R_S = \frac{I_a R_A}{I_g}$$

$$= \frac{I_a R_A}{(I - I_a)} \text{ divide N & KOT by } I_a. \quad \& \quad R_S = \frac{I_g}{I - I_a} \cdot N$$

$$\therefore R_S = \frac{R_A}{\left(\frac{I}{I_a} - 1\right)}$$

$$R_S = \frac{1}{N-1} R_A \quad \text{where } N = \frac{I}{I_a} = \text{multiplying factor of shunt}$$

$$\therefore R_g = \frac{R_a}{(N-1)} \quad \text{--- (1)}$$

The above can also be written as

$$N = 1 + \frac{R_a}{R_g}$$

\therefore It is clear that to increase the range of ammeter N times, the shunt must have a resistance of R_g .

* Shunts of AC ammeter

A shunt is usually used to extend the range of DC ammeter but they are also used to extend the range of AC ammeter also.

When a shunt is used to extend the range of an AC ammeter, the inductances of both shunt & ammeter is taken into consideration.

If L_a & L_g be the inductances of ammeter along with shunt & that of the shunt, the ratio of two impedances is given by

$$\frac{Z_a}{Z_g} = \frac{\sqrt{R_a^2 + \omega^2 L_a^2}}{\sqrt{R_g^2 + \omega^2 L_g^2}} \quad \text{--- (2)}$$

The above ratio must be constant for all frequencies, so that the emf dev bias ammeter & shunt remains constant for all frequencies. However this is possible only when the time constants of the ammeter & the shunt are same

$$\text{i.e } T_a = T_g$$

$$\text{ie } L_a/R_a = L_g/R_g = k.$$

we know that the multiplying factor of shunt is

$$N = \frac{I_a + I_s}{I_a} = \frac{I_a + I_s}{I_a} = 1 + \frac{I_s}{I_a} = 1 + \frac{V_z s}{V_{za}}$$

$$\therefore N = 1 + z_a/z_g$$

$$= 1 + \frac{\sqrt{R_a^2 + \omega^2 L_a^2}}{\sqrt{R_g^2 + \omega^2 L_g^2}}$$

$$= 1 + R_a \frac{\sqrt{1 + \omega^2 (L_a/R_a)^2}}{R_g \sqrt{1 + \omega^2 (L_g/R_g)^2}}$$

$$N = \frac{1 + R_a \sqrt{1 + \omega^2 k^2}}{R_g \sqrt{1 + \omega^2 k^2}} = 1 + R_a/R_g$$

$N = 1 + R_a/R_g$ \therefore the above equation shows that a shunt can also be used to extend the range of an ac ammeter.

* Multiplexer

A multiplexer is a non-inductive high resistance used to extend the range of a dc voltmeter.

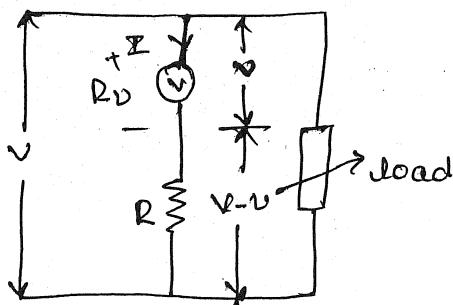


Fig.

Let us consider a low range voltmeter whose range has to be increased upto V volts, which is connected in series with the multimeter.

Let R be the resistance of multimeter which is connected in series with the voltmeter to extend its range.

Let v be the applied voltage.

R_v - resistance of the voltmeter

$I = \text{current through the voltmeter}$

$$\text{Then } v = IR_v \quad \& \quad R = \frac{V-v}{I}$$

$$\Rightarrow RI = V-v \quad \text{divide LHS \& RHS by } v$$

$$\frac{RI}{v} = \frac{V}{v} - 1 = N - 1$$

Where $N = \frac{V}{v}$ = multiplying factor of multimeter

$$\frac{RI}{v} = N - 1 \quad | \quad \text{where } v = IR_v$$

$$\therefore \frac{RI}{IR_v} = N - 1$$

$$R/R_v = N - 1$$

$$\therefore N = 1 + R/R_v \quad \text{or } R = R_v(N-1) \quad \text{--- (1)}$$

Hence to increase the range of voltmeter by N times, the multimeter must have the resistance of $(N-1) R_v$.

Multimeter for A.C voltmeter

A multimeter is used to extend the range of the voltmeter & they can also be used to extend the

ranges of AC voltmeter, when multiplier is used to extend the range of AC voltmeter it has to satisfy the condition that the total impedance of the voltmeter and the multiplier circuit must be constant at all frequencies.

To satisfy the above condition, the inductance of the multiplier should be very small, so that the total inductance of the whole circuit will be small.

Let L = inductance of the voltmeter, then the current through the voltmeter is given by:

$$I = \frac{V}{\sqrt{(R+R_v)^2 + \omega^2 L^2}}$$

The voltage drop across the voltmeter is given by

$$v = I \sqrt{R_v^2 + \omega^2 L^2}$$

$$\text{ie } v = \frac{V \sqrt{R_v^2 + \omega^2 L^2}}{\sqrt{(R+R_v)^2 + \omega^2 L^2}}$$

$$\frac{V}{v} = \frac{\sqrt{(R+R_v)^2 + \omega^2 L^2}}{\sqrt{R_v^2 + \omega^2 L^2}} = N \text{ the multiplying factor}$$

* A PMMC instrument gives a full scale deflection of 200mV & 20mA. Explain how the above instruments can be used i) a voltmeter of range 0-300V
ii) an ammeter of 0-100A range.

\Rightarrow i) As voltmeter \rightarrow Let R be the resistance connected

In Series with the small range voltmeter.

$$\therefore V = V + IR$$

$$\text{ie } 300 = 100 \times 10^{-3} + 20 \times 10^{-3} R$$

$$\therefore R = 14995 \Omega$$

ii) As ammeter

Let R_g be the resistance of the shunt connected across the ammeter.


$$\begin{aligned}\therefore R_g / I_g &= I - I_a \\ &\approx 100 - 20 \times 10^{-3} \\ &\approx 99.98\Omega\end{aligned}$$

$$\& I_a / R_g = I_g R_g$$

$$\begin{aligned}\therefore R_g &= \frac{I_a R_a}{I_g} \\ &\approx \frac{20 \times 10^{-3} \times 5}{99.98} \\ &\approx 0.001 \Omega\end{aligned}$$

$$\therefore R_g = 0.001 \Omega$$

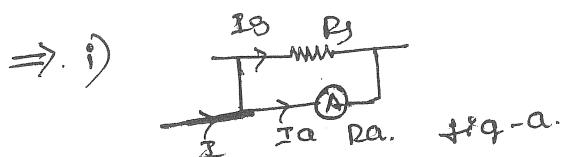* A moving coil instrument has a resistance of 5 Ω & it gives full scale reading of 50mA. calculate i) the shunt resistance required to increase the range to 200A ii) the series resistance required to type it as a voltmeter of range 0-750V iii) power consumed in both the cases.



Given $I = 200A$
 $I_a = 50mA$

$$\therefore I_g = I - I_a \\ = 200 - 50 \times 10^{-3} \\ = 199.95 A$$

We know that $I_a R_a = I_g R_g$.

$$\therefore R_g = \frac{I_a R_a}{I_g} = \frac{50 \times 10^{-3} \times 5}{199.95}$$

$$\therefore R_g = 0.0012503 \Omega$$

$$R_g = \underline{1.2503 m\Omega}$$

$$\begin{aligned} \text{power consumed in the shunt} &= I_g^2 R_g \\ &= (199.95)^2 \times 1.2503 \text{ mA} \\ &= 49.99 W \end{aligned}$$

\therefore the power consumed by the voltmeter is small hence it is neglected.

ii) voltmeter.

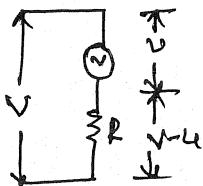


fig-b)

the total voltage is given by

$$V = v + IR$$

$$750V = IRv + IR$$

$$= 50 \times 10^{-3} \times 5 + 50 \times 10^{-3} R$$

$$\therefore R = 14995 \Omega$$

∴ the power consumed by the scale

$$I^2 R = (50 \times 10^{-3})^2 \times 14995$$

$$= \underline{37.4875 W}$$

* Instrument Transformer

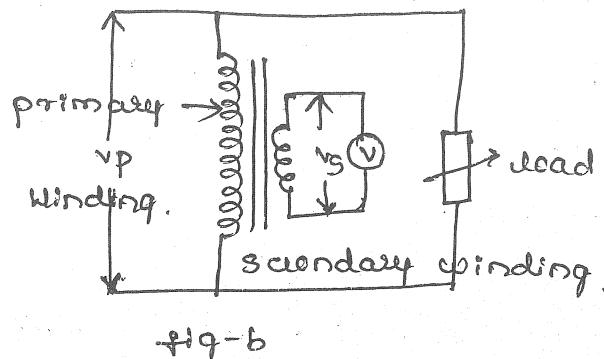
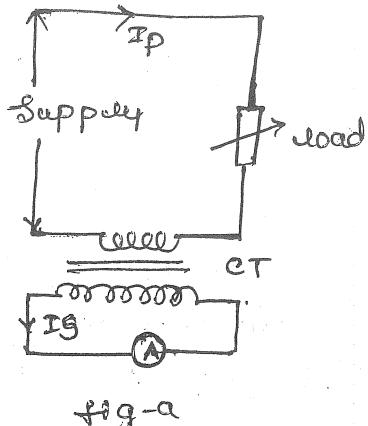


fig-b

Instrument transformers are used to extend the range of AC instruments.

- * If the \times ter is used to extend the range of AC ammeter it is known as current Transformer.
- * If the \times ter is used to extend the range of AC voltmeter it is known as potential Transformer.
- * Instrument transformers are used to measure high voltages and high currents along with low range ammeter and voltmeter respectively.
- * fig-a, shows how a CT is used to measure large current along with low range ammeter
- * The primary winding of CT consisting of only few no of turns which are connected in series with load through which large current I_p flows
- * The secondary winding of CT consisting of large no of turns which is connected to an ammeter through which a small current I_s is flowing. The I_p is measured by

$$I_p = n I_s \quad \text{where } n = N_s / N_p = \text{turns ratio.}$$

N_s = no of turns in the Secondary winding

N_p = no of turns in the primary winding.

- * fig b, shows how a potential transformer is used to measure large voltage using low range voltmeter
- * The primary winding of PT consisting of large no turns N_p which is connected across the large voltage which is to be measured.
- * However the secondary winding consists of only few no of turns N_s across which a low range voltmeter is connected, whose range is enough to measure the secondary voltage V_s .

Now the value of N_p is $N_p = N_s \frac{V_s}{V_p} = \frac{N_s}{N_p} = \text{turns ratio}$

* Advantages of Instrument transformer

- 1) When IT's are used to extend the range of an instrument their readings do not depend on the constant R, L & C as in case of shunts and multipliers.
- 2) The CTs are standardized at 5A secondary winding current & voltage & they are standardized to the 110V secondary winding voltage which are very moderate ratings. Thus a 5A ammeter can measure upto 1000A using 1000/5A CT. Similarly a 110 voltmeter can measure voltage upto 100kV using 100kV/110V PT. Hence very cheap & moderate rating instruments are used to measure large current & large voltage.
- 3) As secondary windings of CT & PT are standardized it is possible to standardize the instruments around these ratings & replacement of IT's is easy.
- 4) The low rating secondary windings of IT's

are electrically isolated from high rating primary windings.

5) There is low power consumption in the metering circuit.

6) Several instruments can be operated using a single instrument transformer.

* Ratios of Instrument Transformer

Three different ratios are defined for ITS.

i) Transformation Ratio (R) [Actual Ratio]

The transformation ratio of an IT is defined by it is the ratio of the magnitude of the actual primary phasor to the magnitude of the actual secondary phasor.

$$\text{Transformation Ratio} = \frac{\text{primary phasor}}{\text{secondary phasor}}$$

$$TR = \frac{\text{Magnitude of the actual primary winding ch}}{\text{magnitude of the actual secondary ch}}$$

$$\text{e.g. CT} = I_p / I_s$$

$$\text{for PT} = V_p / V_s$$

$$= \frac{\text{Magnitude of actual primary ch voltage}}{\text{Magnitude of actual secondary ch voltage}}$$

$$= \frac{V_p}{V_s}$$

ii) Nominal Ratio :- (k_n)

The nominal ratio of an instrument transformer is defined by the ratio of rated primary ch current or voltage to the rated secondary ch current or voltage.

$$k_n = \frac{\text{rated primary ch}}{\text{rated secondary ch}}$$
 for CT.

$$k_v = \frac{\text{rated primary winding voltage}}{\text{rated secondary winding voltage}} \quad \text{for PT.}$$

* Turns Ratio (n)

The turns ratio of an instrument transformer is defined as

$$\text{for CT} \quad n = \frac{\text{NO of turns in the secondary coil}}{\text{NO of turns in the primary coil}} \text{ ie } N_s/N_p$$

$$\text{for PT} \quad n = N_p/N_s$$

* Ratio correction factor (RCF)

The RCF of an instrument transformer is the ratio of its transformation ratio to its nominal ratio. $RCF = R/k_v$ or $R = RCF \times k_v$

* Burden of an IT

The burden of an IT is the permissible load across the secondary winding terminals expressed in volt-Amperes at the rated secondary terminal voltage or rated secondary current, with errors not exceeding the limits for particular class.

$$\text{Total secondary winding burden} = \frac{(\text{secondary coil induced voltage})^2}{\text{total impedance of secondary circuit.}}$$

$$\text{* Secondary winding burden due to load} = \frac{(\text{secondary coil terminal voltage})^2}{\text{impedance of the load on secondary winding.}}$$

* Current Transformer

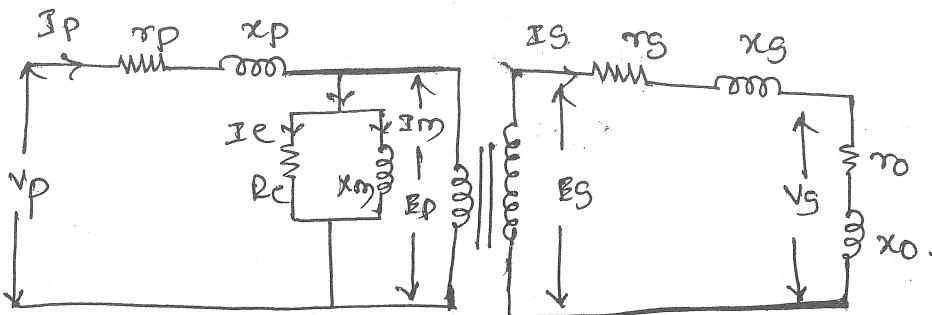


fig-a equivalent circuit of CT

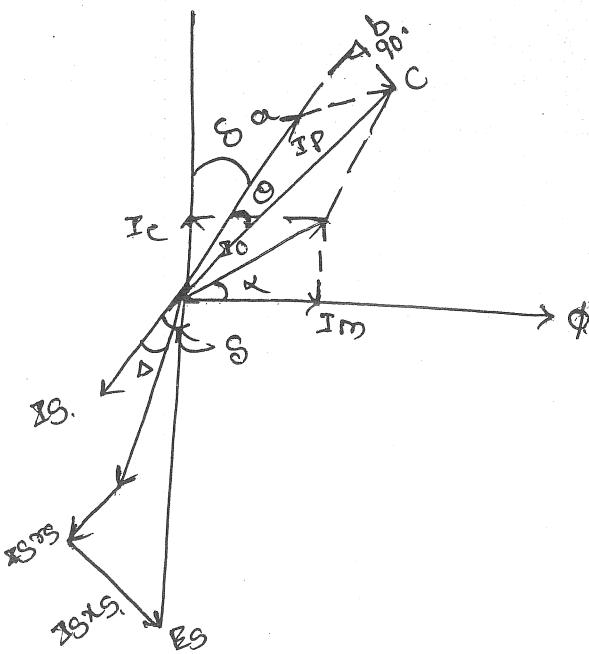


fig-b) vector diagram of CT

$$n = \text{turns ratio} = \frac{\text{no of secondary turns}}{\text{no of primary turns}} = \frac{N_s}{N_p}$$

r_s, x_s = resistance & reactance of the secondary winding respectively.

r_p, x_p = resistance & reactance of the primary winding respectively

N_p = primary applied voltage

E_p, E_s = primary & secondary induced voltage respectively

V_S = Secondary terminal voltage

ϕ = flux of X_{TE}

I_0 = exciting current

I_m = magnetizing component of I_0

I_e = core loss component of I_0

θ = phase angle of X_{TE}

S = Angle b/w E_S & I_S ie $\tan^{-1} \left[\frac{x_g + x_e}{r_g + r_e} \right]$

Δ = phase angle of the secondary load circuit
 $= \tan^{-1} x_c/r_c$

α = angle b/w I_0 and flux ϕ

$$* R = \frac{I_P}{I_S} = n + \frac{I_0}{I_S} \sin(\alpha + S)$$

$$= n + I_0/I_S \sin \alpha \cdot \cos S + \cos \alpha \sin S$$

$$= n + I_0 \sin \alpha \cdot \cos S + I_0 \cos \alpha \sin S$$

$$R = n + \frac{I_e \cos S + I_m \sin S}{I_S}$$

II.

* phase angle θ

$$\theta = \frac{180}{\pi} \left[\frac{I_m \cos S - I_e \sin S}{n I_S} \right] \text{ degrees}$$

* Errors in current transformer

i) Ratio error ii) phase angle error

$$\text{Ratio error} = \frac{\text{Nominal ratio} - \text{Actual ratio}}{\text{Actual ratio}} = \frac{k_n - R}{R}$$

$$\therefore \text{ratio error} = \frac{k_n - R}{R} \times 100$$

* The phase angle is given by

$$\theta = \frac{180^\circ}{\pi} \left[\frac{I_m \cos \phi - I_e \sin \phi}{NIS} \right] \text{ degrees.}$$

The instrument burden is largely resistive with negligible inductance and hence θ is very small.

If we will get the equation for transformation Ratio

$$R_{IS} = R = N_t I_e / N_S \quad & \theta = \frac{180^\circ}{\pi} \left[\frac{I_m}{NIS} \right] \text{ degrees}$$

from the above equations it is clear that the ratio error is mainly due to the iron loss component I_e of exciting current I_0 & phase angle error is mainly due to the magnetizing component I_m of exciting cln I_0 .

* Design features of current transformer

1) Number of primary Amper-turns

In order to keep ratio and phase angle errors of a current transformer as small as possible, it is necessary that the exciting current I_0 and hence, the exciting amper-turns $N_p I_0$ must be a small proportion of the total Number of primary amper-turns $N_p I_p$. The primary amper-turns should be at least of the order 500 to 1000 to give accurate measurements.

When low loss alloy such as mu metal is used as the core material, the cln through the bar primary of CT may be at least 100A & it gives accurate measurements.

2) core:- To minimize the exciting cln I_0 to reduce the errors in the CT. The core must have low reluctance

Small iron loss. The flux density in the core may be limited to $0.1 \text{ wb}/\text{m}^2$. The three forms of core normally used for the construction of core of CT are 1) rectangular type 2) shell type 3) ring type.

* The rectangular type is built of L shaped punchings. The windings are placed on one of the shorter limbs, with primary normally wound over the secondary. This type of core structure is suitable for high voltage work.

* In shell type the windings are placed on central limb & hence they provide considerable protection to the windings.

* In ring type of core of core, the secondary winding is uniformly distributed over the core & the primary winding is single bar.

* Windings :- The secondary leakage resistance of CT increases its ratio error and leakage resistance should be kept as small as possible. The secondary leakage resistance can be reduced by placing the windings close together.

* Insulation :- The coils of CT are separately wound & they are insulated from tape and varnish for lower line voltages. However the windings are wound over one another on cylinders of bakelite and mounted on a sheet steel tank filled with transformer oil. For higher voltage the transformer enclosed in a tank, which is filled with insulating compound.

* Turns compensation

Turns compensation is used in most current transformers in order to obtain the transformation ratio (k)

is nearly equal to nominal ratio (k_n), if the turns ratio is made equal to nominal ratio of the CT then we get the equation for transformation ratio of CT is $R = n_t I_s / I_g$ where n_t = turns ratio.

from the above equation we find that by reducing the no of secondary turns by 1% will reduce R.

* open circuiting the secondary circuit of current transformer

In a current transformer, the number of primary ampere-turns is a fixed quantity & it is not reduced when the secondary circuit is opened, as in case of power transformer. ∴ if the secondary circuit of CT is opened, when CT is flowing in the secondary circuit, A very high flux density is produced in the core causing the absence of demagnetizing ampere turns.

This high flux density results in increased induced voltage in the secondary winding, which may damage the insulation & cause danger to operator. ∴ the secondary of CT should never be open excepted when the current is flowing through the primary winding. //

* A 1000/5A, 50Hz current transformer has a bar primary and a rated secondary burden of 15VA. The secondary winding has 185 turns and a leakage reactance of 0.96mH. The load burden is purely resistive. At rated

load, the magnetisation mmf is 20A and core loss excitation is 12A. Find the ratio and phase angle errors.

$$\Rightarrow Z_S = \frac{E_S}{I_S} = \frac{E_S I_S}{I_S^2} = \frac{15}{5^2} = 0.6 \Omega = R_S \quad (\because \text{Secondary burden is purely resistive})$$

$$X_S = 2\pi \times 50 \times 0.96 \times 10^{-3}$$

$$X_S = \underline{0.3 \Omega}$$

$$\delta = \sin^{-1} \frac{X_S}{R_S} = \sin^{-1} \frac{0.3}{0.6} = \sin^{-1} 0.5$$

$$\therefore \sin \delta = 0.5 \quad \text{and} \quad \cos \delta = \sqrt{1 - 0.5^2} = 0.866.$$

$$n = N_S / N_P = 195 / 1 = 195 \quad k_n = \frac{1000}{5} = 200.$$

$$I_m = \frac{20}{1} = 20A, \quad \text{and} \quad I_e = \frac{12}{1} = 12A$$

$$R = n + I_e \frac{\cos \delta + i m \sin \delta}{i S} = 195 + \frac{12 \times 0.866 + 20 \times 0.5}{5}$$

$$= 195 + 4.0784$$

$$= \underline{199.0784}$$

$$\therefore \therefore \text{Ratio error} = \frac{k_n - R}{R} \times 100 = \frac{200 - 199.0784}{199.0784} \times 100 = 0.463\%$$

$$\theta = \frac{180}{\pi} \left[\frac{I_m \cos \delta - I_e \sin \delta}{n S} \right] \text{ degrees.}$$

$$= \frac{180}{\pi} \left[\frac{20 \times 0.866 - 12 \times 0.5}{195 \times 5} \right] \text{ degrees}$$

$$= 0.665^\circ = 89^\circ 31' \cancel{\cancel{\cancel{\parallel}}}$$

* Theory of potential Transformer

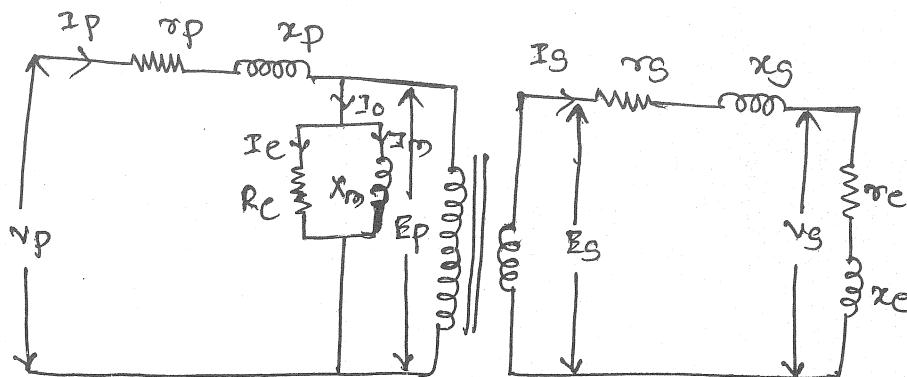


fig-a) equivalent circuit of PT

The above fig shows equivalent circuit diagram of PT

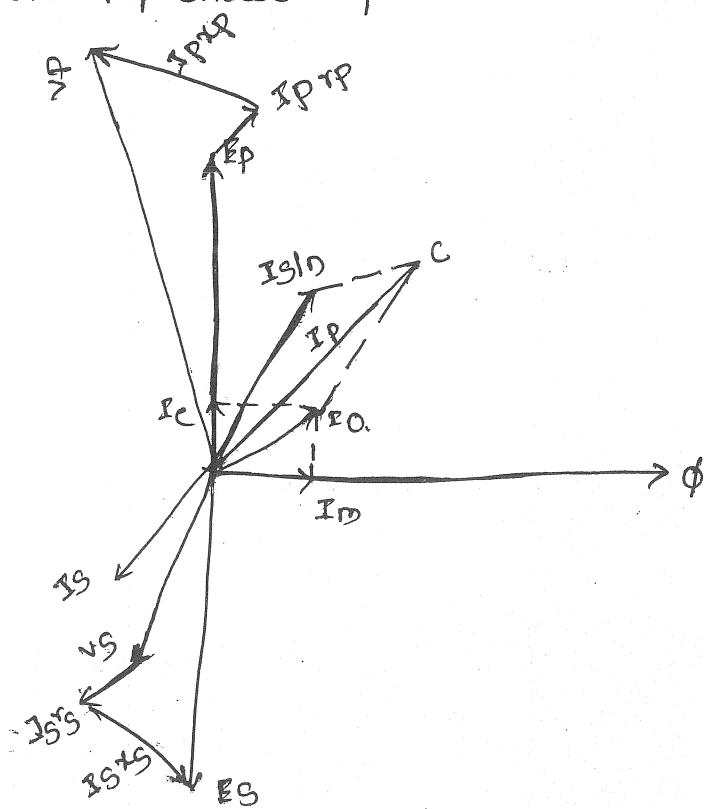


fig-b) phasor diagram of PT

ϕ = Working flux in the core of the transformer.

I_0 = exiting current or no-load current

I_m = Magnetising component of exiting current

I_e = core loss component of exiting cb.

v_p = primary applied voltage

E_p = primary induced voltage

E_s = Secondary induced voltage

V_s = Secondary terminal voltage

N_p, N_s = primary & secondary winding turns respectively

r_p, x_p = resistance & reactance of primary wdg
respectively,

r_s, x_s = resistance & reactance of secondary wdg
respectively

r_e, x_e = resistance & reactance of load respectively

Δ = phase angle of the secondary load circuit

$$= \tan^{-1} x_e/r_e$$

* Expression for actual ratio (R)

$$\text{Turns ratio } n = N_p/N_s = E_p/E_s$$

$$R = \frac{V_p/V_s}{n} = n + n \frac{r_s(\cos \Delta + x_s \sin \Delta) + I_e r_p + I_m x_p}{V_s}$$

$$R - n = n \frac{r_s(\cos \Delta + x_s \sin \Delta) + I_e r_p + I_m x_p}{V_s}$$

$$\text{where } R_g = r_s + \frac{r_p^2}{n^2}$$

$$x_g = x_s + \frac{x_p^2}{n^2}$$

$$\text{*phase angle } \theta = \frac{I_s}{V_s} (x_s \cos \Delta - r_s \sin \Delta) + \frac{I_e x_p - I_m x_p}{n V_s} \text{ radian}$$

$$\frac{x_p}{n^2} = x_g \quad \frac{r_p}{n^2} = R_g$$

* Reduction of errors in potential transformer.

Both ratio error & phase angle error can be minimized in p.t by making certain modifications in the design of P.T.

- 1) Reduction of magnetizing (I_m) & iron loss components of exciting current (I_0).

$$R-n = n \cdot g (R_s \cos \Delta + X_s \sin \Delta) + I_{eP} + I_m^2 p.$$

vs.
from the above equation, it is clear that R depends on secondary current I_S , magnetizing current I_m & iron loss component of exciting current. Hence ratio error can be minimized by reducing I_m & I_e , which can be achieved by using short magnetopath, good quality of core material, & suitable precaution in the assembly of the core.

- 2) By reducing the resistance & leakage reactance

\Rightarrow the resistances of windings can be reduced by using thick conductors & by usage of small length of feed. The leakage reactance can be reduced by reducing the leakage fluxes, & reduced leakage fluxes can be obtained by placing the windings as close as possible.

- 3) Turns compensation

At the no-load condition $I_S = 0$, the actual ratio

exceeds the turns ratio (N) by the amount $I_{eP} + I_m^2 p$ vs
Hence in order to reduce the ratio error, the secondary

turns must be reduced such that the actual ratio (R) must be equal to nominal ratio (k_N)

40

* Characteristics of potential transformer

1) effect of secondary burden (VA)

With increase in the secondary burden secondary current increases which leads to increase of primary current. Hence winding voltage drop will increase on both sides of PT [i.e. Both secondary & primary winding voltage]. ∴ for the given supply voltage v_p , the value of load voltage v_S decreases & the ratio increases. [$\because R = N \propto \frac{1}{v_S}$] Ratio error increases & it becomes more negative due to the secondary burden.

2) effect of p.f on secondary burden

If the p.f of the secondary burden is reduced then the angle Δ increases & which makes I_p to shift towards to I_o . The voltage v_p comes closer to v_S , with E_p & E_S respectively which results in increase of v_p relative to E_p . but anyhow supply voltage v_p is constant ∴ E_p is gets reduced. Similarly the load voltage v_S is reduced relative to E_S . ∴ the transformation ratio is increased

3) Effect of frequency.

At a constant voltage, if the frequency is increased the flux is reduced. Hence both I_m & I_p are reduced, this decrease of value is not much as compared with the

Increase of leakage reactance due to increase of frequency which causes the increased leakage reactance drops & ratio of voltage are increased.

25

End

- * A $500/100$ V PT has the following constants $R_p = 47.25 \Omega$, $R_s = 0.45 \Omega$, primary reactance $x_p = 33.1 \Omega$, $x_s = \text{negligible}$. The no load primary current is 0.1 A at 0.6 p.f. calculate
- ① the no load angle b/w the primary winding & reverse secondary voltage.
 - ② the value of the secondary winding current at upf when $\theta = 0^\circ$.
- $\Rightarrow \therefore n = 500/100 = 5$
- $$I_e = I_0 \cos \phi = 0.1 \times 0.6 = 0.06$$
- $$\sin \phi = \sqrt{1 - \cos^2 \phi} = \sqrt{1 - (0.6)^2} = 0.8$$
- $$I_m = I_0 \sin \phi = 0.1 \times 0.8 = 0.08$$

We have

$$\textcircled{1} \quad \theta = \frac{IS/n}{n} (x_p \cos \Delta - R_s \sin \Delta) + I_e x_p - I_m x_p$$

at no load $I_g = 0$.

$$\therefore \theta = \frac{I_e x_p - I_m x_p}{n} = \frac{0.06 \times 33.1 - 0.08 \times 47.25}{5 \times 100}$$

$$\theta = -12.92$$

$$\textcircled{2} \quad \text{at upf} \quad \cos \Delta = 1 \quad \sin \Delta = 0$$

$$\therefore \theta = \frac{IS/n \times x_p + I_e x_p - I_m x_p}{n}$$

$$\frac{IS}{n} \times x_p = I_m x_p - I_e x_p$$

$$\therefore IS = [I_m x_p - I_e x_p] \cdot \frac{n}{x_p}$$

$$\therefore I_S = [0.08 \times 47.25 - 0.06 \times 33.1] \times 5 / \text{see in Aikswarney} \\ = 0.270.$$

26
now $P = V_S I_S = 0.270 \times 100 = 27.0 \text{ watts.}$

* A PT with nominal ratio of 2000/100V R.C.R of 0.995 at a phase angle of 22° is used with a CT of nominal ratio 100/5A, R.C.F of 1.005 & phase angle of 10° to measure the power to a single phase induction load. The meter connected to the IT read correct reading of 102V, 4A & 375 watts determine the true values of voltage, current & power supplied to the load?

$$\Rightarrow \text{for PT } k_D = \text{rated primary / rated secondary} \\ = 2000 / 100V \\ = 20.$$

$$\text{now ratio correction factor R.C.F. } R/k_D = ? \\ \Rightarrow R = R.C.F \times k_D = 0.995 \times 20 = \underline{\underline{19.9}}.$$

$$\text{ratio error} = \frac{k_D - R}{R} \times 100 = \frac{20 - 19.9}{19.9} \times 100 = 0.5025\% = 5.12.$$

$$\text{now } R = V_P / V_S \Rightarrow V_S = V_P / R = 102 / 19.9$$

$$\text{for CT. } k_D = 100 / 5 = 20.$$

$$R.C.F = R / k_D = R / 20 \Rightarrow R = R.C.F \times k_D \\ = 1.005 \times 20 = 20.1.$$

$$\therefore \text{Ratio error} = \frac{k_D - R}{R} \times 100 = \frac{20 - 20.1}{20.1} \times 100 = -0.49\%.$$

$$\text{we have } R = Z_P / I_S$$

$$\Rightarrow Z_P = R / I_S = 24 / 0.1 = 0.199 \quad = \underline{\underline{0.49}}.$$

* Testing of current transformer using Sidsbee's method

Sidsbee's method is a comparison method, Basically there
are two types of Sidsbee's method i.e deflection & null.

* The arrangement for the deflection method is as shown below

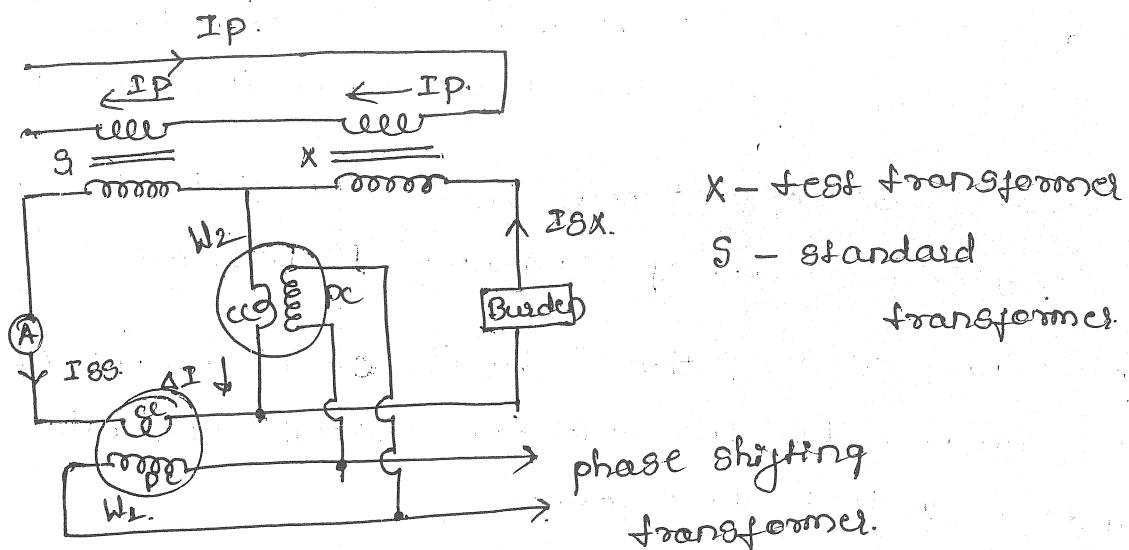


fig - Sidsbee's deflection method.

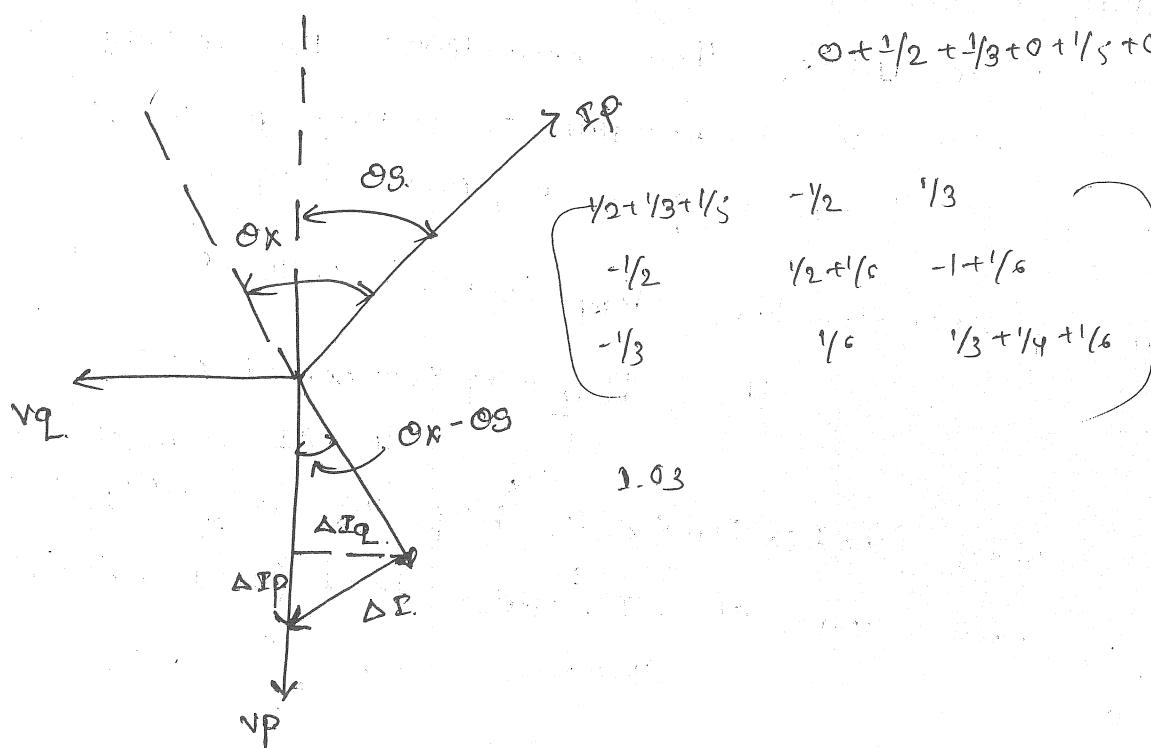


fig-b) phasor diagram of Sidsbee's method.

As shown in the above fig. the ratio and phase angle of the test transformer X is determined in terms of the standard transformer S having same nominal ratio 18° .

- * The primaries of two transformer are connected in series. An adjustable burden is put in the secondary coil of transformer when the transformer is under test.
- * The current coil of Wattmeter W_1 is connected to carry the secondary current of standard transformer S .
- * The current coil of Wattmeter W_2 carries current ΔI which is the difference b/w the secondary current of both standard & test transformer.
- * The pressure coils of wattmeters are supplied in parallel from a phase shifting transformer at a constant voltage.
- * The phase of voltage is adjusted such that the wattmeter W_1 reads zero. Under these conditions the voltage V is in phase with I_{Ss} . The position of voltage phasor is for this case is shown by v_q in given phasor diagram.

$$\text{Reading of Wattmeter } W_1. \quad W_{1q} = v_q I_{Ss} \cos 0^\circ = 0. \quad \text{--- (1)}$$

$$\text{Wattmeter } W_2 \quad W_{2q} = v_q X \text{ component of } \text{--- (2)}$$

in ΔI in phase with

$$v_q = v_q I_{Ss} \sin(\phi_x - \phi_s) \quad W_{2q} = v_q I_{Ss} \sin(\phi_x - \phi_s)$$

ϕ_x = phase angle of C.T., i.e. under test (i.e. test X)
 ϕ_s = " " " Standard C.T.

Now the phase of voltage v is shifted through 90° & now it occupies the position so v_p is in phase with I_{SS} .

$$\text{Reading of wattmeter } W_1 \text{ is } W_{1P} = V_p I_{SS} \cos 90^\circ = V_p I_{SS} \quad \text{--- (3)}$$

$$\text{Reading of wattmeter } W_2 \text{ is } W_{2P} = V_p \times \text{component of } \Delta Z \text{ --- in phase with } v_p.$$

$$\therefore W_{2P} = V_p \times \Delta Z_P = V_p [I_{SS} - I_{SX} \cos(\alpha_x - \theta_S)] \quad \text{--- (4)}$$

If the voltage is considered as same for both the test condition then $V_p = V_Q = V$.

∴ the equation (3) (4) & (4) becomes

$$W_{1Q} = V I_{SS} \cos 90^\circ = 0 \quad W_{1P} = V I_{SS} \quad \text{--- (5)}$$

$$W_{2Q} = V I_{SX} \sin(\alpha_x - \theta_S) \quad W_{2P} = V [I_{SS} - I_{SX} \cos(\alpha_x - \theta_S)] \quad \text{--- (6)}$$

∴ We have

$$W_{2Q} = V I_{SX} \sin(\alpha_x - \theta_S)$$

$$W_{2P}/V = V I_{SS} \cos(\alpha_x - \theta_S)$$

$$\begin{aligned} W_{2P} &= V [I_{SS} - I_{SX} \cos(\alpha_x - \theta_S)] \\ &= V I_{SS} - V I_{SX} \cos(\alpha_x - \theta_S) \\ &= W_{1P} - V I_{SX}. \end{aligned}$$

as $\alpha_x - \theta_S$ is
very small
 $\therefore \cos(\alpha_x - \theta_S) \approx 1$

$$\therefore V I_{SX} \approx W_{1P} - W_{2P}$$

Actual ratio of transformer under testing $R_x = I_P / I_{SX}$
Actual ratio of standard transformer is
desired ratio of standard transformer is
 $R_S = I_P / I_{SS} \quad \text{--- (7)}$

taking the ratio equation. ⑤ & ⑥ i.e actual ratio of test transformer and Standard transformer.

$$20 \quad R_x/R_s = \frac{I_p/I_{Sx}}{I_p/I_{SS}} = \frac{I_{SS}}{I_{Sx}} \quad \text{Multiplying N & D by } v$$

$$\therefore R_x/R_s = \frac{v I_{SS}}{v I_{Sx}} = \frac{W_{1P}}{W_{1P} - W_{2P}} = \cancel{\text{divide N & D by}} \quad W_{1P}$$

$$\therefore R_x/R_s = \frac{1}{1 - (W_{2P}/W_{1P})} \approx 1 + W_{2P}/W_{1P}$$

$$\therefore R_x = R_s \left[1 + \frac{W_{2P}}{W_{1P}} \right]$$

We have $W_{2q} = V I_{Sx} \sin(\phi_x - \phi_S)$ & $W_{2p} = V I_{SS} - V I_{Sx} \cos(\phi_x - \phi_S)$

$$\Rightarrow \sin(\phi_x - \phi_S) = W_{2q} / V I_{Sx} \quad \text{④} \quad \cos(\phi_x - \phi_S) = \frac{W_{2p} - V I_{SS}}{V I_{Sx}} \quad \text{⑤}$$

\Rightarrow We have $V I_{SS} = W_{1P}$ -

$$\therefore \cos(\phi_x - \phi_S) = \frac{W_{1P} - W_{2P}}{V I_{Sx}} \quad \text{⑥}$$

divide equation ④ by ⑥

$$\frac{\sin(\phi_x - \phi_S)}{\cos(\phi_x - \phi_S)} = \frac{W_{2q} / V I_{Sx}}{W_{1P} - W_{2P} / V I_{Sx}}$$

$$\therefore \tan(\phi_x - \phi_S) = \frac{W_{2q}}{W_{1P} - W_{2P}}$$

$$\text{or } (\phi_x - \phi_S) = \frac{W_{2q}}{W_{1P} - W_{2P}} \text{ rad.}$$

phase angle of test transformer is $\Theta_x = \frac{W_2 q}{W_{1p} - W_{2p}} + \Theta_g$ rad

W_{2p} is very small \therefore it is neglected

$$\therefore \Theta_x = \frac{W_2 q}{W_{1p}} + \Theta_g \text{ rad} \quad \textcircled{9}$$

from the above equation it is clear that, if the ratio & phase angle error of standard transformer is known then we can calculate the error of test transformer.

W_2 is a sensitive instrument it carry a ch of 0.25%

* difference between CT & PT.

- 1) The secondary of the CT can be open circuited, when the primary winding is carrying a current, but however in PT the secondary can be kept open circuited without carrying any damage to the transformer or operator.
- 2) The primary current in CT is independent of the secondary circuit conditions, whereas the primary current in PT depends on the secondary burden.
- 3) The excitation current of a CT vary over a wide range of normal operation whereas the exciting current of PT is almost constant under normal operation.
- 4) As the current transformer are connected in series with the line a small voltage exist across its primary terminals, whereas in PT, full voltage is applied across the terminals as they are connected across the line.
- * The exciting ch of CT is 2A lagging 40° to the secondary voltage reversed. The CT has a bar primary and a nominal ratio of 100/1A. The external burden is 1.5Ω & the resistance of the secondary winding is 0.25Ω , when

1A of current flowing through the secondary winding
calculate the actual ratio of ω & its phase angle

$$\Rightarrow n = \frac{2\pi f P}{I_B} = 100/\sqrt{2} = 100$$

$$Z_S = 1.5 + j0.25 = 1.75 \quad \text{as } X_S = 0.820$$

$$\alpha = 90^\circ - 40^\circ = 50^\circ$$

$$R = n + \frac{I_0}{I_B} \sin(\alpha + \delta)$$

$$= n + 2/\sqrt{2} \sin(50^\circ + 0^\circ)$$

$$= 100 + 1.532$$

$$R = \underline{101.532}$$

$$\theta = \frac{180}{\pi} \left[\frac{I_0 \cos(\alpha + \delta)}{n I_B} \right]$$

$$= \frac{180}{\pi} \left[\frac{2 \cos(50^\circ + 0^\circ)}{100 \times \sqrt{2}} \right]$$

$$= 0.784^\circ = 44.195^\circ$$

3, 15, 21, 25, 28, 35, (40, 46, 50, 54, 61, -)

Magnetic Measurements

(1)

The measurement of various property of Magnetic Material is known as Magnetic Measurement.

* The magnetic material play an important role in the operation of Electrical Machine hence measurement of various characteristics of magnetic material is important.

* The Magnetic Measurement includes:

- 1) Measurement of flux density B in a specimen of ferromagnetic material.
- 2) measurement of magnetizing force H , producing the flux density B , in air.
- 3) determination of $B-H$ curve & hysteresis loop.
- 4) determination of eddy current & hysteresis loss.
- 5) testing of permanent magnets.

* Type of test:- Many methods are used for testing of magnetic materials, & attempt is made to reduce hysteresis. They are →

i) Ballistic test :- These tests are generally used for obtain determination of $B-H$ curves and hysteresis loops of ferromagnetic material.


* In this method direct current is used to provide adjus. field mmf for the magnetic circuit, ballistic galvanometer or flux meter is used for the meas^t of flux density.

ii) AC testing :- These tests may be called at power, audio or radio frequency, these tests give the infor-

motion about eddy current & hysteresis lossy in magnetic materials.

iii) Steady State test :- These tests are used for determination of flux density in a specimen, & determination of B-H curve & plotting hysteresis loop.

* Measurement of flux density.

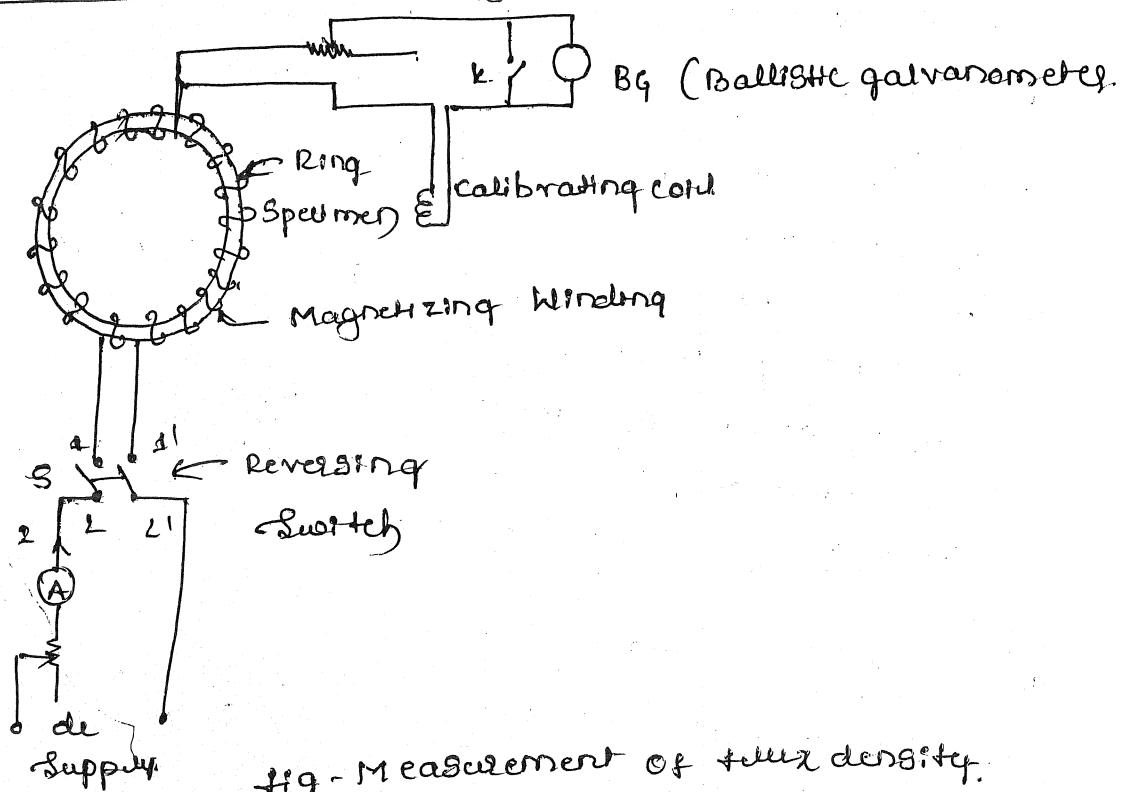

Let us consider the steady measurement of flux density in a ring specimen as shown above a coil with sufficient number of turns wound on a ring specimen.

* As shown above the coil is connected to the ballistic galvanometer.

* The magnetizing winding carry a coil I & produce the flux to be measured. The coil I in the magnetizing coil is reversed using reversing switch.

* With the change of direction of current, charge induced emf
in it, This emf drives a current through the ballistic galvanometer, causing the corresponding deflection. (2)

Let ϕ = flux linking with Search coil

N = Number of turns of Search coil

R = Resistance of ballistic galvanometer circuit

t = Time required to reverse current, i.e. time

required to reverse the flux ϕ .

The avg emf induced in the Search coil is

$$e = N \frac{d\phi}{dt} \text{ volt}$$

Initial flux is ϕ , after reversal $-\phi$.

$$\therefore d\phi = \phi - (-\phi) = 2\phi$$

$$dt = t$$

$$\therefore e = N \frac{2\phi}{t} \text{ v.}$$

the avg current through the ballistic galvanometer is

$$i = e/R = \frac{N 2\phi}{R t} \text{ v.}$$

charge Q , discharged through the galvanometer during t say $\times 10^3$

$$Q = i t = \frac{N 2\phi t}{R t} = \frac{2N\phi}{R} \text{ coulombs}$$

Now the deflection of galvanometer is proportional to charge i . $\therefore Q \propto \theta$,

$$\frac{2N\phi}{R} \propto \theta,$$

$$\text{or } \phi \propto \frac{k\theta R}{2N}$$

They if A is the area of cross section of the specimen
then flux density is given by

$$B = \frac{\Phi}{A} = \frac{R k \Theta_1}{2NA} \text{ wb/m}^2, \text{ Then flux density}$$

can be measured from deflection of the ballistic galvanometer.

* correction of Air flux

In the above discussion, it is assumed that the flux is uniform throughout the specimen and area of cross section of search coil and specimen is equal.

But practically the cross-section of search coil is higher than that of the specimen. Hence total flux entering with the search coil is sum of the flux in the specimen and flux existing in the air gap b/w search coil & the specimen.

\therefore Total flux observed = flux in Specimen + flux in air gap coil & Specimen

Let B' = observed value of flux density

B_f = true value of flux density


A_c = area of cross section

$$B'A = B_f A + \mu_0 H (A_c - A)$$

$$B_f = B' - \mu_0 H \left[\frac{A_c - A}{A} \right]_x$$

* Measurement of Magnetizing force H.

(3)

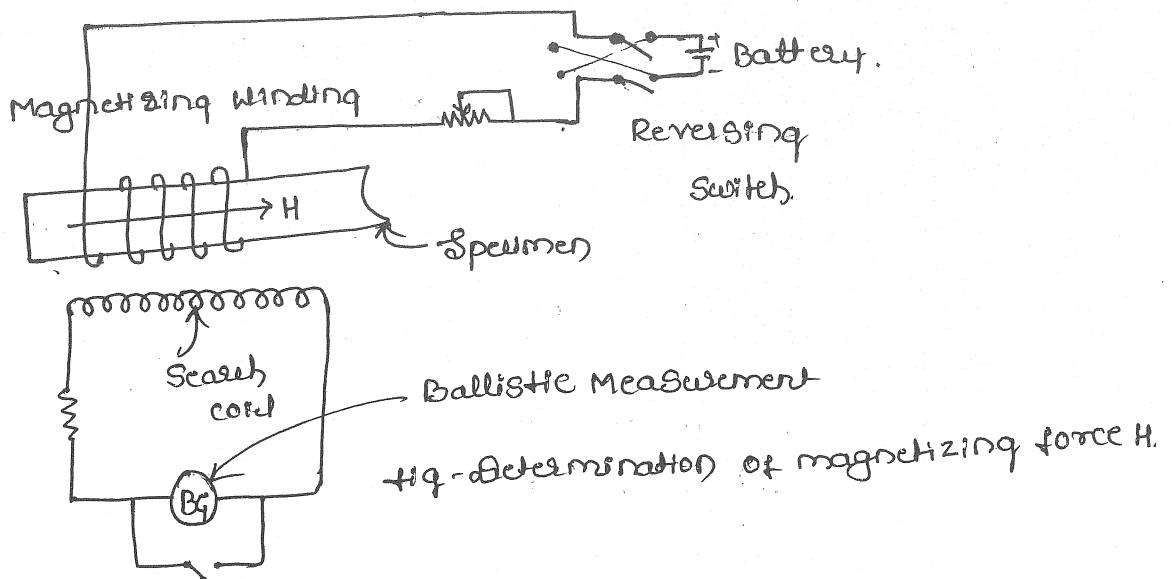

The magnetizing force H is also measured by using a search coil and a ballistic galvanometer the arrangement is as shown above

* In Guts method H can't be obtained directly but it is calculated by measuring flux density by the method of current reversal.

* The position of search coil as shown above, which is used for the measurement of flux density B_0 in air, by reversing current I with the help of reversing switch.

* The search coil used for Guts measurement is called H coil, once B_0 is measured then H can be obtained as

$$H = B_0 / \mu_0 A M$$

where $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$.

\therefore the search is to be placed in the air gap itself
if H in the air gap is to be measured

* If the magnetising force H , within the ferro-magnetic material is to be obtained, then H is measured on the surface of the specimen as tangential components of field are equal in magnitude for both the sides of the interface.

The value of H inside a specimen is calculated by

$$H = \frac{NI}{d} \text{ AT/m}$$

Where d = mean circumference of the ring mm

N = no of turns of Specimen.

I = current flowing through Specimen

* permeability * permameter

Most of the methods employed in magnetic testing are designed to avoid the errors and difficulties of the simpler ring or bar tests. These methods include the good quality of both bar and ring specimens.

1) Hopkinson permeameter (Bar and Yoke method)

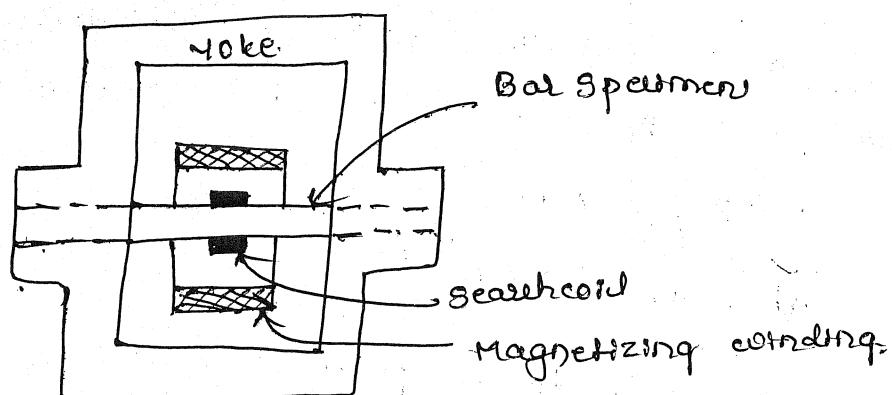


fig-Bar and Yoke method.

As shown in the above fig, the test coil is wound on the central part of the Bar Specimen. (4)

- * The bar is clamped b/w two halves of massive iron yoke, whose reluctance is now compared to that of the bar specimen.
- * The yoke provide the return path for the flux & bar specimen is wound with a magnetizing winding.

Let $N = \text{No of turns on the magnetizing winding}$

$I = \text{current in the magnetizing winding}$

$a = \text{length of the bar specimen b/w two halves}$

of the yoke

$A_S = \text{area of cross section of Specimen}$

$\mu_S = \text{permeability of the specimen when the}$

magnetizing current I .

$R_y = \text{Reluctance of yoke}$

$R_j = \text{reluctance of the joints b/w the bar}$

specimen and yoke

$\phi = \text{flux in the magnetic circuit}$

now the reluctance of the specimen is $R_S = 1/\mu_S A_S$

$\phi = \frac{\text{mmf}}{\text{reluctance of the magnetic circuit}}$

reluctance of the magnetic circuit

$$\therefore \phi = \frac{NI}{R_y + R_j + \left(\frac{1}{\mu_S A_S}\right)} \quad (1)$$

\therefore the flux density in the specimen

$$B = \phi / A_S = NI / A_S \left(R_y + R_j + \frac{1}{\mu_S A_S} \right) \quad (2)$$

$$\text{Magnetizing force } H = \frac{\Phi}{AS} = \frac{NI}{AS(R_y + R_j + 1/\mu_s A)}$$

Let $m = \frac{\text{reluctance of (yoke+joints)}}{\text{reluctance of Specimen}}$

$$= \frac{R_y + R_j}{1/\mu_s A} = \frac{\mu_s A (R_y + R_j)}{d} \quad \textcircled{2}$$

$$H = \frac{NI}{d(1+m)} \quad \textcircled{4}$$

$$= \frac{NI}{d(1 + \frac{\mu_s A}{d} (R_y + R_j))}$$

now the value of m is made small by keeping the reluctance of the yoke & that joints to a small This can be done carefully by fitting into the yoke and making the cross section of yoke larger.

If m is made small then we have

$$H = \frac{NI}{d} (1-m) \quad \textcircled{2}$$

If the value of flux density is measured is equal way by using a ballistic galvanometer.

* Measurement of Leakage factor

(5)

In electrical Machines and other devices, the flux crossing the air gap is called useful flux, while the flux in actual pole is called total flux. The useful flux is less than the total flux due to leakage flux.

* The leakage is specified by a factor called leakage factor which is the ratio of the total flux to the useful flux denoted by λ .

$$\therefore \lambda = \frac{\text{Total flux}}{\text{useful flux}}$$

* The arrangement for leakage factor measurement is as shown below.

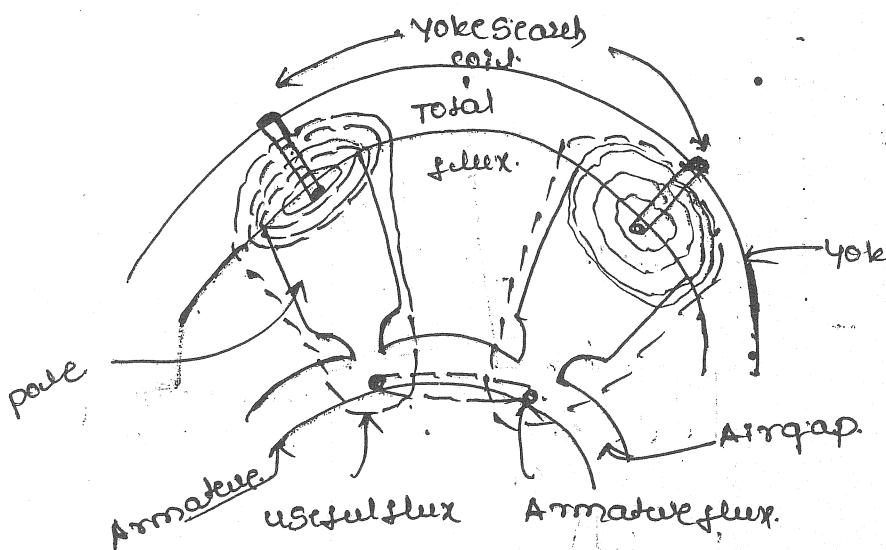


fig - Measurement of leakage factor.

* As shown above the yoke of machine carries total flux produced by the field winding wound on poles.

* Two search coils are wound on yoke of the machine

- one each on the either side of pole as shown above
- * to measure the total flux the two search coils are connected in series & the coils are connected to the fluxmeter which gives total flux of machine.
 - * The flux which reaches armature through airgap is called useful flux.
 - * Finally the ratio of two readings are obtained, which is the leakage factor of the machine.
 - * The search coils with only one turn are preferred in such measurement so that the flux meter directly give the reading of the required flux.
 - * Measurement of iron loss using wattmeter method.

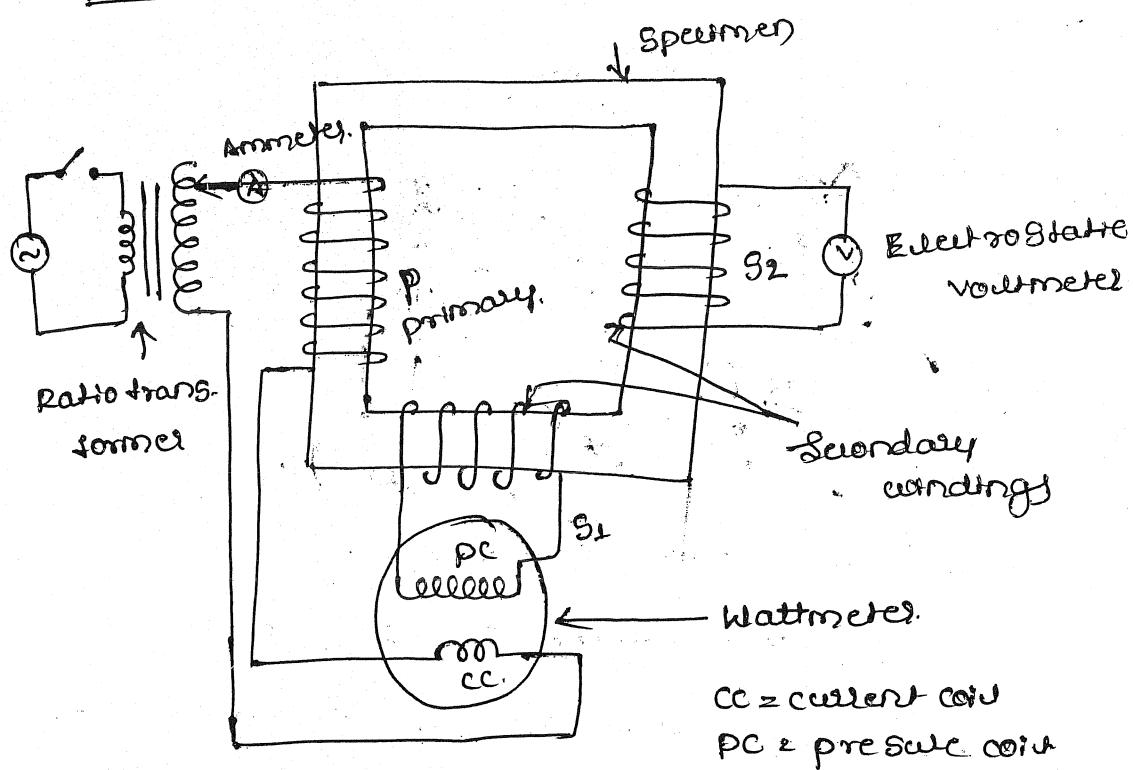


fig - Measurement of iron loss using wattmeter method.

- * The above fig shows the connection diagram for the measurement of total iron loss by wattmeter method
- * The weight and cross section of specimen is determined before the test
- * The four magnetizing coils are connected together to form a primary winding, it is connected to the xtra secondary through ce. of the wattmeter
- * The pc is connected ^{across} to one of the secondary windings, & other secondary winding is connected to the very high impedance Electrostatic voltmeter.
- * The frequency of supply is adjusted to the required value, The wattmeter is LPF wattmeter with apf = 0.2.

* Theory

The supply voltage is adjusted using the tappings on the secondary of the ratio transformer, till the required maximum flux density B_m is reached in the specimen. The voltage induced in the secondary S_2 is measured on voltmeter & the wattmeter reading is adjusted.

The voltage measured by the voltmeter is given by, $E = 4k_f(B_m' A_S) + N_2$ (1) Where $B_m' A_S = \Phi_m$

Where k_f = form factor = 1.11 for sinusoidal flux

B_m' = Apparent value of max flux density in esb/m²

A_S = cross-sectional area of specimen in m²

N_2 = No of turns in winding S_2

f = frequency in Hz

$$B_m' = \frac{E}{4\pi f A_S + N_2} \quad \text{--- (2)}$$

* The secondary winding S_2 encloses the flux in air gap b/w specimen & the coil, in addition to the flux in specimen.

$$\therefore B_m = B_m' - M_{OH} \left[\frac{A_c - 1}{A_g} \right] \quad \text{--- (3)}$$

Where B_m = maximum flux density required

A_c = cross section of coil in m^2

A_g = cross section of specimen in m^2

H_m = magnetizing force required to develop max flux density in A/m

* The H_m can be obtained from B-H curve for the specimen

* The wattmeter reading (W) consists of

V_{PC} = voltage across the PC in V

I_{PC} = current through the PC in A

r_p = resistance of PC in Ω

r_S = resistance of the secondary winding in Ω

E = voltage induced in S_2 . V = voltmeter reading

The voltage induced in S_1 is same as S_2

\therefore voltage induced in S_1 is E .

neglecting the leakage resistance of S_1 , & leakage resistance of PC by it is highly resistive

resistance of PC by it is highly resistive

$$B = Ipc r_p + Ipc r_S \approx Ipc (r_p + r_S) \quad \text{--- (4)}$$

$$\text{while } V = Ipc r_p.$$

\therefore The total iron loss (P_I) in Specimen + total copper loss in the secondary circuit $= \frac{WB}{V}$

Total copper loss in the secondary circuit is

$$= I^2 pc (r_p + r_S) = E^2 / (r_p + r_S) \quad \text{--- (5)}$$

$$\therefore P_I = \frac{WB}{V} - \frac{E^2}{(r_p + r_S)} \quad \left| \begin{array}{l} \text{where } B = Ipc (r_p + r_S) \\ V = Ipc r_p. \end{array} \right.$$

$$= \frac{W Ipc (r_p + r_S)}{Ipc r_p} - \frac{E^2}{(r_p + r_S)} \quad \text{divide Nr & Dr by } Ipc r_p$$

$$= W \left[1 + \frac{r_S}{r_p} \right] - \frac{E^2}{(r_p + r_S)} \text{ watt.}$$

However by conducting test at different frequencies iron loss can be separated from hysteresis loop.

* Measurement of Air gap flux

The various methods for the measurement of airgap flux are →

- ① Deflection of a pivoted magnetic needle \rightarrow the classical magnetometer method.
- ② The rapid rotation of search coil through 180° - for example - classical earth indicator.
- ③ continuous rotation of a search coil fitted with a commutator to give a dc output.

- ④ continuous rotation of search coil fitted with supports to give an ac output.
- ⑤ The force on a current - carrying conductor in the field
- ⑥ The effect of field on the magnetization of a small piece of soft iron by an ac in a magnetizing winding.

* Measurement of field strength by withdrawal of search coil.

- 1) In this method a search coil is placed in a magnet field & the terminals of search coil are connected to ballistic galvanometer.
- 2) The search coil is suddenly withdrawn from the magnetic field, due to which the flux linking with the search coil changes.
- 3) The change of flux induces an emf in the search coil which causes the galvanometer to deflect & we can measure from the galvanometer the flux density & field strength.

* Measurement of constant field strength by Nuclear Magnetic Resonance.

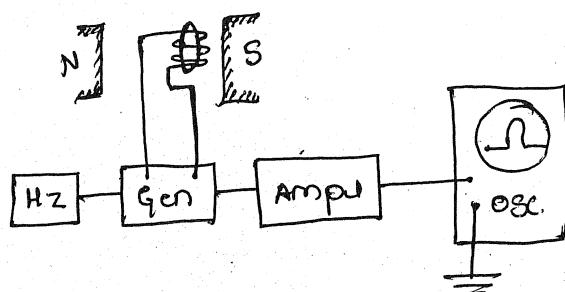


fig - Measurement of field strength by nuclear magnetic resonance

When an alternating magnetic field of high frequency is superimposed on atomic nuclei in a constant magnetic field, resonance absorption of energy from high-frequency field is liable to occur at a specific ratio of the constant field strength H to frequency f of the alternating field.

The laws of quantum mechanics postulate that the magnetic moment of hydrogen nucleus may be oriented either in the same direction as that of the external magnetic field or in opposition to it.

The orientation of proton magnetic moment can be changed by application of an energy quantum hf where h is Planck's constant & f is frequency.

The difference between the two energy states of the proton amounts to $2m_p H$ where m_p is the proton magnetic moment.

Evidently, $hf = 2m_p H$ & we know that $\omega = 2\pi f$
 $\& f = \omega/2\pi$.

$$\therefore \frac{h \times \omega}{2\pi} = 2m_p H.$$

$$H/4\pi = \frac{m_p H}{\omega}$$

$$\therefore H/4\pi$$

$$\omega = \frac{4\pi m_p H}{h}$$

$$= \nu_p H.$$

$$\text{or } H = \frac{2\pi f}{\nu_p} = \omega/\nu_p. \quad \text{---(1)}$$

Where ν_p is gyromagnetic ratio of nucleus, i.e. the ratio of magnetic moment to the mechanical moment.

According to this method, the magnetic strength of a constant field is determined by measuring

the frequency at which nuclear magnetic resonance occurs. Resonance is detected by sharp change in the amplitude of the resonance curve traced on the screen of the cathode-ray oscilloscope at a change in the oscillator frequency. This method is more suitable for the measurement of field having a magnet strength of 800 to 1.6×10^6 A/m. The accuracy of measur. may within $\pm 0.01\%$.

Module - 4, Electronic and digital Instrument

* Essential of electronic instruments

* Comparison

Electronic meter

1) The electronic components such as rectifiers, transistors, diodes etc are used.

2) Amplifiers are present.

3) Low level signal detection is possible.

4) power consumption is low.

5) Loading effects are less.

6) sensitivity is high.

7) Input impedance is very high.

8) The frequency range is very high.

9) The accuracy is very high.

10) The meters are compact and portable.

11) The meters are not rugged.

conventional analog meter

1) The electronic components are not used.

2) Amplifiers are absent.

3) Low level signal detection is not possible.

4) power consumption is high.

5) very severe loading effects.

6) sensitivity is less.

7) Input impedance is low.

8) The frequency range is limited.

9) The accuracy is comparatively less.

10) The meters are not compact and portable.

11) The meters are rugged.

* Electronic instruments

ordinary conventional instruments such as ammeter, voltmeter, ohmmeter & wattmeter measure the current, voltage, resistance, & power. The sensitivity of these instruments is very small, they can't be constructed for full scale sensitivity less than 50mA or 10mV for full scale sensitivity less than 50 . In such case the Electronic instruments use the amplifier to measure the value.

* The advantages of Electronic instruments are

- 1) Detection of low level signals :- It is possible to measure the currents & voltages of smaller range than 50mA & 10mV using electronic ammeter & voltmeter.
- 2) Low power consumption :- The sensitivity of an ordinary voltmeter is about $20\text{k}\Omega/\text{V}$ for $0 - 0.5\text{V}$ range voltmeter & has an input resistance of $10\text{k}\Omega$ & full scale current of 50mA , But However the electronic voltmeter have an input resistance of $10\text{M}\Omega$ to $100\text{M}\Omega$ & it has less loading effect & the power consumption of electronic instrument is far less than the conventional instrument

* High frequency range → With the help of electronic voltmeter the voltage of source can be measured whose frequency can vary from zero Hz to several hundred of MHz, However the response of these electronic instruments can also be made independent of the frequency.

- v) Bi-electrode instruments are used to measure both low as well as high voltage.
- v) The response of electrostatic instrument is faster & more reliable.
- vi) Electronic instruments can be used to monitor remote signals.

* True RMS Reading Voltmeter

Measuring thermocouple

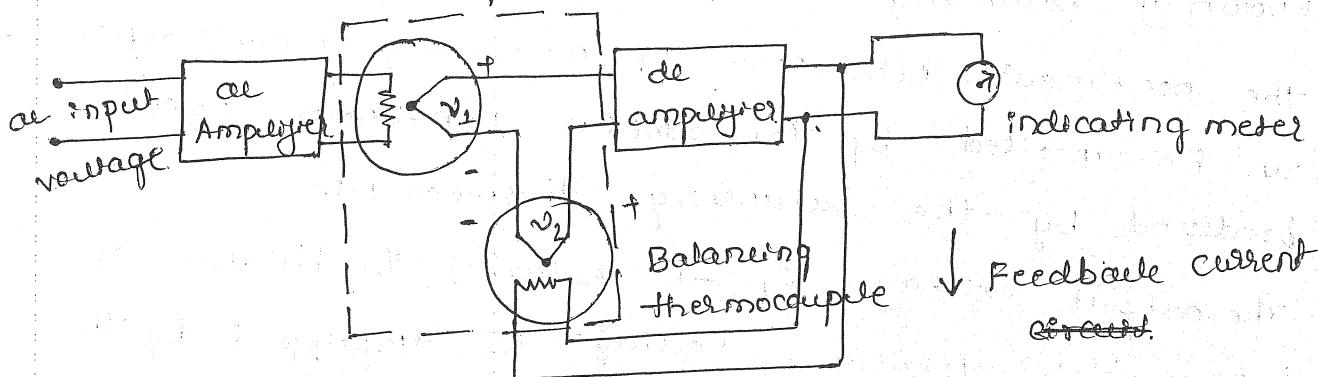


fig- True rms Reading voltmeter.

- 1) True rms value of the voltage, of complex wave-forms of any type i.e sine, square, saw tooth etc can be accurately measured with the help of true rms reading voltmeter.
- 2) Initially an ac supply voltage of any complex waveform is applied to the input terminal of the meter, the input voltage is amplified with the help of ac amplifier.
- 3) The amplified voltage is applied to the heating element of measuring thermocouple.
- 4) Thermocouple is a junction of two dissimilar metals whose contact potential is a function of the temperature of the junction.

- ⑤ The heat produced in the measuring thermocouple increases the temperature of thermocouple & produces a voltage of V_1 , which is proportional to E^2 rms of the applied voltage.
- ⑥ One difficulty with this technique is, that the thermocouple is often nonlinear in its behaviour this difficulty can be overcome by connecting another thermocouple known as balancing thermocouple.
- ⑦ The nonlinear behaviour of measuring thermocouple can be cancelled by the similar nonlinear effect produced by the balancing thermocouple.
- ⑧ The output voltage V_1 is disturbed by the balance of bridge. This unbalance voltage is employed by the amplifier & feedback to the heating element of balancing thermocouple.
- ⑨ The balance of the bridge is achieved when the sufficient amount of heat is produced in the balancing thermocouple due to feedback. It produces an output of both the thermocouples.
- ⑩ The output voltage of both the thermocouples are equal & opposite in direction hence the bridge is balanced.
- ⑪ When the bridge is balanced the output voltage of the measuring thermocouple V_1 becomes equal to the balancing thermocouple. $V_2 = V_1 = V_1 - V_2$
- ⑫ When the bridge is balanced the dc flowing through the balancing thermocouple becomes equal

to rms value of ac current flowing through the measuring thermocouple. This dc current is directly proportional to the rms value of input voltage & which is indicated by indicating meter.

* Electronic multimeter (VOM)

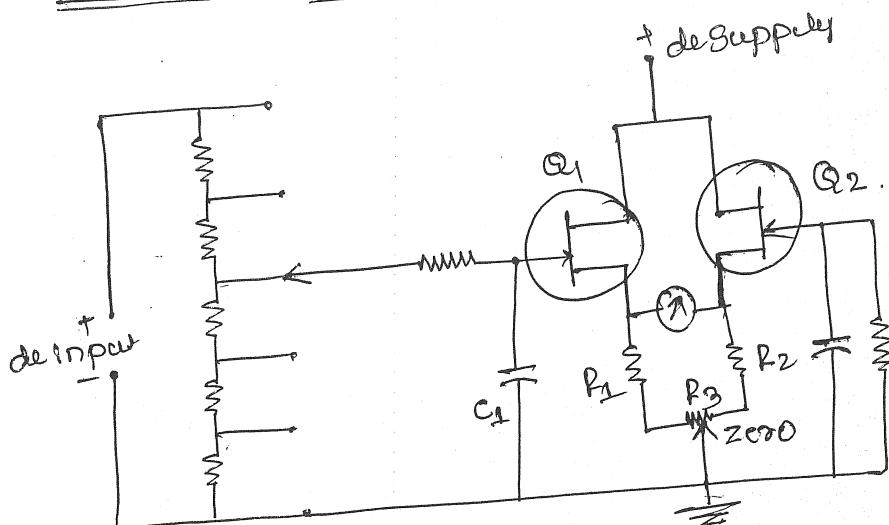



fig - Electronic multimeter.

An electronic multimeter is also called as volt-ohm meter if it is one of the most important laboratory instrument, which is used to measure both dc and ac voltages & resistance.

The above fig shows schematic diagram of electronic multimeter it consisting of following elements.

- 1) A balanced bridge dc amplifier with an indicating meter.
- 2) An input Range Switch, to limit the magnitude of input voltage to the desired value.

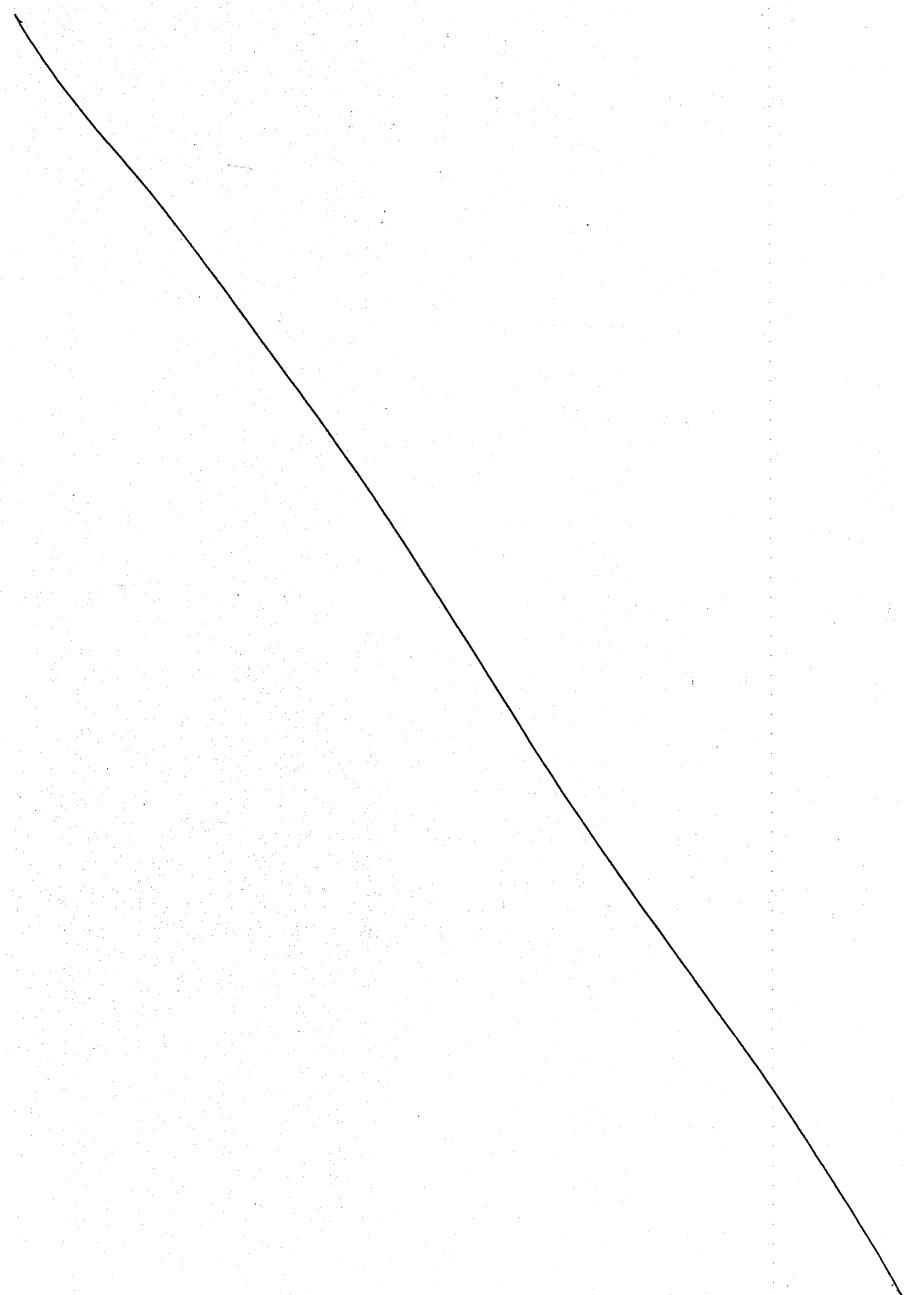- 3) A rectifier to convert ac input to a proportional dc-voltage
- 4) internal battery & additional circuitry, for the measurement of resistance
- 5) A functional switch to select various functions



In addition to the above all elements if has built in
power supply for operation on ac power line &
one or more battery for the operation of portable
measuring instrument.

- The balanced bridge de employed consists
of two FET's (Field effect transistors), They must have the
same current gain for the thermal stability of the circuit
- * The two FET's will form the upper arm of bridge which
the Resistor R_1 , R_2 & with zero adjustment resistor R_3
will form the lower arm of bridge.
 - * The indicating meter is connected in between the two
source terminal of FET's
 - * When there is no input supply the gate terminal of
FET is at its ground potential & no. drain flow through the
indicating meter. under this condition the bridge is balanced
 - * Due to small difference in the operating characteristics
of two FET's & Slight tolerance bin the various
resistors of the bridge etc. there must be slight
unbalance in drain current & indicating meter shows
small deflection from zero.
 - * the balance of bridge can be done by adjusting
 R_3 resistor. this electronic multimeter can be used
either as a voltmeter or ohm meter.

Q1 Q2, 804,
S.

* Electronic voltmeter \Rightarrow ① When a +ve voltage is applied to drain gate terminal of FET Q₁, its drain current increases due to which the voltage at the source terminal increases.

- ② Then there is a unbalance bias in the source voltage of Q₂, due to which the pointer of the indicating meter deflects on the scale, which gives the applied input voltage.
- ③ The maximum voltage that can be applied to the gate of Q₂ is determined by its operating range, which is usually of the order of few volts.

The range of input voltages to be measured

can be easily extended with the help of range switch as shown below.

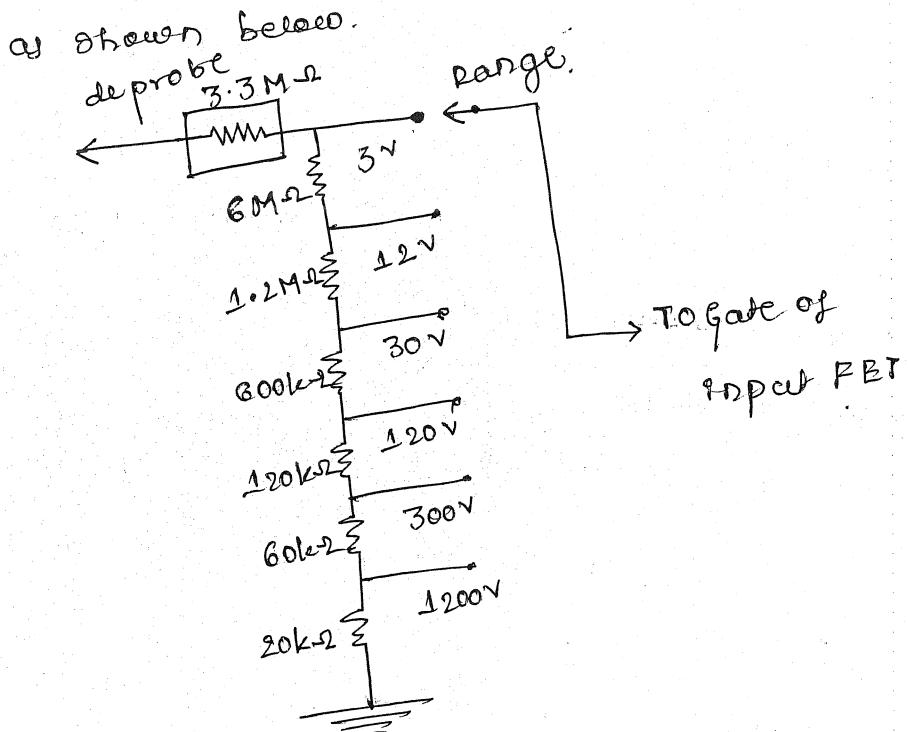


fig - Range switch

- * The unknown dc input voltage is applied through ⑤ a large resistor in the probe body to a resistive voltage divider, with a range switch at 3V position, as shown above.
- * The voltage at the gate of the input FET Q₁ is developed across $8M\Omega$ of the total resistance $11.3M\Omega$ & the circuit is arranged so that the indicating meter should deflect to full scale with 3V.
- * With the range switch on 12V position the gate voltage is developed across $\underline{2M\Omega}$ of the total resistance $\underline{11.3M\Omega}$ & input voltage of 12V is required for full scale deflection of the indicating meter.
- * The range switch allows the selection of the desired voltage range from 3V to 1200V.

* Electronice ohmmeter

- When the electronice multimeter is used as electronice ohmmeter, the function switch on the front panel of ohmmeter is placed on OHMS position. The meter is biased by internal battery.
- The unknown resistance is connected in series with the internal battery & the meter measures the voltage drop across the unknown resistance.
- The resistance range selector switch along with amplifier & indicating meter is as shown below.

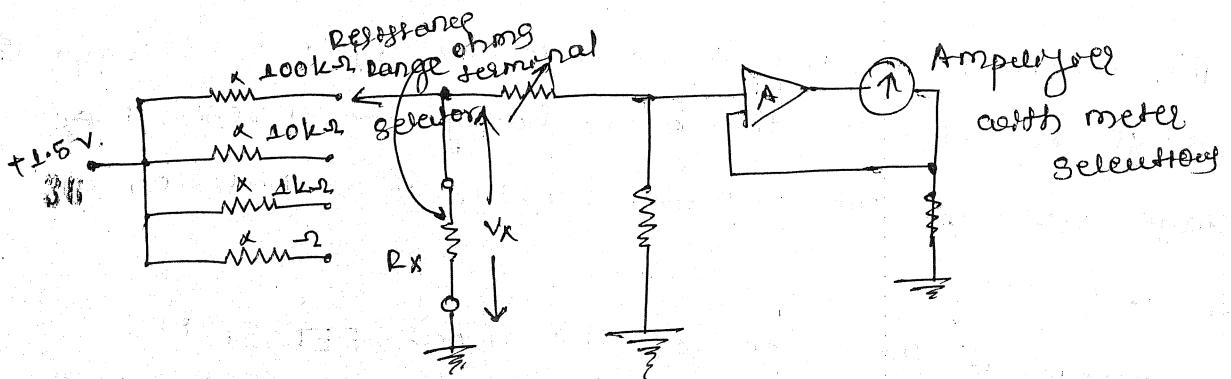


fig - resistance range selector circuit

- ④ A separate divider network is used for the purpose measuring the resistance, which provides different ranges.
- ⑤ When the unknown resistance R_x is connected to the OHMS terminal of the multimeter, it is connected to ground with an internal battery of 1.5V. This internal battery supplies the current through the one of the resistors of range & unknown resistor to ground.
- ⑥ The voltage drop across R_x is determined by the meter applied to the input of bridge amplifier due to which the indicating meter shows the deflection.
- ⑦ the voltage drop V_x is directly proportional to unknown resistance value R_x .

* attendance

K * 100

R - 4.5, 4.12, 1.28,

4.34, 4.62, 4.43, 4.46, 4.47, 4.48, 4.49, 4.51

6.2, 6.3

* Digital voltmeters

(6)


A DVM displays the measurement of dc or ac voltage as discrete numerically, unlike a pointer deflection on a scale in analog meter.

* The general outstanding operating & performance characteristics of a DVM are as follows.

- i) Measurement Range :- From $\pm 1,000,000\text{V}$ to $\pm 10,00,000\text{V}$ with automatic range selection and overload indication.
- ii) Accuracy :- The accuracy is high as $\pm 0.005\%$ of the reading.
- iii) Stability :- 0.002% for a short term period of 24 hours and 0.008% for a long period of 6 monthly.
- iv) Resolution :- 1 part in 10^6 i.e. 1mV can be read on 1V range voltmeter.
- v) Input characteristics :- The input resistance is about $10M\Omega$ & input capacitance is about 40nF .
- vi) calibration :- The calibration is independent of the measuring circuit & is derived from stabilized from reference source.
- vii) output signal :- The output to printer is BCD for digital processing or recording.

* Classification of digital voltmeters

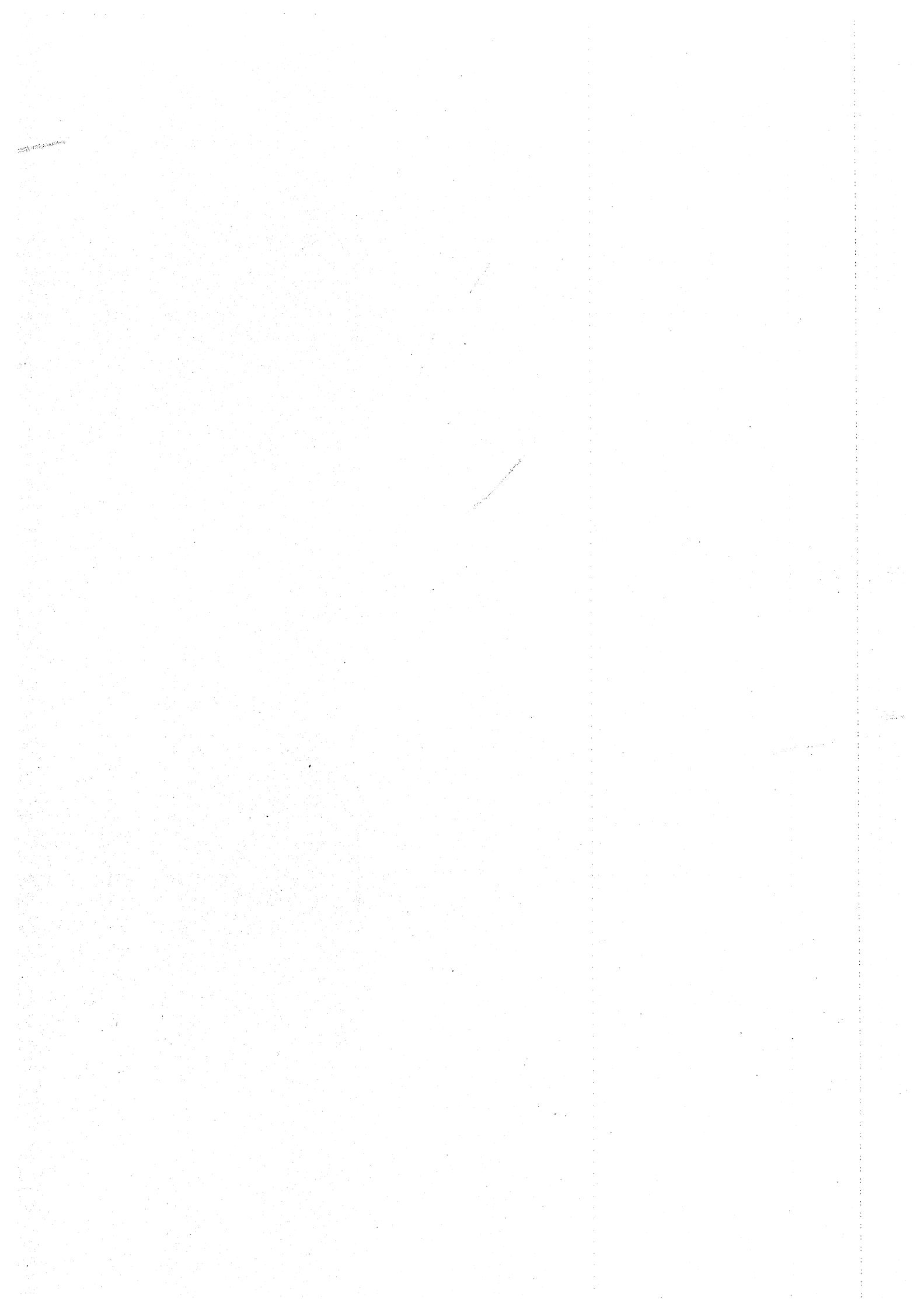- 1) ramp type of DVM ② Integrating DVM
- 2) potentiometric DVM ③ Succesive-approximation DVM



* Ramp type DVM

(H)

- ① The principle of operation of Ramp type of DVM is based on the measurement of time taken by a linear ramp voltage to rise from 0V to the level of input voltage or it's time taken to decrease from the level of input voltage to zero volt.
- ② This time can be measured with the help of electronic time-interval counter. & the no of counts are displayed as a digital number on electronice indicating tubes.
- ③ Now the conversion of voltage to a time interval is illustrated with the help of waveform as shown below.

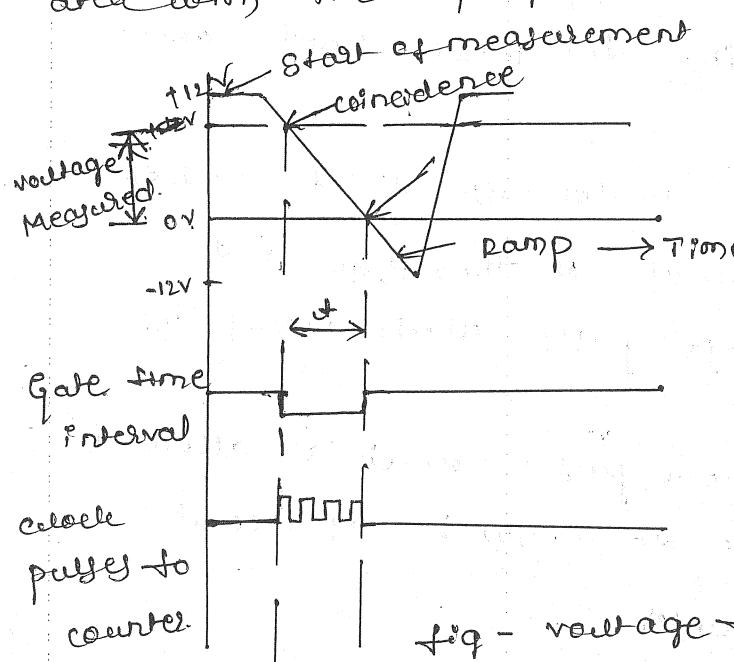


fig - voltage to time converted.

- ④ As shown in the above fig at the start of measurement cycle, a ramp voltage is initiated, which may be a ~~ramp~~ going ~~or~~ -ve going.
- ⑤ In the above a -ve going ~~input~~ ramp voltage is continuously compared with the input voltage. At the certain instant when ramp voltage becomes equal to the input voltage

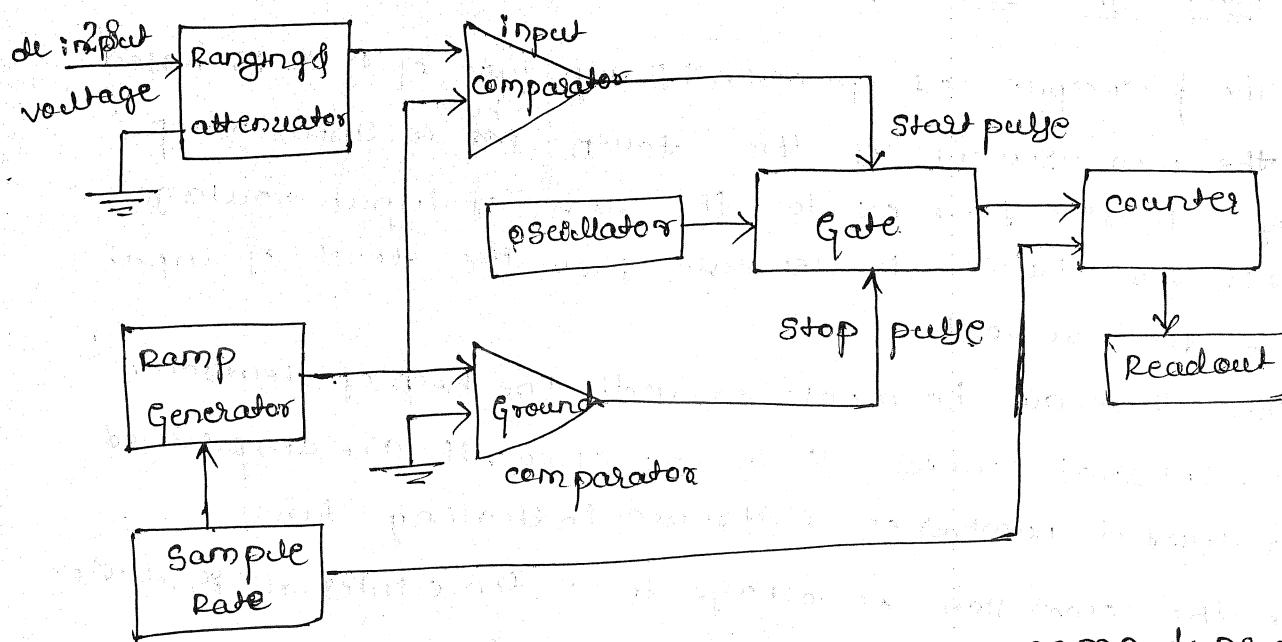


Fig - b . Block diagram of ramp-type DVM.

a comparator will produce the the pulse which opens the gate as shown in fig b.

- ⑤ A ramp voltage continues to decrease & it reaches a zero volt. or ground potential, at this type 2nd comparator generates an output pulse which closes the gate.
- ⑥ An oscillator generates decade pulse which are allowed to pass through the gate to a number of decade counting units (DCU). or counted.
- ⑦ The total number of pulses are displayed in decimal number with the help of indicator tube associated with DCU'S. It is measure of the magnitude of the input voltage.

* Integrating type of DVM

(8)

29


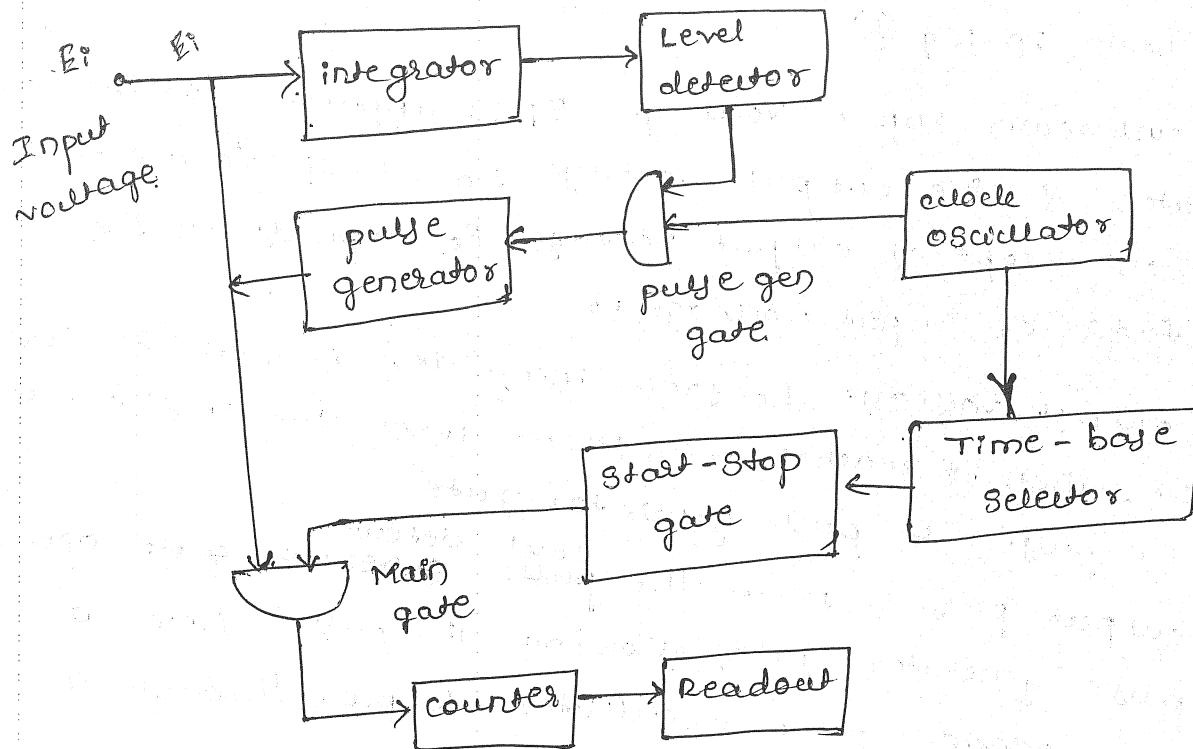


fig - a) integrating - type DVM

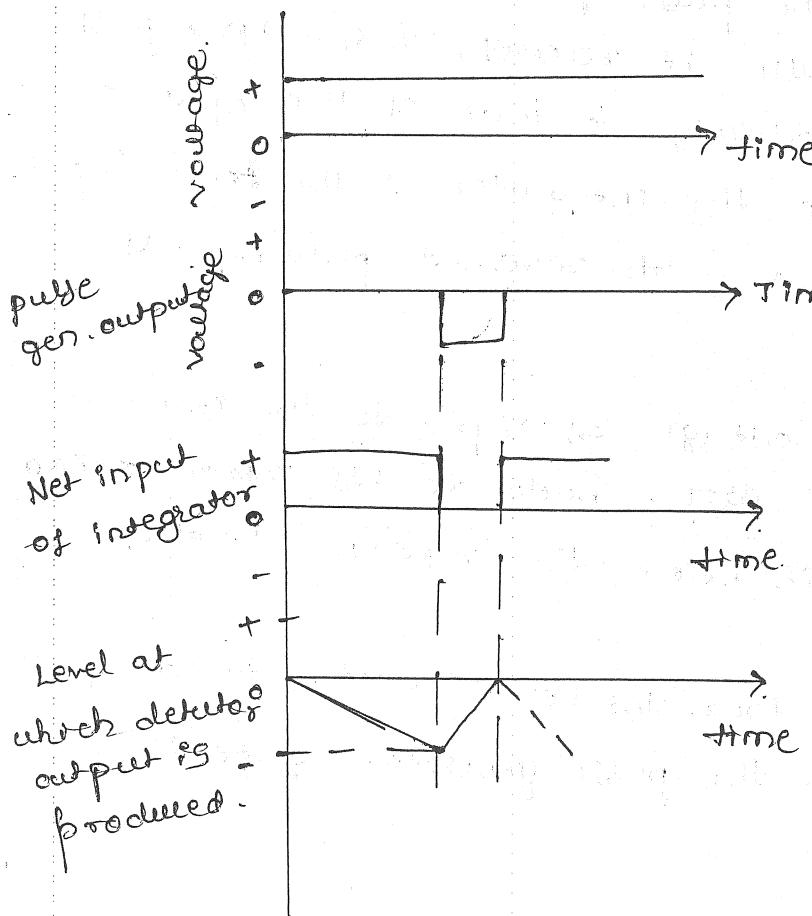

1) The Block diagram of integrating type of DVM is as shown in fig (a) & the corresponding waveforms are shown in fig (b).

- 2) The unknown input voltage E_i is applied to the integrator & the output voltage E_o starts to increase. Here the slope of output voltage E_o depends on the magnitude of input voltage E_i .
- 3) The output voltage E_o from integrator is fed to level detector, when it reaches a reference level, the level detector sends a pulse to pulse generator gate.
- 4) The output pulse from the ~~pulse generator gate~~ opens the pulse generator gate, allowing the pulse from a fixed ~~magnitude~~ clock oscillator to pass through the pulse generator.
- 5) The output pulse of the pulse generator is of fixed magnitude & every pulse it receives. This output pulse is have the opposite polarity to that of the input voltage & which is feedback to the integrator. \therefore the total input to the integrator is now with reversed polarity as shown in fig (b).
- 6) due to the reversed voltage as input to the integrator the output voltage E_o drops back to its input voltage original level, which is below the reference level of level detector. \therefore there is no output from the level detector to the pulse generator gate & hence the pulse generator gate is closed.

⑧ When the pulse generator gate is closed there is no pulse from the clock oscillator will pass to pulse generator to trigger it.

⑨ When the output voltage will pass from the pulse generator. E_i is again restored & E_0 starts increasing the same procedure will repeat. Then the output voltage E_0 will be in sawtooth waveform, whose rise time depends on the value of output voltage E_0 & fall time depends on the width of the output pulse from the pulse generator.

⑩ The frequency of the sawtooth wave may be measured by counting the number of pulses for the given time interval.

⑪ The pulses from the clock oscillator are applied to the time base selector. The 1st pulse passes through the start-stop gate, produce an output which is applied to the main gate. Then it opens the main gate applied to the pulse generator through main gate.

⑫ Due to this the same output pulse will pass from the pulse generator through main gate. The next pulse from the time base selector closes the start-stop gate hence the main gate is also closed.

⑬ Now the counter & readout meter will read ready number of pulses that have passed during the specified

time interval. Indicator gives the voltage to be measured. The amplitude & width of the pulse from the pulse generator can be adjusted to make the counter to read voltage directly.

* potentiometer DVM:

32

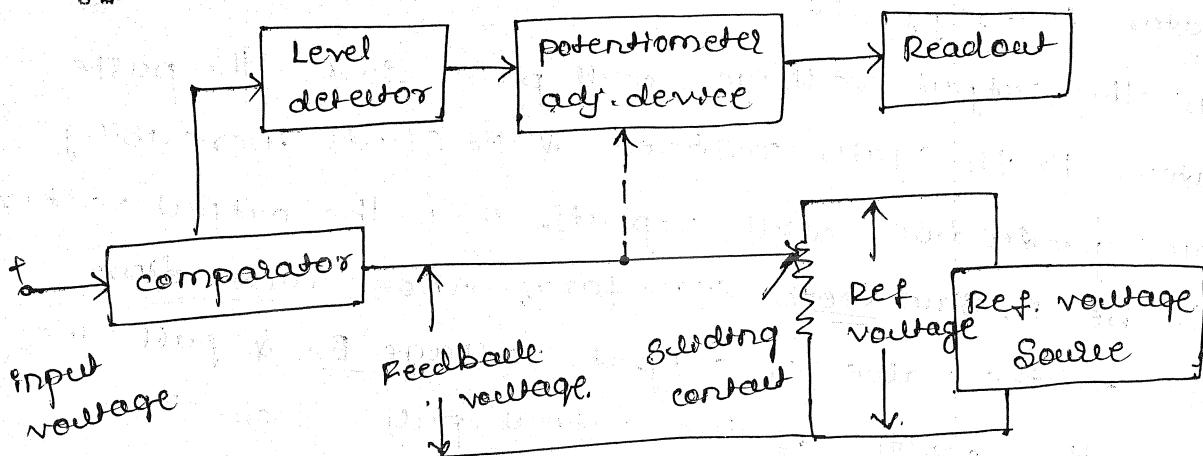


fig - Block diagram of potentiometer type dvm.

- 1) The block diagram of potentiometer type of dvm is as shown above, in which the unknown voltage is compared with the reference voltage whose value is fixed.
- 2) When the unknown voltage is applied to the meter, the balance is automatically obtained & the unknown voltage is directly read with the help of readout meter provided in the circuit. Hence this potentiometer is also known as self balancing potentiometer.
- 3) The unknown voltage is filtered & attenuated to a suitable level. The input voltage is applied to the comparator, which is also known as error detector.
- 4) The unknown voltage is obtained from the fixed voltage source & it is applied to the potentiometer R.
- 5) The value of feedback voltage depends on the position of setting contact.

* The unknown voltage & reference voltage are compared in the comparator & its output is the difference of both the voltages, which is known as error signal.

33

* The error signal is amplified and fed to the potentiometer adjustment device, which moves the sliding contact of the potentiometer.

* The direction of the movement of sliding contact depends on whether the feedback voltage is larger or input voltage is larger.

* The movement of sliding contact stops when the feedback voltage is equal to the unknown voltage. here there is no error signal & no input to the potentiometer adjustment device.

* The position of the potentiometer adjustment device at this point is indicated in numerical form on the digital readout device. the reading of this readout gives the value of the unknown voltage.

* The automatic adjustment of the sliding contact is done by a two phase servomotor.

* Successive - Approximation A/D

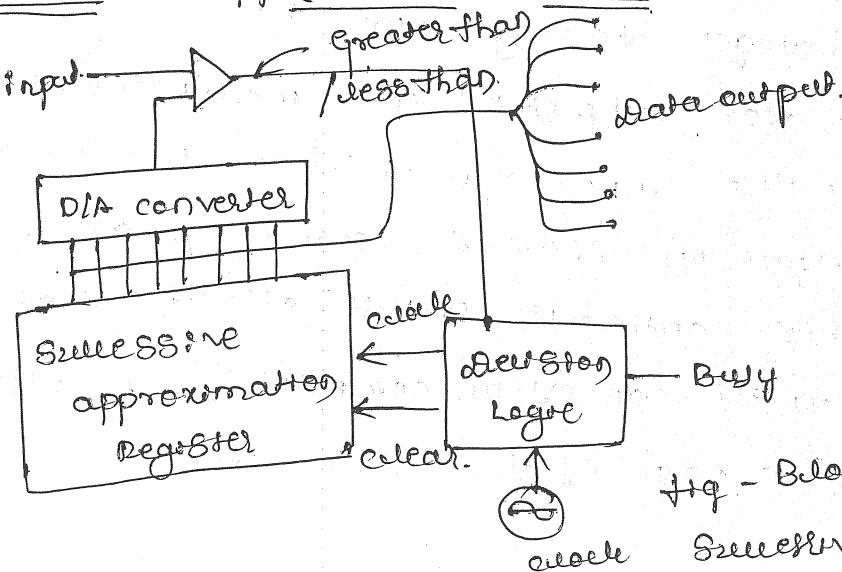


Fig - Block diagram of

Successive - Approximation A/D

- 1) A very effective & relatively inexpensive method of A/D conversion is the method of Successive Approximation method.
 - 2) This is a electronic implementation which is known as regression. The electronic implementation of the successive approximation is a straightforward & the block diagram of D/A converter follows this principle.
 - 3) As shown in the above fig. D/A converter provides estimate & it is compared with the input signal. An estimate is a numeral which is approximately around the voltage which is to be measured. However equal to ∞ greater than 0, less than decision is made by the comparator.
- (4) A special shift register known as Successive approximation register (SAR) is used to control D/A converter & they have the estimate.
- (5) At the beginning of the conversion all the outputs from SAR is ^{logic} zero.
- (6) If the estimate is greater than input, the comparator output is high & the 1st SAR bit serves state 1 & output changes to logic one.
- (7) If the comparator output is low, means the estimate is lesser than the input signal then the 1st bit remains in logic one state & second bit becomes logic one state this continues until all the states to all states until conversion completed. An estimate is made on the edge of the SAR clock.

Q-meter

(11)

A meter is an instrument, which is used to measure some of the electrical properties of inductive coils & capacitors. The principle on which Q-meter works is the principle of resonance.

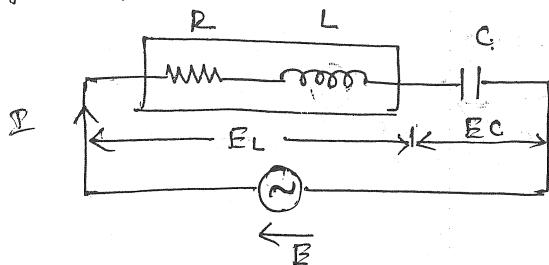


fig-a) Series resonant circuit

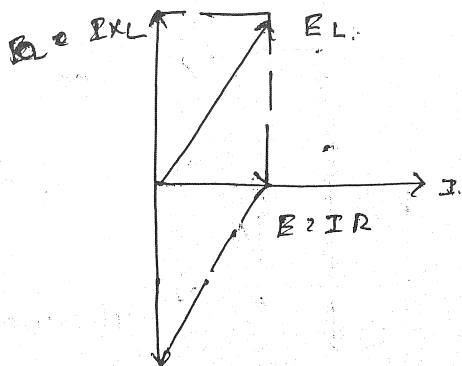


fig-b) Vector diagram

The above fig-a & fig-b represent a series resonant circuit & vector diagram respectively. At resonance p.f. of the circuit is unity & we have certain condition at the resonance

$$X_L = X_C \quad \text{--- (1)}$$

$$E_C = I X_C = I X_L \quad \& \quad E = I R \quad \text{--- (2)}$$

where E = applied voltage, I = current in the circuit

X_L = inductive reactance of the coil,

R = resistance of the coil

X_C = capacitive reactance of the capacitor


E_C = voltage across the capacitor.

The Q factor of the circuit is the no voltage modification of the current under resonant condition

$$\text{i.e. } Q = X_L / R = X_C / R = E_C / E \quad \text{--- (3)}$$

from the above equation it is clear that if E is maintained constant then voltmeter connected across

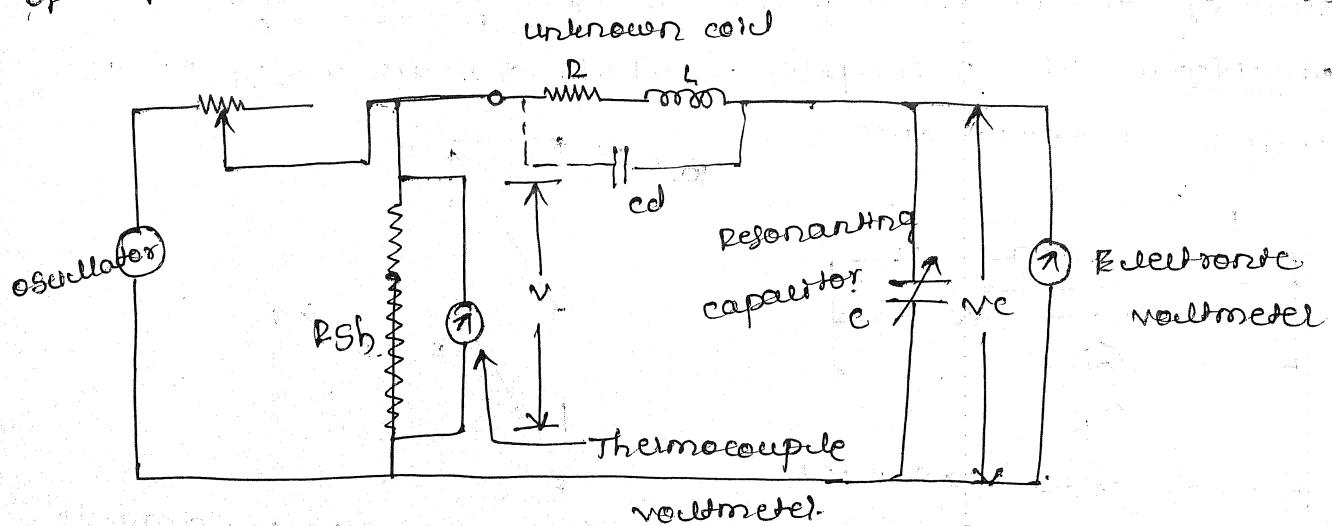capacitor directly read α factor of the circuit.
 Now, the circuit diagram for the measurement of α factor is as shown below.



$\text{fig} - \alpha$ -meter circuit

- AS shown in the above fig a wide-range of oscillator with the frequency range of 50kHz to 50MHz is fed a power supply to the circuit, this oscillator supply current to a low value shunt resistance R_{sh} . However the value of shunt resistance R_s is of the order 0.02Ω .

- The low value shunt resistance introduces a very low resistance into the oscillatory circuit & therefore it represents a voltage source of magnitude E with small internal resistance.
- The voltage E across the shunt is measured with thermocouple voltmeter.
- Now the voltage across the variable capacitor i.e. E_C is measured by the electronic voltmeter whose scale is calibrated to read the α factor directly.
- To measure the α factor of the circuit, the inductive coil is connected across the test terminals of the circuit.

Instrument & the circuit is tuned to resonance (12) either by varying the frequency of the supply from the oscillator or by varying the value of resonating capacitor. If the electronic voltmeter is not calibrated to read the α factor of the coil.

The two voltage ratios E_C/E are noted at the resonance the ratio of both the voltages gives the α factor $\alpha = \alpha^2 E_C/E$ — (ii)

The real value of the α factor is slightly more than the value indicated by the meter.

Now the inductance of the coil can be calculated by the known values of the frequency & the capacitance of the resonating capacitor.


$$x_L = x_C \Rightarrow 2\pi f L = 1/2\pi f C$$

At resonance

$$\therefore L = 1/(2\pi)^2 C$$

* Measurement of Low impedance component

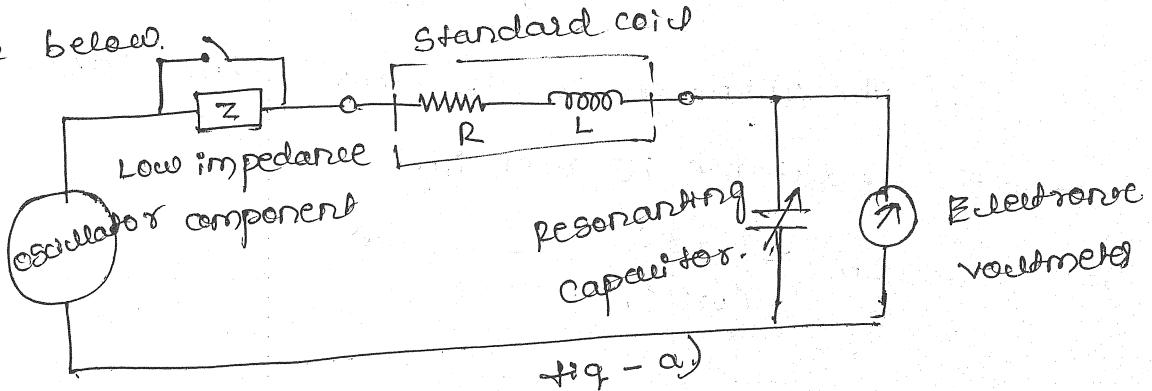The low impedance component seeks a low value resistors, small coils & high value capacitors are measured by connecting them in series with the measuring circuit as shown below.



① As shown in the above fig the component whose value is to be measured i.e. z is connected in series with a standard coil whose R & L are already known & which is connected across test terminals.

② two measurements are to be made, in the 1st meas the unknown component z is short circuited by small shorting strap & the value of resonating capacitor is adjusted to C_1 for which the circuit is under resonant condition. the corresponding values of α & Q factor Q_1 are noted as follow.

$$\text{At resonance } X_L = X_C \Rightarrow \omega L = 1/\omega C_1 \quad \text{--- (1)}$$

$$Q_1^2 \frac{\omega L}{R} = \frac{1}{\omega C_1 R} \quad \text{--- (2)}$$

* In the 2nd measurement the ~~the~~ shorting strap is opened & the value of resonating capacitor is adjusted to value C_2 at which the circuit is under resonant condition. the value of Q_2 is noted as follow

$$X_L^2 X_C^2 \\ \Rightarrow X_L^2 + X_m^2 = X_C^2 \quad \text{where } X_m^2 \text{ reactance of the unknown impedance}$$

$$X_m^2 = X_C^2 - X_L^2 \\ = X_C^2 - X_{C_2}^2 \\ = \frac{1}{\omega C_2} - \frac{1}{\omega C_1} = \frac{C_1 - C_2}{\omega C_1 C_2} \quad \text{--- (3)}$$

If the unknown z is small inductance then the value of inductance is given by

$$L_m = \frac{C_1 - C_2}{C \omega^2 C_1 C_2} \quad \text{--- (4)}$$

L_m is inductive if $C_1 > C_2$ & L_m is capacitive if $C_1 < C_2$ (13)

Now the resistance R_m of the unknown impedance z is calculated by $R_2 = XC_2 / Q_2$ where $R_2 = R + R_m = \text{total}$ resistance of the circuit.

$$\therefore R_m = R_2 - R$$

$$= \frac{XC_2}{Q_2} - \frac{XC_1}{Q_1} = \frac{1/\omega C_2 Q_2 - 1/\omega C_1 Q_1}{\omega C_1 C_2 Q_1 Q_2} = \frac{C_1 Q_1 - C_2 Q_2}{\omega C_1 C_2 Q_1 Q_2} \quad (3)$$

* If the unknown impedance is purely resistive then the value of capacitor is $C_1 = C_2$

$$\therefore R_m = \frac{Q_1 - Q_2}{\omega C_1 C_2} \quad (4)$$

Now Q -factor of unknown impedance is

$$Q_m = \frac{X_m}{R_m} = \frac{C_1 - C_2 / \omega C_1 C_2}{C_1 Q_1 - C_2 Q_2 / \omega C_1 C_2 Q_1 Q_2}$$

$$\therefore Q_m = \frac{(C_1 - C_2) Q_1 Q_2}{C_1 Q_1 - C_2 Q_2} \quad (5)$$

If the unknown impedance z is large capacitor then

$$C_m^2 \frac{1}{\omega X_m} = \frac{\omega C_1 C_2}{\omega [C_1 - C_2]} = \frac{C_1 C_2}{C_1 - C_2} \quad (6)$$

By using equation (5) we calculate the Q factor.

* Measurement of High Impedance component

The high impedance components such as high value resistors, inductors & low value capacitors are measured by connecting them in parallel with the measuring circuit as shown below.

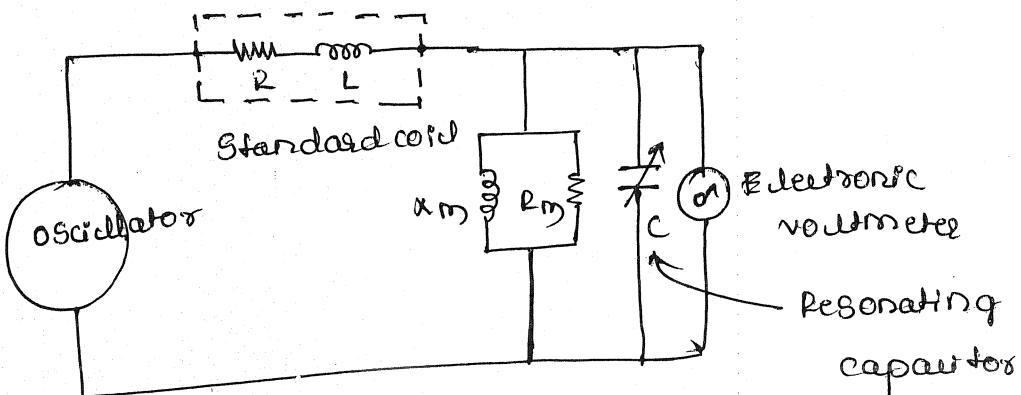


fig -

As shown in the above fig the unknown impedance Z is a parallel combination of X_m and R_m . During 1st measurement the unknown impedance Z is not connected in the circuit & the value of resonating capacitor is adjusted to a value c_1 , at which the circuit is in resonance. At resonance $X_L = X_C \Rightarrow \omega L = 1/\omega c_1$ — ①

$$Q_1^2 \frac{\omega L}{R} = 1/\omega c_1 R$$

* during 2nd measurement the unknown impedance Z is connected in the circuit, now the value of resonating capacitor is adjusted to c_2 at which the circuit is in resonance.

∴ now the reactance of the standard coil X_L is equal to parallel combination of X_m & reactance known reactance of resonating capacitor X_{C_2}

$$\therefore X_L^2 = \frac{X_m X_{C_2}}{X_m + X_{C_2}}$$

$$\text{or } X_L (X_m + X_{C_2}) = X_m X_{C_2}$$

$$\text{or } X_L^2 = \frac{X_m X_{C_2}}{X_{C_2}}$$

$$x_L x_m + x_L x c_2 = x_m x c_2$$

14

$$X_{C_2} X_m = X_L X_m = X_L X_C$$

$$x_m (x_{C_2} - x_L) = x_L x_{C_2}$$

$$\therefore x_m = \frac{x_L x_{C_2}}{x_{C_2} - x_L} = \frac{\frac{1}{\omega C_1} / \frac{1}{\omega C_2}}{\frac{1}{\omega C_2} - \frac{1}{\omega C_1}} = \frac{1}{\omega(C_1 - C_2)} \quad \text{--- (2)}$$

If the unknown impedance is inductive then
 $X_m = \omega L_m$ and hence

$$\therefore Lm^2 \propto m/\omega^2 \propto \frac{1}{\omega^2(c_1 - c_2)}$$

* If the unknown impedance is capacitive then

$$x_m = 1/\omega c_m \quad \text{and} \quad c_m = c_1 - c_2$$

$X_m = 1/\omega C_m$ and $C_m = C_1 - C_2$

* In a parallel resonant circuit, the total resistance of the circuit at resonance is equal to the product of Q-factor of the circuit Q_2 & reactance of the standard coil X_L .

$$\therefore R_T = Q_2 X_L$$

$$= a_2 \times c_1$$

$$\approx Q_2/\omega c_r$$

* The resistance of the unknown impedance R_m is determined by taking conductance $G_2/100$.

$$\therefore G_T = G_m + G_L = 1/R_T^2 \omega_{C_1} / Q_2$$

$$\text{now } g_m \approx g_T - g_L$$

$$\frac{1}{R_{\text{mos}}} = \frac{1}{R_T} - \frac{1}{R_L}$$

$$= \frac{\omega_0 C_1}{C_2} - R^2 / (R^2 + \omega_0^2 L^2)$$

$$V_{Rm} = \frac{\omega C_1}{Q_2} - \frac{1}{R} \left[\frac{1}{1 + Q_1^2} \right]$$

normally the value of Q_1 is very large $\therefore 1 + Q_1^2 \approx Q_1^2$

$$\therefore V_{Rm} = \frac{\omega C_1}{Q_2} - \frac{1}{R Q_1^2}$$

$$= \frac{\omega C_1}{Q_2} - \frac{1}{R Q_1 \cdot Q_1}$$

$$= \frac{\omega C_1}{Q_2} - \frac{1}{R Q_1 \cdot \frac{1}{\omega C_1 R}}$$

$$= \frac{\omega C_1}{Q_2} - \frac{\omega C_1}{Q_1} = \frac{\omega C_1 Q_2 - \omega C_1 Q_2 - \omega C_1 (Q_1 - Q_2)}{Q_1 Q_2} = \frac{\omega C_1 (Q_2 - Q_1)}{Q_1 Q_2}$$

$$\text{or } R_m = Q_1 Q_2 / (\omega C_1 (Q_1 - Q_2))$$

now Q factor of the circuit is $Q_m = \frac{R_m}{X_m}$

* Errors

i) Error due to distributed capacitance.

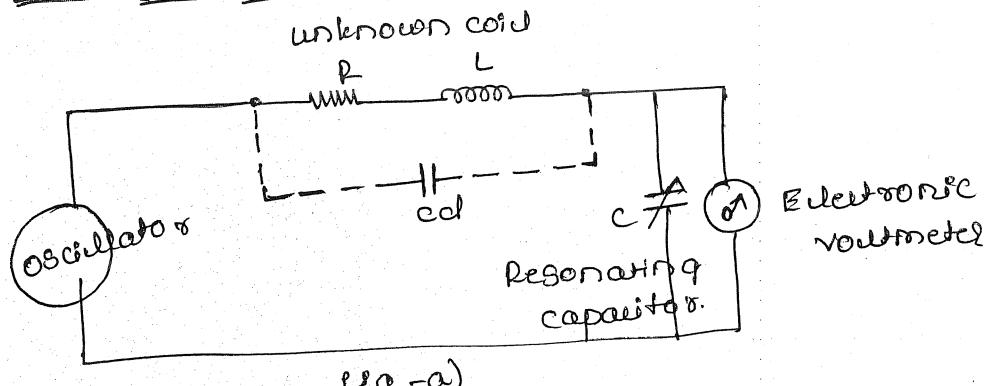


fig-a)

The distributed capacitance cd or self capacitance of the measuring circuit is the important source of error during the measurement of Q factor & inductance of the coil. The value of cd of a coil is measured by making two measurements

at two frequency of the circuit as shown below (15)

The coil under test is directly connected
in test terminal of the measuring circuit. The resonating
capacitor is tuned at two different frequencies f_1 &
 f_2 . & two values of C_1 & C_2 are noted down.

$$\text{Normally } f_2 = 2f_1$$

$$\text{Then } f_1 = \frac{1}{2\pi\sqrt{L[C_{1+cd}]}} \quad \text{--- (1)}$$

$$\& f_2 = \frac{1}{2\pi\sqrt{L[C_{2+cd}]}} \quad \text{--- (2)}$$

$$\text{as } f_2 = 2f_1 \Rightarrow f_2 = \frac{2}{2\pi\sqrt{L[C_{2+cd}]}} \quad \text{--- (3)}$$

from equations (2) & (3)

$$\frac{1}{2\pi\sqrt{L[C_{2+cd}]}} = \frac{2}{2\pi\sqrt{L[C_{2+cd}]}}$$

squaring on both the side

$$\frac{1}{L[C_{2+cd}]} = \frac{4}{L[C_{2+cd}]}$$

$$\frac{1}{C_{2+cd}} = \frac{4}{C_{2+cd}}$$

$$\therefore cd = C_2 - 4C_2$$

However the effective value of Ω with cd is

less than the true value of Ω of the coil.

True value of Ω factor is given by

$$\Omega = \Omega_e \frac{C + cd}{C}$$

where Ω_e is the effective value of Ω or
indicated value of Ω .

ii) Error due to insertion resistance R_{sh} .

The value of insertion resistance is very small is of the order 0.02Ω . The error due to R_{sh} depends on the magnitude of the unknown impedance. However the error due to insertion resistance R_{sh} is neglected, if the coil resistance is 10Ω , but it must be considered when coil resistance is 0.1Ω .

iii) Error due to residual inductance of the instrument

The residual inductance of the instrument is very small, of the order 0.015mH and affects the measurment of only small inductors of values less than 0.5mH . However its effect may be neglected when higher values of inductances are measured.

iv) Error due to conductance of Q voltmeter.

The conductance of the Q voltmeter has a shunting effect on the tuning capacitor at high frequencies. However this effect is usually neglected.

* A standard coil is connected across the terminals of a Q meter and resonance is attained, when the frequency of the supply is 160kHz and the value of the resonant capacitor is 200PF and the Q factor read is 80. An unknown impedance is connected in series with a standard coil and resonance is obtained when the value of the resonant capacitor is 180PF and the Q factor read

is 50, frequency of the supply being the same.
calculate the resistance and inductance of the coil. (16)

⇒ Solution :-

$$R_m = \frac{C_1 Q_1 - C_2 Q_2}{\omega C_1 C_2 Q_1 Q_2}$$

$$= \frac{200 \times 10^{-12} \times (80 - 180) \times 10^{-12} \times 50}{2\pi \times 160 \times 10^3 \times 200 \times 10^{-12} \times 180 \times 10^{-12} \times 80 \times 50}$$

$$R_m = \underline{\underline{48.354 \Omega}}$$

$$X_m = \frac{C_1 - C_2}{\omega C_1 C_2} = \frac{200 \times 10^{-12} - 180 \times 10^{-12}}{2\pi \times 160 \times 10^3 \times 200 \times 10^{-12} \times 180 \times 10^{-12}}$$

$$= \underline{\underline{552.62 \Omega}}$$

$$L_m = \frac{X_m}{2\pi f} = \frac{552.62}{2\pi \times 160 \times 10^3} = 0.5497 \text{ mH.}$$

* A coil is tuned to resonance at 600kHz with a resonating capacitance of 40nF. At 800kHz, the resonance is obtained with a resonating capacitance of 17.5nF. Find the self-capacitance of the coil and its inductance

$$\Rightarrow C_d = \frac{C_1 - 4C_2}{3} = \frac{175 \times 10^{-12} - 4 \times 40 \times 10^{-12}}{3} = 5 \times 10^{-12} = 5 \text{ nF}$$

$$f_1 = \frac{1}{2\pi\sqrt{L(C_1 + C_d)}}$$

$$300 \times 10^3 = \frac{1}{2\pi\sqrt{L(175 \times 10^{-12} + 5 \times 10^{-12})}} \\ \approx 1.564 \text{ mH}$$

$$L = \frac{1}{(2\pi \times 300 \times 10^3)(180 \times 10^{-12})}$$

* Compute the value of the shunt capacitance of a cold when the Q meter circuit is tuned to resonance

i) When $f_1 = 2 \text{ MHz}$, $C_1 = 450 \text{ pF}$ and ii) when $f_2 = 5 \text{ MHz}$,

$$C_2 = 60 \text{ pF}$$

$$\Rightarrow f_1 = \frac{1}{2\pi\sqrt{L[C_1+cd]}} \quad \text{and} \quad f_2 = \frac{1}{2\pi\sqrt{L[C_2+cd]}}$$

$$\text{or } \frac{f_2}{f_1} = \frac{\sqrt{L[C_2+cd]}}{\sqrt{L[C_1+cd]}} \quad \text{or} \quad \frac{f_2^2}{f_1^2} = \frac{C_2+cd}{C_1+cd}$$

$$\frac{5^2}{2^2} = \frac{450 \times 10^{-12} + cd}{60 \times 10^{-12} + cd}$$

$$\therefore cd = 14.29 \text{ pF}$$

* A cold coil with a resistance of 12Ω is connected across the test terminal of a Q meter circuit and resonance occurs when the frequency of the oscillator is 1000 kHz and the capacitance of resonating capacitor is 45 pF calculate the % error introduced in the calculated value of Q due to an insertion resistance of 0.02Ω across the oscillator?

$$\Rightarrow \text{Actual value of Q-factor } Q_a = \frac{1}{wCR}$$

$$Q_a = \frac{1}{2\pi \times 1000 \times 10^3 \times 45 \times 10^{-12} \times 12} = 176.84$$

$$\text{Indicated value } Q_i = \frac{1}{wC(R+0.02)}$$

$$= \frac{1}{2\pi \times 1000 \times 10^3 \times 45 \times 10^{-12} \times (12+0.02)}$$

$$= 176.54$$

$$\% \text{ error} = \frac{Q_a - Q_i}{Q_a} = \frac{176.84 - 176.54}{176.84} \times 100 = 0.17\%$$

* Electronic energymeter

(17)

An electronic energymeter has the following advantages over the conventional energymeter.

- 1) There are no friction losses.
- 2) The various adjustment for low load, full load, pt, creeping etc, are not necessary.
- 3) The common errors found in the conventional energymeter are not found in electronic energymeter.
- 4) Accuracy is more which is about $\pm 1\%$.

*

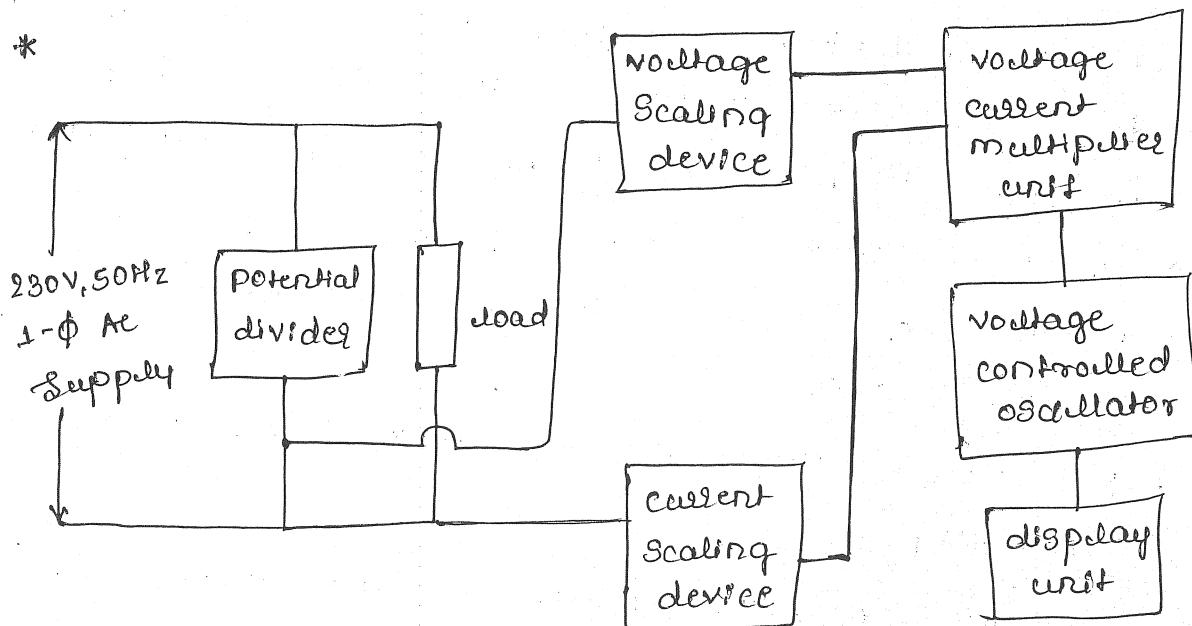


Fig- Electronic Energy meter.

The block diagram of Electronic Energy meter is as shown above, An electronic energymeter extensively uses integrated circuit for operation.

* The measurement of energy is basically a process of the measurement of power & the time duration of its consumption.

- * The electronic energymeter operates in two stages. In the 1st stage it acts as wattmeter and measures the power consumed by the load in watts.
- * In the 2nd stage the power consumed for a particular interval of time is monitored. However the conversion of watts into watt-hour takes in the 2nd stage.

The operation of electronic energymeter is explained with the help of block diagram as shown above.

- The average power is equal to the mean product of the instantaneous voltage across the load & instantaneous current through it. The supply voltage is brought to proper level by voltage scaling device.
- * Another voltage developed by the CDS is proportional to the load current is determined by the current scaling device.

- * Both these voltages are feed to a quadrant voltage CDS multiplier unit
- * multiplier performs product of alternating voltage & CDS, oscillator generates a square wave, the frequency of which depends on the output current of the quadrant multiplier which depends on the power dependent CDS & frequency pulse.
- * The combination of power dependent CDS & frequency pulse dependent CDS gives the energy consumed by the load in watt hour.
- * The analog signal is converted to converted to digital using ADC and displayed on display unit.

Module - 5 - Display devices.


In any electrical & electronic measurements, it is necessary to display the information about the quantity being measured, in order to have a record of what is to be measured.

- * A recorder is a device whose function is to record the value of a quantity which is to be measured.
- * A recorder helps to preserve the experimental data which could be obtained at any instant & it also gives the information about waveforms, transient behaviour & phase relationships of the quantity recorded in the different parts of circuit.

* Segmental displays.

The segmental displays are either 7 or 14 segmental, depending on whether the display is numeric or alphanumeric.

* Seven Segment display.

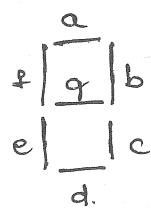

The above fig shows a 7 segment display, used for numeric display. It consists of seven segments a, b, c, d, e, f, and g.

Fig - 7 segment display. * By illuminating proper segments any number can be displayed.

* As shown above if all the segments are illuminated the digit displayed is 8.

* If only the segment $f \& g$ is illuminated then the displayed digit is 1. like this way all the digits from 0 to 9 is displayed.

0 1 2 3 4 5 6 7 8 9

fig-Seven Segment display of digits

* The display is incandescent & it operates on 110V voltage (12.48 V) and it requires 10 to 50mA current when using LEDs, LCDs are also used for 7 segment displays.

b) Fourteen Segment display

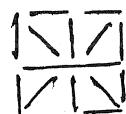


fig-a) 14



fig-b) display of alphabets A, B & C.

Segment display

for the display of alphanumeric, a fourteen segment display is used, as shown above.

* Nixie tube:



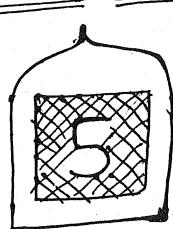


fig-a) Front view

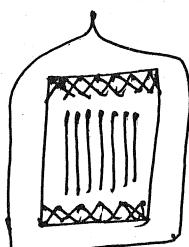

b) Side view

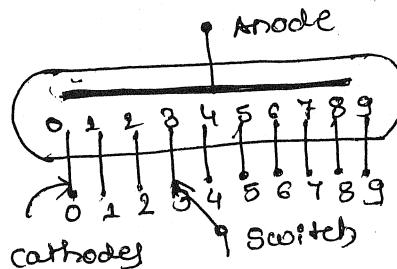

c) Schematic diagram

A nixie tube is a non-polarized digital display device as shown in fig a, b & c.

- * It is a cold cathode glow discharge tube, which is popularly known as nixie tube. The display works based on the principle that, when gas breaks down, a glow discharge is produced.
- * A gauge electrode with a +ve voltage supply functions as anode, as shown above it consisting of 10 separate cathode wires, each in the shape of numeral from 0 to 9.
- * The electrodes are enclosed in a gas filled envelope with connecting pins at the bottom, usually a neon gas is used which gives an orange red glow; when it is activated, different gases can be used for different colours.
- * It consisting of one anode & 10 cathode, when -ve voltage is applied to the selected cathode, a simple gas discharge & selected digit will light.
- * The nixie tubes are bulkier in size than seven segment displays.
- * Modern nixie not only display decimal digits from 0 to 9 but it also display decimal symbol, + and - signs.
- * They have 15 cathode segments, which are used to display numbers as well as alphanumeric characters.

* Light Emitting diode (LED)

The LED is a device which produce visible light, when it is energised.

* LEDs are semiconductor diodes which normally use gallium arsenide and gallium arsenide phosphide, which emit visible electromagnetic radiation, red in colour under forward biased condition.

* However the combination of other semiconductor materials give other colours such as amber, green, yellow etc.

* due to lower power requirement, high operating speed & high reliability made LED's are favoured type of displays.

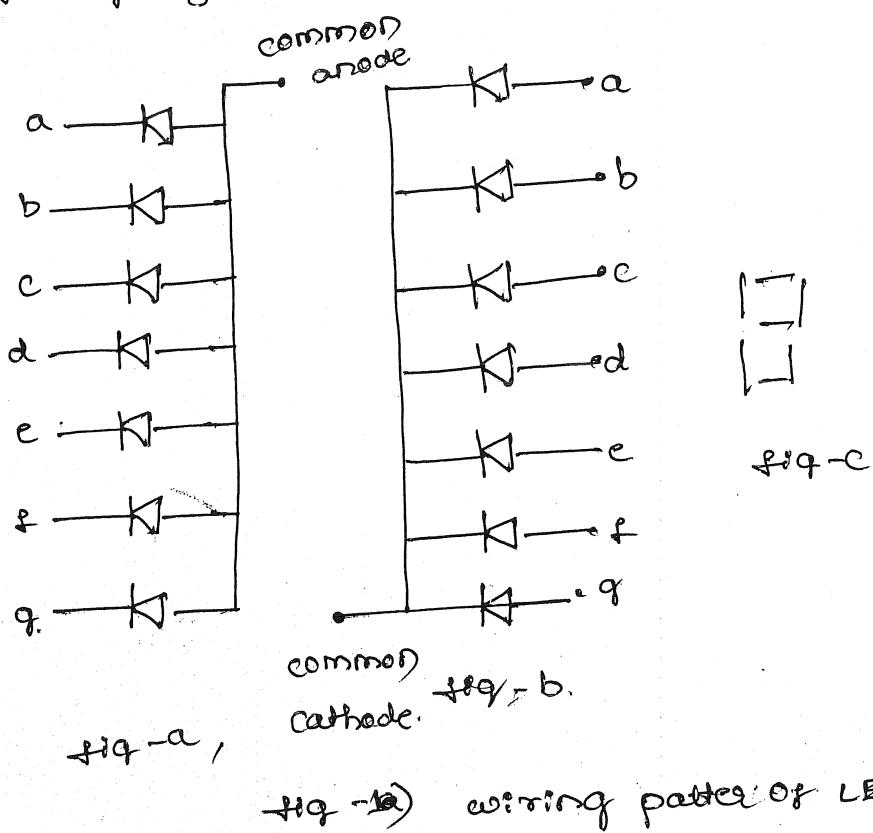


Fig - a) wiring pattern of LED.

* Liquid crystal display (LCD)

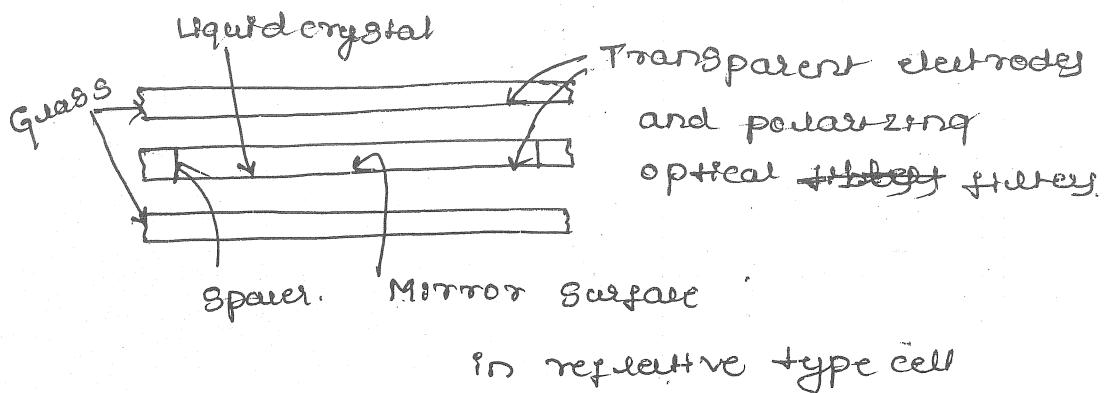


fig-a) construction of LC cell

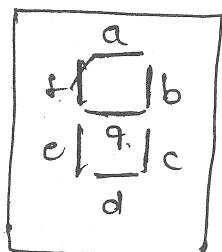


fig-b) Liquid crystal cell, 7 segment display

- * The liquid crystals exhibit properties of liquid as well as solid. They are the compounds having crystalline arrangement of molecules, but they still flow like liquid.
- * However the liquid crystal displays do not emit or generate light, but they alter externally generated illumination.
- * depending on the principle of operation there are two types of LCDs.
 - i) dynamic scattering LCD.
 - ii) field effect LCD.

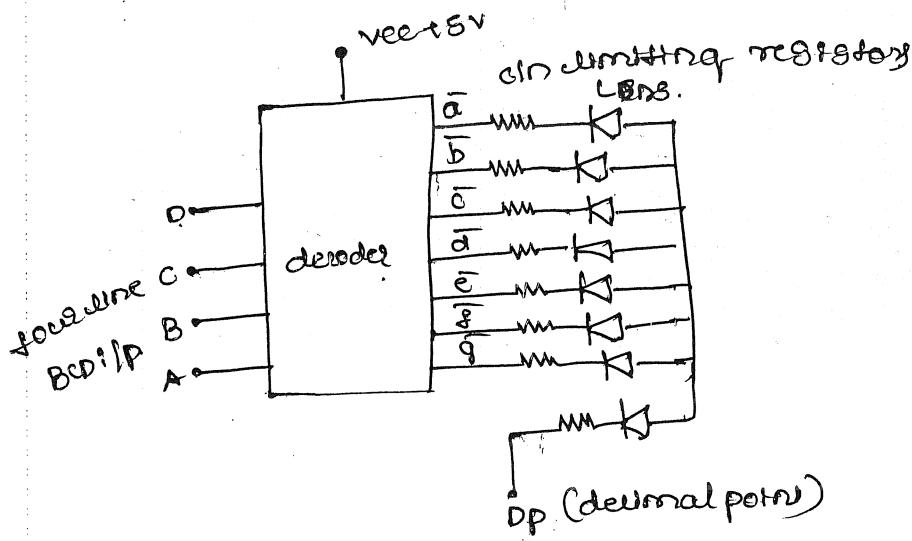


fig -2) LED 7 Segment display driver.

The above fig a represents the wiring pattern of LED 7 segment display having common anode for all seven segments. & fig b represents common cathode display.

The common cathode LEDs have to be driven by 'active-high' decoder ICs and the common anode LEDs are driven by active low decoders which is connected to seven-segment display as shown above.

Current limiting resistors are included in series with each of the LED's corresponding to the seven segments.

* An additional LED corresponding to the decimal point is also provided in the display along with current limiting resistor. The value of series resistor is 250Ω & R_s is 20mA .

* principle of operation

The cross section of field effect liquid crystal cell is as shown in fig a.

* The liquid crystal material may be one of several organic compound that exhibit the optical property of crystal.

* As shown above it consists of two glass plates, a liquid crystal ^{not} film is sandwiched b/w two glass sheets with transparent electrodes deposited on the inside face.

* When the cell is energized, the liquid crystal material twists & the light passes through the cell which allows the light to pass through the optical filter and cell disappears into the background.

* When cell is energized, there is no twisting of light & energized cell in 7-segment display stand out against the background as shown in fig b.


* advantages of LCD

- 1) Low cost
- 2) uniform brightness with good contrast
- 3) less consumption of energy

* disadvantages

- 1) Reliability is less.
- 2) Limited temp range
- 3) slow speed @ if require an ac drive

* Liquid vapour display.

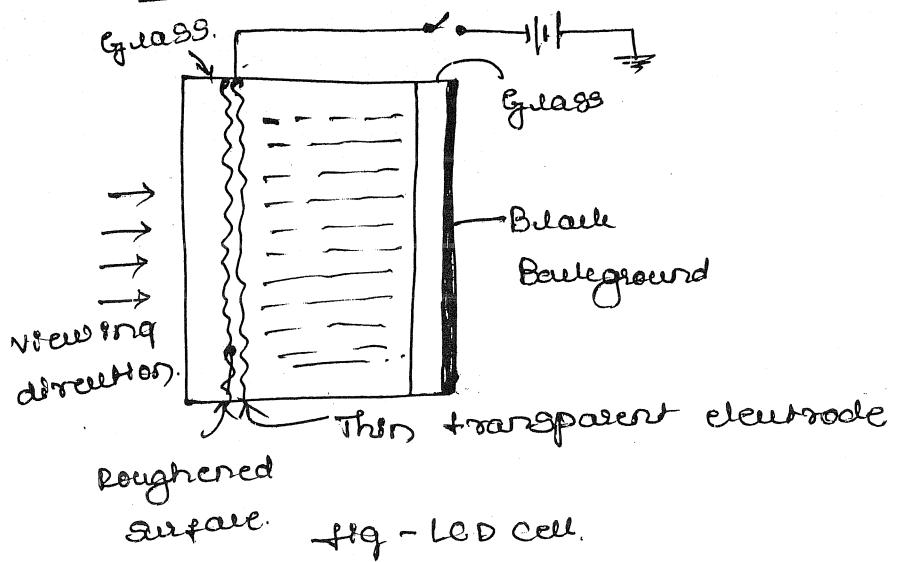

The construction of liquid vapour display is as shown in the above fig,

As shown above it consisting of two glass plate with transparent liquid enclosed in it.

* The background of a rear glass is totally black.
* The voltage drive is used to heat a transparent electrode.

In during OFF condition of the display, only the black background is viewed through transparent glass electrode.

* To make display on, voltage is applied to the electrode, generating heat in electrode.

* which evaporate the liquid, ∴ around the roughened surface vapour films & vapour bubbles are formed.

* due to which there is discontinuity in the glass plate & liquid surface hence light scattering.

tales plate

* However, refractive index of the liquid should be close to the glass.

* The draw back of LCD is Speed of operation is very low.

* Dot Matrix display.

A dot matrix display uses a LED at each dot location in Matrix. A matrix is formed with the wiring patterns.

* The most commonly used dot matrices are 5x7, 5x8, 7x9, out of these three patterns, 5x7 wiring pattern is most commonly used.

* The wiring patterns may be a common anode or common cathode type.

* Bar graph display.

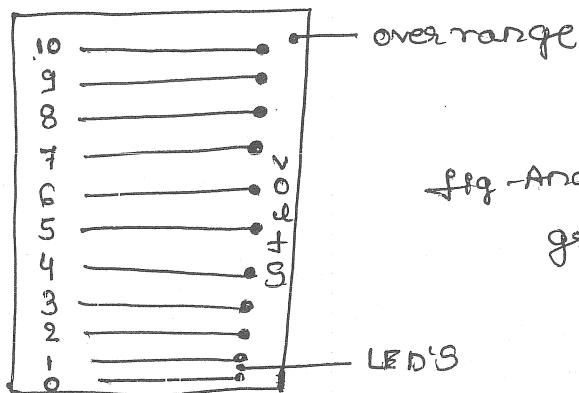


fig-Analog meter using bar graph of LED'S.

The bar graph display is an analog display. In this display, the display elements are arranged in a column in a linear array.

* The dot LEDs are independently driven so that

the length of the array correspond to the voltage or current measured

- * They are used in panel meters which accept analog input signals & produce equivalent display of input signal.

[* Incandescent

A Seven - segment display is a set of seven bar-shaped LED or LCD elements arranged to form a square. A few seven segment displays are other illuminated devices such as incandescent or gas-plasma ("neon") lamps.

- * An incandescent bulb, incandescent lamp or incandescent light globe is an electric light with a wire filament heated to such a high temperature that it glows with visible light.
- * The filament is heated by passing an electric current through it, it is protected from oxidation with a glass or quartz bulb which is filled with inert gas.
- * Fluorescent (vacuum fluorescent display) - is a display device which is commonly used on consumer-electronics equipment such as video cassette recorders, car radios & microwave ovens. A VFD - ~~works~~ operates ~~such as~~ CRT.]

* Character formats

The choice between the display devices and recorders depend on i) the expected use of the output
ii) The information content of the output.

The 1st factor depend on whether whether the O/P is useful for human observation or to be stored for other purpose or it is an input to the digital computer.
The 2nd factor is influenced by the fact that the output is single valued or is in the form of time or frequency.

* depending on the type of output format required, the devices are divided into following types

1) Single no output device :- In such device the output is time invariant quantity over a particular period of time, and it is displayed as a single number representing the value of quantity being measured.
+ the single number may be a short interval of time
for example - indicating instruments & digital display device

2) Time domain output device => In such a device, the O/P being measured is the function of time, & display unit are not satisfactory except for outputs which change very slowly with time.

If the information is to be stored for a particular time, then storage type CRT can be used.

3) Machine interruptible output device :- In such a device, the O/P must be in such format that, a machine

a m/c must be able to read it

- * The m/c interruptible output may be in the analog form or digital form
- * A ~~single~~ recorded on a magnetic tape, punched card, a floppy disc or hard disc may be used as an input for output devices like digital display unit, a printer or a digital computer.

* Incandescent & Fluorescent displays

There are various types digital display units in the visual form. The LED and LCD displays are very popular & they are most commonly used in hand held m/cs like calculators





- * Some of the other forms used in displays are Incandescent & Fluorescent displays.
- * Incandescent displays can be made in wide range of sizes and colours & they are brightest displays
- * the main disadvantage of Incandescent display is a low reliability due to segment failure
- * The incandescent displays have seven segment filaments contained within a single vacuum envelope & they are compatible with 5V TTL voltages
- * Multiplexing is not advantageous for this type of display, since each of the display segment require a diode to prevent leakage paths.
- * The fluorescent displays are mainly used in calculators & the colour of display is blue-green

The character height is upto 1.5cm, their low ZTMA , and low voltage (30V) are ideal for multiplexing.

* display multiplexing.

In a display device the digits are driven by a decoder. By time sharing the decoder, it is possible to reduce the count of components & interconnections in display systems.

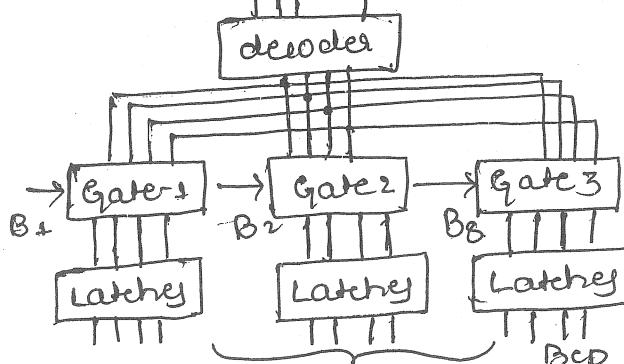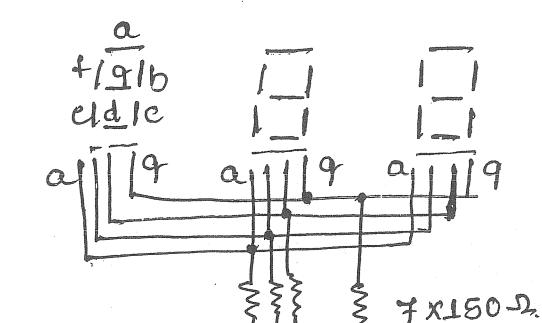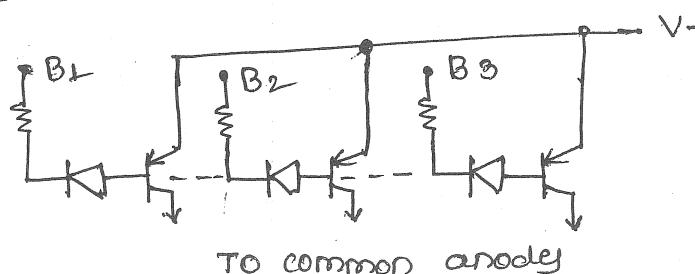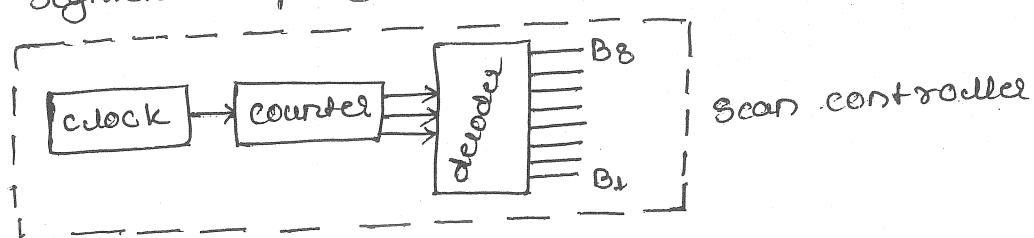A typical circuit scheme for multiplexing eight seven segment displays is as shown below.



+9 - multiplexed
+ - segment display

BCD trip to be displayed

- The input in BCD form is applied to the latch whose outputs are fed to the open collector gates
- * The outputs of gate are "wired-OR" and fed to a single "BCD to Seven Segment" decoder
 - * The seven segments of each of the eight display digits are parallel & fed from through the decoder through current limiting register.
 - * at any instant, however, only one of the digits is displayed as selected by decoder output from the Scan collector.
 - * For any particular digit ^{to be} Selected, the transistor connected to common anode of that digit is turned ON & gate corresponding to that digit is enabled.
 - * In this way each digit is enabled sequentially
 - * Other displays such as incandescent & fluorescent displays can also be multiplexed in similar way

* Zero Suppression

- In multi digit displays with dp. (decimal point) it is advantageous to suppress zeros preceding the significant digits & following the decimal point
- * for example the display ~~0007.200~~ may be display as 7.2, ~~in order to support~~
 - * The decoder device of many seven segment displays with ^{additional} input / output control named as ripple blanking input (RBI) & Ripple blanking off (CBO).

RBO assuming a '1' level when the character being measured
(displayed) is a '0'

* The application of this '1' level by RBI for the
decoder in the next lower significant digit position
will ensure that the displayed character is zero.


* The RBO of the second decoder will furnish form
RBI for the next lower significant decoder

* Since the suppression of the least significant
integer is zero, which is not usually desired.

* A similar procedure in the reverse order is used
for the banning of trailing edge zeros

cd

d

 

* Cathode Ray tube (CRT)

The CRT is the heart of CRO, The CRT generates the electron beam, accelerate the beam, deflect the beam. The main parts of CRT are

- i) Electron gun ii) deflection System
- iii) Fluorescent screen iv) glass tube
- v) Base.

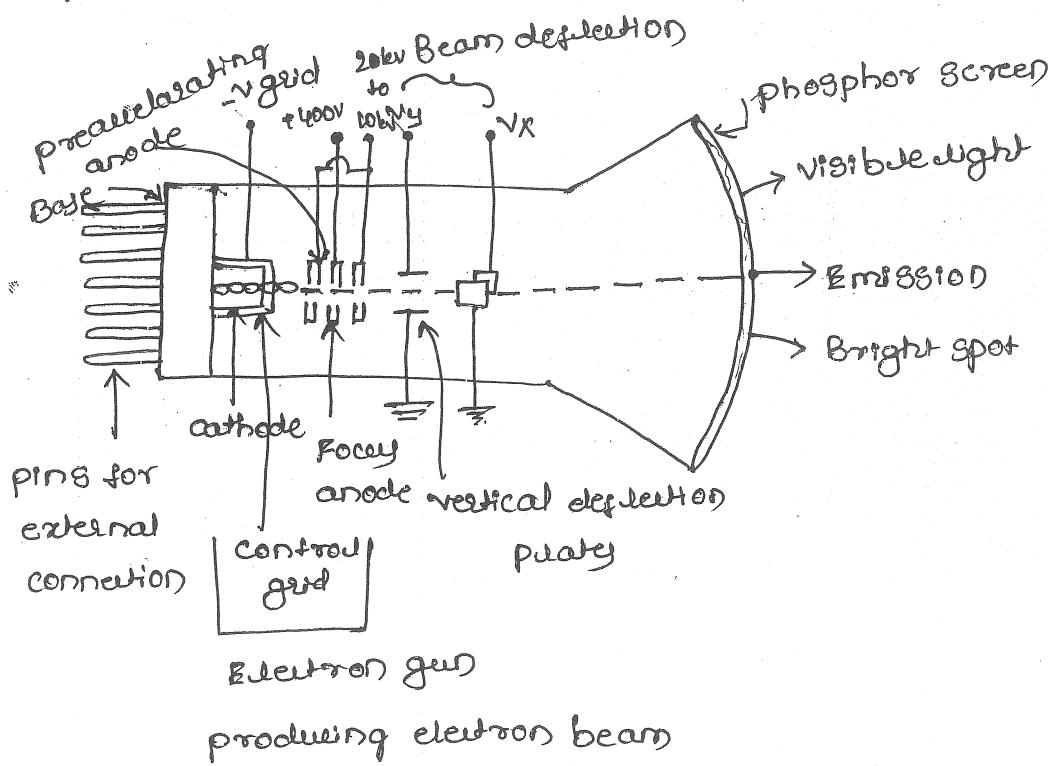


fig - cathode Ray tube.

* electron gun :- The electron gun section of CRT provides sharply focused electron directed toward the fluorescent-coated Screen.

* Initially thermally heated cathode emits the electrons, The control grid is at its negative potential w.r.t to cathode. & it controls the no of electrons in beam

- * The momentum of the electrons determine the intensity, or brightness, of the light emitted from the screen due to bombardment.
- * The light emitted is usually of the green colour.
- * The electrons are -vely charged, a repulsive force is created by the applying ~~to~~ -ve voltage to the control grid.
- * The similar charge on the electron repel each other To compensate for such repulsion force, an adjustable field is created b/w two cylindrical anodes called the focusing anode.
- * The preaccelerating and accelerating anode are connected to a common +ve high voltage which vary b/w 2kV to 10kV.
- * The focusing anode is connected to a lower +ve voltage of about 400V to 500V

* Deflection System

When the electron beam is accelerated it passes through the deflection system, with which beam can be positioned anywhere on the screen.

- * The deflection system of CRT consists of two pairs of metal plates referred as vertical and horizontal deflection plates. One terminal is grounded and another terminal is connected to certain Vtq.

- * A +ve ^{v_y}V_y is applied to the Y-input terminal, causing the beam to deflect vertically.
- Similarly a +ve voltage is applied to X-HP terminal which causes the electron beam to deflect horizontally.
- * The amount of vertical or horizontal deflection is directly proportional to the corresponding applied voltage.
- * When the voltages are applied simultaneously to vertical and horizontal deflecting plates, the electron beam is deflected due to the resultant of these two voltages.
- * The face of the screen can be considered as an X-Y plane. The (x,y) position of the beam spot is directly influenced by horizontal and vertical voltages applied to the deflection plates V_x & V_y respectively.
- * The horizontal deflection (x) produced is proportional to the horizontal deflecting voltage V_x, applied to X-Input.

$$\therefore x \propto V_x$$

$$x = k_x V_x \text{ where } k_x \text{ is proportionality constant.}$$
- * Similarly, the vertical deflection (y) produced will be proportional to the vertical deflecting voltage V_y, applied to the y-Input.

$$\therefore y = k_y V_y, k_y \text{ is the vertical sensitivity}$$

will be expressed as cm/volt or division/volt

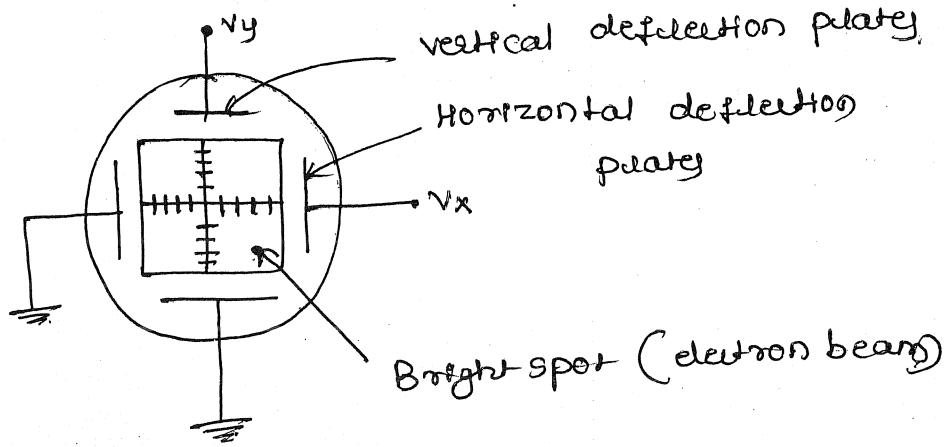


fig- Arrangement of plates in CRT

* Fluorescent Screen

The light produced by the screen does not disappear immediately after the signal becomes zero.

* The time period for which the trace remains on the screen after the signal becomes zero is known as "persistance".

* The persistance may be as short as a few microseconds or as long as tens of seconds or even minutes.

* Medium persistence traces are mostly used for general purpose applications.

* Long persistence traces are used in the study of transients. However it helps in the study of transients since the trace is still seen on the screen after even the transient has disappeared.

* Short persistance is extremely needed for high speed phenomena.

* The screen is coated with a fluorescent material called phosphor which emits light when

bombardeed by the electrons. various phosphors are available which differ in colour, persistence and efficiency.

* glass tube

All the components of CRT are enclosed in an evacuated glass tube called envelope, which allows the emitted electrons to move freely from one end of the tube to other end.

* Base :- The base is provided to the CRT through which the connections are made to the various parts.



* Recording device.




A recorder records both electrical & non-electrical as a function of time & it relates the signals of various quantity recorded.

* Electrical quantities such as current, voltage etc can be read directly & non electrical quantity such as pressure, temperature, speed etc are indirectly by 1st converting them into electrical quantity in the form of signal using transducer or sensors.

* Recording device are of two types namely

- i) Analog Recorders ii) digital recorders.

* X-Y recorders.

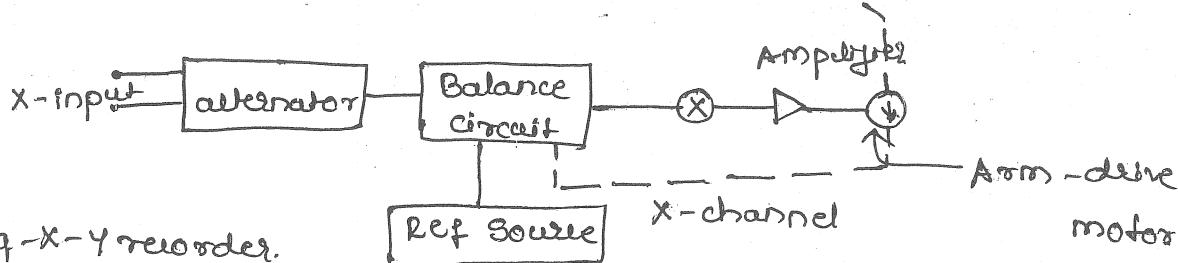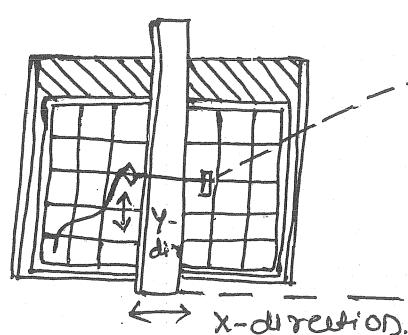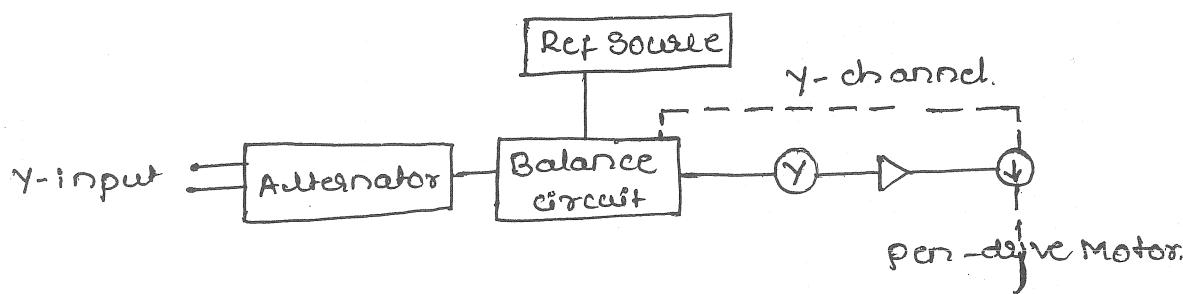

Hq-X-Y recorder.

Above fig shows an X-Y recorder, it consists of a pair of servo-systems, a driving recording pen in two axes through a proper sliding pen and moving arm arrangement, with reference to a stationary paper chart.

- * attenuators are used to bring the input signals to the certain level acceptable by the recorder
- * as shown above the signal entry each of the two channels, the signal is attenuated to a certain range of the recorder
- * each signal is then passed to a balance circuit, where it is compared with an ref voltage. ~~so that~~
- * The error signal is the difference b/w the two input signal voltage and the reference voltage.
- * The signal is amplified with the help of amplifier in order to actuate a servomotor, which is used to balance the arm & hold it in balance w.r.t the value of the quantity being recorded.
- * The above action takes place in both X and Y axes simultaneously, they giving a record of one quantity as a variable with respect to other quantity.
- * An X-Y recorder may have sensitivity of 10 mV/mm , a scanning speed of 1.5 m/s & a frequency response of 6 Hz for both axes, the accuracy of recorder is about $\pm 0.5\%$.

The use of X-Y recorder in Laboratory supports many meas & tests such as

- 1) Speed-torque characteristics of motor.
- 2) Regulation curves of power amplifiers.
- 3) plotting stress-strain & hysteresis curves.
- 4) variation of resistance with temp' curves etc.
- 5) plotting the characteristics of electronic devices such as vacuum tubes, zener diodes, rectifiers, transistors etc.

* Galvanometric Recorder

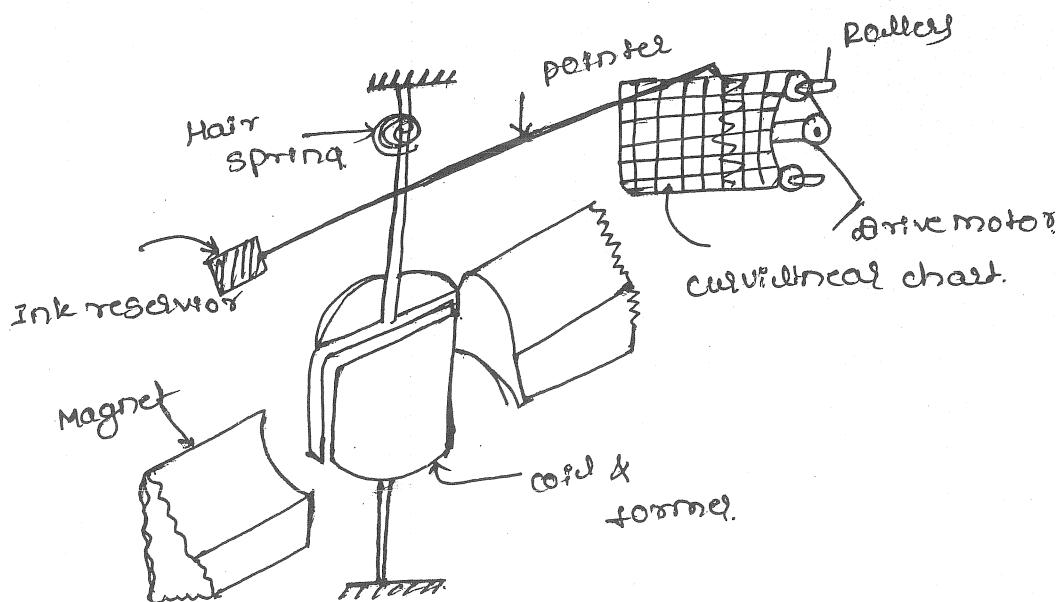


fig-a) Galvanometric type recorder.

* principle of operation

The galvanometric type of recorder is a strip chart type recorder, this type of recorder is based on the principle of D'Arsonval movement, if any D'Arsonval galvanometer. The galvanometer produces the deflection

When current passes through the coil

- * The deflection of galvanometer produces torque which is used for recording purpose
- * The coil which is passed through the coil is directly proportional to the physical quantity to be measured.
- * construction :- The above fig shows galvanometric type of recorder, as shown above the moving coil with pointer is kept in the strong magnetic field. The pen-ink srm is fitted to pointer for recording the input signal.
- * The pen-ink srm consisting of recording pen at one end and ink reservoir at other end.
- * due to gravity & capillary action, ink flows from reservoir to pen through tube.
- * The paper is pulled with the help of pull mechanism which is given by motors.
- * operation :- The pointer starts deflection when current flows through the coil, as current is related to I.P. signal flowing through the coil, the magnetic field density changes.
- * The variation of magnetic field is according to the I.P. coil, the change in magnetic field interacts with magnetic field produced by the permanent magnet used, which causes the rotation of moving coil in angular direction.

- * as the coil is moving as per the IIP current, the pen is deflected across the pen & IIP signal is to be recorded.
- * if the amplitude IIP signal is more the deflection of the pointer is more, when the pointer comes to rest the pen also comes to rest, the pointer comes to rest due to torque exerted by the hairspring.
- * the recorder by curvilinear slit of tracing, the paper used in this recorder is generally heat sensitive & pen-ink mechanism is replaced with a heated tip stylus.

* Advantages

- 1) The slit is comparatively inexpensive
- 2) The galvanometric type recorder records very low frequency of signals
- 3) It offers multiple channel operation.
- 4) As the speed of paper is determined by the gear ratio, we can change the speed of paper as per requirement.

* disadvantages

- 1) It is having very small bandwidth of about 0-10Hz
- 2) It is having small sensitivity of about 0.4V/mm
- 3) It can record fast varying signals such as current, voltage or power.
- 4) Its performance is affected by friction losses due to large mass of the moving coil & stylus.

* Circular chart Recorder

It is basically a graphic recorder which records the data on a flat circular chart, the below fig shows Circular chart Recorder.

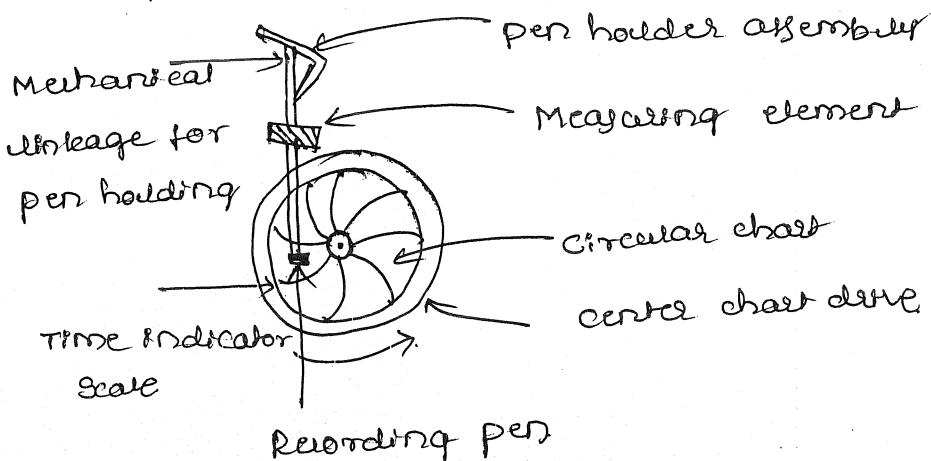


fig- circular chart recorder.

* It consists of important blocks namely measuring element, operating mechanism, chart drive & recording device.

* A circular chart with scale printed on it is mounted on flat plate supported with spring.

* a measuring element operate with operating mechanism through mechanical linkage which is used to pass parameter measured by the measuring element, to the recording device.

* different types of drive are used to drive circular chart. The drives are mechanical pneumatic, electric type.

* The most commonly used drive is synchronous.

* Frequency Modulator Recording. (FM) recording.

The major disadvantage of direct recording is that it is difficult to record dc signals, this difficulty can be overcome by using FM recording.

* principle of operation:

In the FM recording, the carrier frequency f_c is modulated by the input signal. FM recording uses the variation of frequency to carry the required information instead of varying the amplitude.

* The modulating signal is recorded using the recording head in normal way & then reproduced signal is passed through FM demodulator, low pass filter to get original signal.

* operation

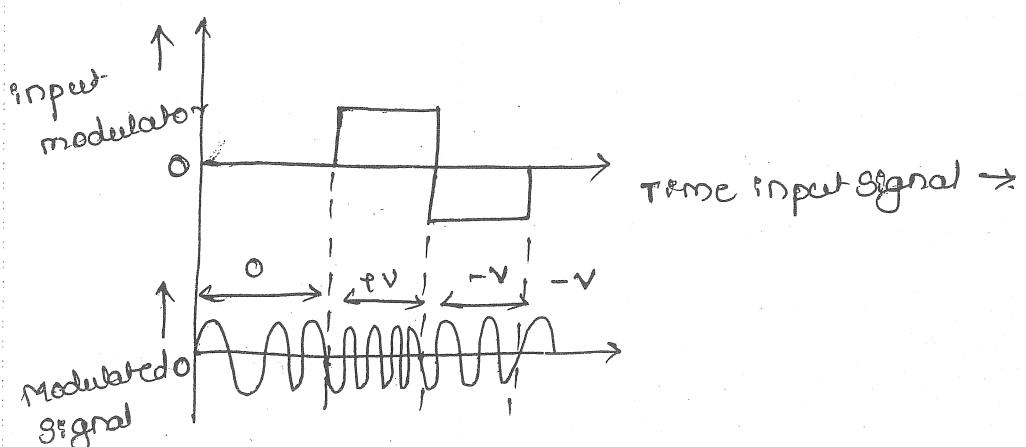
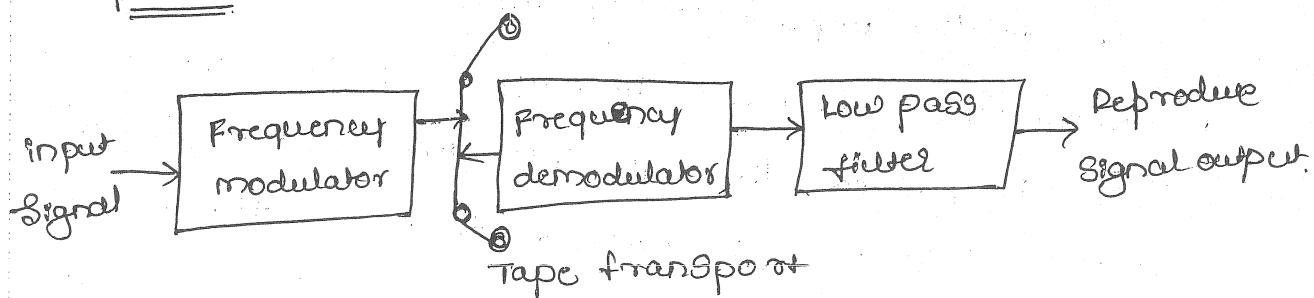


fig-Basic FM Recording system.

- * In this system, the carrier frequency is called as center frequency f_c , this frequency is modulated by the level of the input signal.
- * When the input signal is zero, the modulator contains only the center frequency oscillation.
- * The +ve ilp voltage deviates the carrier frequency by specified % in one direction, the -ve voltage deviates the carrier frequency by specified % in other direction.
- * When ilp is dc, the modulated ilp is a signal of constant frequency & when ilp is ac modulated output is a signal of variable frequency.
- * However the frequency variation is directly proportional to the amplitude of input signal.
- * during the playback, the output of the reproducing head is passed through FM demodulator. The demodulated signal is passed through the filter which removes carrier frequency f_c and the unwanted signals.
- * FM demodulator converts the difference b/w center frequency and frequency on the tape to a voltage which is proportional to frequency difference.
- * The frequency deviation selected is $\pm 40\%$ about carrier frequency. When tape speed is changed there is proportional change in the carrier frequency, \therefore de signal the wavelength λ remains same ^{for}.

$\lambda = V/f$ and speed V changes, the frequency also changes

* There are two factors related to FM recording

i) percentage deviation

ii) deviation ratio.

* Percentage deviation :- It is defined by the ratio of carrier deviation to center frequency. It is denoted by M .

$$\therefore \text{percentage deviation } M = \frac{\Delta f}{f_c} \times 100. \text{ It is also}$$

known as modulation index.

* Deviation ratio :- It is the ratio of carrier deviation from center frequency to the signal frequency or modulating frequency. denoted by S

$$S = \frac{\Delta f}{f_m} \quad \text{where } f_m = \text{modulating frequency.}$$

& Advantages of FM recording

i) FM recording is used mainly to record dc component.

ii) It has wide frequency range of from 0 Hz to several kHz.

iii) Amplitude variation is neglected in FM recording

& input signal is correctly recorded.

iv) FM recording is used for recording non electrical quantity such as force, pressure etc.

v) used for multiplexing in the instrumentation & process plant.

* Disadvantages

i) The tape speed fluctuations affect FM recording.

- 2) For FM recording high speed is required
- 3) It is expensive.
- 4) the circuitry used for FM recording is complicated compared to direct recording.