



### FIRST INTERNAL ASSESSMENT

Sem: III<sup>rd</sup>

Subject: Electrical & Electronic Measurements

Sub. Code: 17EE36


Date: 12/09/2018

Time: 3PM to 4PM


Max. Marks: 30

*Note: Answer two full questions..*

Q.No	Description of Questions	Marks	CO	RBT Level
1	a The resonant frequency of an ac series circuit given by $f_r = 1/2\pi\sqrt{LC}$ determine the values of a and b.	6	206.1	L <sub>1</sub> ,L <sub>2</sub> ,L <sub>3</sub>
	b Define sensitivity of Wheatstone bridge & derive the expression for sensitivity of bridge in terms of voltage sensitivity of galvanometer.	6	206.1	L <sub>1</sub> ,L <sub>2</sub> ,L <sub>3</sub>
	c Explain the sources and detectors used in ac bridges.	3	206.1	L <sub>1</sub> ,L <sub>2</sub>
<b>OR</b>				
2	a With neat circuit diagram describe the operation of Maxwells inductance capacitance bridge for the measurement of inductance & Q factor.	6	206.1	L <sub>1</sub> ,L <sub>2</sub> ,L <sub>3</sub>
	b With neat sketch explain the operation of fall of potential method for the measurement of earth resistance.	6	206.1	L <sub>1</sub> ,L <sub>2</sub>
	c Explain the shielding of bridge elements in ac bridges.	3	206.1	L <sub>1</sub> ,L <sub>2</sub>
3	a Derive the balancing equation of kelvins double bridge.	6	206.1	L <sub>1</sub> ,L <sub>2</sub> ,L <sub>3</sub>
	b With neat sketch explain the operation of Megger.	6	206.1	L <sub>1</sub> ,L <sub>2</sub>
	c The thevenins equivalent voltage of a Wheatstone bridge is 25mv and the galvanometer current is 20μA. The resistance of the galvanometer is 50Ω. The ratio arms have resistances of 1000Ω and 5000Ω respectively. Find the value of the standard resistance for which the above conditions are satisfied. The value of the resistance to be measured is 600Ω.	3	206.1	L <sub>1</sub> ,L <sub>2</sub> ,L <sub>3</sub>
<b>OR</b>				
4	a With neat sketch obtain the general equilibrium equation for ac bridges.	5	206.1	L <sub>1</sub> ,L <sub>2</sub> ,L <sub>3</sub>
	b Discuss the method of determining capacitance and dissipation factor using low voltage Schering Bridge.	6	206.1	L <sub>1</sub> ,L <sub>2</sub> ,L <sub>3</sub>
	c List out limitations of Wheatstone bridge.	4	206.1	L <sub>1</sub> ,L <sub>2</sub>

  
Course Coordinator  
[ Prof. S.G.Huddar ]

  
Module Coordinator  
[ Prof.S.S.Birade ]

  
HOD  
[ Dr.B.V.Madiggond ]



S J P N Trust's  
Hirasugar Institute of Technology, NDS

Inculcating Values, Promoting Prosperity  
Approved by AICTE and Affiliated to VTU Belgaum.

E & E Dept  
Exam  
IA Scheme  
2018-19 (Odd)

SCHEME OF EVALUATION IA - 1<sup>st</sup>

Page No : 01/04

SEM: 3 <sup>rd</sup>	SUBJECT: E & EM	SUBJECT CODE: 17EE3C	DATE: 12/09/18	
Q.No.	Bits	DESCRIPTION	Marks	CO's
1	a	The resonant frequency of an ac series circuit is $f_r = 1/2\pi LC$ , determination of the value of a & b	06	206.1
	b	definition of sensitivity of Wheatstone bridge & derivation of sensitivity of bridge in terms of $\delta V$	06	206.1
	c	Explanation for sources and detectors	03	206.1
		<u>OR</u>		
2	a	Neat sketch of Maxwell's inductance bridge operation & measurement of L & Q factor of bridge	02 + 04	206.1
	b	neat sketch of fall of potential method & operation of fall of potential method for the measurement of earth resistance	02 + 04	206.1
	c	Explanation for shielding of bridge elements in ac bridges	03	206.1
3	a	Derivation for balancing equation for kelvin's double bridge	06	206.1
	b	neat sketch of megger + operation of megger	02+04	206.1
	c	determination for the standard resistance value	03	206.1
4	a	neat sketch of ac bridge & general equilibrium equation of ac bridge	05	206.1
	b	determination of capacitance & dissipation factor of low voltage Schering bridge	06	206.1
	c	Limitations of Wheatstone bridge	03	206.1



S J P N Trust's  
**Hirasugar Institute of Technology, NDS**

Inculcating Values, Promoting Prosperity  
 Approved by AICTE and Affiliated to VTU Belgaum.

E & E Dept

Exam






IA Scheme

2018-19 (Odd)

**SCHEME OF EVALUATION IA - 1<sup>st</sup>**

Page No : 02/04

SEM: 3 <sup>rd</sup>	SUBJECT: E & EM	SUBJECT CODE: 17EE36	DATE: 12/09/18
----------------------	-----------------	----------------------	----------------

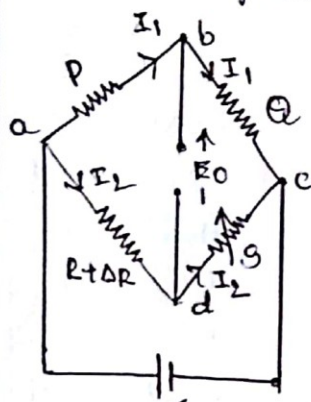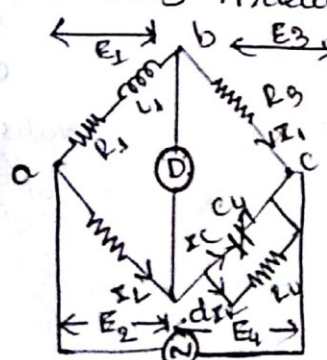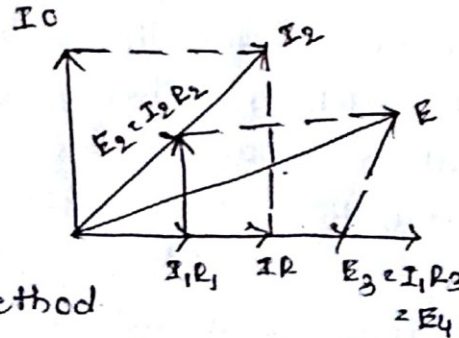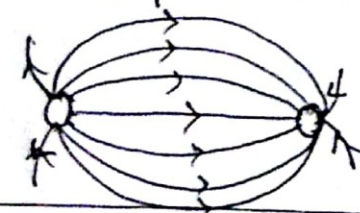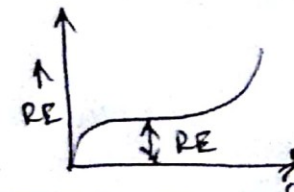Q.No.	Bits	DESCRIPTION	Marks	CO's
1)	a	$f_r = \frac{1}{2\pi} L a c b$ $[T^{-1}] = [ML^2T^{-2}I^{-2}]^a [M^{-1}L^{-2}T^4I^2]^b$ <p>By solving above expression we get  <math>a = -1/2</math> &amp; <math>b = -1/2 \therefore f_r = \frac{1}{2\pi} \sqrt{LC}</math></p>	06	206.1
	b	<p>Sensitivity of Wheatstone bridge <math>S_B = \frac{\Delta C}{ARIR}</math></p>  $V_{db} = E_0 = E \left[ \frac{R+\Delta R}{R+\Delta R+S} - \frac{R}{R+S} \right]$ $E_0 = ES\Delta R / (R+S)^2$ $S_V = \frac{\Delta C}{E_0} \Rightarrow \Delta C = S_V E_0$ $S_B = S_V E S R / (R^2 + S^2 + 2RS)$	06	206.1
	c	<p>Explanation for sources &amp; detectors of ac bridge</p>	03	206.1
		<u>OR</u>		
2	a	<p>Maxwell's inductance capacitance bridge.</p>  	06	206.1
	b	<p>Fall of potential method.</p>  	06	206.1



**SCHEME OF EVALUATION IA - 190**

Q.No.	Bits	DESCRIPTION	Marks	CO's
SEM: 3 <sup>rd</sup>		SUBJECT: E & E M	SUBJECT CODE: 17EE34	DATE: 12/09/18
		<p>Shielding of bridge elements in a bridge</p>	05	206.1
3	a	<p>Balancing equation for kelvin's double bridge</p> <p>fig - kelvin's double bridge</p> $P/Q = R/S$ <p>fig-c</p>	06	206.1



**SCHEME OF EVALUATION IA -19**

Page No : 04/04

SEM: 3rd	SUBJECT: E & EM	SUBJECT CODE: A7EE3L	DATE: 12/09/18
----------	-----------------	----------------------	----------------

Q.No.	Bits	DESCRIPTION	Marks	CO's
-------	------	-------------	-------	------

b Meqgel

fig-Meqgel.

c.  $Z_g = R_0 / R_0 + R_g \Rightarrow R_0 = 1950 \Omega$   
 $R_0 = R_B / R_{tS} + P_Q / P_{tQ} = 1868.67 \Omega$

4 a

$Z_1 || L_1 || X || Z_4 || L_4 = Z_2 || L_2 || X || Z_3 || L_3$

$R_1 R_4 + j(X_1 R_4 + R_1 X_4) - X_1 X_4$   
 $= R_2 R_3 + j(R_2 X_3 + X_2 R_3) - X_2 X_3$

b low voltage Schering bridge.

$r_1 = R_3 C_4 / C_2$  &  $C_1 = R_4 / R_3$   
 $\tan \delta = \omega C_1 r_1 = \omega C_4 R_4$

- c. Limitations of Wheatstone bridge  
 (A) Resistance of lead  
 (B) contact resistance (C) Thermo-electric effect