

Transformer and generator

Module - I

Single phase Transformer :- operation of practical transformer under no-load and on load with phasor diagram. Equivalent circuit, OC & SC test, all day efficiency, Voltage Regulation & Significance.

practical transformer on no load with phasor diagram

practical transformer has iron loss and small amount of primary Cu loss.


The primary I_0 under no load has to supply these losses denoted as I_0

$$\bar{I}_0 = \bar{I}_c + \bar{I}_m$$

$I_m \rightarrow$ purely reactive component or magnetizing component to produce flux.

$I_c \rightarrow$ which supplies total losses called power component or wattful component or core loss component I_0 .

Phasor diagram

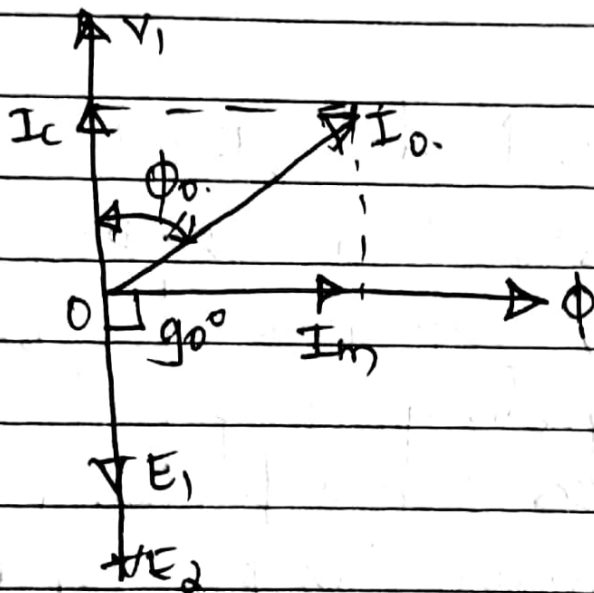

$$I_m = I_0 \sin \phi_0 \quad \text{--- (1)} \quad I_c = I_0 \cos \phi_0 \quad \text{--- (2)}$$


$$I_0 = \sqrt{I_m^2 + I_c^2}$$

$$W_0 = V_1 I_0 \cos \phi_0 = V_1 I_c$$

$$W_0 = V_1 I_0 \cos \phi_0 = P_1^0 = \text{Iron loss}$$

Because I_0 is 3 to 5% of F.L. rated I_n

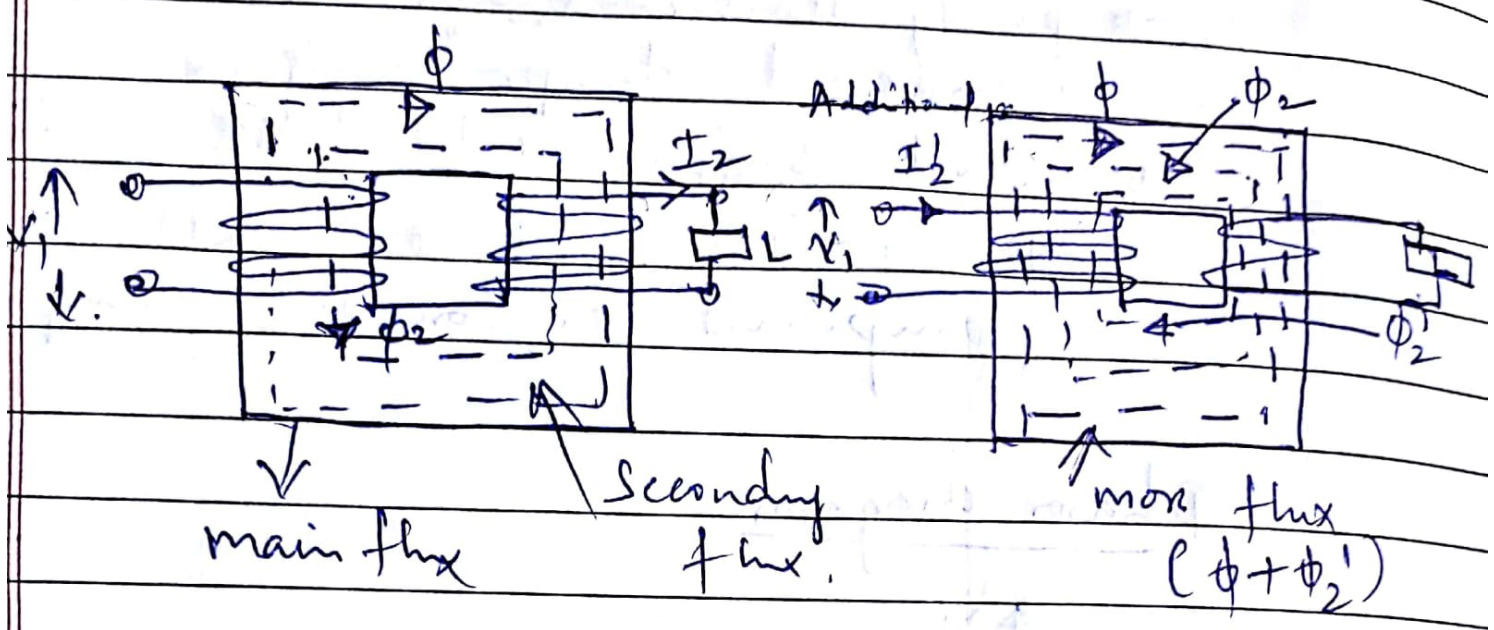practical transformer on load (mmf Balancing on load)



Transformer is loaded, $|I_1|$ & $|I_2|$ is determined by load. Resistive load \rightarrow $\xrightarrow{I_2} X_2$, Inductive load $\xrightarrow{I_2} X_2$, Capacitive $\xrightarrow{I_2} X_2$

$N_2 I_2$ - demagnetising ampere turns, produces ϕ_2 which opposes main ϕ flux (magnetising).

ϕ_2 Reduces main flux ϕ , $E_1 \downarrow$ (Reduces).

$V_1 - E_1$ increases due to which primary draws more current from supply.

I_2' Additional current or load component of primary clu.

→ I_2' is antiphase with I_2 which sets up its flux ϕ_2' opposes ϕ_2 and helps main flux ϕ . ϕ_2' neutralises ϕ_2 .

→ $N_1 I_2'$ mmf balances $N_2 I_2$

→ flux in core is again maintained at constant level.

Key point :- Thus for any load condⁿ, no load to full load flux in core is practically constant.

→ I_2' neutralises changes in load, where flux & core losses are constant for all loads. Hence transformer is constant flux machine

→ As balanced (mmf).


$$N_2 I_2 = N_1 I_2'$$

$$I_2' = \frac{N_2 I_2}{N_1} = K I_2 \quad \text{--- (1)}$$


When ~~primary~~ transformer is loaded, primary c/c I_1

$$I_1 = I_0 + I_2' \quad \text{--- (2)}$$


Resistive load

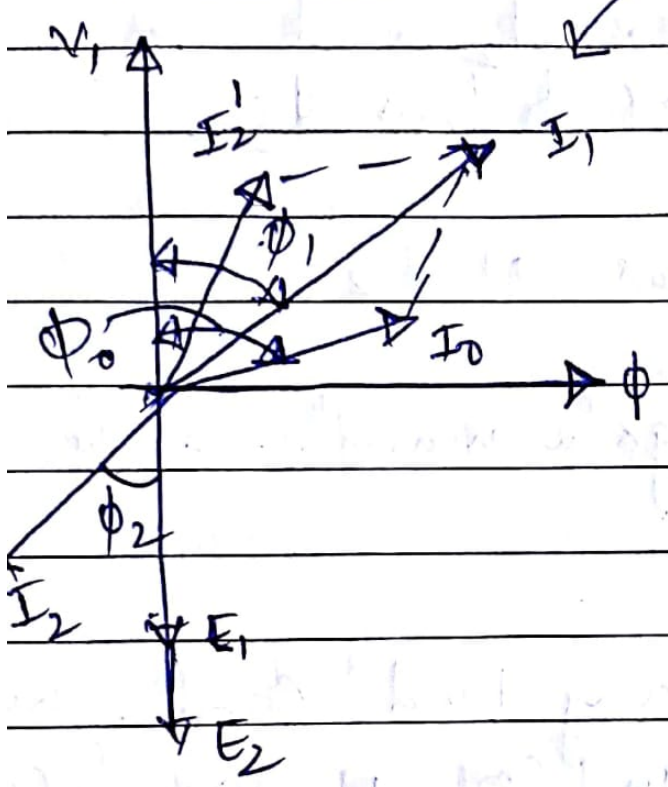

Inductive load

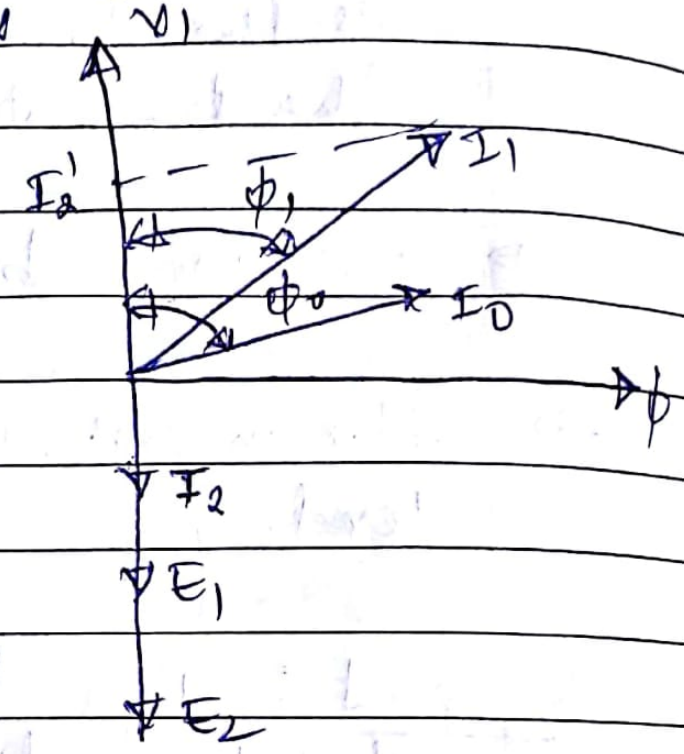

Capacitive load

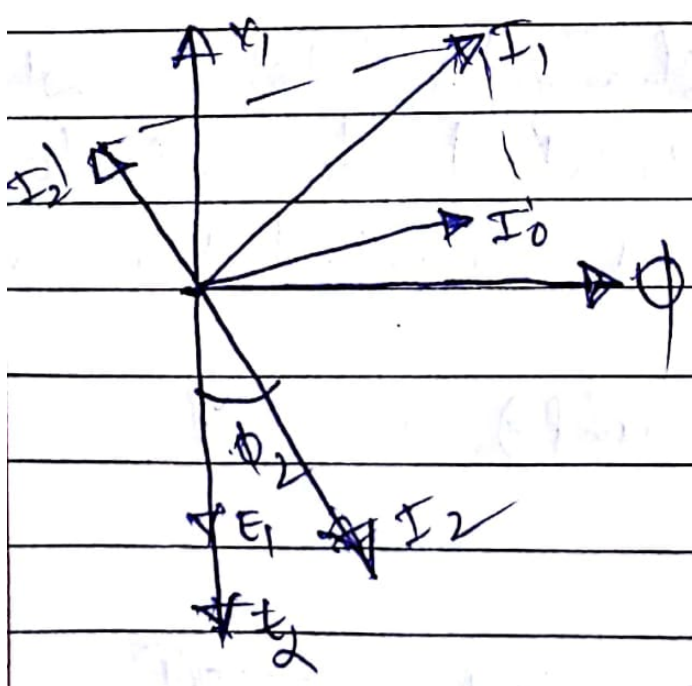

No load

* The no-load c/c of transformer is 5A at 0.3 pf when supplied at 230V, 50 Hz. The No of turns on primary winding is 200. Calculate:

- i) max value of flux in core
- ii) core loss
- iii) magnetising current

Solⁿ $I_0 = 5A, \cos \phi_0 = 0.3, V_1 = 230V, N_1 = 200.$

i) $E_1 = 4.44 f \phi_m N_1$ --- $f = 50 \text{ Hz}$,

$E_1 = V_1 = 230V$

$230V = 4.44 \times \phi_m \times 50 \times 200$

$\phi_m = 5.18 \text{ mWb}$

ii) Core loss = $P_i = \text{power i/p on no load}$
 $= V_1 I_0 \cos \phi_0$

$= 230 \times 5 \times 0.3 = 345 \text{ W}$

iii) $I_m = I_0 \sin \phi_0$ --- $\phi_0 = \cos^{-1}(0.3)$
 $= 72.54^\circ$

$I_m = 5 \sin(72.54^\circ) = 4.7696 \text{ A}$

- * A single phase transformer has turns ratio of 144/432 and operates at maximum flux of 7.5×10^{-3} Wb at 50 Hz. When on no load the transformer takes 0.24 kVA at p.f. of 0.26 lag from the supply. If the transformer supplies a load of 1.2 kVA at a p.f. of 0.8 lag, determine
- magnetizing Ch.
 - primary Ch.
 - primary p.f.

Solⁿ $N_1 = 144, N_2 = 432, \phi_m = 7.5 \times 10^{-3}$ Wb, $f = 50$ Hz
 $V_1 = 4.44 N_1 \phi_m f = 4.44 \times 144 \times 7.5 \times 10^{-3} \times 50$
 $V_1 = 239.76$ V

No load kVA = $V_1 \times I_0$

$\therefore 0.24 \times 10^3 = 239.76 \times I_0$

i.e. $I_0 = 1$ A & $\cos \phi_0 = 0.26$ lag (given).

i) $I_m = I_0 \sin \phi_0 = 1 \times 0.9656 = 0.9656$ A.

ii) load kVA = 1.2 and $\cos \phi_2 = 0.8$


$$I_2 = \frac{\text{load kVA}}{V_2} = \frac{1.2 \times 10^3}{V_2}$$

$$V_2 = V_1 \times \frac{N_2}{N_1} = 719.28 \text{ V}$$

$$I_2 = \frac{1.2 \times 10^3}{719.28} = 1.6683$$

$$K = \frac{N_2}{N_1} = \frac{432}{144} = 3$$
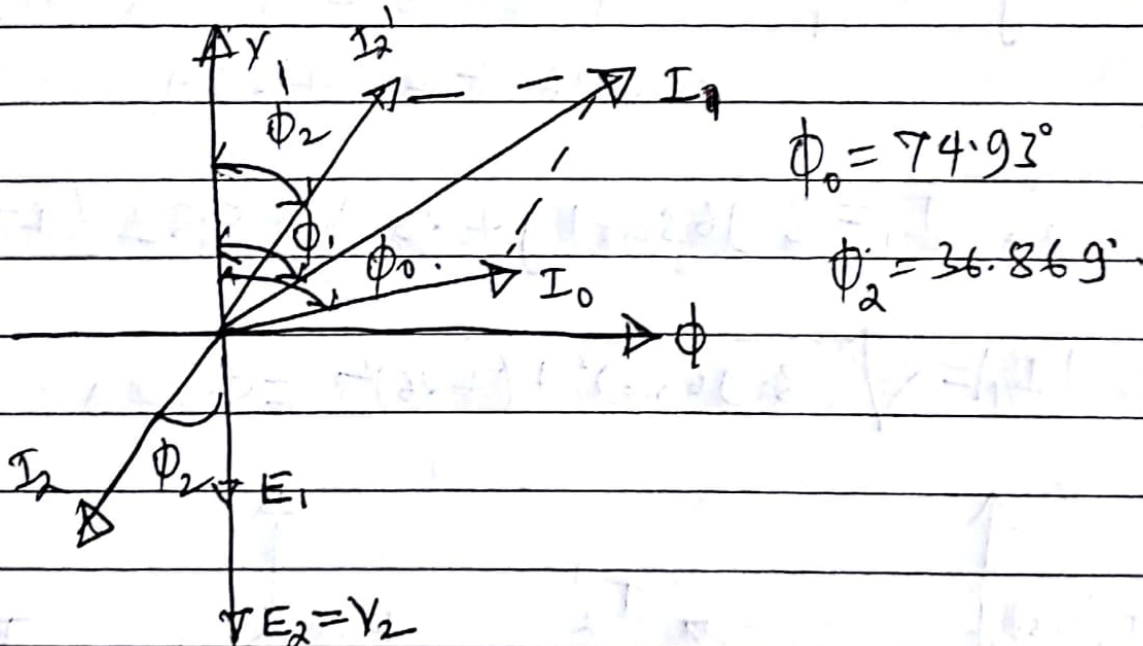
$$I_2' = K I_2 = 3 \times 1.6683 = 5 \text{ A}$$




$$I_0 \cos \phi_0 = 0.26 \text{ A}$$

$$I_0 \sin \phi_0 = 0.9656 \text{ A} \quad I_0 \cos \phi_0$$

$$I_2' \cos \phi_2 = 5 \times 0.8 = 4 \text{ A}$$

$$I_2' \sin \phi_2 = 5 \times 0.6 = 3 \text{ A}$$

$$\vec{I}_1 = \vec{I}_0 + \vec{I}_2'$$

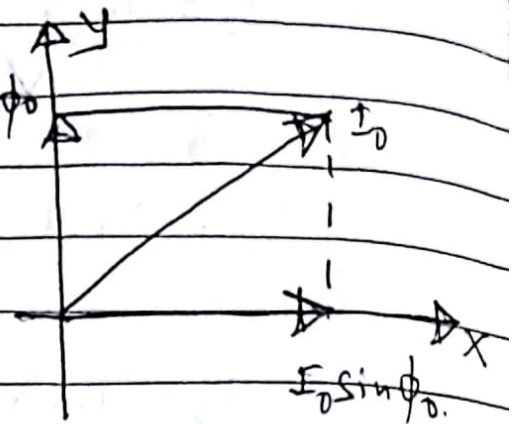

$$\therefore \text{X component of } I_1 = I_0 \sin \phi_0 + I_2' \sin \phi_2$$



$$= 0.9656 + 3 = 3.9656 \text{ A}$$

$$\therefore \text{Y component of } I_1 = I_0 \cos \phi_0 + I_2' \cos \phi_2$$

$$= 0.26 + 4 = 4.26 \text{ A}$$

$$\therefore \vec{I}_1 = 3.9656 + j4.26 \text{ A} = 5.82 / 47.04^\circ$$

$$|I_1| = \sqrt{(3.9656)^2 + (4.26)^2} = 5.82 \text{ A}$$

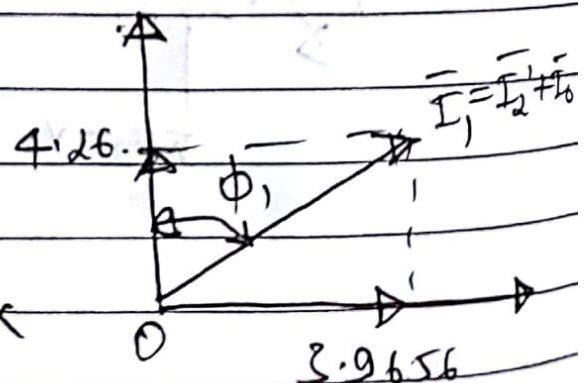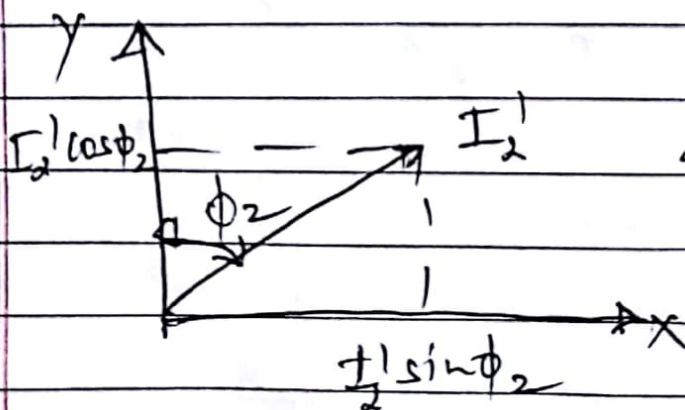

iii) Note that ϕ is measured w.r.t V_1 axis
i.e. y-axis

$$\phi_1 = 90^\circ - 47.04^\circ = 42.96^\circ$$

Rectangular to polar given angle w.r.t x axis
 $\cos \phi_1 = 0.7318$ lag — Power p.f.

Note:- Remember that ϕ_1 is angle b/w V_1
and I_1 & as V_1 is vertical, ϕ_1 is
measured with respect V_1 . So do not
convert Rectangular to polar as it gives
angle w.r.t to axis & we want w.r.t y axis

Effect of winding Resistances

Resistance will not only cause power loss but
also voltage drops.

$$\vec{E}_1 = \vec{V}_1 - \vec{I}_1 R_1 \quad \text{--- (1)}$$

$$\vec{E}_2 = \vec{V}_2 - \vec{I}_2 R_2 \quad \text{--- (2)}$$

→ $I_1 R_1$ & $I_2 R_2$ purely resistive drops in phase
(I_1 & I_2).

Equivalent Resistance

→ Transfer without affecting performance to make calculation easy.

→ Total Cu loss = $I_1^2 R_1 + I_2^2 R_2$

$$= I_1^2 \left[R_1 + \frac{I_2^2 R_2}{I_1^2} \right]$$

$$= I_1^2 \left[R_1 + \frac{1}{k^2} R_2 \right]$$

$$= I_1^2 R_1 + I_1^2 \frac{1}{k^2} R_2$$

→ $\frac{R_2}{k^2}$ is resistance shifted to primary

Causes same Cu loss with R_1 as R_2 causes with I_2

→ Equivalent resistance of secondary ref to primary

$$R_2' = \frac{R_2}{k^2}$$


→ Equivalent resistance of transformer ref to primary

$$R_{ie} = R_1 + R_2' = R_1 + \frac{R_2}{k^2}$$

$$\text{Total Cu loss} = I_1^2 R_{ie} = I_1^2 R_1 + I_2^2 R_2$$

Key point = HV side \rightarrow Low c_m side \rightarrow High resist side
 LV side \rightarrow High c_m side \rightarrow low resistance side

Effect of leakage Reactance

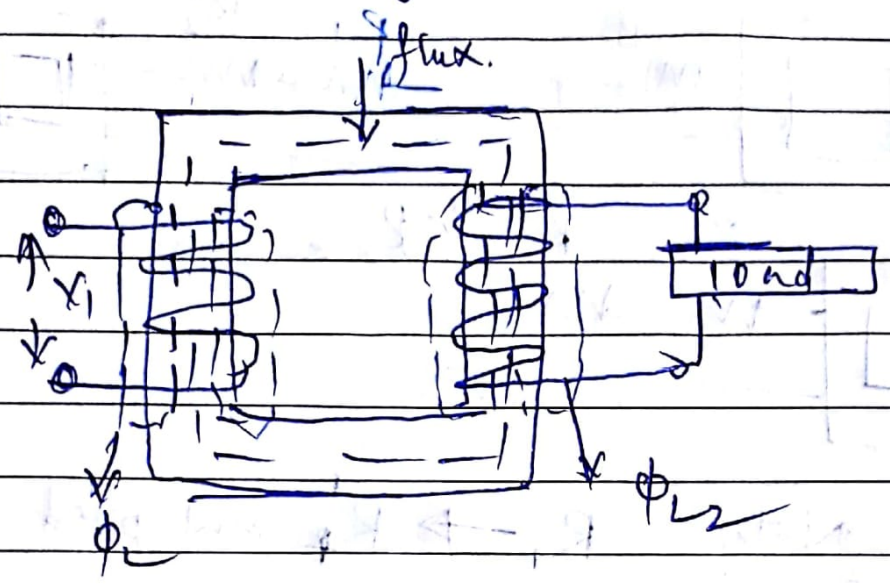

\rightarrow Assumption total ϕ links both ϕ & second. but not true some part of flux ϕ of both take air path & link to same which is leakage flux. Thus two leakage fluxes ϕ_{L1} & ϕ_{L2}

- $\rightarrow \phi_{L1}$ is primary leakage flux. $\phi_{L1} \rightarrow I_1$
- $\rightarrow \phi_{L2}$ is Secondary " $\phi_{L2} \rightarrow I_2$

- \rightarrow Due to ϕ_{L1} there is self induced emf e_{L1}
- \rightarrow Due to ϕ_{L2} there is " " e_{L2}

- V_1 has to overcome voltage e_{L1} to produce E_1 while induced emf E_2 has to overcome e_{L2} to produce V_2
- Thus. Self induced emf's are treated as voltage drops across fictitious reactances.
- Reactances are X_1 & X_2 → leakage reactance
- $e_{L1} = I_1 X_1 = \text{drop}$, $e_{L2} = I_2 X_2 = \text{drop}$
- Goal :- Avoid leakage flux both windings are placed on same limb.

Equivalent - leakage reactance


$$X_{le} = X_1 + X_2' \quad \text{where } X_2' = X_2 / k^2$$

$$X_{de} = X_2 + X_1' \quad X_1' = k^2 X_1$$

$$X_{de} = X_2 + X_1' \quad , \quad X_1' = k^2 X_1$$

$$k = \frac{X_2}{X_1}$$

Equivalent Impedance

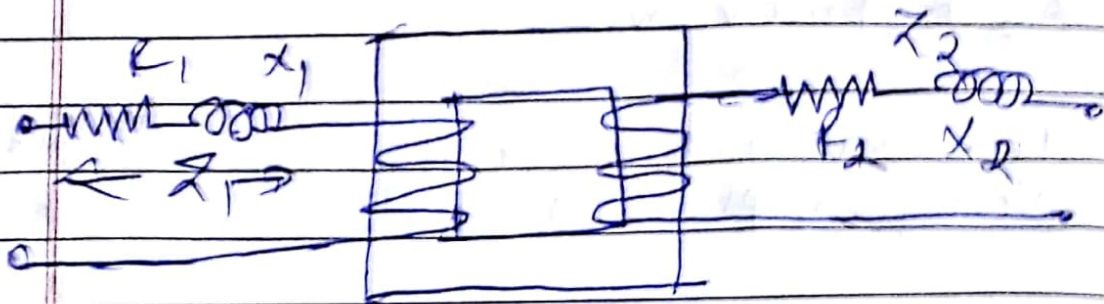

$$Z_1 = R_1 + jX_1 \Omega$$

$$Z_2 = R_2 + jX_2 \Omega$$

Magnitude $Z_1 = \sqrt{R_1^2 + X_1^2}$





$$Z_2 = \sqrt{R_2^2 + X_2^2}$$

$$Z_{1e} = Z_1 + Z_2' = Z_1 + \frac{Z_2}{k^2} \quad \left. \begin{array}{l} \text{equivalent} \\ \text{impedance} \end{array} \right\}$$

$$Z_{2e} = Z_2 + Z_1' = Z_2 + k^2 Z_1$$

$$Z_{1e} = \sqrt{R_{1e}^2 + X_{1e}^2} \quad Z_{2e} = \sqrt{R_{2e}^2 + X_{2e}^2}$$
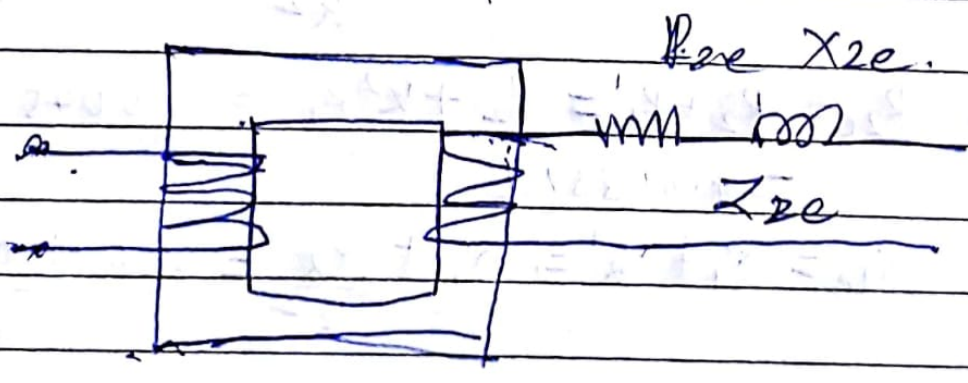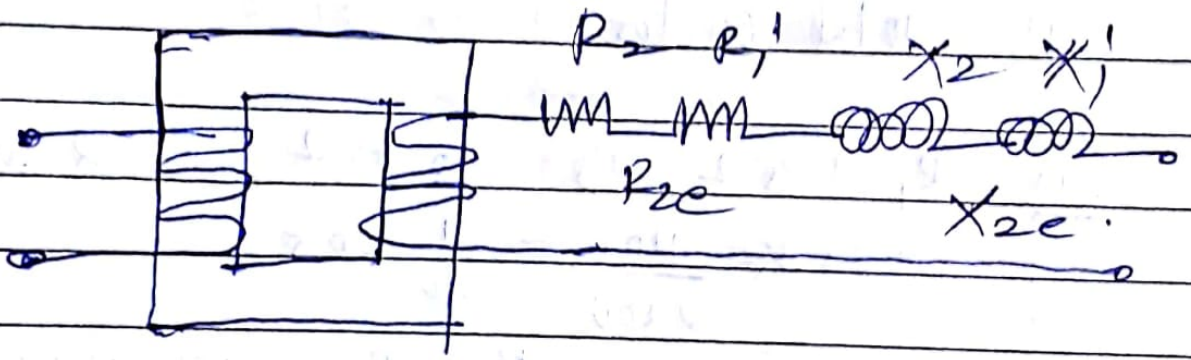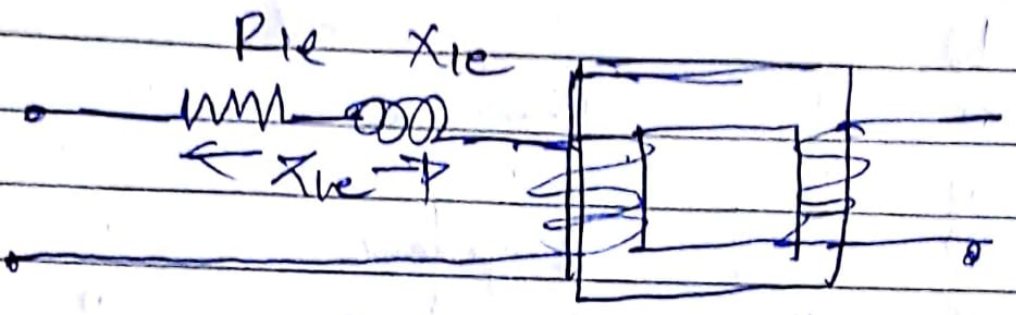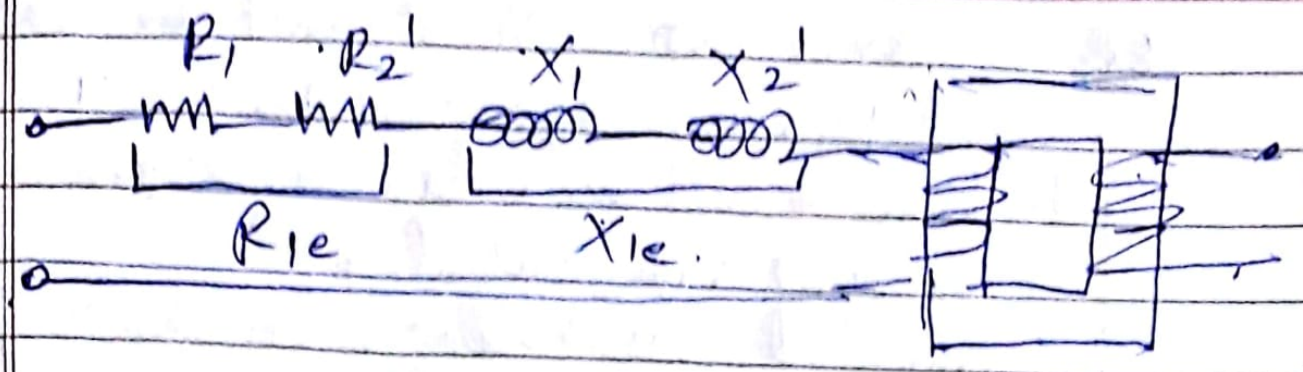
$$Z_{2e} = k^2 Z_{1e}, \quad Z_{1e} = \frac{Z_{2e}}{k^2}$$



Ex^o 5: A 15kVA, 2200/110V transformer has $R_1 = 1.75 \Omega$, $R_2 = 0.0045 \Omega$. The leakage reactances are $X_1 = 2.6 \Omega$ and $X_2 = 0.0075 \Omega$. Calculate

- Equivalent resistance referred to primary.
- " " " " Secondary
- " " Reactance " " Primary
- " " " " " " Secondary
- " " Impedance " " Primary
- " " Impedance " " Secondary
- total Cu loss

Solⁿ:- $R_1 = 1.75 \Omega$, $R_2 = 0.0045 \Omega$, $X_1 = 2.6 \Omega$, $X_2 = 0.0075 \Omega$

$$K = \frac{110}{2200} = \frac{1}{20} = 0.05$$

a) $R_{1e} = R_1 + R_2' = R_1 + \frac{R_2}{K^2} = 1.75 + \frac{0.0045}{(0.05)^2} = 3.55 \Omega$

b) $R_{2e} = R_2 + R_1' = R_2 + K^2 R_1 = 0.0045 + (0.05)^2 \times 1.75 = 0.00887 \Omega$

c) $X_{1e} = X_1 + X_2' = X_1 + \frac{X_2}{K^2} = 2.6 + \frac{0.0075}{(0.05)^2} = 56 \Omega$

d) $X_{2e} = X_2 + X_1' = X_2 + K^2 X_1 = 0.0075 + (0.05)^2 \times 2.6 = 0.014 \Omega$

$$e) Z_{1e} = R_{1e} + j X_{1e} = 3.55 + j 5.6 \Omega$$

$$\therefore |Z_{1e}| = \sqrt{3.55^2 + 5.6^2} = 6.6304 \Omega$$

$$f) Z_{2e} = R_{2e} + j X_{2e} = 0.00887 + j 0.014 \Omega$$

$$|Z_{2e}| = \sqrt{(0.00887)^2 + (0.014)^2} = 0.01657 \Omega$$

g) F.L. in loss, Calculate F.L. in.

$$I_1 = (F.L.) = \frac{25 \times 1000}{2200} = 11.36 \text{ A}$$

$$\therefore \text{total in loss} = I_1^2 R_{1e} = (11.36)^2 \times 3.55$$

$$= 458.419 \text{ W}$$


Gross checked.

$$I_2 = \frac{25 \times 1000}{110} = 227.272 \text{ A}$$

$$\text{total in loss} = I_1^2 R_1 + I_2^2 R_2$$

$$= 458.419 \text{ W}$$

phasor diagram

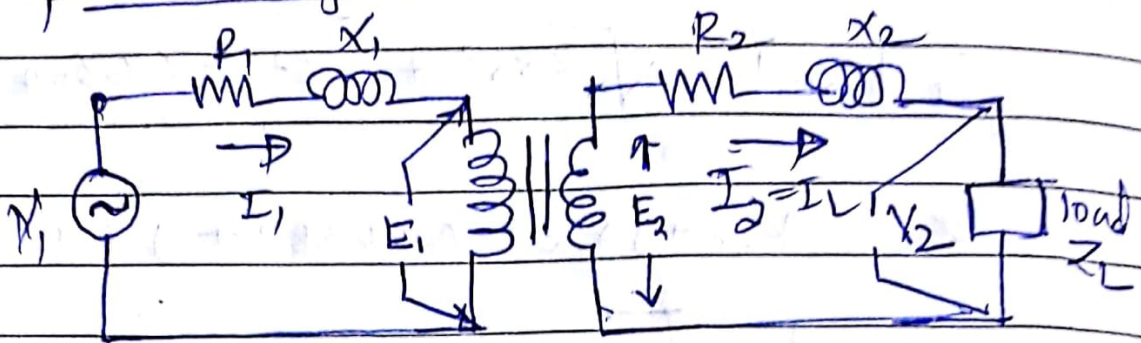

$$\therefore \bar{V}_1 - \bar{I}_1 R_1 - \bar{I}_1 X_1 + \bar{E}_1 = 0$$

$$\bar{V}_1 = -\bar{E}_1 + \bar{I}_1 R_1 + \bar{I}_1 X_1 \quad \text{--- } \otimes$$

$$= -\bar{E}_1 + \bar{I}_1 (R_1 + jX_1)$$

$$= -\bar{E}_1 + \bar{I}_1 Z_1 \quad \text{--- } \textcircled{1}$$


$$\therefore \bar{E}_2 = \bar{V}_2 + \bar{I}_2 R_2 + \bar{I}_2 X_2$$

$$\bar{E}_2 - \bar{I}_2 R_2 - \bar{I}_2 X_2 - \bar{V}_2 = 0$$

$$\bar{V}_2 = \bar{E}_2 - \bar{I}_2 (R_2 + jX_2)$$

$$= \bar{E}_2 - \bar{I}_2 Z_2 \quad \text{--- } \textcircled{2}$$

unity p.f load, $\cos\phi_2 = 1$

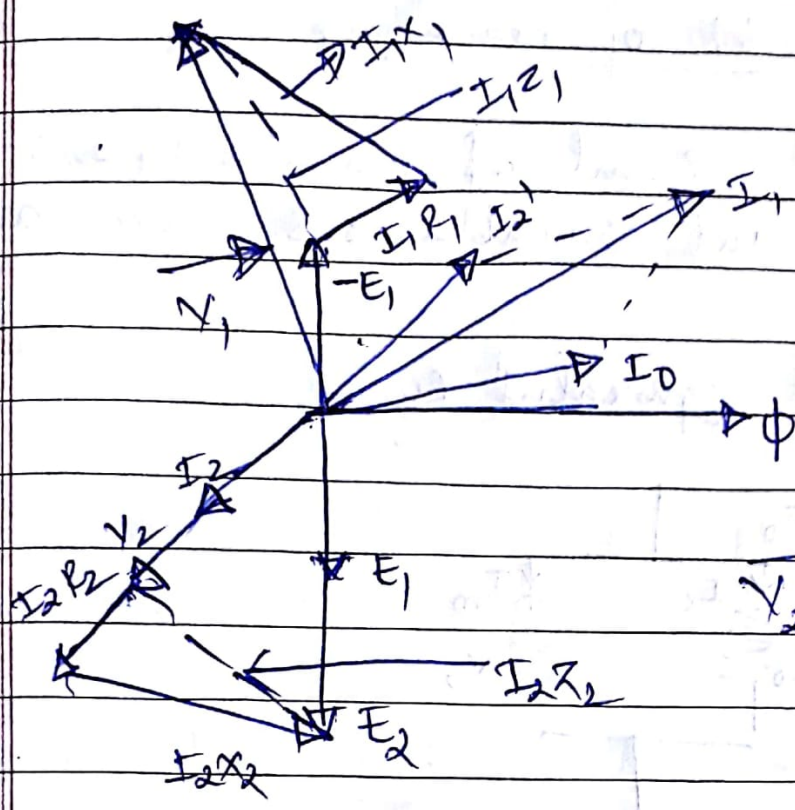


$$-E_1 + I_1 R_1 = V_1$$

$$I_2' = -I_2$$

$$V_2 + I_2 R_2 = E_2$$

10/8/18

lagging p.f

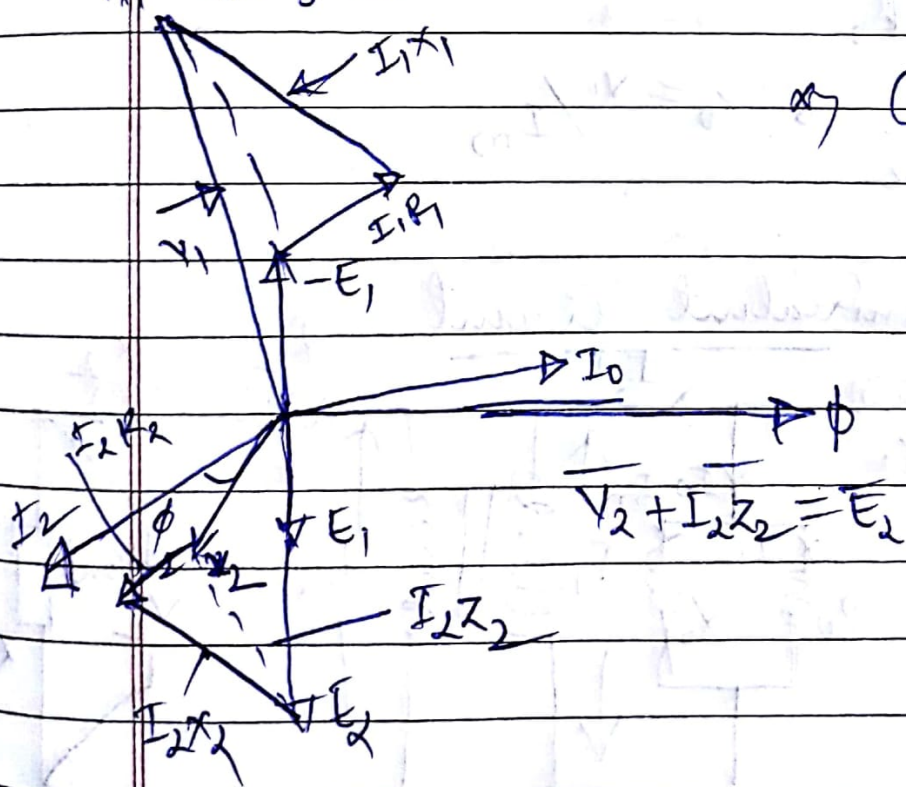


∴ Capacitive load work

$$V_2 + I_2 R_2 = E_2$$

Equivalent ckt of Transformer

→ equivalent circuit of machine means combination of fixed and variables, resistance and reactance


No load Equivalent circuit

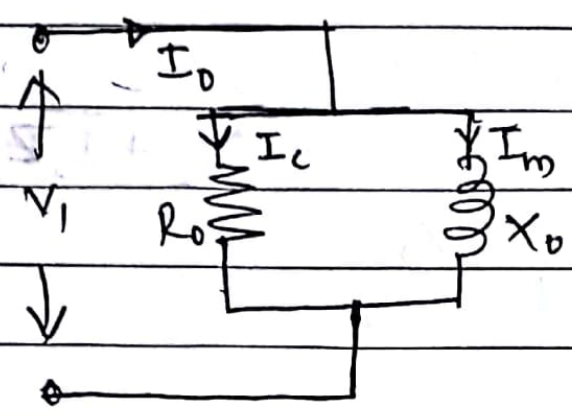

exciting circuit, $R_0 || X_0$, no load Resistance R_0 , Reactance X_0

$$R_0 = \frac{V_1}{I_c} \quad \& \quad X_0 = \frac{V_1}{I_m}$$

load Equivalent circuit

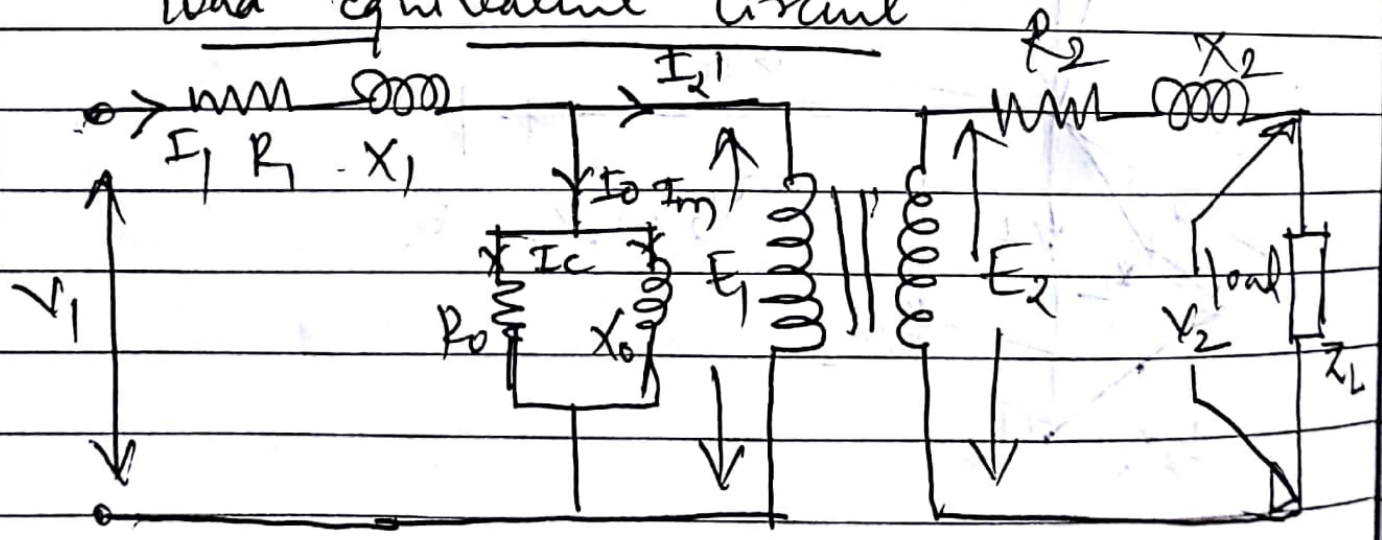


Secondary parameters to primary

$$R_2' = \frac{R_2}{k^2}, \quad X_2' = \frac{X_2}{k^2}, \quad Z_2' = \frac{Z_2}{k^2}$$

$$E_2' = \frac{E_2}{k}, \quad I_2' = k I_2, \quad k = \frac{N_2}{N_1}$$

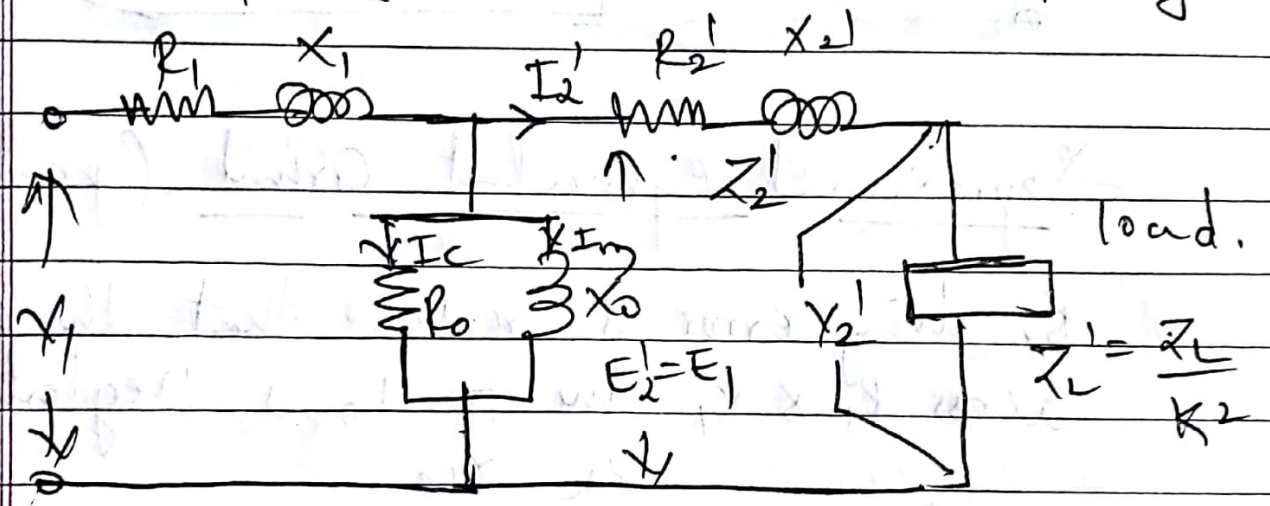Exact equivalent circuit referred to primary




Primary parameters to secondary

$$R_1' = k^2 R_1, \quad X_1' = k^2 X_1, \quad Z_1' = k^2 Z_1$$


$$E_1' = k E_1, \quad I_1' = I_1 / k, \quad I_0' = I_0 / k$$

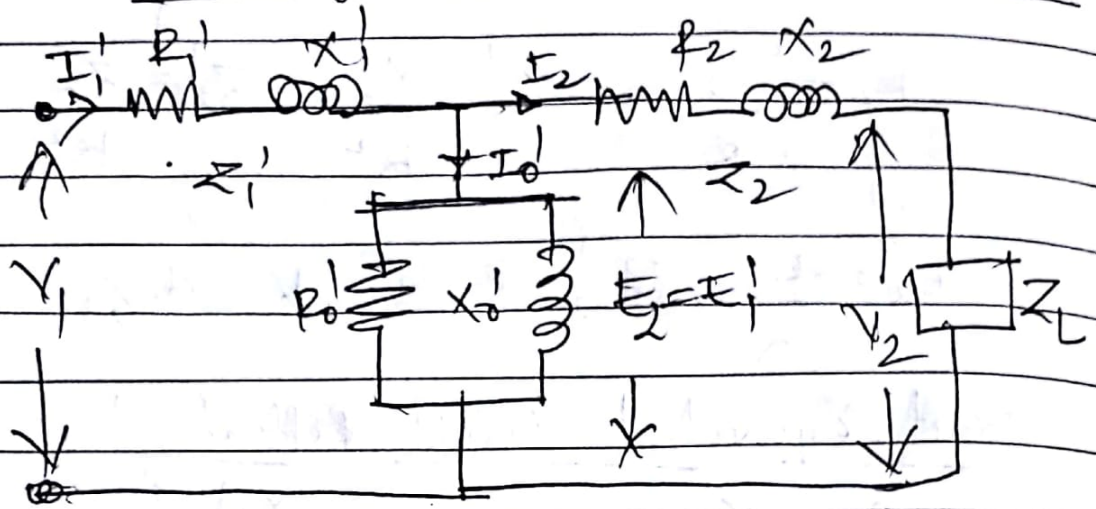exact equivalent circuit left to secondary



Approximate equivalent circuit (primary)

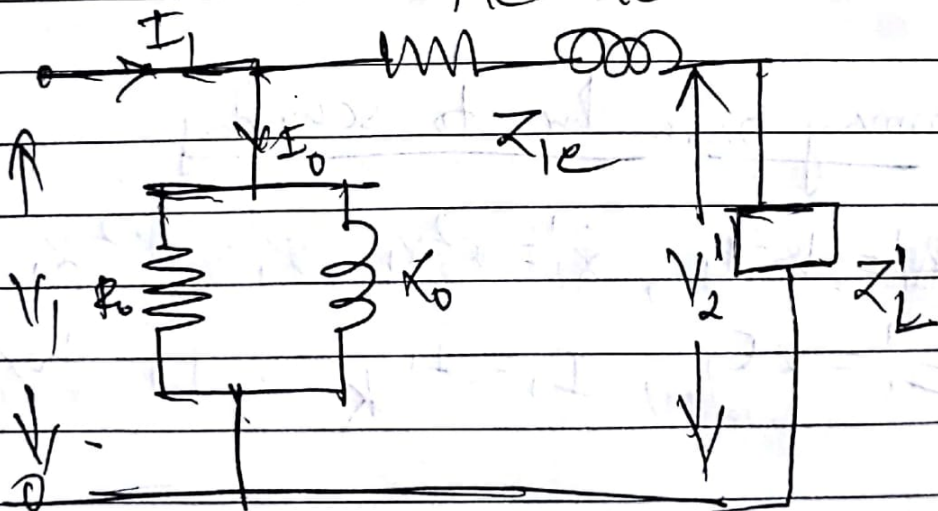By doing error is created that the drop across R_1 & X_1 due to I_0 is neglected.




* The equivalent circuit of 200/400V, step up transformer has following parameters referred to LV side:

Equivalent resistance = 0.15Ω , Eqⁿ reactance = 0.37Ω
 core loss component of resistance = 600Ω ,
 magnetizing reactance = 300Ω

When transformer is supplying load of 10A at p.f. of 0.8 lag, calculate

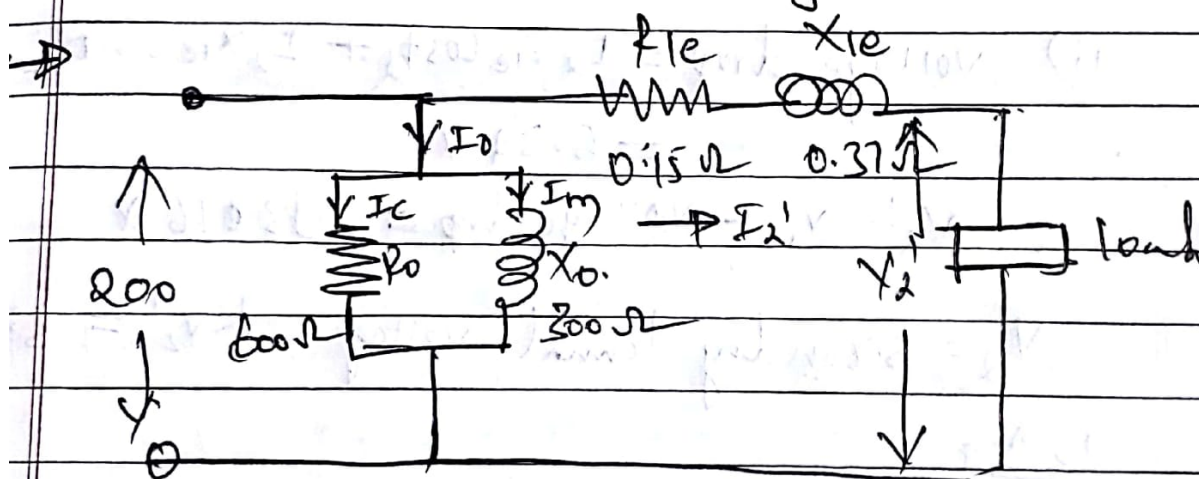- i) primary current ii) secondary terminal voltage



$$K = \frac{400}{200} = 2, \quad I_2' = KI_2 = 2 \times 10 = 20A$$

$$\cos \phi_2 = 0.8, \quad \phi_2 = 36.86^\circ$$

$$I_2' = 20 \angle -36.86^\circ = 16 - j12A$$

$$V_1 = 200 \angle 0^\circ V$$

$$I_C = \frac{V_1}{R_0 + jX_0} = \frac{200 \angle 0^\circ}{600 \angle 0^\circ} = 0.333 \angle 0^\circ = 0.333 + j0A$$

$$\underline{I_m} = \frac{V_1}{0 + jX_0} = \frac{200 \angle 0^\circ}{300 \angle 90^\circ} = 0.666 \angle -90^\circ \text{ A.}$$

$$= 0 - j0.666 \text{ A.}$$

$$\underline{I_0} = \underline{I_c} + \underline{I_m} = 0.333 - j0.666 \text{ A.}$$

$$\underline{I_1} = \underline{I_0} + \underline{I_2'} = (16 + 0.333) - j(12 + 0.666) \text{ A}$$

$$= 16.333 - j12.666 \text{ A} = 20.668 \angle -37.793^\circ \text{ A.}$$

i) $|I_1| = 20.668$

ii) Voltage drop = $I_2' R_{e2} \cos \phi_2 + I_2' X_{e2} \sin \phi_2$
 $= 6.84 \text{ V.}$

$$\underline{V_2'} = V_1 - \text{Voltage drop} = 493.016 \text{ V}$$

$$V_2 = \text{secondary terminal voltage} = KV_2' = 386.32 \text{ V.}$$

13 Aug

Megha, Suhashini

All day Efficiency of Transformer

$$\eta = \frac{\text{o/p power}}{\text{i/p power}} = \text{power efficiency.}$$

It is not true measure of performance of some special types of transformer as distribution transformer

Distribution transformer — residential & Commercial loads.

load varies on such during period of day.

- Most period of day hrs are working at 30 to 40% of F.L or even less than that the primary of such transformer is energised at its rated voltage for 24 hours, to provide continuous supply to consumer.
- Core loss which depends on voltage take place continuously for all loads. but Cu loss depends on load loadⁿ.
- For no load Cu loss is negligible small while on F.L gives at its Rated value hence power efficiency η cannot give true measure of true efficiency of such transformer.
- In such transformer energy o/p is calculated in (kWh). energy spent in supplying various losses is also determined by kWh.
- The ratio of total energy output to total energy i/p (o/p + losses) calculated.

Such ratio is called Energy η or All day η of transformer.

→ Performance of various distribution transformers is compared.

$$\% \text{ All day } \eta = \frac{\text{O/P energy in kWh during}}{\text{I/P energy in kWh a day}}$$
$$= \frac{\text{O/P energy}}{\text{O/P energy} + \text{Energy Spent T+L}}$$

* Find All day η of 1ϕ transformer having max η for 98% at 15 kVA at upf and load as follows.

- 12 hrs - 2 kW at 0.5 pf lag
- 6 hrs - 12 kW at 0.8 pf.
- 6 hrs - no load.

Given:- $\eta_{\max} = 98\%$ at 15 kVA, $\cos\phi = 1$

$$\% \eta_{\max} = \frac{[\text{VA for } \eta_{\max}] \times \cos\phi}{[\text{VA for } \eta_{\max}] \times \cos\phi + 2P_i} \times 100$$

$$\therefore 0.98 = \frac{15 \times 10^3 \times 1}{15 \times 10^3 \times 1 + 2P_i} \quad \text{i.e. } P_i = 153.061 \text{ W}$$

$$P_{cu} \text{ at } 15 \text{ kVA} = P_i = 153.061 \text{ W}$$

$$\text{Energy } \frac{\text{Wh}}{\text{h}} = [2 \times 12] + [12 \times 6] = 96 \text{ kWh}$$

Energy spent due to iron loss.

$$= P_i \times 24 \text{ hrs} = 3.673 \text{ kWh}$$

To Calculate energy spent due to Cu loss:

i) load 1, 2 kW, $\cos \phi = 0.5$

$$\text{kVA supplied} = \frac{\text{kW}}{\cos \phi} = \frac{2}{0.5} = 4 \text{ kVA}$$

$$\text{load 1 } P_{cu} = P_{cu} \text{ at } 15 \text{ kVA} \times \left(\frac{4}{15}\right)^2$$

$$= 153.061 \times 0.0711 = 10.8843 \text{ W}$$

$$\therefore \text{Energy spent} = \text{load 1 } P_{cu} \times \text{hrs} = 10.88 \times 12$$

$$= 130.56 \text{ Wh} = 0.1306 \text{ kWh}$$

ii) Load 2, 12kW at $\cos\phi = 0.8$ for 6 hrs.

$$\therefore \text{KVA Supplied} = \frac{\text{KW}}{\cos\phi} = \frac{12}{0.8} = 15 \text{ KVA.}$$

$$\text{load 2 } P_m = P_m \text{ at } 15 \text{ KVA} = 153.061 \text{ W.}$$

$$\therefore \text{Energy spent} = 153.061 \times 6 = 918.366 \text{ Wh}$$

$$= 0.9183 \text{ kWh.}$$

iii) No copper loss for no load

$$\text{Total energy spent} = 3.6734 + 0.1306 + 0.91836 = 4.7224$$

$$\text{All day } \eta = \frac{\text{Total energy o/p in 24 hrs}}{\text{T.E o/p in 24 hrs} + \text{Energy spent in 24 hrs}} \times 100$$

$$= \frac{96}{96 + 4.722} \times 100 = 95.311\%$$

14 Aug

① megha, Su Kashis, Sushma, merush.

② .v ↓, maha, Sway,

Indirect loading Tests on Transformer

→ η & R of any load & p.f. predetermined. by Indirect.

→ equivalent circuit parameters

① o.c ② s.c.

Advantages

O.C. Test

Wiring, connection, Input meters.

Voltmeter Resistance is high.

| | | |
|--------|-------|-------|
| V_o | I_o | W_o |
| Rating | | |

The o/p power is zero, cu losses are low, No i/p power is used mag loss

R_o & X_o if meters are connected in secondary.

& we can find R_o & X_o .

Short Circuit Test (Impedance test)

low voltage test as reduced voltage test

V_{sc} I_{sc} W_{sc}

Rating

$$W_0 = P_i = I_{rm} \text{ loss}$$

$$W_0 = V_0 I_0 \cos \phi_0$$

$$\cos \phi_0 = \frac{W_0}{V_0 I_0}$$

$$I_c = I_0 \cos \phi_0 \quad \& \quad I_m = I_0 \sin \phi_0$$

$$R_0 = \frac{V_0}{I_c} \Omega \quad X_0 = \frac{V_0}{I_m} \Omega$$

$$W_{sc} = (P_m) F.L = F.L \text{ in loss}$$

$$W_{sc} = V_{sc} I_{sc} \cos \phi_{sc}$$

$$\cos \phi_{sc} = \frac{V_{sc} I_{sc}}{W_{sc}}$$

$$W_{sc} = I_{sc}^2 R_{ie} = \text{in loss}$$

$$R_{ie} = \frac{W_{sc}}{I_{sc}^2}$$

$$Z_{ie} = \frac{V_{sc}}{I_{sc}} = \sqrt{R_{ie} F.L}$$

$$X_{ie} = \sqrt{Z_{ie}^2 - R_{ie}^2}$$

$$\eta = \frac{\eta \times (\text{VA Rating}) \cos \phi}{\eta (\text{VA Rating}) \cos \phi + W_0 + \eta^2 W_{sc}} \times 100$$

Voltage Regulation and its Significance

Beoz vtz drop at primary & secondary (Temperature) it is observed secondary terminal voltage drops from its no load value (E_2) to load value V_2 as load & load chn ↑.

This decrease in secondary terminal voltage expressed as fraction of no load secondary terminal voltage is called Regulation of transformer

$$E_2 = (\text{no load}) \quad V_2 = (\text{given load})$$

$$\% \text{ Voltage Regulation} = \frac{E_2 - V_2}{V_2} \times 100.$$


$$E_2 - V_2 / V_2 \text{ (per unit Reg'n)}$$

Secondary terminal voltage does not depend only on magnitude of load chn but also nature of P-f of load.

If V_2 is determined for full load and specified pf load the Reg'n is called F.L. Regulation.

As load chn I_L increases, voltage drop tend to increase and V_2 drops more & more
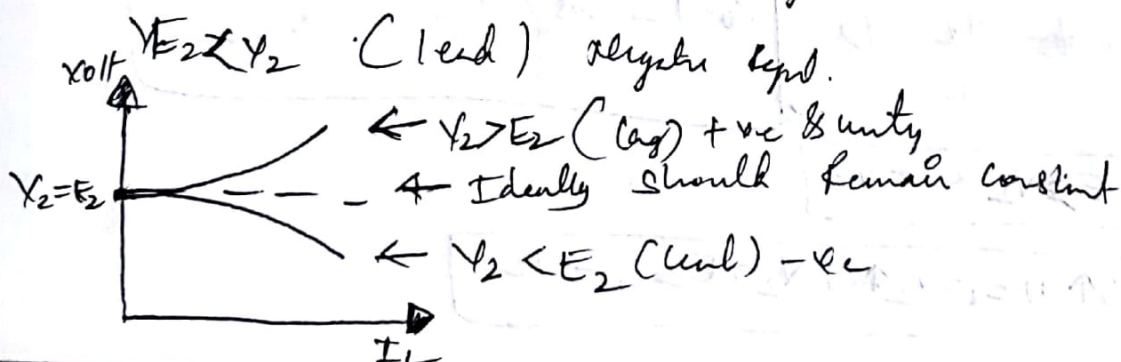
$$V_2 < E_2 \text{ (lagg pf) positive Reg'n}$$



Approximate voltage drop = $E_2 - V_2 = I_2 R_e \cos \phi_2 + I_2 X_e \sin \phi_2$

Constants of transformer

$$\% R = \left\{ \left(\frac{I_2 R_e}{E_2} \right) \cos \phi + \left(\frac{I_2 X_e}{E_2} \right) \sin \phi \right\} \times 100$$

$$\frac{I_2 R_e}{E_2} \text{ or } \frac{I_1 R_e}{E_1} \text{ is per unit resistance drop (NR)}$$

$$V_x = \frac{I_2 X_e}{E_2} = \frac{I_1 X_e}{E_1} = \text{per unit reactance drop} \times 100 \text{ (percent)}$$

$$\% R = [V_R \cos \phi + V_x \sin \phi] \times 100$$

$$V_R = \frac{I_2 R_e}{V_2} = \frac{I_1 R_e}{V_1}$$

$$V_x = \frac{I_2 X_e}{V_2} = \frac{I_1 X_e}{V_1}$$

Zero voltage regulation

At a certain leading pf $E_2 = V_2$ ($R=0$) ($E_2 \uparrow$)

For zero Rg

$$E_2 = V_2 \Rightarrow E_2 - V_2 = 0$$

$$V_R \cos \phi - V_x \sin \phi = 0 \Rightarrow V_R \cos \phi = V_x \sin \phi$$

$$\tan \phi = \frac{V_R}{V_x}$$

$$\cos \phi = \cos \left\{ \tan^{-1} \left(\frac{V_R}{V_x} \right) \right\}$$

lag & up $E_2 > V_2$ & +ve

lead, $V_2 \uparrow \Rightarrow E_2 = V_2 \uparrow \Rightarrow V_2 > E_2, -ve$

Condⁿ max vty Regn

$$\% R = [V_R \cos \phi + V_X \sin \phi] \times 100$$

Diff with ϕ

$$\frac{d(R)}{d\phi} = -V_R \sin \phi + V_X \cos \phi = 0$$

$$\tan \phi = \frac{V_X}{V_R} = \frac{X_{1e}}{R_{1e}} = \frac{X_{2e}}{R_{2e}}$$

$$\cos \phi = \frac{R_{2e}}{Z_{2e}} = \frac{R_{1e}}{Z_{1e}} \quad \sin \phi = \frac{X_{1e}}{Z_{1e}} = \frac{X_{2e}}{Z_{2e}}$$

As $\tan \phi$ is +ve

max vty Regn occurs at lagging pt.

mag of max vty Regn is

$$P_{max} = \left[V_R \frac{R_{1e}}{Z_{1e}} + V_X \times \frac{X_{1e}}{Z_{1e}} \right] -$$


$$= \left[\frac{I_1 R_{1e} \times R_{1e}}{V_1 Z_{1e}} + \frac{I_1 X_{1e} \times X_{1e}}{V_1 Z_{1e}} \right]$$

$$P_{max} = \frac{I_1}{V_1 Z_{1e}} [R_{1e}^2 + X_{1e}^2] = \frac{I_1 Z_{1e}}{V_1} = 2P_u$$

Sumpner test (Back to back test)

Regulation also follows
 $\frac{1}{2} \eta \text{ FL of each tr}$
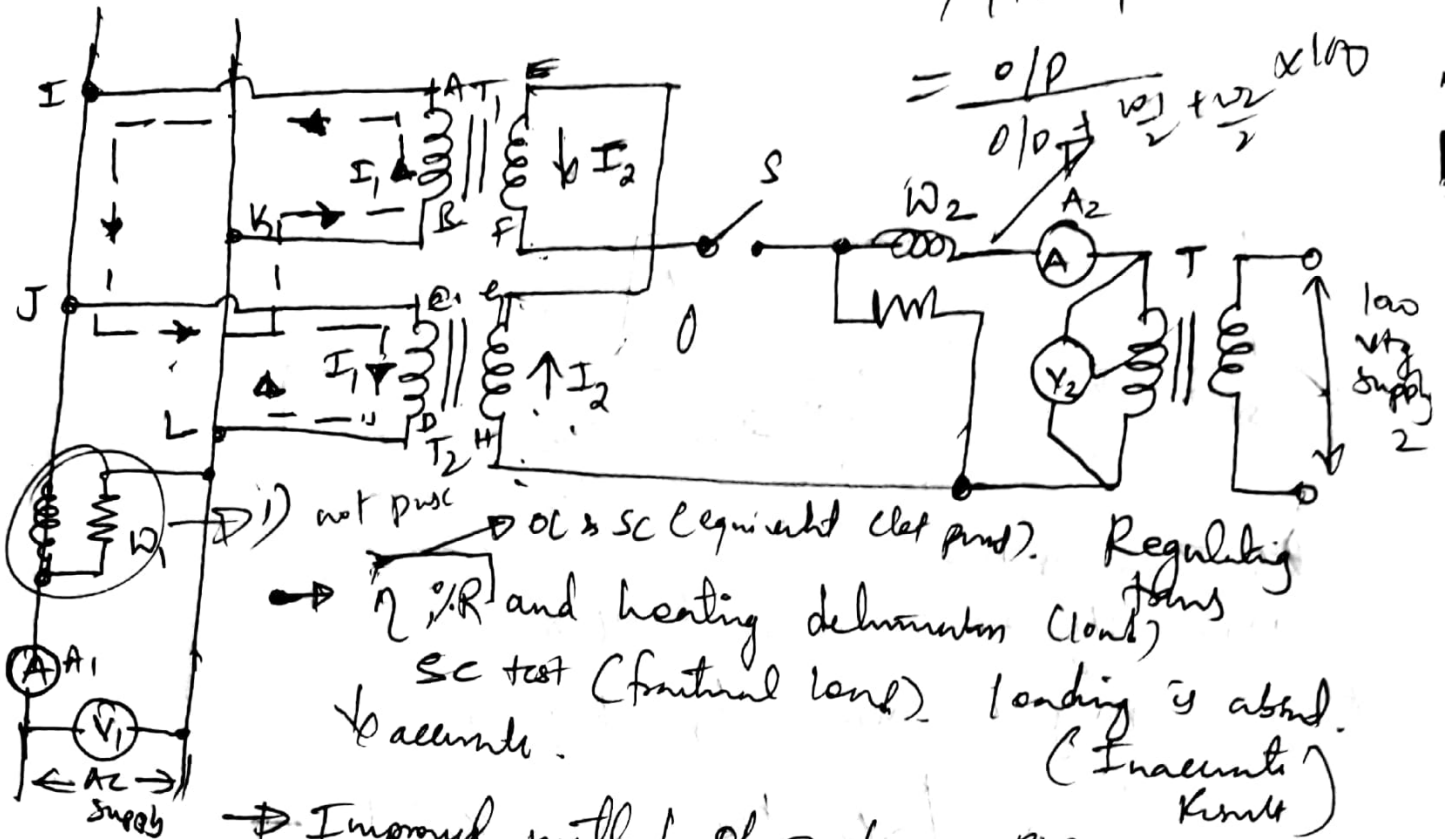
$$= \frac{0/P}{0/P + \frac{W_1 + W_2}{2}} \times 100$$



1) not possible
 OC & SC equivalent circuit. Regulation found
 → η , %R and heating determination (loads)
 SC test (fractional load). Loading is absent.
 (Inaccurate results)
 → Improved method of determining %R & η then OC test

- 2) Two identical transformer, one tr is loading on another, power taken from supply is that much used for losses
- 3) a) Primaries are connected in parallel across V_1
 b) Secondaries series opposite
 c) Secondaries are supplied from another low voltage supply

$$P_1 \text{ per tr} = \frac{W_1}{2} (T_1 \& T_2)$$

$$(1/2) \text{ FL per tr} = \frac{W_2}{2}$$

A direction & distance

! A 5kVA, 220/110 volts 1 ϕ transformer has max η of 96.97% at 0.8 p.f lag. It has core loss of 50W & Full load regulation at 0.8 p.f lag is 5%. Find η & R_e at F.L 0.9 p.f lag. 93.23, 3.96%.

Soln: 5kVA, 220/110V, η_{max} 96.97%, $\cos\phi = 0.8$, $P_i = 50W$

At η_{max} $P_{cu} = P_i = 50W$.

$$\% \eta_{max} = 0.9697 = \frac{\eta \times 5 \times 10^3 \times 0.8}{\eta \times 5 \times 10^3 \times 0.8 + 2 \times 50}$$

$$4000\eta + 100 = 4124.9871\eta$$

$\eta = 0.8$ i.e. η_{max} occurs at 80% of F.L

$$P_{cu(\eta_{max})} = 50 = 0.8^2 (P_{cu})_{FL}$$

$$P_{cu(FL)} = 78.125W$$

$$I_1(FL) = \frac{5 \times 10^3}{220} = 22.7272A$$

$$P_{cu(FL)} = I_1(FL)^2 R_e = 78.125 \quad R_e = 0.1512\Omega$$

Reg at 0.8 (F.L) is 5%.

$$5 = \frac{22.7272 [0.1512 \times 0.8 + X_{le} \times 0.6]}{220} \times 100$$

$$X_{le} = 0.605\Omega$$

Find η at F.L for $\cos\phi = 0.9$ lag is

$$\% \eta = \frac{5 \times 10^3 \times 0.9}{5 \times 10^3 \times 0.9 + 50 + 78.125} \times 100 = 93.231\%$$

$$\% R = \frac{22.72 [0.1512 \times 0.8 + 0.605 \times 0.435]}{220} \times 100 = 3.963\%$$

* The η at up of 6600/384V, 200kVA, 1 ϕ tr is 98% at both F.L & H.L. The p.f on N.L is 0.2 & F.L Regulation at 1pt of 0.8 is 4%. Draw equivalent circ. Ref to LV side

$$\text{Soln } \% \eta_{F.L} = 0.98 = \frac{200 \times 10^3 \times 1}{200 \times 10^3 \times 1 + P_i + P_{cu}(F.L)}$$

$$\therefore P_i + P_{cu}(F.L) = 4081.6326 \quad - (1)$$

$$\% \eta_{H.L} = \frac{\frac{1}{2} \times 200 \times 10^3 \times 1}{\frac{1}{2} \times 200 \times 10^3 \times 1 + P_i + P_{cu}(F.L) \times \frac{1}{4}} \times 100$$

$$\therefore P_i + \frac{1}{4} P_{cu}(F.L) = 2040.8163 \quad - (2)$$

Solve (1) & (2).

$$P_{cu}(F.L) = 2721.088 \text{ W} \quad \& \quad P_i = 1360.544 \text{ W} \quad = 0.7 = (\dots)$$

$$I_1(F.L) = \frac{200 \times 10^3}{6600} = 30.303 \text{ A}$$

$$P_{cu}(F.L) = 2721.088 = (I_1)^2 \times R_{e} = 30.303^2 \times R_{e}$$

$$R_{e} = 2.9632 \Omega$$

$$\% R = 3.4 = \frac{30.303 [2.9632 \times 0.8 + X_{le} \times 0.6]}{26600} \times 100$$

$$X_{le} = 10.569 \Omega$$

$$K = \frac{384}{6600} = 0.05818. \quad \text{equival. ckt } R_{eff}$$

$$R_{2e} = K^2 R_c = 0.01 \Omega. \quad X_{2e} = K^2 X_{lc} = 0.0357 \Omega$$

$$\cos \phi_0 = 0.2 \quad \& \quad P_i = 1360.544 \text{ W}$$

$$W_0 = P_i = V_1 I_0 \cos \phi_0 \Rightarrow 1360.544 = 6600 \times I_0 \times 0.2$$


$$I_0 = 1.0307 \text{ A}$$

$$I_c = I_0 \cos \phi_0 \Rightarrow 0.2061 \text{ A}, \quad I_m = I_0 \sin \phi_0 = 0.1 \text{ A}$$

$$R_0 = \frac{V_1}{I_c} = \frac{6600}{0.2061} = 32023.29 \Omega, \quad X_0 = \frac{V_1}{I_m} = \frac{6600}{0.1} = 65316.9 \Omega$$

R_{eff} to LV
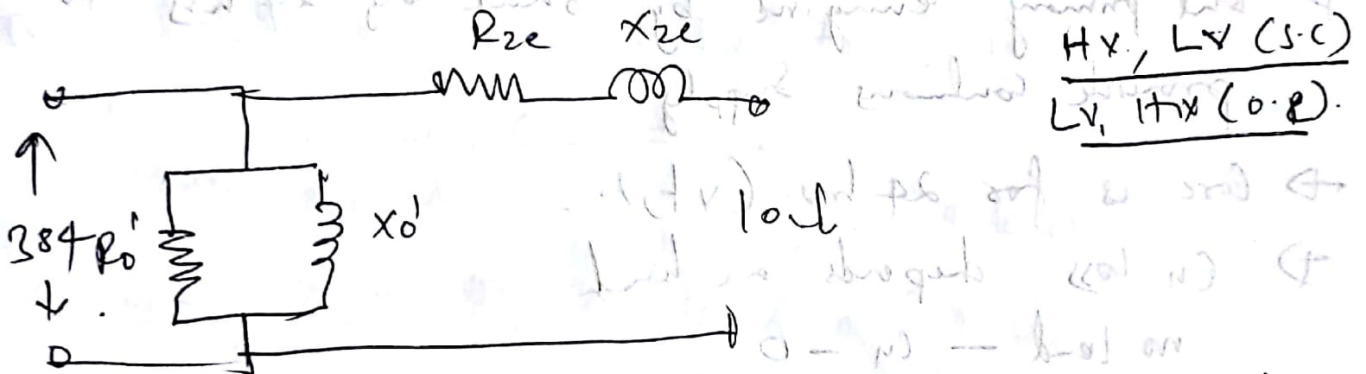
$$R_0' = K^2 R_0 = 1084 \Omega, \quad X_0' = K^2 X_0 = 2212 \Omega$$



→ A 5kVA, 500/250 V, 50 Hz, 1 ϕ T_{test} gave following readings

O.C. Test : 500 V, 1 A, 50 W (LV side open) HV: LV

S.C. Test : 25 V, 10 A, 60 W (LV side short) HV: LV

Determine i) η on F.L, 0.8 lag p.f. $\eta = 97.32\%$

ii) $\%R$, $\%X$ on F.L, 0.8 leading p.f. $R = -1.95\%$

iii) η on 60% of F.L, 0.8 lag p.f. $\eta = 97.103\%$

iv) Draw equivalent ckt R_{eff} to primary.

iii) No Cu loss for no load

$$\therefore \text{Total energy spent} = 2.6734 + 0.1306 + 0.91836 \\ = 4.72236 \text{ kWh}$$

$$\therefore \text{All day } \eta = \frac{\text{Total energy o/p in 24 hrs}}{\text{Total energy o/p in 24 hrs} + \text{Energy spent in 24 hrs}} \\ = \frac{96}{96 + 4.72236} \times 100 = 95.311\%$$

* There are two 100 kW transformers. Each has a max η of 98%. but in one transformer max η occurs at F.L while, in the other it occurs at H.L. Each transformer is on F.L for 4 hrs, on H.L for 6 hrs & one tenth load for 14 hrs per day. Determine all day η of each transformer.

→ Trans 1, % η_{\max} at F.L.

$$0.98 = \frac{100 \times 10^3}{100 \times 10^3 + 2P_i} \quad \text{i.e. } P_i = 1020.4081 \text{ W} = (P_{cu})_{FL}$$

$$\text{Energy spent for iron loss} = 1020.4081 \times 24 = 24.489 \text{ kWh}$$

$$\text{Energy o/p for 24 hrs} = 100 \times 4 + \frac{1}{2} \times 100 \times 6 + \frac{1}{10} \times 100 \times 14 \\ = 840 \text{ kWh.}$$

Energy spent in Cu loss

Load 1: 4 hrs, F.L.

$$E_1 = (P_{cu})_{FL} \times 4 = 1020.4081 \times 4 = 4.081 \text{ kWh}$$

Load 2: 6 hrs, $\eta = 0.5$

$$P_{cu} = \eta^2 \times P_{cu, FL} = 255.102 \text{ W}$$

$$E_2 = 255.102 \times 6 = 1.5306 \text{ kWh}$$

28, 30, 32, 34, 35, 36, 39, 41,
42, 43, 46, 47, 52

load 3 : 14 hrs, one tenth load ie $\eta = 0.1$

$$P_{lm} = \eta^2 \times P_{lm F.L} = 10.204 \text{ W}$$

$$E_3 = P_{lm} \times 14 = 0.1428 \text{ kWh}$$

$$\begin{aligned} \text{Total Energy spent} &= P_i + E_1 + E_2 + E_3 \\ &= 30.2434 \text{ kWh} \end{aligned}$$

$$\begin{aligned} \text{All day } \eta &= \frac{\text{o/p}}{\text{o/p} + \text{Energy spent}} \times 100 = \frac{840}{840 + 30.2434} \\ &= 96.524\% \end{aligned}$$

Transformer 2% η_{lm} occurs at $\eta = 0.5$

$$\% 0.98 = \frac{0.5 \times \text{o/p}}{0.5 \times \text{o/p} + 2P_i} \times 100$$

$$P_i = 510.204 \text{ W}, P_{lm} = 510.204 \text{ W at } \eta = 0.5$$

$$P_{lm(H.L)} = \eta^2 \times P_{lm(F.L)}$$

$$P_{lm F_2} = 2040.8163 \text{ W} = 2.0408 \text{ kW}$$

$$\begin{aligned} P_i &= \text{Energy spent for run loss} = 510.204 \times 24 \\ \text{o/p} &= 840 \text{ kWh} \end{aligned} \quad = 12.2448 \text{ kWh}$$

Energy spent in cu loss

load 1 $E_1 = 2040 \times 4 = 8.1632 \text{ kWh}$

2 $E_2 = 0.5^2 \times 2040.81 \times 6 = 3.061 \text{ kWh}$

3 $E_3 = (0.1)^2 \times 2040.81 \times 14 = 0.285 \text{ kWh}$

$$\text{Total energy spent} = 23.75 \text{ kWh}$$


$$\text{All day } \eta = \frac{840}{840 + 23.75} = 97.24\%$$

Introduction Three phase transformer

- generation voltage (3 ϕ) — 13.2kV, 22kV or higher
- Transmission power — 110kV, 132kV, or 400kV.
- So gen to Transmission 3 ϕ trs reqs. (step up) (Transmission)
- Distribution — 6600V, 440V, 230V etc (step down) (utilization)
- interconnected 3 single phase transformer or single 3 ϕ trs

Construction of 3 ϕ


Core type

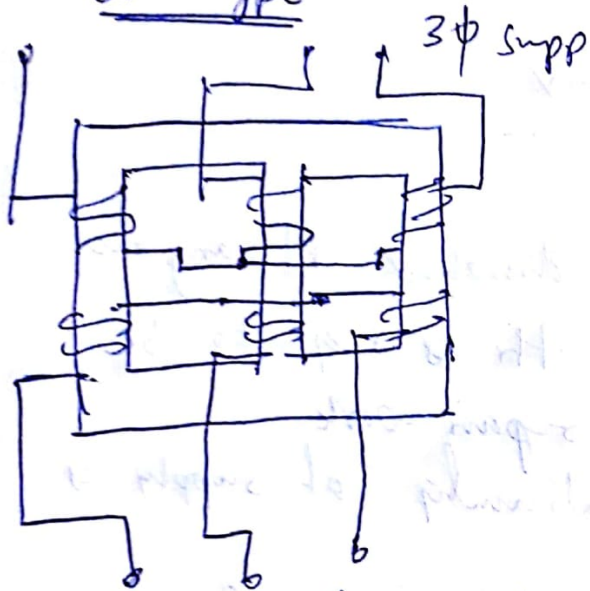

each
3 legs, 2 yokes, limb has
primary & secondary, one phase,
Two windows, flux in
one leg down in other
two legs.

to lead secondary

Shell type construction

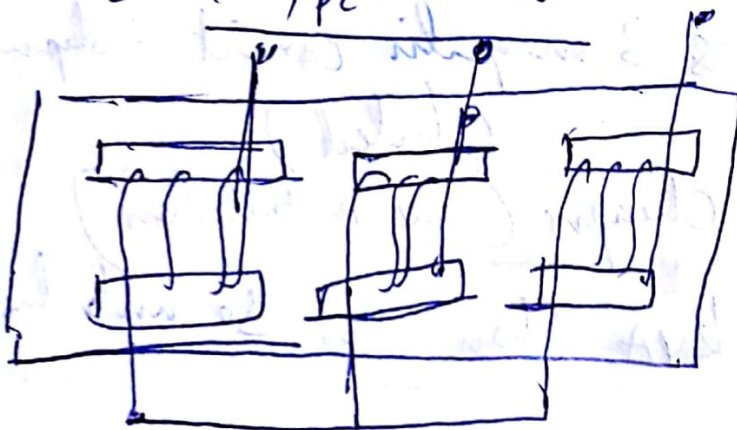

Advantages of single 3 ϕ transformer over bank

- 1) occupies less space for same rating
- 2) weights less 3) cost is less
- 4) easy for operator (one unit) 5) Transported easily
- 6) core size & material less
- 7) more efficient 8) 3 terminals are brought out & 6 terminals
- 9) overall bus bar structure, switch gear & installation simpler.

3- Bank of single phase transformer

- 3 transformers are identical.
- Saving in Iron. Advantage drawback if any one phase becomes faulty whole thr is reqd to be removed from service, for repair work.
- reliability is improved & continuity of supply is maintained
- possible to replace the single phase from spares
- 3 ϕ electrically connected & 3 magnetic circuit independent. (linked)
- preferred in mines, cheaper (one installation)
- one thr with higher kVA than other so unbalanced load supply

Bring word out

* A 2300/230 V, 500 kVA, 50 Hz Distribution transformer
 core loss of 1600 W at rated vty & cu loss 705 kW F.L.
 During day loaded as

| % load | 0% | 20% | 50% | 80% | 100% | 125% |
|--------|----|-----|-----|-----|------|------|
| P.f | - | 0.7 | 0.8 | 0.9 | 1 | 0.85 |
| Hrs | 2 | 4 | 4 | 5 | 7 | 2 |

Determine all day $\eta = 98.04\%$

Que (29/8/17)




3, 4, 10 | 11, 12, 16, | 26, 28, 30 | 31, 32, 34, 35, 36, | 41, 43, 46, 48,
 49.

Three phase Tfo Converter

→ Voltages can be raised or lower

- i) $\lambda - \lambda$ ii) $\Delta - \Delta$ iii) $\lambda - \Delta$ iv) $\Delta - \lambda$ v) open delta or
- v) connection vi) Scott connection or T-T conn.

$\lambda - \lambda$

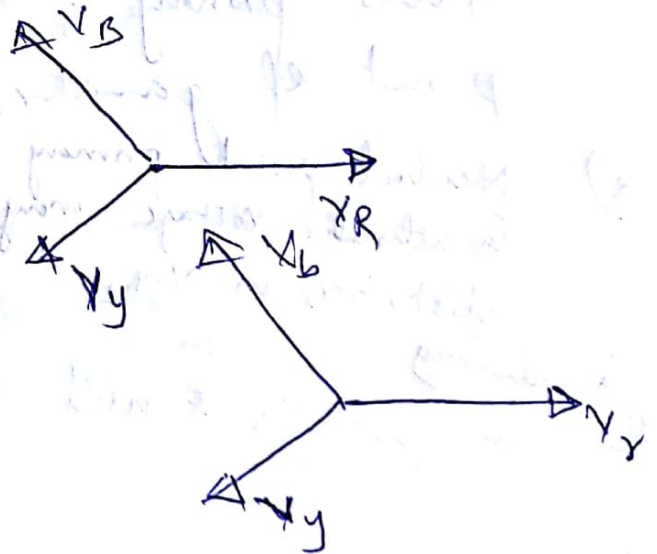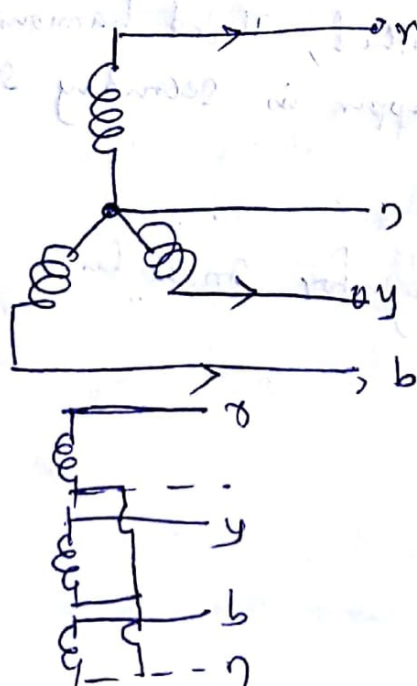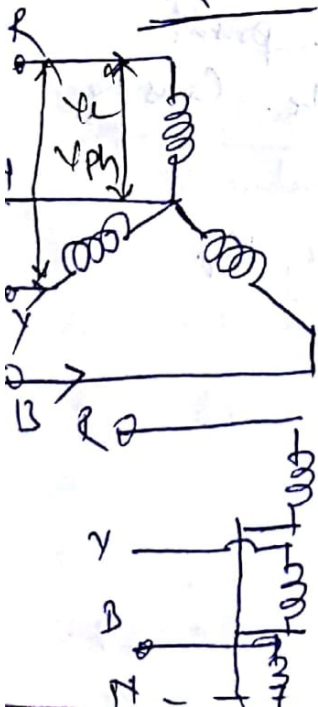

$$V_{ph1} = \frac{V_{L1}}{\sqrt{3}}, \quad V_{ph2} = k \left(\frac{V_{L1}}{\sqrt{3}} \right) \text{ as } \frac{V_{ph2}}{V_{ph1}} = k$$

$$V_{L1} = \sqrt{3} V_{ph1}$$

~~$$V_{L2} = \sqrt{3} V_{ph2}$$~~

$$V_{L2} = \sqrt{3} V_{ph2} = \sqrt{3} k \left(\frac{V_{L1}}{\sqrt{3}} \right) = k V_{L1}$$

Advantage $V_{ph} = \frac{V_L}{\sqrt{3}}$

- 1) less no. turns reqd, stress on insulation is less,
 Costlier economical
- 2) $I_L = I_{ph}$, wdg any high cty, $\frac{a \uparrow}{\text{mechanically strong, heavy leads of}} \uparrow$
 Bears

Short ckt

- 3) no phase shift betw primary & secondary vty
- 4) neutral, suitable for 3 ϕ four wire system





Disadvantage secondary (small high vty thr)

if load is unbalanced (performance not satisfactory)
 shifting of neutral point is possible. So to prevent
 this primary is to be connected to star
 point of generator.

a) Neutral point primary earthed, Third harmonic present
 in alternator voltage may appear in secondary side. Causing
 distortion in V_{ph2}


disadvantage
 Rare in practice & used only for small high vty thr

Delta-Delta Connection

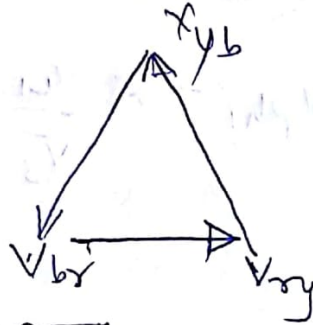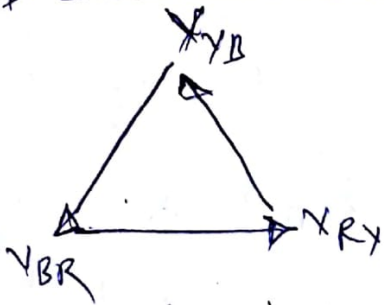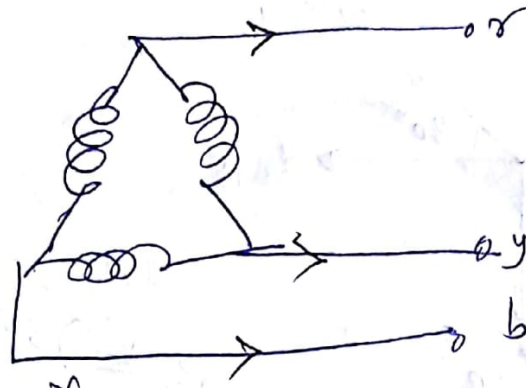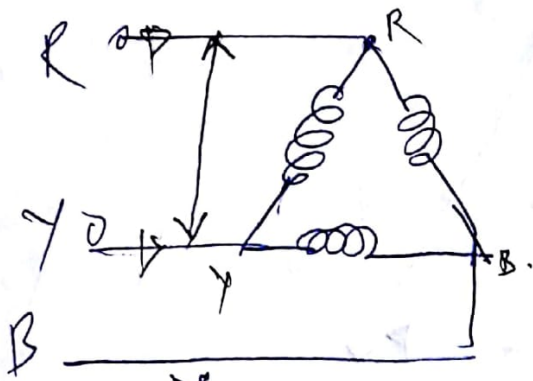

30
4 | 12, 16 | 30 | 34 | 44, 46 |

Large low vtg thr.
no phase shift

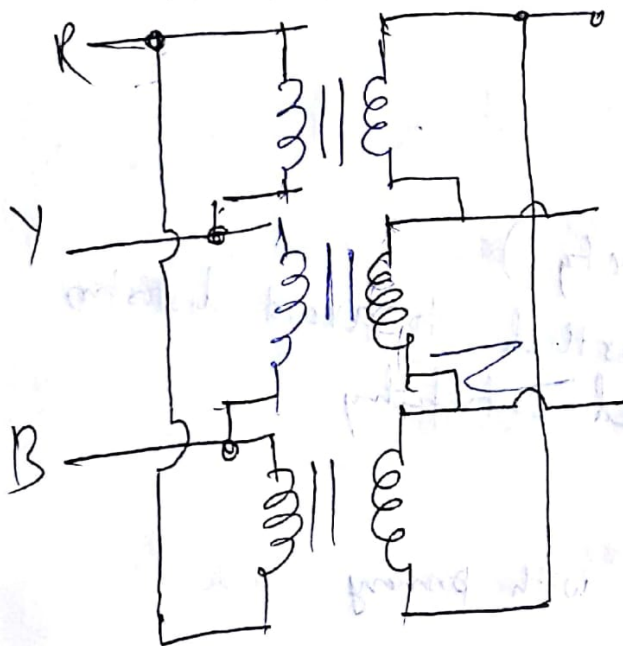

$$V_{L1} = V_{ph1}$$


$$k = \frac{V_{ph2}}{V_{ph1}} \rightarrow V_{ph2} = k V_{ph1}$$

$$V_{L2} = V_{ph2} = k V_{L1}$$

Advantages

- 1) secondary vtg sinusoidal, Im contain 3rd harmonic component, where Delta provides closed path for circulation.
 - 2) Allows unbalanced loading (vtg remains constant) ^{phase}
 - 3) Bank of 3 Thr, operated on 2 if 1 is disable Redundant
 - 4) no distortion in secondary vtg
 - 5) $V_{ph} = V_L$ (more turns), But $I_{ph} = I_L / \sqrt{3}$ (a \downarrow), economical
- Disadv :- absence of neutral point (no 3 phase four wire sys)

Star - Delta

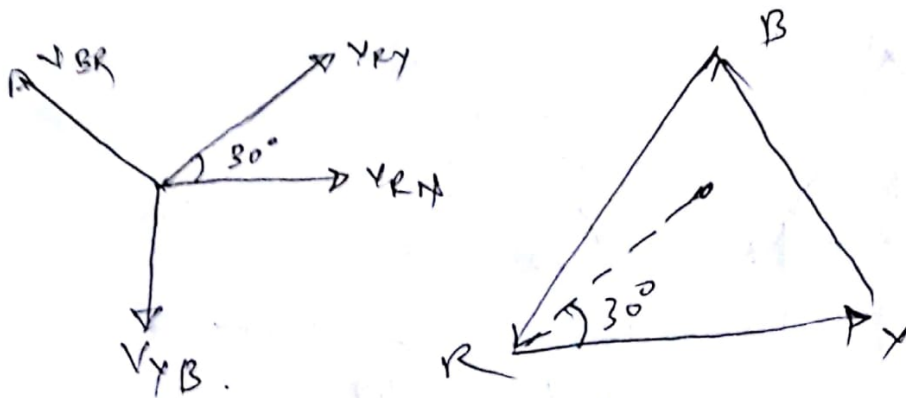

$$V_{ph1} = V_{L1} / \sqrt{3}, \quad V_{ph2} = K V_{ph1} = K \frac{V_{L1}}{\sqrt{3}}$$

$$\therefore V_{ph2} = V_{L2}$$

$$V_{L2} = K \frac{V_{L1}}{\sqrt{3}}$$

Adv

- 1) As primary star (large high vty)
- 2) neutral available primary earthed to avoid distortion
- 3) large unbalanced loads handled satisfactorily

Disadv

Secondary vty is not in phase with primary.

D-d

primary $V_{L1} = V_{ph1}$ $K = V_{ph2} / V_{ph1}$

$$V_{ph2} = K V_{ph1}$$

$$\text{Star, } V_{L2} = \sqrt{3} V_{ph2} \Rightarrow (\sqrt{3} K) V_{ph1} \\ = (\sqrt{3} K V_{L1})$$

Adv

- 1) primary Δ wdg cross section is less.
- 2) neutral available (3 ϕ , four wire sys)
- 3) no distortion due to 3rd harmonic component.
- 4) star connection (saving in insulation)
- 5) large unbalanced load handling

Disadv

phase betw second & primary

- A 3 ϕ step down tr is connected to 6600 V main bit takes 10A. Calculate secondary line vty, line c/n, o/p for

- a) Δ - Δ b) Δ -d c) Δ - Δ d) Δ -d $k = 1/12$

Turns Ratio/phase is 12. Draw connection dgm

Soln: $V_{L1} = 6600 \text{ V}$ $I_{L1} = 10 \text{ A}$.

a) $V_{L2} = 550 \text{ V}$, $I_{L2} = 120 \text{ A}$, $\text{o/p} = \sqrt{3} V_{L2} I_{L2} = 114.315 \text{ kW}$.

b) Δ -d , $V_{L2} = 550 \text{ V}$, $I_{L2} = 120 \text{ A}$, $\text{o/p} = 114.315 \text{ kW}$

c) Δ - Δ



$V_{L2} = 317.543 \text{ V}$, $I_{L2} = 207.846$,

$\text{o/p} = \sqrt{3} V_{L2} I_{L2} = 114.315 \text{ kW}$.

c) Δ -d

$V_{L2} = 952.62$, $I_{L2} = 69.282$, $\text{o/p} = 114.315 \text{ kW}$.

Open delta or V-V connection

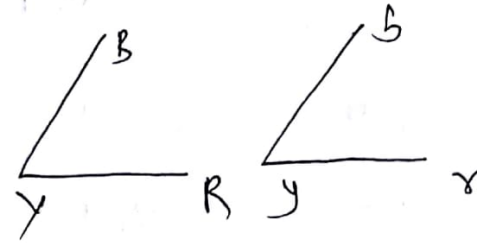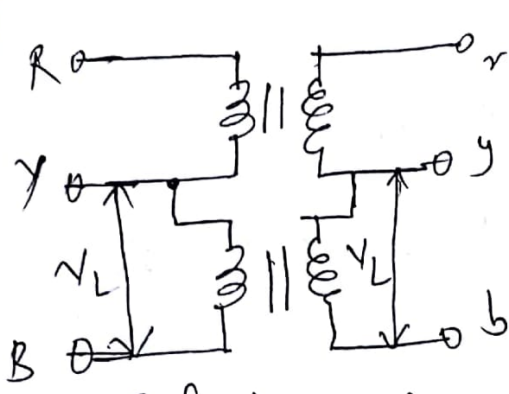


Hand pain

Reduced Capacity, future load will increase


V-V bank load carried = $\frac{2}{3}$ of capacity of $\Delta-\Delta$ bank

but load carried by V-V bank is only 57.7%


It can be proved

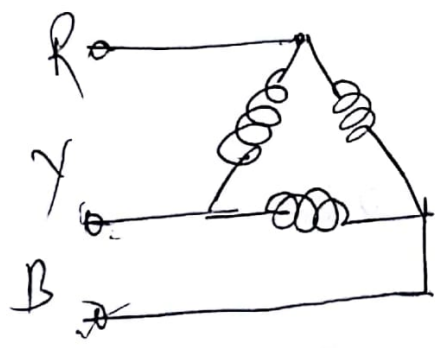


$\Delta-\Delta$

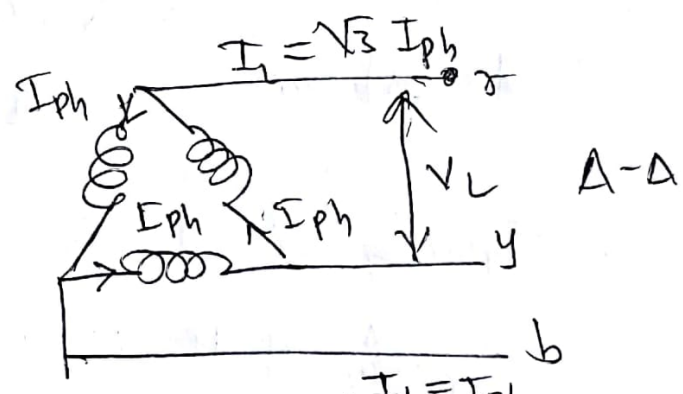

$\Delta-\Delta$

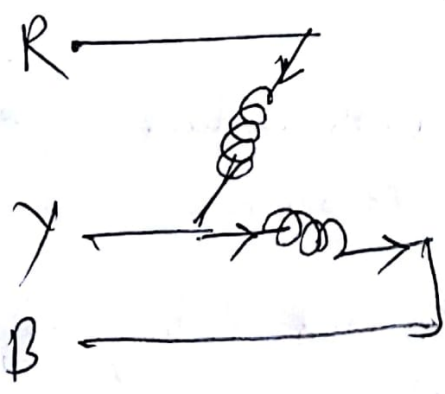

V-V

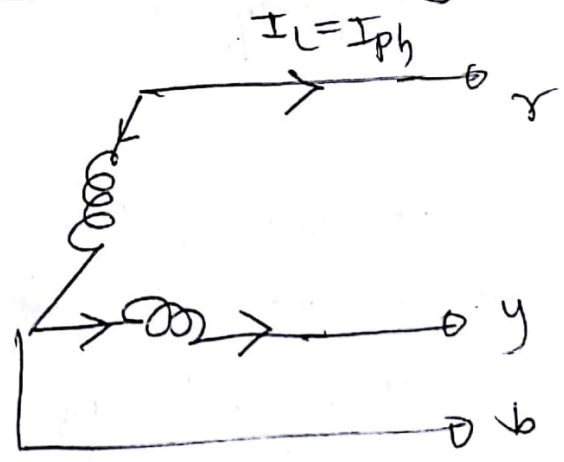

$$\Delta-\Delta \text{ Capacity} = \sqrt{3} V_L I_L = \sqrt{3} V_L (\sqrt{3} I_{ph})$$

$$\Delta-\Delta \text{ Capacity} = 3 V_L I_{ph}$$

$$V-V \text{ Capacity} = \sqrt{3} V_L I_L = \sqrt{3} V_L I_{ph}$$

$$\frac{V-V \text{ Capacity}}{\Delta-\Delta \text{ Capacity}} = \frac{\sqrt{3} V_L I_{ph}}{3 V_L I_{ph}} = \frac{1}{\sqrt{3}} = 0.577 = 57.7\%$$

Its not 66.7%

$$\text{Reduction in Rating} = \frac{66.67 - 57.735}{57.735} \times 100 = 15.47\%$$

The overload each transformer given as (3 operating one reserved)

$$\frac{\text{Total load in } V-V}{VA/\text{transformer}} = \frac{\sqrt{3} V_L I_{ph}}{V_L I_{ph}} = \sqrt{3} = 1.732$$

$$\frac{\text{Operating Capacity of thr in } V-V}{\text{Available Capacity of thr in } V-V} = 0.866$$

Available Capacity of thr in V-V

Slow

Advantages

- 1) if one is not operate, can continue with Reduced Capacity
- 2) 3 ϕ load is small, V-V connection economical.
- 3) If there is possibility of increase in load future, add one transformer, capacity can be increased
- 4) connection acts as automatic standby

Disadvantage

- 1) Avg pf at which V-V bank is operating is less than that with load. This power pf is 86.6% of balanced load pf.
- 2) V-V bank operate at diff. pf except for balanced up.
- 3) The terminal vtgs available on secondary side become unbalanced. This may happen even though load is perfectly balanced.

$$P_1 = KVA \cos(30 - \phi), \quad P_2 = KVA \cos(30 + \phi).$$

→ Δ - Δ bank. Consisting of 3 40kVA, 2300/230V tfr supplies a load of 80kVA. If one is removed, find for resulting V-V connection

- i) kVA load carried by each tfr
- ii) percent of rated load carried by each tfr.
- iii) Total kVA rating of V-V bank
- iv) Ratio of V-V bank to Δ - Δ bank tfr rating
- v) percent increase in load on each tfr when bank is converted into V-V bank.

12,49,

(more, explanation, more problems, proper notes, loudly, clarity, doubts)

* A balanced 3 ϕ load of 30 kVA, at a power factor of 0.866 lagging, is connected to two tfr connected in open delta, to a 230V 3 ϕ system. Find the power delivered by each tfr

Solⁿ: 30 kVA is total load, $\cos\phi = 0.866$ i.e. $\phi = 30^\circ$

\therefore operating capacity of each tfr = $30/2 = 15$ kw

$$\frac{\text{operating capacity}}{\text{Available}} = 0.866 \Rightarrow \text{Available kVA} = \frac{15}{0.866} = 17.32 \text{ kw}$$

$$\therefore P_1 = \text{kVA} \cos(30 - \phi) = 17.32 \times \cos(0) = 17.32 \text{ kw}$$

$$P_2 = \text{kVA} \cos(30 + \phi) = 17.32 \times \cos(60) = 8.66 \text{ kw}$$

$$\text{Check } 30 \text{ kVA} \times 0.866 = 25.98 \text{ kw} = P_1 + P_2$$

* Two tfr connected in open delta supply a 400 kVA balanced load operating at 0.866 pf lagging. The load vty is 440V. Find i) kVA supplied by each tfr ii) kW supplied by tfr

Solⁿ: total load to be supplied = 400 kVA

operating capacity each tfr = $\frac{400}{2} = 200$ kVA.

$$i) \frac{\text{operating capacity}}{\text{Available}} = 0.866 \Rightarrow \text{Available} = \frac{200}{0.866} = 230.946 \text{ kw}$$

99) kw supplied by each thr is

$$P_1 = kVA \times \cos(30 - \phi) \quad \& \quad P_2 = kVA \cos(30 + \phi)$$





$$\phi = 30^\circ$$

$$P_1 = 230.946 \cos(0) = 230.946 \text{ kw}$$

$$P_2 = 230.946 \cos(60) = 115.474 \text{ kw}$$

$$P_1 + P_2 = 346.419 \text{ kw} = 460 \text{ kVA} \times 0.866 \text{ kw}$$

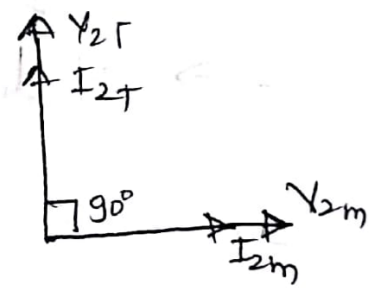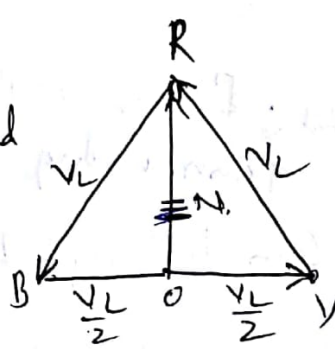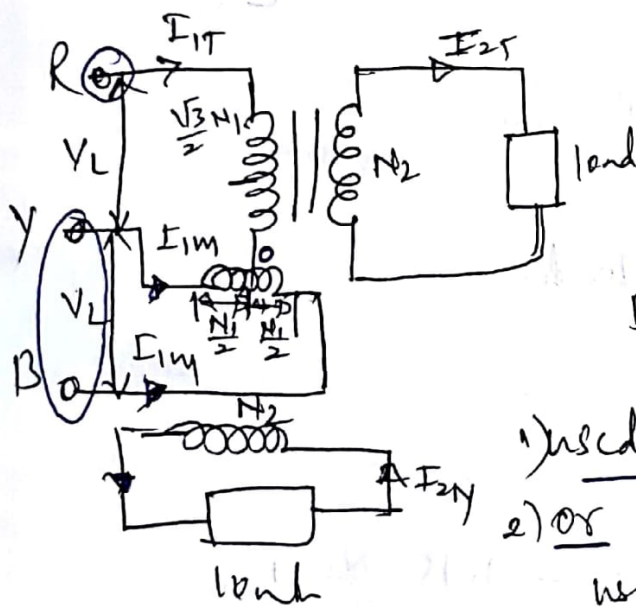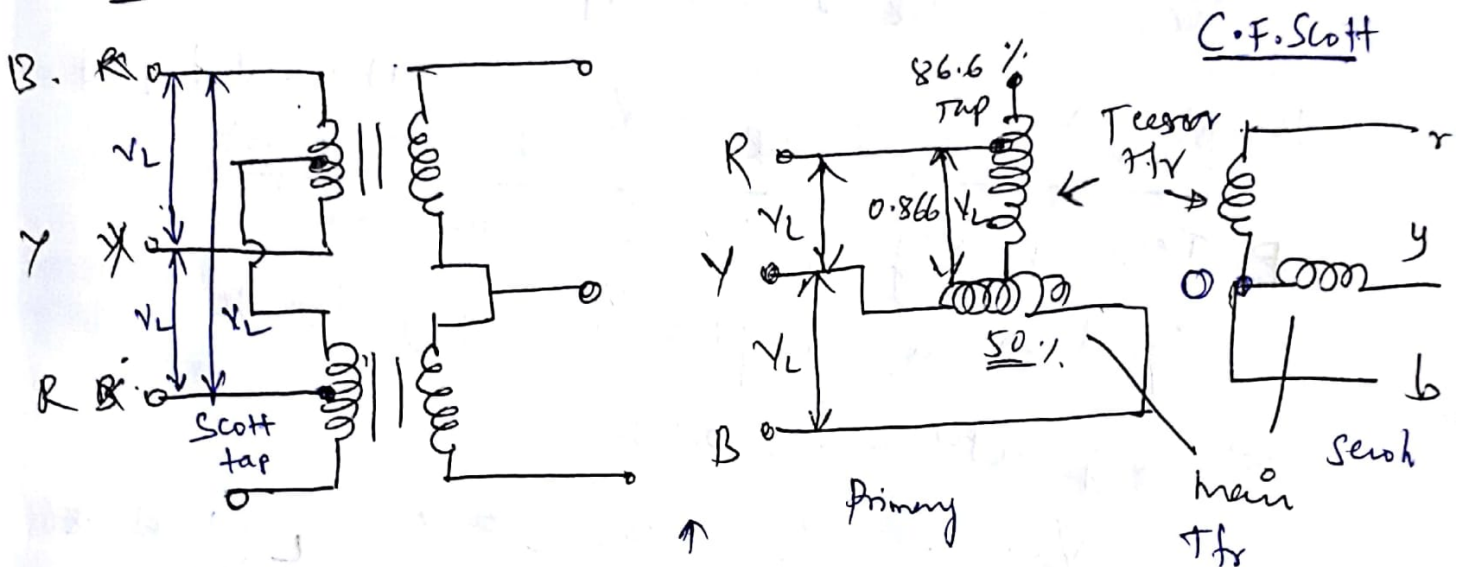Conversion of three phase to two phase (Scott Connection)



- 1) used for furnaces (2 phase electric)
- 2) or three phase load can be used from available 2 φ supply

→ 50% tapping main thr (Two thr with diff rating) or (Identical thr with tapping for interchangeability & provision of spares).

→ 86.6% tapping teaser thr.

→ one end Teaser thr is connected to centre tapping on primary wdg main thr. [Two phase 3 wire system obtain]

→ Two ends of main thr & 86.6% tapping point on T-T connected to supply (Balanced)

→ N_1 turns connected beto (Y & B)
 → $V_{RY} = V_{YB} = V_{BR} = V_L$ (line vtgs)

[E_t is same in primary & equal no turns on secondary]
 pf $\sqrt{3}/2 N_1$

→ $V_{Po} = \sqrt{3}/2 V_L$ & $V_{RN} = V_L/\sqrt{3}$

N is neutral point
 O is not

→ Terminal vtg on secondary having equal in magn & phase diff of 90° beto them

→ vtg betw N & O will be

$$\frac{\sqrt{3}}{2} V_L - \frac{1}{\sqrt{3}} V_L = 0.288 V_L \approx 0.29 V_L \quad (\frac{1}{3} \text{ of } 0.866)$$

→ N divides P_o in 2:1 Ratio
 Teaser winding

→ let us consider upf load.

$$K = \frac{I_{1T}}{I_{2T}} = \frac{N_2}{N_1}$$

$$I_{1T} = I_{2T} \times \frac{N_2}{\left(\frac{\sqrt{3}}{2} N_1\right)} = 1.15 \frac{N_2}{N_1} I_{2T}$$

$$I_{1T} = 1.15 I_{2T}$$

Each half of p.w main thr carries ch of I_{1m} .
 Consisting two parts

$$1) I_{1m} = \frac{N_2}{N_1} I_{2m} = k I_{2m}$$

i.) equal to one half of heavy ch $\frac{1}{2} I_{1T}$

$$= \frac{I_{1T}}{2} = \frac{1.15 k I_{2T}}{2} = 0.58 k I_{2T}$$

The line ch on primary side ultimately give by

$$I_R = I_{1T}$$



$$I_Y = I_{1m} - \frac{I_{1T}}{2}$$

$$I_B = -I_{1m} - \frac{I_{1T}}{2}$$

magnitude

$$I_R = I_{1T}, \quad I_Y = I_B = \sqrt{(I_{1m})^2 + \left(\frac{1}{2} I_{1T}\right)^2}$$

11, 12, 18, 19, 25, 41, 43,
 48, 49, 52,

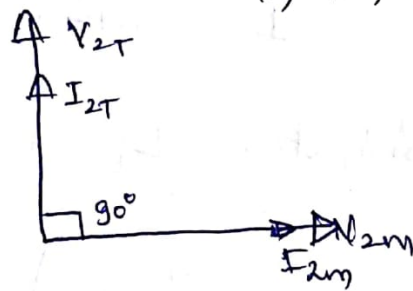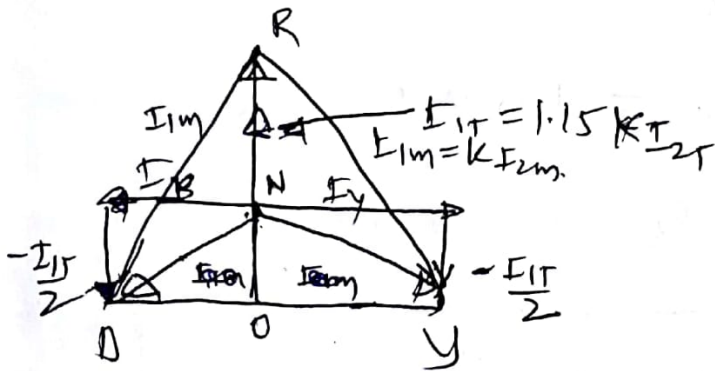

→ $-\frac{I_{1T}}{2}$ no effect on core & does not take part in balancing secondary Amp turns of main thr.


→ when two phase load of upf is balanced the 3 ϕ side also balanced.

→ consider two phase load at 1 pt

→ The 3 ϕ side is again balanced as Ckt drawn from 3 ϕ system are equal balanced & lag by angle ϕ .

→ let us consider equal ckt at a pt of $\cos\phi$ lagging

$$I_{aT} = I_{am} = I_2$$

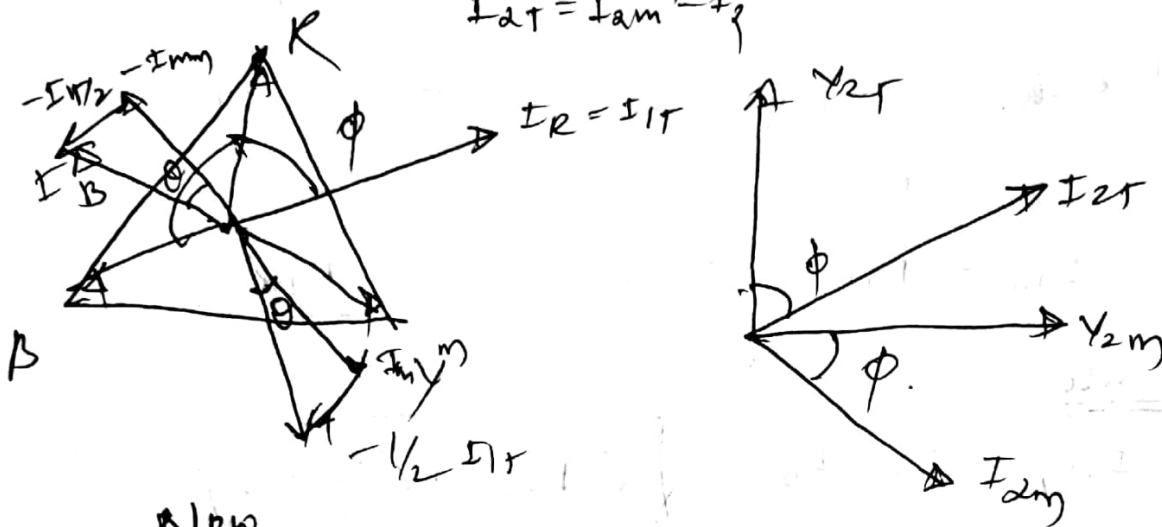

Now

$$I_m = k I_{2m} = k I_2$$

$$I_{IT} = 1.15 k I_{2T} = 1.15 k I_2$$

Substituting $I_R = 1.15 k I_2$

$$I_y = I_B = \sqrt{(k I_2)^2 + \left(\frac{1}{2} \cdot 1.15 k I_2\right)^2} = 1.16 k I_2$$

Thus all ckt in primary side equal in magint

$$\tan\theta = \frac{\frac{1}{2} I_{IT}}{I_m} = \frac{\frac{1}{2} (1.15 k I_2)}{k I_2} = 0.58 \quad \theta = 30$$

* Two electric furnaces are supplied with 1 ϕ ^{cbn} ~~cbn~~ at 80V from a 3 ϕ , 11000V. system by means of two single phase Scott connected thr with similar secondary wdg, when the load on one furnace is 500kw & on the ^{line} other 800kw, what ckt will flow in each of 3 lines

i) At up. t ii) 0.8 pf lag. 6, 12, 18, 24, 30, 32, 33, 35, 37, 38, ~~43~~, 44, 51, 54, 55.

3 | let them (1k not in your control). let them see.
01, 11, 12, 30, 33, 42, 48, 50, Don't care let them.

Solⁿ

Furnace 1 (500kw) - 80V
Furnace 2 (800kw) - 80V

$$I_{2T} = \frac{P}{V \cos \phi} = \frac{500 \times 10^3}{80 \times 1} = 6250 \text{ A}$$

main thr $K = \frac{V_2}{V_1} = \frac{80}{11000} = 7.27 \times 10^{-3} = 0.00727$

(Ternr thr) $K = 1.1547 \times K(\text{main thr}) = 8.394 \times 10^{-3} = 0.0084$

$I_{R} = I_{1T} = K(\text{Ternr Thr}) \times I_{2T} = 0.0084 \times 6250 = 52.46 \text{ A}$

(main thr) $I_{2m} = \frac{P}{V \cos \phi} = \frac{800 \times 10^3}{80 \times 1} = 10,000 \text{ A}$

$I_{1m} = K(\text{main thr}) \times 10,000 = 0.00727 \times 10,000 = 72.7 \text{ A}$

Total ckt current = $\sqrt{(72.7)^2 + (26.2)^2}$

$I_T = I_B = 77.28$


Σ (Tue) 15/09/17

9, 11, 12, 43, 48,




Tue (Afternoon)

04, 12, 53,

At up

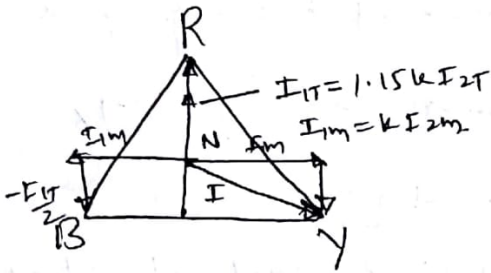


At tags

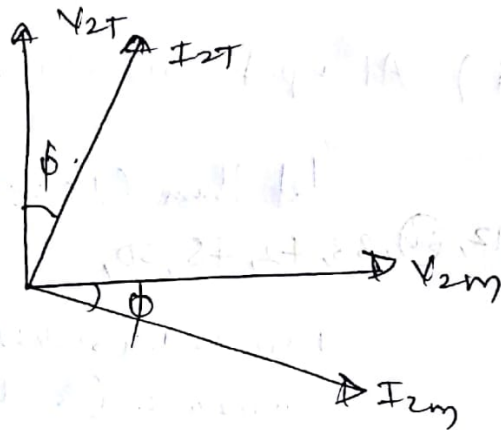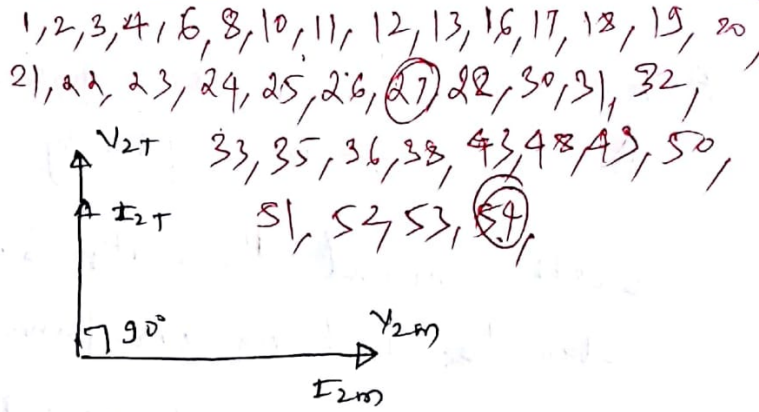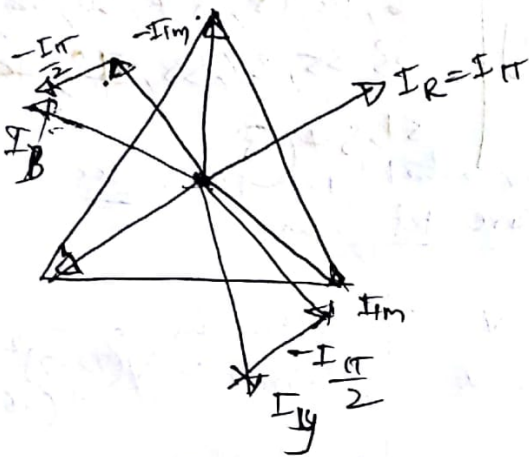

* Two 110 volt single phase electric furnace take load of 500kw and 800kw respectively at pf of 0.71 lag & are supplied from 6600V, 3φ, 50hz mains through Scott connected transformer combination. Calculate the Ch in Bφ line neglecting transformer losses. Draw phasor diagram

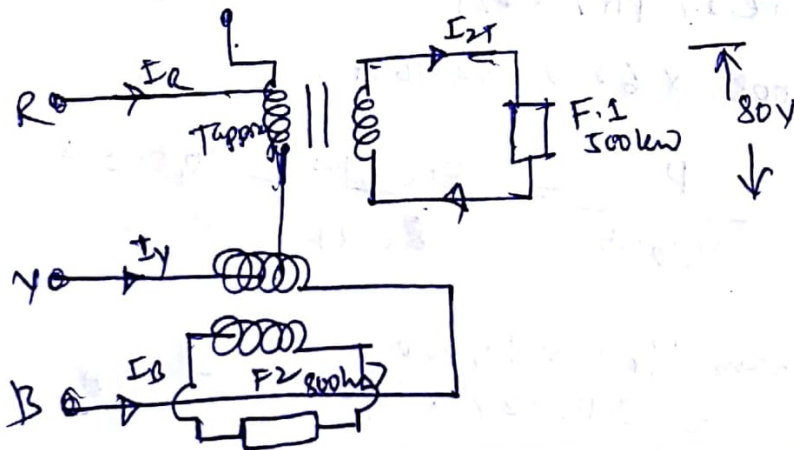
$$I_R = 197.13 \text{ A} \quad I_y = I_B = 144.94 \text{ A}$$




Labelling of Transformer terminals

Page

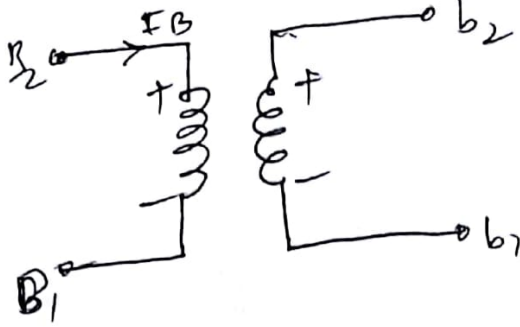Thur (9/11/19, 21, 28, 30, 32, 43, 48, 59, 85)



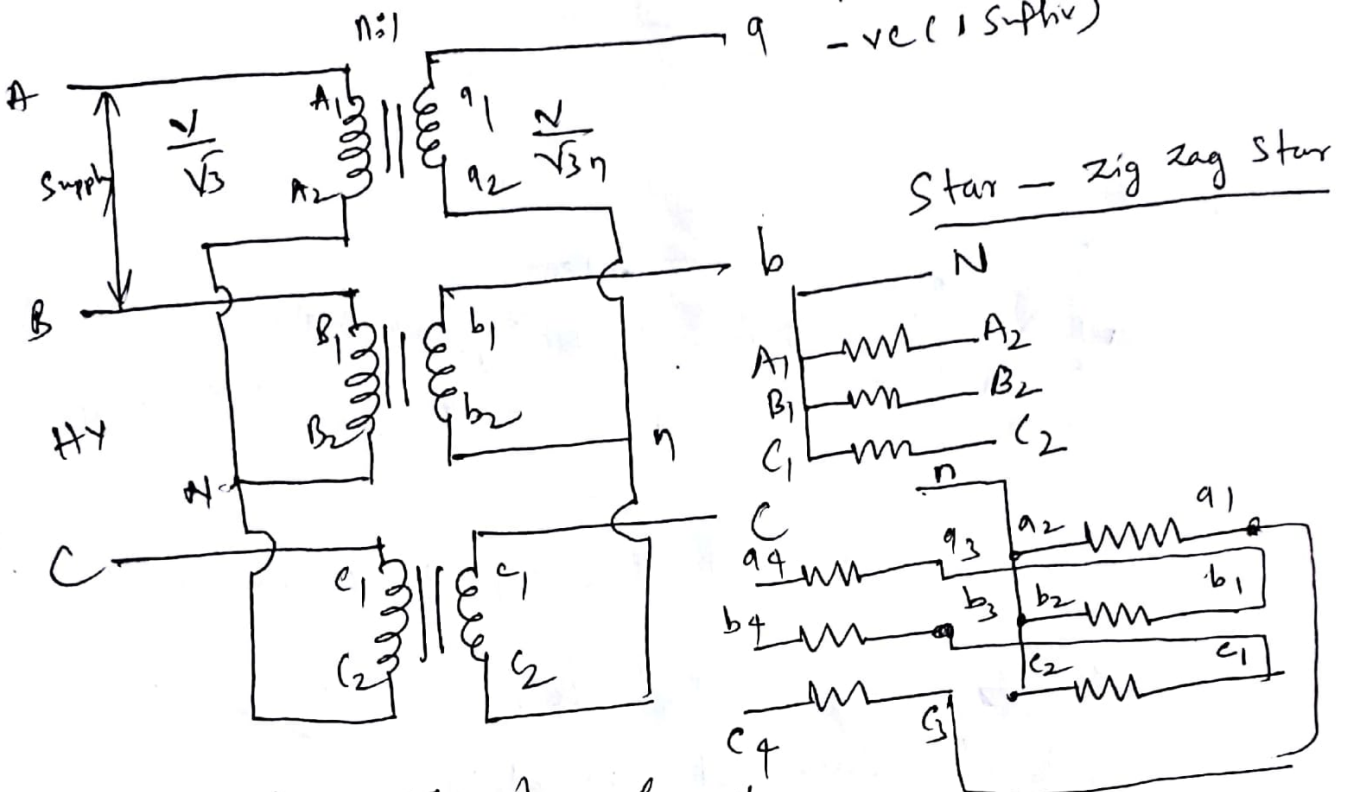HV (Capital letters)
 LV (Small letters)
 +ve (2)
 -ve (1 Supply)



Three phase Three phase groups

- Vector dgm of primary & secondary emf are useful to describe characteristics, advantages & disadvantages
- Construction of vector dgm principles
 - 1)

6, 11, 12, 13, 18, 22, 30, 33, 8