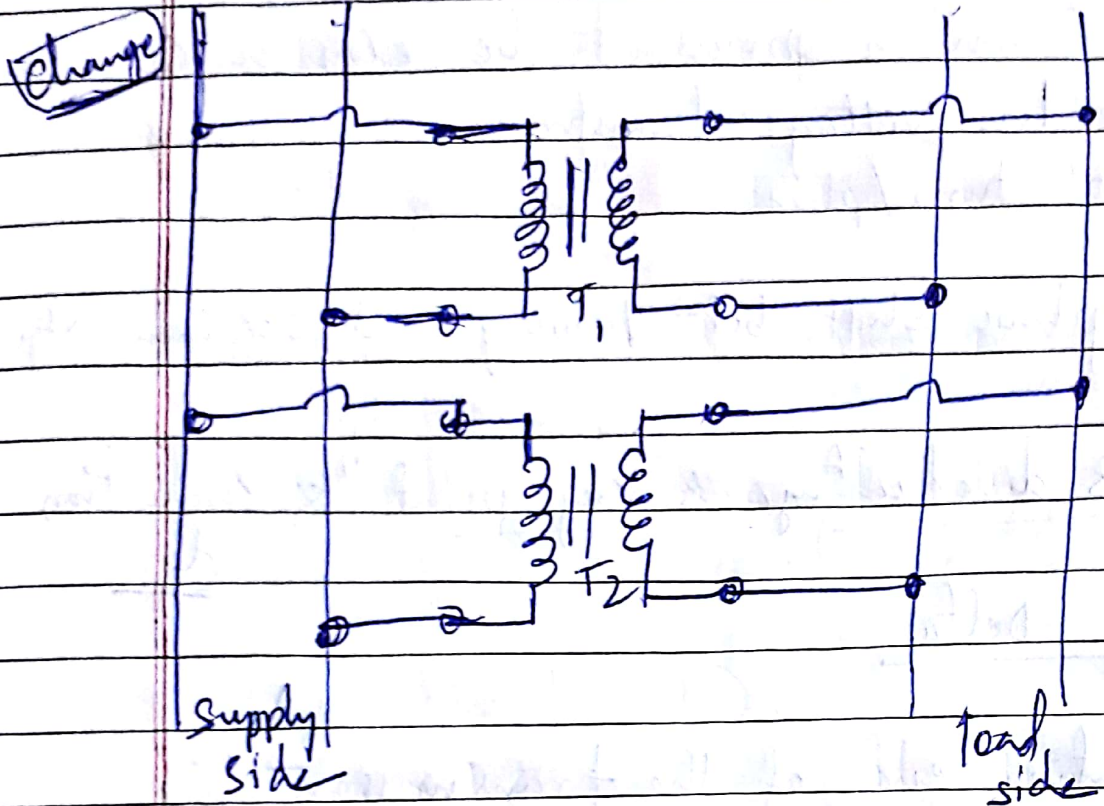


Unit 2Parallel operation of transformers

Why parallel connection?

load $>$ kVA Rating, share load, burden on 1 Transformer, spare parts interchangeably & storage easy.

→ primary supply bus bars & secondary load bus bars connected

→ Two or more connected in parallel to carry common load

- If one tfr is of reduced capacity for a particular load we can remove or replace with higher capacity or additional unit is inserted to share load with same connection.
- Additional unit is said parallel with first one.
- Satisfactory operation in parallel load must be satisfied.

Need of parallel operation

- i) $\text{load} > \text{Capacity individual transformer}$
Second unit will share that load.
- ii) Power system reliable a parallel operation needed. If any one fault occurs, it can be removed & other units in parallel can maintain supply.
- iii) According to power demand, transformer in parallel can be switched on or off which reduced tfr losses and makes overall system more efficient & economical.

iv) when no of transformer are connected in parallel, cost of Standby unit is much less


Conditions of parallel operation

- 1) Supply system and frequency. Same
- 2) Same polarity
- 3) Voltage Ratio Same of both
- 4) %Z equal in magnitude & X/R Same
(avoid circulating c/n & operation at different p.f.)
- 5) $Z_{eq} \propto \frac{1}{kVA \text{ (Individual)}}$ (if different kVA rating to avoid circulating c/n)

2nd explanation

0 degree phase displacement or 180 degree phase difference & series closed circuit.

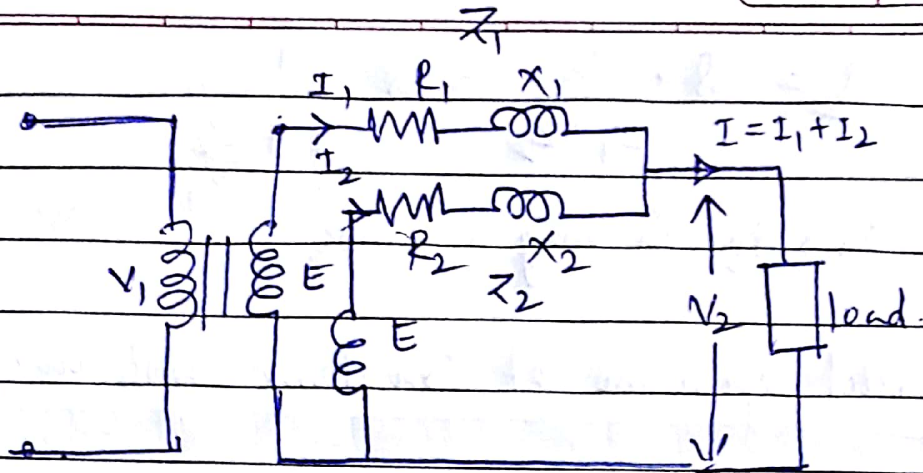Load sharing in case of ~~Identical~~ or similar thr with equal voltage ratio



→ no load secondary V is same $E = E_1 = E_2$ (in phase)

→ equivalent impedance

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad \therefore Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

→ w.k.T $I_1 Z_1 = I_2 Z_2 = I Z_{eq}$

$$I_1 = \frac{I \cdot Z_{eq}}{Z_1} = \frac{I Z_2}{Z_1 + Z_2} \quad \& \quad I_2 = \frac{I Z_{eq}}{Z_2} = \frac{I Z_1}{Z_1 + Z_2}$$

Multiply by V_2

$$V_2 I_1 = V_2 I \frac{Z_2}{Z_1 + Z_2} \quad V_2 I_2 = V_2 I \frac{Z_1}{Z_1 + Z_2}$$

$V_2 I \times 10^{-3}$ is ϕ , i.e. combined load in kVA.


kVA Carried by each tr

$$\phi_1 = \phi \frac{Z_2}{Z_1 + Z_2} = \phi \cdot \frac{1}{1 + \frac{Z_1}{Z_2}}$$

$$Q_2 = Q \cdot \frac{z_1}{z_1 + z_2} = Q \cdot \frac{1}{1 + \frac{z_2}{z_1}}$$

Q_1 & Q_2 in mag & phase.

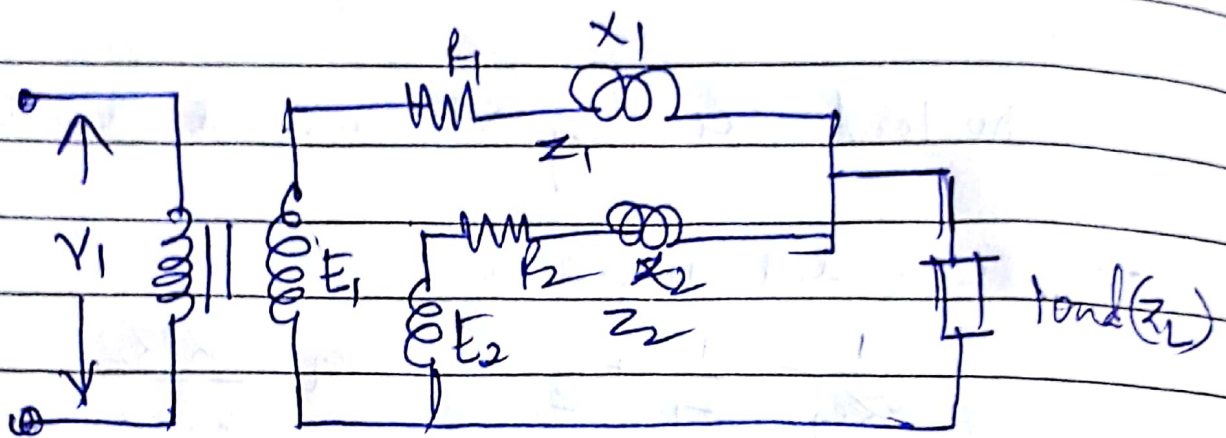parallel operation of Transformer with unequal Ratio (ctg)



Voltage Ratio of $1 > 2$. $| E_1 > E_2$.

$$V = E_1 - E_2$$

$$I_c = \frac{E_1 - E_2}{z_1 + z_2}$$

Circuit dg we have

$$E_1 = V_2 + I_1 z_1 \quad \& \quad E_2 = V_2 + I_2 z_2 \quad I_L = I_1 + I_2$$

$$V_2 = I_L z_L = (I_1 + I_2) z_L$$

$$E_1 = (I_1 + I_2)Z_L + Z_1 I_1 \quad \text{--- (a)}$$

$$E_2 = (I_1 + I_2)Z_L + I_2 Z_2 \quad \text{--- (b)}$$

Subtract a * b

$$E_1 - E_2 = I_1 Z_1 - I_2 Z_2$$

$$I_1 = \frac{(E_1 - E_2) + I_2 Z_2}{Z_1}$$

Substitute this in (b)


$$E_2 = I_2 Z_2 + \left[\frac{(E_1 - E_2) + I_2 Z_2}{Z_1} + I_2 \right] Z_L$$

$$* \quad I_1 = \frac{E_1 Z_2}{Z_L (Z_1 + Z_2)} + \frac{E_1 - E_2}{Z_1 + Z_2} \quad \bigg| \quad I_2 = \frac{E_2 Z_1}{Z_L (Z_1 + Z_2)} - \frac{E_1 - E_2}{Z_1 + Z_2}$$



Two transformers A & B are connected in parallel to a load of $(2 + j1.5) \Omega$. Their impedances in secondary terms are $Z_A = (0.15 + j0.5) \Omega$ and $Z_B = (0.1 + j0.6) \Omega$. Their no load terminal voltages are $E_A = 207 \angle 0^\circ \text{ V}$ and $E_B = 205 \angle 0^\circ \text{ V}$. Find the power output and pf of transformer.

Auto transformer

What, How, which, why, when, where

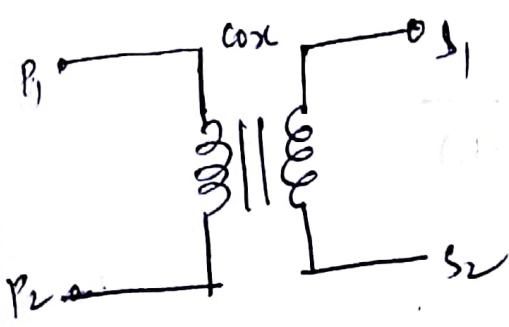

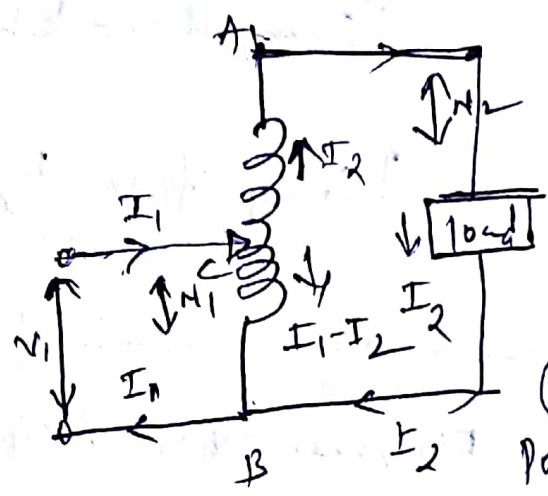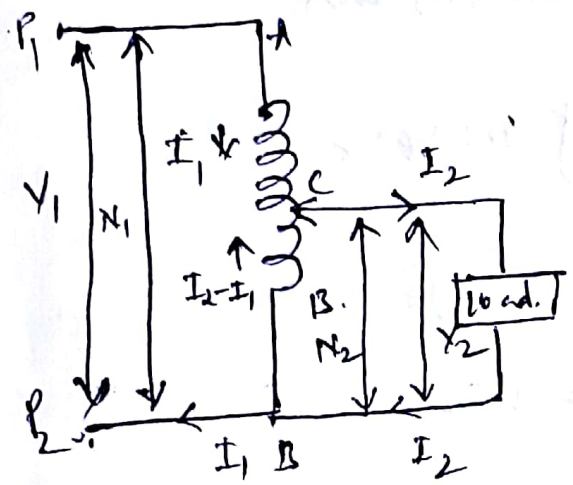Power transfer electrically isolated Induction



Electrically connected Conduction & induction Power transfer

i) Step down Auto transformer

ii) Step up auto transformer

$N_2 < N_1, V_2 < V_1$
 $AB = N_1, BC = N_2$
 $k < 1$

$N_2 > N_1, V_2 > V_1$
 $AB = N_2, BC = N_1$
 $k > 1$

$$k = \frac{V_2}{V_1} = \frac{I_1}{I_2} = \frac{N_2}{N_1}$$

Copper Saving in auto transformer (step down and

$W_{TW} \propto [N_1 I_1 + N_2 I_2]$

$W_{AT} \propto [(N_1 - N_2) I_1 + N_2 (I_2 - I_1)]$

Ratio $\frac{W_{TW}}{W_{AT}} = \frac{N_1 I_1 + N_2 I_2}{[(N_1 - N_2) I_1 + N_2 (I_2 - I_1)]} = \frac{N_1 I_1 + N_2 (I_1/k)}{[N_1 I_1 - N_2 I_1 + N_2 I_1/k - N_2 I_1]}$

$k = I_1/I_2 = N_2/N_1$
 $I_2 = I_1/k, N_2 = k N_1$

$$\frac{W_{TO}}{W_{AT}} = \frac{N_1 I_1 + \cancel{K} N_1 \left(\frac{I_1}{K} \right)}{N_1 I_1 + \cancel{K} N_1 \left(\frac{I_1}{K} \right) - 2(K N_1) I_1}$$

$$= \frac{2 N_1 I_1}{2 N_1 I_1 - 2 K N_1 I_1} = \frac{1}{(1-K)}$$

$$W_{AT} = (1-K) W_{TO}$$

$$\therefore \text{Saving in } W = W_{TO} - W_{AT} = W_{TO} - (1-K) W_{TO} = K W_{TO}$$

$$\boxed{\text{Saving of } W = K W_{TO}} \rightarrow \text{Step down.}$$

$$\boxed{\text{Saving of } W = \frac{1}{K} W_{TO}} \rightarrow \text{Step up.}$$

Power transfer in autotransformer (step down)

$$I/p \text{ power} = V_1 I_1 \quad ; \quad o/p \text{ power} = V_2 I_2$$

$$P_t = \text{Power transfer inductively}$$

$$= (N_2) [I_2 - I_1]$$

$$= K N_1 \left[\frac{I_1}{K} - I_1 \right] = N_1 I_1 - K N_1 I_1 = (1-K) V_1 I_1$$

$$= (1-K) I/p \text{ power}$$

$$\text{Remaining } P_c = K (I/p \text{ power})$$

$$P_c = (\text{load power o/p}) - P_t$$

* gives more output (C & I) \rightarrow Higher η .

VA Rating of Autotr (Compare VA of Auto & two wdg)

Step down

$$K = \frac{V_2}{V_1} = \frac{I_1}{I_2} = \frac{N_2}{N_1} \Rightarrow$$

VA rating of Autotransformer

$$(VA)_{AT} = V_1 I_1 = V_2 I_2$$

Primary AC $\rightarrow (V_1 - V_2) I_1$ BC $\rightarrow (I_2 - I_1) V_2$ Secondary

If this used as transformer (dwdg)

$$(VA)_{TW} = (I_2 - I_1) V_2$$

$$(VA)_{TW} = (V_1 - V_2) I_1 = (I_2 - I_1) V_2$$

$$= V_2 I_2 - k V_2 I_2 k$$

$$= \underline{V_2 I_2 (1 - k)}$$

$$(VA)_{TW} = (V_1 I_1 - k V_1 I_1) = V_1 I_1 (1 - k)$$

$$= V_{AT} (1 - k)$$

$$V_{AT} = \frac{1}{(1 - k)} (VA)_{TW}$$

if $k < 1$, $(1 - k) < 1$, $V_{AT} > (VA)_{TW}$
STEP UP

$$(VA)_{AT} = V_1 I_1 = V_2 I_2$$

BC $\rightarrow V_1 (I_1 - I_2)$ primary; AB $\rightarrow (V_2 - V_1) I_2$

$$(VA)_{TW} = (V_2 - V_1) I_2 = V_1 (I_1 - I_2)$$

$$= V_1 I_1 - V_1 I_2 = V_1 I_1 \left[1 - \frac{1}{k} \right]$$

$$(VA)_{TW} = \left[\frac{k - 1}{k} \right] (VA)_{AT}$$

$$VA_{(AT)} = \left[\frac{k}{k - 1} \right] (VA)_{TW} = \left[\frac{1}{1 - 1/k} \right] (VA)_{TW}$$


As $k > 1$, $\left[1 - 1/k \right]$ is less than one

$$VA_{AT} > (VA)_{TW}$$



[Induction & conductor]

Conversion of two way tr to Auto tr


two way tr

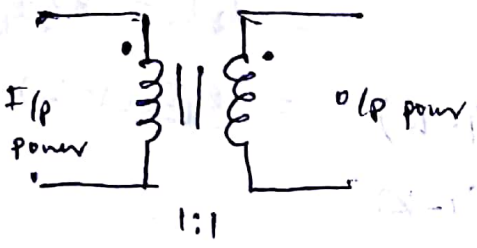

Additive polarity connecting

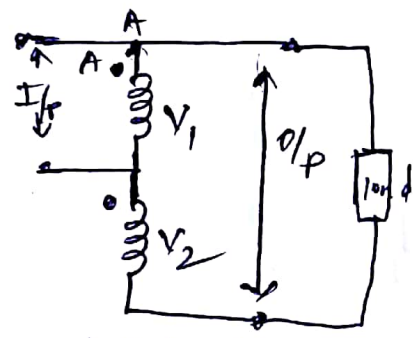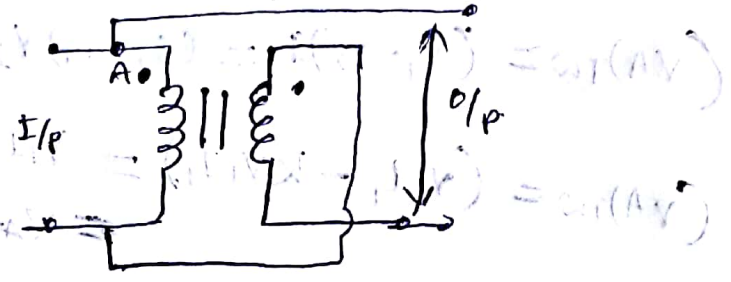

Auto transformer

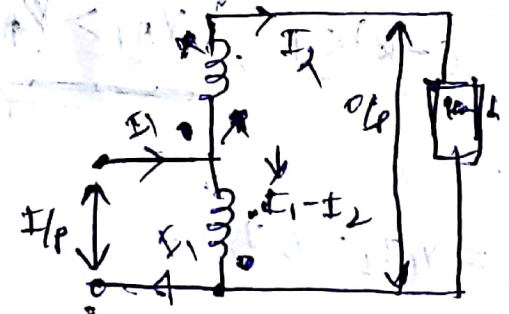

Step up auto tr

[don't discuss]


Same

Same

$V_1 \ 1/p$

$V_1 + V_2 \ (o/p) \rightarrow$

Subtractive polarity connection

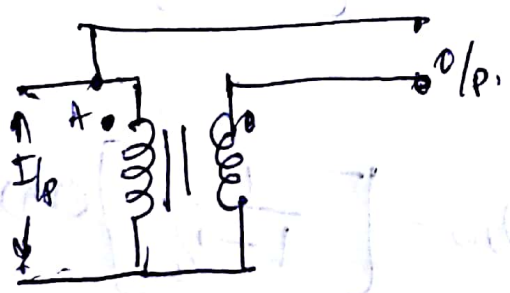

Advantages of AutoTr

μ less is less, $I^2R \downarrow$, $\eta \uparrow$ (Higher), $V_{AT} > V_{TW}$, R & X is less (voltage Regn is Superior), Smooth & continuous variation of voltage

Let other think abt you if you think

Limitation of AutoTr

(2 Closs), $I_{sc} \uparrow$ Short ckt on secondary).

- Section to primary & secondary opened full vty appear across secondary and danger of accidents.
- No electrical separation risky in high vty levels.
- Economical only when vty Ratio. than 2

Application

- ① As a starter [like Induction, synchronous m/c]
- ② As a booster.
- ③ As a furnace transformer [at eq^r supply]
- ④ for Interconnecting systems which are operated roughly at same voltage.
- ⑤ used as variac [device giving smooth & continuously]
- ⑥ Dimmstat. [Cinema Hall] ⑦ In control system as well as Appliances.

Tell them to see


Comparison with Two wdg Tr

<u>Two wdg</u>	<u>AutoTr</u>	<u>Two wdg</u>	<u>AutoTr</u>
1) Two	1) one	5) size & Cost is high	5) less
2) electric isolation	2) no electric isolation	6) vty Regn is poor	6) Superior
3) μ more	3) μ less	7) R & X are more	7) R & X are less
4) η less	4) η high	8) μ losses are more	8) μ losses are less

Equivalent Circuit of Autotr

- | | |
|---------------------------------|------------------------------------|
| 9) power transfer by induction | 9) By induction as well as conduct |
| 10) variable (cannot) | 10) variable |
| 11) KVA rating is less (autotr) | 11) KVA is more than (2 way) |

Equivalent Circuit of tr

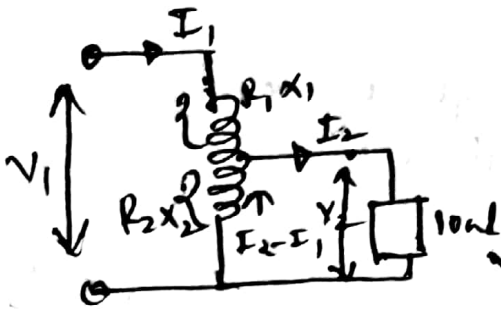

$$V_1 = E_1 + I_1(R_1 + jX_1) - (I_2 - I_1)(R_2 + jX_2) \quad \text{--- (a)}$$

$$E_2 = V_2 + (I_2 - I_1)(R_2 + jX_2) \quad \text{--- (b)}$$

$$E_2 = E_1/k$$

$$V_1 = \frac{V_2}{k} + (I_2 - I_1)(R_2 + jX_2) + I_1(R_1 + jX_1)$$

$$+ I_1(R_2 + jX_2) - \frac{I_1}{k}(R_2 + jX_2)$$

$$V_1 = \frac{V_2}{k} + I_1(R_2 + jX_2) - I_1 k (R_2 + jX_2) + I_1(R_1 + jX_1)k + I_1(R_2 + jX_2)k - I_1(R_2 + jX_2)k$$

k^2

$$= \frac{V_2}{k} + \frac{I_1}{k^2}(R_2 + jX_2) - \frac{I_1}{k}R_2 - \frac{I_1}{k}jX_2 + I_1R_1 + I_1jX_1$$

$$+ I_1R_2 + jX_2 I_1 - \frac{I_1}{k}R_2 - \frac{jX_2 I_1}{k}$$

$$= \frac{V_2}{k} + I_1 \left[R_1 + R_2 \left[\frac{1}{k^2} - \frac{2}{k} + 1 \right] + j \left[X_1 + X_2 \left(\frac{1}{k^2} - \frac{2}{k} + 1 \right) \right] \right]$$


$$V_1 = \frac{V_2}{k} + I_1 \left[R_1 + R_2 \left(\frac{1}{k} - 1 \right)^2 + j \left[X_1 + X_2 \left(\frac{1}{k} - 1 \right)^2 \right] \right]$$

$$V_1 = V_2' + I_1 R_{ie} + I_1 j X_{ie} \quad \text{--- (3)}$$

$$R_{ie} = R_1 + R_2 \left[\frac{1}{k} - 1 \right]^2$$


= Equivalent resistance
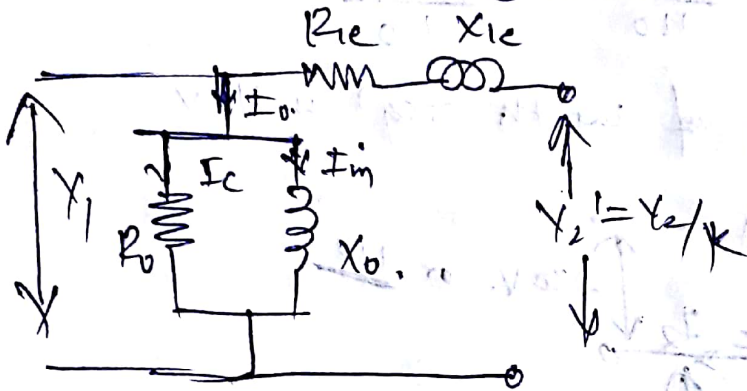
$$X_{ie} = X_1 + X_2 \left(\frac{1}{k} - 1 \right)^2 = \text{Eqm Inductance ref to pms}$$



Wed
4, 12, 14, 43,

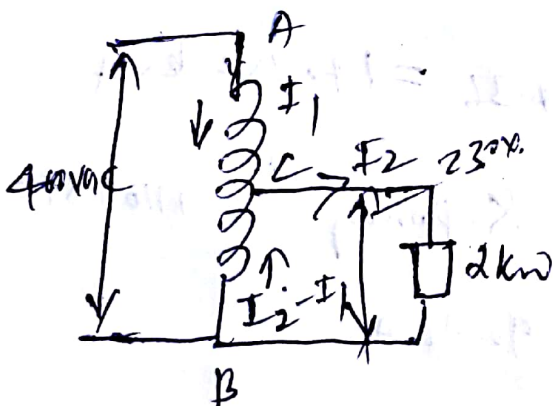* The fig shows an Autotfr used to supply a load of 2kw at 230V from a 400V AC supply. Find chs in parts AC & BC, neglecting losses and no load ch. Also find cu saving due to use of autotfr instead of using two wdg ftr. Assume purely Resistive load.



$$P = V_2 I_2 = 2 \times 10^3$$

$$I_2 = \frac{2 \times 10^3}{230} = 8.69 \text{ A}$$

$$k = \frac{V_2}{V_1} = \frac{230}{400} = 0.575 = I_1 / I_2$$

$$I_1 = k I_2 = 5 \text{ A} = AC \parallel$$

$$BC = I_2 - I_1 = 8.69 - 5 = 3.69 \text{ A}$$

$$\text{Cu saving} \equiv \text{KW TW} = 0.575 \times \text{KW TW} = 57.5\%$$


* A 10kVA, 230/110V. thr is to be used as an autothr
 what will be voltage ratio & o/p rating of autothr.

Soln:- two wdg thr = 230/110V
 kVA = 10kVA.

$$\therefore C_{in} \text{ in } 230V \text{ wdg} = \frac{VA \text{ Rating}}{230} = \frac{10 \times 10^3}{230} = 43.478 \text{ A}$$

$$C_{in} \text{ in } 110V \text{ wdg} = \frac{VA \text{ Rating}}{110} = \frac{10 \times 10^3}{110} = 90.90 \text{ A.}$$

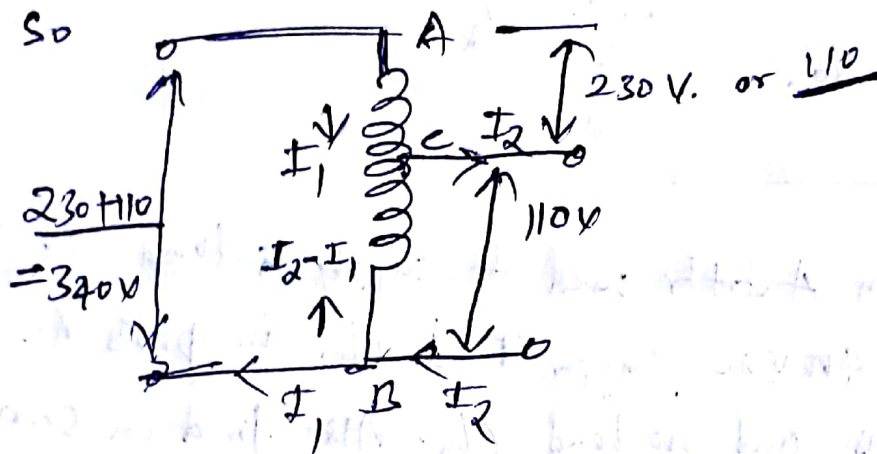let us assume o/p vty of auto thr sec^r is 110V



$$K = \frac{V_2}{V_1} = \frac{110}{340} = 0.323 = \frac{I_1}{I_2} \Rightarrow I_2 = \frac{43.47}{0.323}$$

$$I_2 = 134.36 \text{ A}$$


$$\text{o/p rating} = V_2 I_2 = 110 \times 134.36 = 14.782 \text{ kVA}$$

Note:- Take secondary as 230 & primary 230 + 110 = 340

$$K = \frac{V_2}{V_1} = \frac{230}{340} = 0.676, \quad I_1 = 90.90 \text{ A.}$$

$$\frac{I_1}{K} = I_2 \Rightarrow 133.04 \Rightarrow V_2 I_2 = \underline{\underline{30.600 \text{ kVA}}}$$

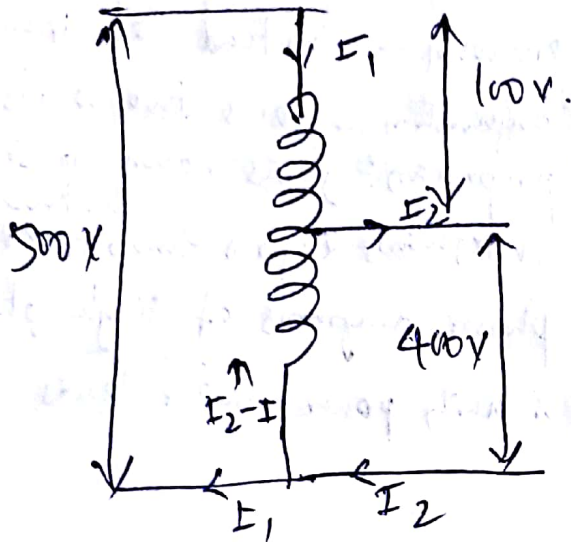* A 400/100V, 10 kVA, 2 wdg transformer is to be employed as an autotransformer to supply a 400V circuit from 500V source. When tested as a 2 wdg transformer at rated load of 0.85 pf lagging, its η is 97%. Determine its kVA & η as autotransformer (0.8).



Two wdg

$$\% \eta = \frac{\text{KVA} \times \cos \phi}{\text{KVA} + P_i + P_m}$$

$$0.97 = \frac{10 \times 10^3 \times 0.85}{10 \times 10^3 \times 0.85 + P_i + P_m}$$

$$\left(8500 \times 0.97 + 0.97 (P_i + P_m) \right) = 10 \times 10^3 \times 0.85$$

$$P_i + P_m (FL) = 262.886 \text{ W}$$

$$\eta_{AT} = \frac{\text{VA} \cos \phi}{\text{VA} \cos \phi + P_i + P_m (FL)} \times 100$$

$$I_1 = \frac{\text{VA rating}}{100 \text{ V}} = \frac{10 \times 10^3}{100} = 100 \text{ A}$$

New kVA Rating of auto H

$$= \frac{V_1 I_1}{100} = \frac{500 \times 100}{100} = 50 \text{ kVA}$$

$$\therefore \eta_{AT} = \frac{50 \times 10^3 \times 0.8}{50 \times 10^3 \times 0.85 + 262.886} \times 100 = 99.9\%$$

Indian Standard 7500V

Tap Changing Transformer

How much


Power system networks using

The Transformation Ratio


the voltage can be varied

The Tappings are provided on windings as lead to


provide different vtg. (1)

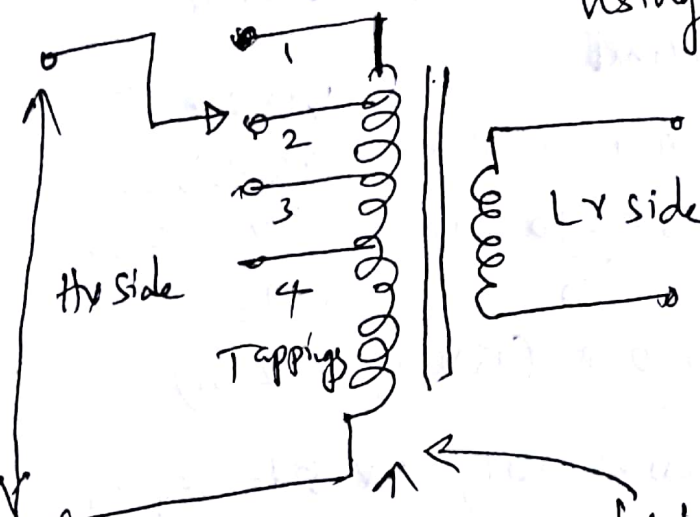

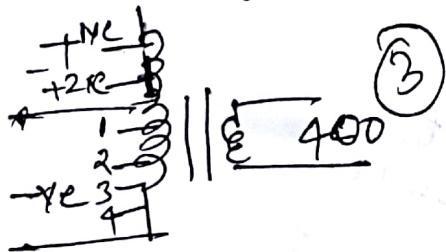The Tappings can be on high voltage, low voltage or both. (2)



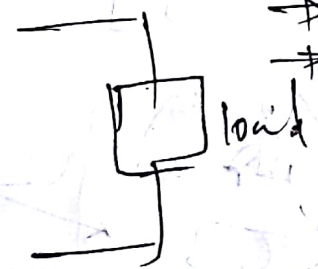- Constant voltage at consumer
- Control active power & Reactive power (4)



locating of Tappings at phase end, neutral point



Why tapings are on HV side

Plan each work

- 1) Fine voltage Regulation possible with high voltage wdg as it carries large no of turns
- 2) cannot interrupt high current (difficulties) (beoz tapping)
- 3) easier & simpler to provide tapings (HV). (LV near core)
- 4) At light load, on LV side voltage increases, it is req^d to decrease the vty by adjusting tapping in HV side (large no of turns). $\phi \& B_m \downarrow$ core loss \downarrow $\eta \uparrow$.
- 5) If tapings are provided on LV side then the exact vty Regulation may not be provided.

3 ϕ , 11 kV/415V, delta/star, $E_t = 15V$


$$\frac{415}{\sqrt{3}} = 240V, \text{ no of turns} = \frac{240}{15} = 16,$$

- 1, 12, 24, 26, 30, 31, 33, 43, 45, 46, 52, 53, 1/16 \neq

minimum no of tapping is one. (15V or 6.28%)


if 5% is desired it is not possible with LV side tapping

Off Circuit Tap changing

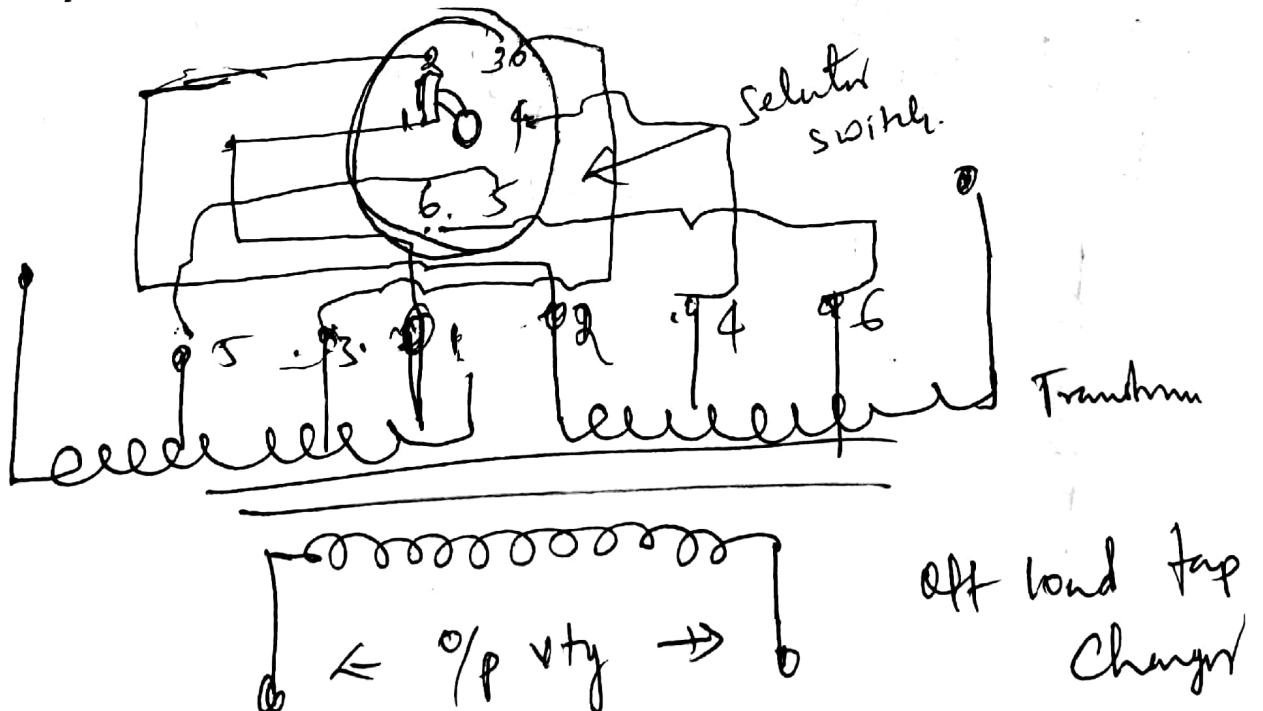

- Tappings are changed when tr is disconnected from supply
- As per requirement tappings are taken out
- manually operated selector switches are provided (vertical tapping switches & free plate switches).
- $\pm 5\%$ change in steps
- Insulating base on which six brass or Cu terminals are mounted. tap changer
- Taps of wdg are connected to terminals of ~~switch~~ tap changer
- Contacts mounted on shaft
- ex Selector switch (tap 1 & 2) (total used)
- Contact moved one point left (1 & 6) (Cutting (2 & 6))
- (6 & 5) [Cutting (1 to 5) & (2 to 4)]

on load tap changing

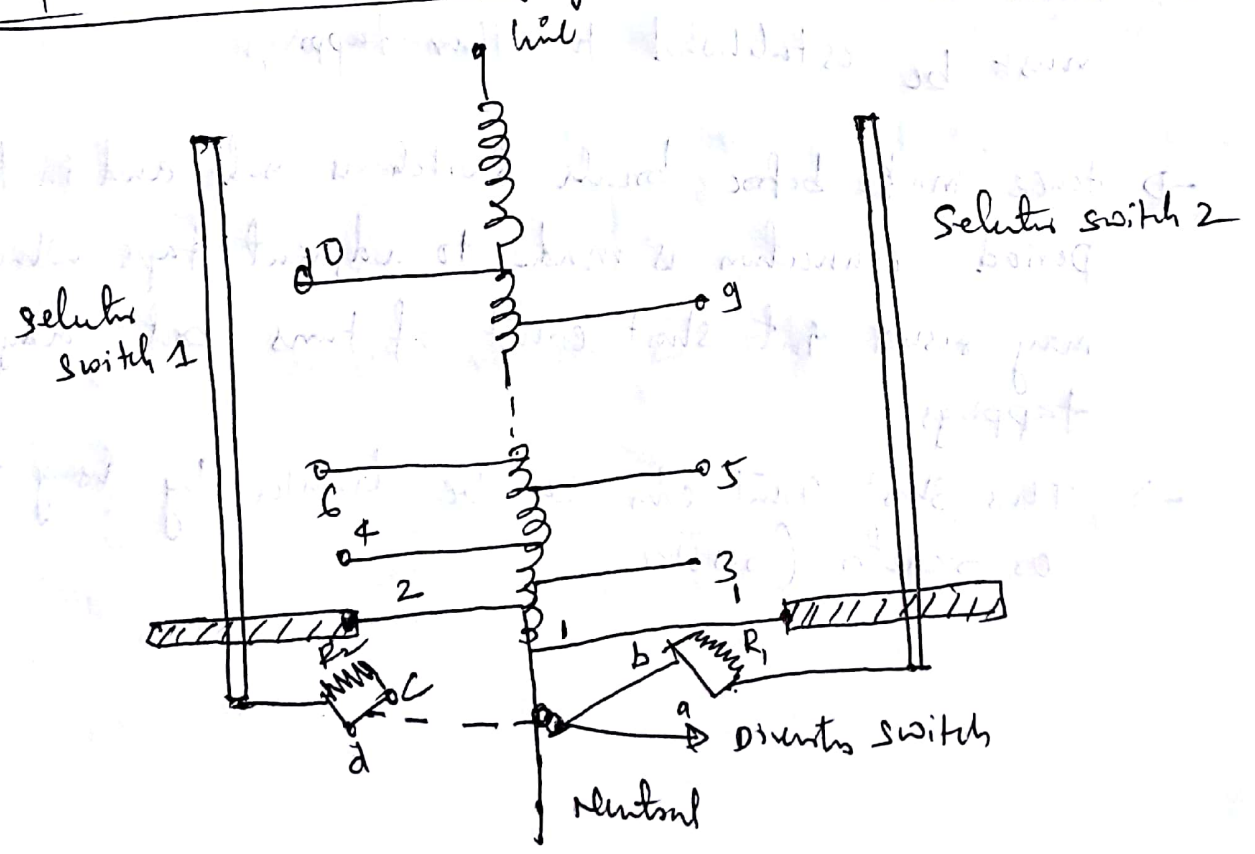

- load condⁿ have to maintain vtg on secondary side with
 → an arrangement.
- If this works without off load off it is called OLTC
- without intumptions in supply, tap changing gear
 Should change turns Ratio.
- neutral end of HV (Tapping on winding)
- Tap changer is in form of selector switch.
 (motor, operated mechanism, remote control or manual)
- vital factor is continuity of circuit.
- As selector switch should not break ch, Additional
 Separate oil filled compartment is used to mount
 disconnector switch. which breaks the load ch by
 Interrupted arc which can form carbon.
- main consideration when one tapping is opened, contact
 must be established to other tappings
- Hence make before break switch is used and in transition
 period connection is made to adjacent taps which
 may result into short circuit of turns bet^w adjacent
 tappings.
- This short circuit ch can be limited by using resistor
 or reactor (resistor)

→ Selector switch 1 & 2 are provided on taps 1 & 2 respectively. Page
 → Director switch is connecting tap 1 to neutral terminals of wdg.

If we want to change tap from position 1 & 2 then following is sequence of operations

i) Resistance R_1 is short circuited as a & b are closed. The load ch. flows through contact 'a' from tap

This is running position at tap 1.

ii) With help of external operating mechanism, director switch is moved to open the contact 'a'. Load ch. flows through R_1 resistance & contact b.

iii) The contact 'c' closes to open R_1 when moving contact of director switch continues movement to left. The R_1 & R_2 are now connected across tap 1 & 2 so that load ch. flows through these resistances to mid point of b & c.

iv) With further movement of DS to left makes contact b open. Now load ch. flows from tap 2 through R_2 & c.

v) The load ch. flows from tap 2 through d which is running position of tap 2.

* The primary & secondary vltage of auto transformer are 230V & 75V respectively. Calculate the ch. in different parts of winding when load ch. is 200A. Calculate Cu saving.

65, 134.7, 32.8%

(2) || 111
 2, 6, 30, 33, 41, 43, 47, 48, 49, 51, 54, 55