








SECOND INTERNAL ASSESSMENT

Sem: III EC
 Date: 17/10/2018

Subject: Network Analysis
 Time: 11a.m-12 noon

Sub. Code: 17EC35
 Max. Marks: 30


Note: Answer two full questions..

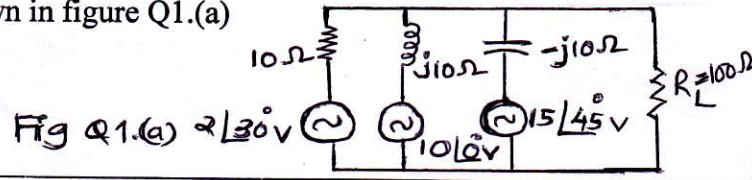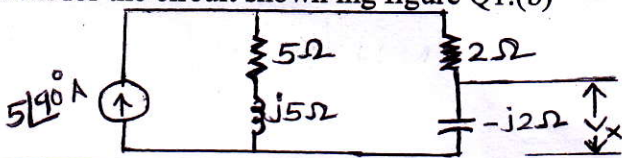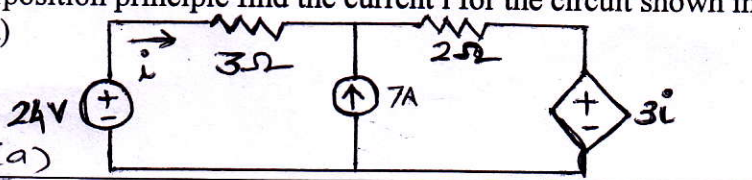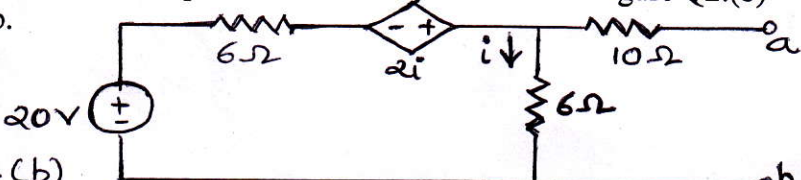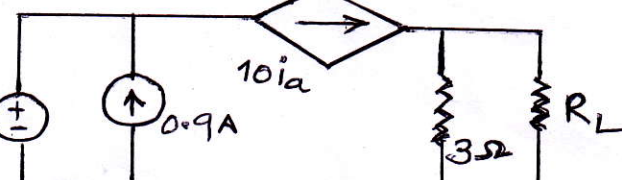
| Q. No | Description of Questions | Marks | CO | RBT Level |
|-----------|--|-------|--------|-----------|
| 1 | a Using Millimans theorem find the current through load resistance R_L for the circuit shown in figure Q1.(a)  Fig Q1.(a) $2/30^\circ V$ 10Ω $j10 \Omega$ 10Ω $-j10 \Omega$ $R_L = 100 \Omega$ $15/45^\circ V$ | 7 | C205.2 | L4 |
| | b State Reciprocity theorem. Verfiy Reciprocity theorem for the circuit shown ing figure Q1.(b)  Fig Q1.(b) $5/90^\circ A$ 5Ω $j5 \Omega$ 2Ω $-j2 \Omega$ | 8 | C205.2 | L4 |
| OR | | | | |
| 2 | a Using Superposition principle find the current i for the circuit shown in figure.Q2.(a)  Fig Q2.(a) $24V$ 3Ω $7A$ 2Ω $3i$ | 8 | C205.2 | L4 |
| | b Obtain the Thevenin equivalent of the circuit shown in figure Q2.(b) w.r.t a-b.  Fig Q2.(b) $20V$ 6Ω $2i$ 6Ω 10Ω | 7 | C205.2 | L4 |
| 3 | a Find the value of R_L for maximum power transfer for the network shown in figure Q3.(a)  Fig Q3.(a) $16V$ $0.9A$ $10i_a$ 3Ω R_L | 8 | C205.2 | L4 |
| | b State Maximum power transfer theorem & also prove that $P_{max} = V_{th}^2/4R_L$, where V_{th} is Thevenins voltage. | 7 | C205.2 | L4 |

OR

Please Turn Overleaf

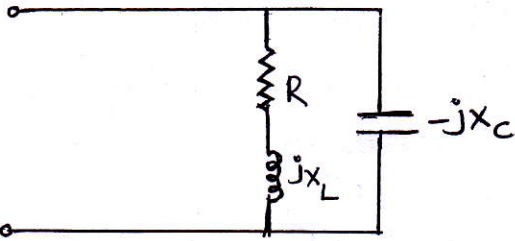

| | | | | | | |
|---|---|---|---|---|--------|----|
| 4 | a | Define Resonance. Obtain the expression for the resonant frequency for the circuit shown in figure Q4.(a) |  | 8 | C205.4 | L4 |
| | b | A series RLC circuit has $R=4\Omega$, $L=1\text{mH}$, $C=10\mu\text{F}$. Calculate resonant frequency, Q factor, half power frequencies & B.W. | | | | |


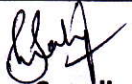


Course Coordinator
Prof. S.S. Malaj


Module Coordinator
Prof. M.M. Gadag


HOD
Dr. V.G. Kasabegoudar

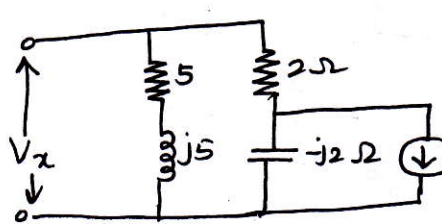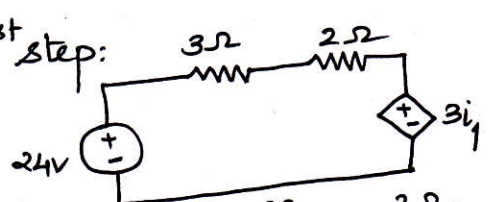

IA - 2 SCHEME OF EVALUATION

| Sem : III rd | Subject : Network Analysis | Sub Code : 17EC35 | Date : 17/10/2018 |
|-------------------------|----------------------------|--|----------------------------|
| Q. No. | Bit | Description | Marks CO's RBT LEVEL |
| 1 | a) | $E = \frac{E_1 Y_1 + E_2 Y_2 + E_3 Y_3}{Y_1 + Y_2 + Y_3} = \frac{2 \angle 30^\circ \times \frac{1}{10} + 10 \angle 0^\circ \times \frac{1}{j10} + 15 \angle 45^\circ \times \frac{1}{-j10}}{\frac{1}{10} + \frac{1}{j10} + \frac{1}{-j10}}$ $E = 9.01 \angle 169.77^\circ$ $I_L = \frac{9.01 \angle 169.77^\circ}{10 + 100 \angle 0}$ $I_L = \frac{9.01 \angle 169.77^\circ}{10 + 100 \angle 0} = 0.082 \angle 169.77^\circ \text{ A}$ | 7 C205. 2 L4 |
| | b) | <p>Using current division principle</p> $I_2 = 5 \angle 90^\circ \times \frac{5 + j5}{7 + j3} = 9.29 \angle 27.8^\circ \text{ A}$ $V_x = I_2 (-j2) = 9.284 \angle 21.8^\circ \text{ V}$ <p>Interchange the positions of $5 \angle 90^\circ \text{ A}$ & V_x in the circuit as</p>  $I_1 = 5 \angle 90^\circ \times \frac{-j2}{7 + j3} = -1.72 + 4.31j$ $V_x = (5 + j5) I_1$ $V_x = 9.284 \angle 21.8^\circ \text{ V}$ | 4+4 C205. 2 L4 |
| 2 | a) | <p>1st step:</p>  $5i_1 + 3i_1 - 24 = 0$ $i_1 = \frac{24}{8} = 3 \text{ A}$ <p>2nd step:</p>  <p>KCL at node 1</p> $i_2 + 7 = \frac{V_1 - 3i_2}{2}$ $V_1 = -3i_2 \quad i_2 = -\frac{7}{4} \text{ A}$ | 4+4 C205. 2 L4 |

Staff-In-Charge

Module Coordinator

HOD

IA - SCHEME OF EVALUATION

| Sem : III EC | | Subject : Network Analysis | Sub Code : 17EC35 | Date : 17/10/2018 | | |
|--------------|-----|---|-------------------|-------------------|-----------|--|
| Q. No. | Bit | Description | Marks | CO's | RBT LEVEL | |
| 2 | b) | <p>$\therefore i = i_1 + i_2 = 3 - \frac{7}{4} = \frac{5}{4} \text{ A} = \frac{5}{4} \text{ A}$</p> <p>$V_{oc} = V_{TH} = 6i = 6 \times \frac{5}{4} = 7.5 \text{ V}$</p> <p>To find R_{TH}</p> <p>$R_{TH} = \frac{V_{oc}}{i_{sc}} = \frac{12}{\frac{120}{136}} = 13.6 \Omega$</p> | 4+3 | C205. 2 | L4 | |
| 3 | a) | <p>$V_{oc} = 3(10i_a)$</p> <p>$= 3 \times 10 \times 0.1$</p> <p>$= 3 \text{ V}$</p> <p>$i_{sc} = 1 \text{ A}$</p> <p>To find $R_{TH} = \frac{V_{oc}}{i_{sc}} = \frac{3}{1} = 3 \Omega$</p> | 4+4 | C205. 2 | L4 | |
| | b) | <p>Max power transfer theorem states that the max power delivered by a source represented by its Thevenin's eqkt ckt is attained when load R_L is equal</p> | 4+3 | C205. 2 | L4 | |

Staff-In-Charge

Module Coordinator

HOD

IA - SCHEME OF EVALUATION

| Sem : III EC | | Subject : Network Analysis | Sub Code : 17EC35 | Date : 17/10/2018 | |
|--------------|-----|--|-------------------|-------------------|-----------|
| Q. No. | Bit | Description | Marks | CO's | RBT LEVEL |
| | | <p>to R_t.</p> $P = i^2 R_L = \left[\frac{V_t}{R_t + R_L} \right]^2 R_L$ $\frac{dP}{dR_L} = V_t^2 \left[\frac{(R_t + R_L)^2 - 2R_L(R_t + R_L)}{(R_t + R_L)^4} \right] = 0$ $R_L = R_t$ $\therefore P_{max} = \frac{V_t^2 R_L}{(2R_L)^2} = \frac{V_t^2}{4R_L}$ | | | |
| 4 | a) | <p><u>Resonance</u>:- A.C ckt's made up of resistors, inductors & Capacitors are said to be resonant circuits when the current drawn from the supply is in phase with the impressed sinusoidal voltage.</p> $Y = Y_L + Y_C = \frac{R - j\omega L}{R^2 + \omega^2 L^2} + j\omega C$ $= \frac{R}{R^2 + \omega^2 L^2} + j \left(\omega C - \frac{\omega L}{R^2 + \omega^2 L^2} \right)$ <p>At resonance, imaginary part is zero.</p> $\omega_r C - \frac{\omega_r L}{R^2 + \omega_r^2 L^2} = 0 \quad \text{or} \quad \omega_r C = \frac{\omega_r L}{R^2 + \omega_r^2 L^2}$ | 3+5 | CO5 | L4 |

Staff-In-Charge

Module Coordinator

HOD

IA - SCHEME OF EVALUATION

| Sem : III EC | Subject : Network Analysis | Sub Code : 17EC35 | Date : 17/10/2018 | | |
|--------------|----------------------------|--|-------------------|----------|-----------|
| Q. No. | Bit | Description | Marks | CO's | RBT LEVEL |
| 4 | b7 | $\omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$ $f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$ $f_r = \frac{1}{2\pi\sqrt{LC}} = 1.591 \times 10^3 \text{ Hz}$ $Q = \frac{\omega_0}{B.W} \quad Q = \frac{\omega_0 L}{R} = 2.499 \times 10^3$ $B.W = f_2 - f_1 \quad f_1, f_2 = 318 \text{ Hz}$ $f_1 = \frac{1}{2\pi} \left[\frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$ $f_2 = \frac{1}{2\pi} \left[\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \right]$ $B.W = \frac{f_r}{Q} = \frac{2 \times \pi \times f_r}{Q}$ $= \frac{2 \times \pi \times 1.591 \times 10^3}{2.499}$ $B.W = 4000 \text{ Hz}$ | 2+1 +2+2 | CO5 4 | L4 |

Staff-In-Charge

Module Coordinator