



FIRST INTERNAL ASSESSMENT









Sem: III
Date: 15/09/17

Sub: Network Analysis
Time: 3:00pm-4:00pm

Sub. Code: 15EC34
Max. Marks: 25

Note: Answer two full questions, draw sketches wherever necessary.

Q. No	Description of Question	Marks	CO
1 a	Using star-delta transformation find the equivalent resistance between A & B for the network shown below (Fig.1).	6	C204.1
1 b	For the network shown below (Fig.2) find the current through resistors 6Ω & 4Ω resistors using mesh analysis?	6	C204.1
OR			
2 a	For the network shown in (Fig.3) determine voltage 'V' using source shifting & source transformation methods?	6	C204.1
2 b	Determine the loop currents i1, i2, i3, i4 in the following network (Fig.4) using mesh analysis?	6	C204.1
3 a	Reduce the Given n/w to a n/w which consists of single voltage source in series with a resistance using source transformation & source shifting methods. (Fig.5)	7	C204.1
3 b	Find the Node voltages at node 1,2 & 3 Using node voltage(Fig.6)	6	C204.1
OR			
4 a	For the network shown below (Fig.7) find the node voltages Vd & Vc using nodal analysis.	7	C204.1
4 b	Find the Node voltages at V1,V2, & V3 in given n/w (Fig.8) using nodal analysis.	6	C204.1

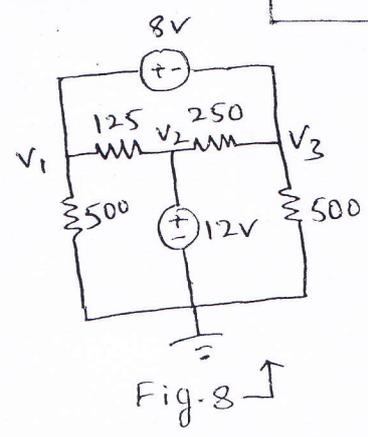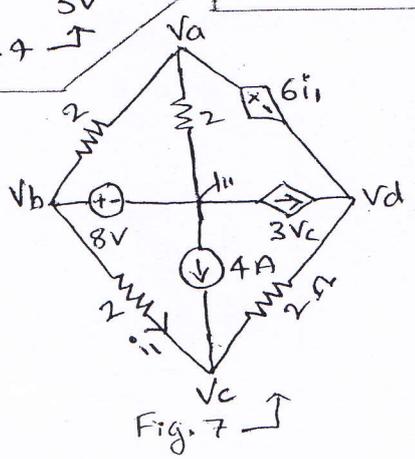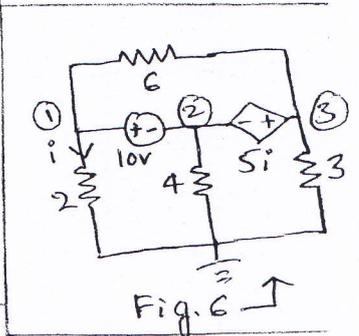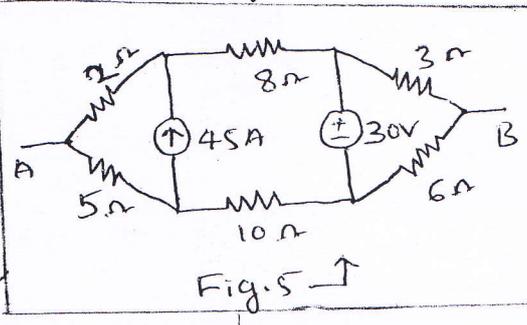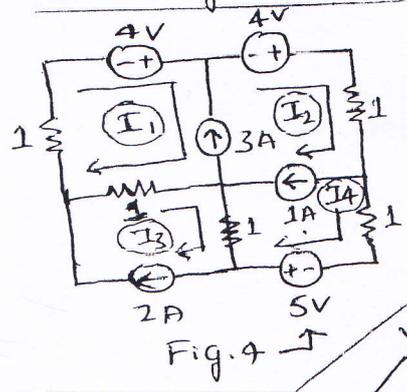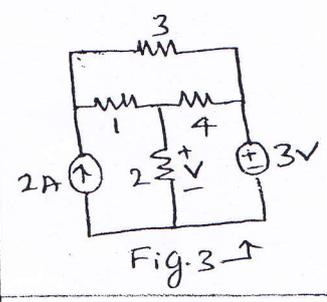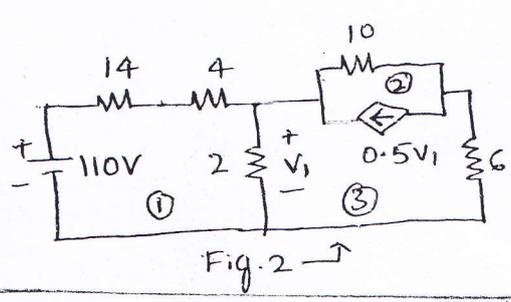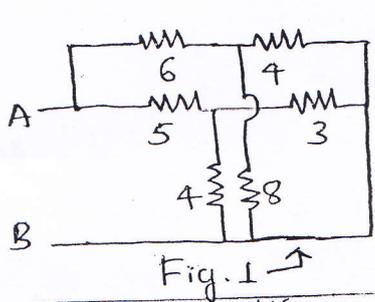



Course Coordinator

Module Coordinator

HOD



I - IA SCHEME OF EVALUATION

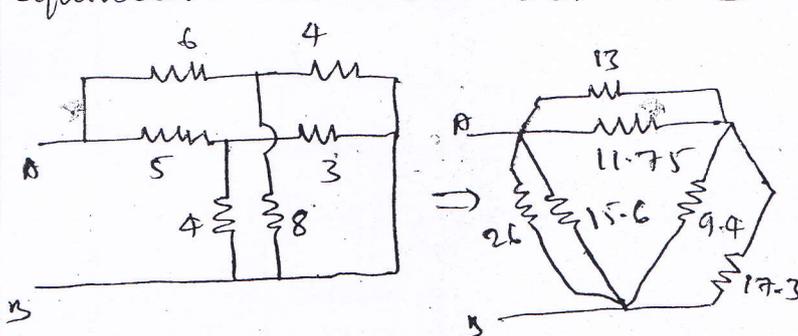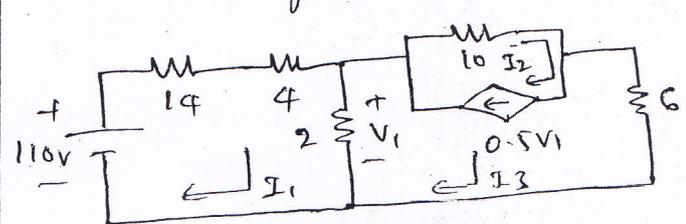Q. No.	Bit	Description	Marks	Mapped CO's
1	a	Using Star-Delta transformation find the equivalent Resistance seen A & B 	6	C204.1
		$R_{AB} = 5.43 \Omega$		
1	b)	Find the current through 6Ω & 4Ω Resistor using mesh analysis 	6	C204.1
		$20I_1 - 2I_3 = 110 \quad \text{--- (1)}$ $-2I_1 + 10I_2 + 8I_3 = 0 \quad \text{--- (2)}$ $I_1 - I_2 = 0 \quad \text{--- (3)}$ <div style="border: 1px solid black; padding: 5px; width: fit-content; margin: 10px auto;"> $I_1 = 5A$ $I_2 = 5A$ $I_3 = -5A$ </div>		



I - IA SCHEME OF EVALUATION

Sem: III		Subject: Network Analysis	Sub Code: ISEC34	Date: 15/09/17	
Q.No.	Bit	Description		Marks	Mapped CO's
2	a	Find the voltage 'V' using source shifting & source transformation. $V = 3V$		6	C204.1
2	b	Using mesh analysis find I_1, I_2, I_3 & I_4 in given network. $2I_1 + I_2 + 2I_4 = 17$ $-I_1 + I_2 + 0I_4 = 3$ $0I_1 + I_2 - I_4 = 1$ $I_1 = 2A$ $I_2 = 5A$ $I_4 = 4A$		6	C204.1

Course Coordinator

Module Coordinator

- IA SCHEME OF EVALUATION

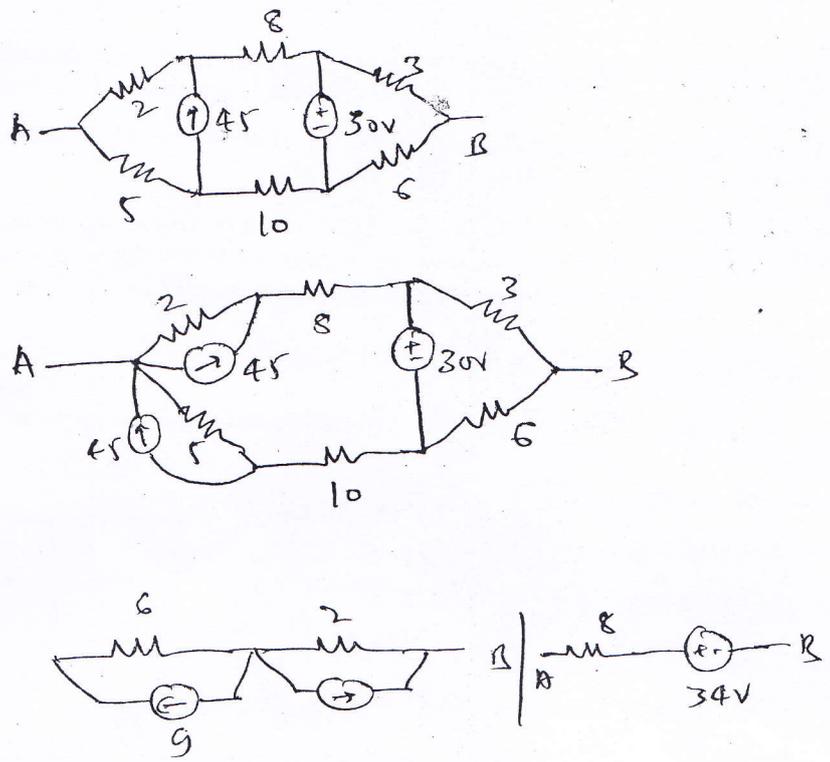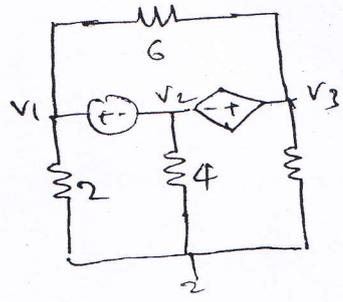Q. No.	Bit	Description	Marks	Mapped CO's
3	a	Reduce given Nlw to Nlw which consists a voltage source in series with a resistance 	7	C204.1
3	b	Find the Node voltages at 1, 2, & 3 using nodal analysis  $0.5V_1 + 0.25V_2 + 0.33V_3 = 0 \quad \text{--- (1)}$ $V_1 - V_2 = 10 \quad \text{--- (2)}$ $V_3 - V_2 = 5i \quad \text{--- (3)}$ $i = \frac{V_1}{2}$ $2.5V_1 + V_2 - V_3 = 0 \quad \text{--- (4)}$ $V_1 = 3.04V$ $V_2 = -6.9V$ $V_3 = 0.65V$	6	C204.1

SECOND INTERNAL ASSESSMENT

Sem: III
Date: 16/10/17

Sub: Network Analysis
Time: 3:00pm-4:00pm

Sub. Code: 15EC34
Max. Marks: 25

Note: Answer two full questions, draw sketches wherever necessary.

Q. No	Description of Question	Marks	CO
1	a) State & Explain Maximum power transfer theorem when load impedance consisting of variable resistance and variable reactance.	6	C204.2
	b) For the network shown in Fig.1 draw the thevenins equivalent circuit.	6	C204.2
OR			
2	a) Using Millman's theorem find I_L through R_L for the network shown in Fig.2.	6	C204.2
	b) Find the current through 16Ω resistor using Nortons theorem in Fig.3.	6	C204.2
3	a) Find the value of load resistance when maximum power is transferred across it and also find the value of maximum power transferred for the n/w in Fig.4	7	C204.2
	b) Define following terms 1.Resonance 2. Q Factor 3. Selectivity 4.Bandwidth	6	C204.3
OR			
4	a) State and Prove Reciprocity Theorem.	7	C204.2
	b) Derive Expression for Quality Factor of Series Resonant circuit.	6	C204.3

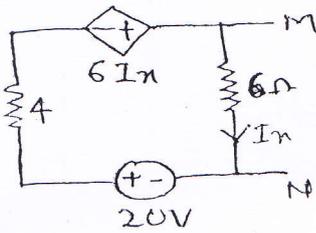


Fig. 1

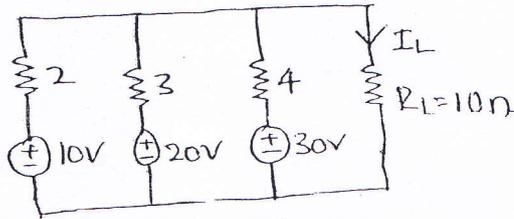


Fig. 2

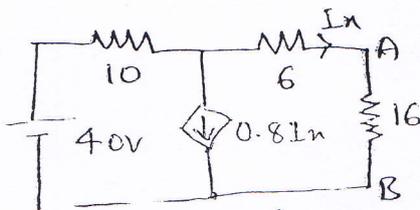


Fig. 3


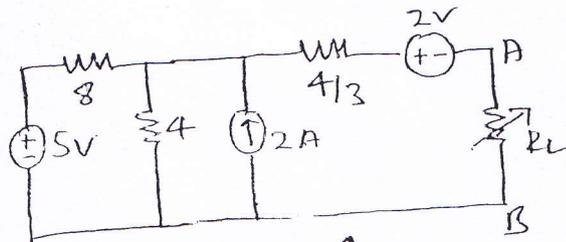
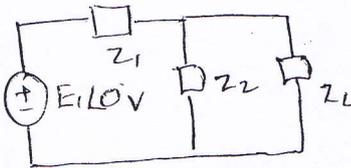
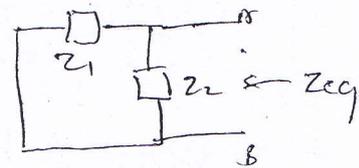
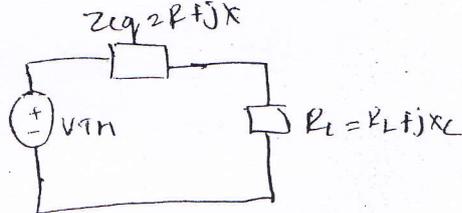


Fig. 4

HOD

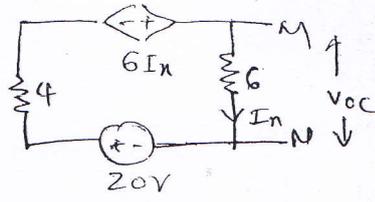

II - IA SCHEME OF EVALUATION





Q. No.	Bit	Description	Marks	Mapped CO's
Sem : <u>III</u> Subject : Network Analysis Sub Code : <u>ISEC34</u> Date : <u>16/10/17</u>				
1	a	<p>Maximum power transfer theorem when load impedance consisting of variable resistance & variable reactance</p>   <p> $Z_{eq} = R + jX$ $Z_L = R - jX$ </p>  <p> $I = \frac{V_{th}}{\sqrt{(R+R_L)^2 + (X+X_L)^2}}$ </p> <p> $X_L = -X$ $R = R_L$ </p>	6	C204-2
	b)	<p>Thevenin equivalent circuit</p>  <p> $V_{OC} = 30V$ $I_{SC} = 8A$ $R_{Th} = 6\Omega$ </p>	6	C204-2

[Signature]
 Course Coordinator

[Signature]
 Module Coordinator



II IA SCHEME OF EVALUATION

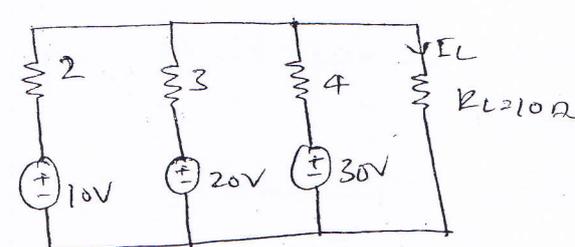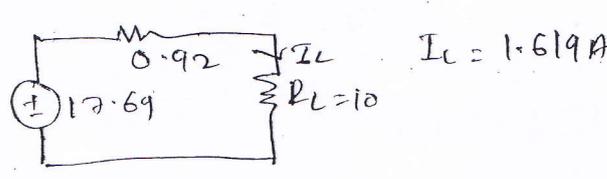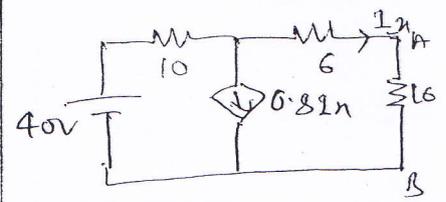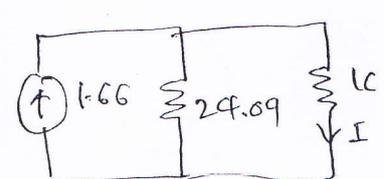Q. No.	Bit	Description	Marks	Mapped CO's
2	a	Millman's theorem to find I_L through R_L  $E = 17.68V$ $Z = 0.92V$ 	6	C204.2
2	b)	Current through 16 ohm resistor using Norton's theorem  $V_{OC} = 40V$ $I_{SC} = 1.66$ $R_{TH} = \frac{V_{OC}}{I_{SC}} = \frac{40}{1.66} = 24.09$  $I = 0.997$	6	C204.2

[Signature]

[Signature]



II - IA SCHEME OF EVALUATION


Sem :	II	Subject : NA	Sub Code : 15EC34	Date : 16/10/17
Q. No.	Bit	Description	Marks	Mapped CO's
4	a)	Derivation & Explanation for the Reciprocity theorem	7	C204.2
4)	b)	Expression for Quality Factor. ma Series resonant CRV	6	C204.3


Coordinator


Moderator



IA - IA SCHEME OF EVALUATION

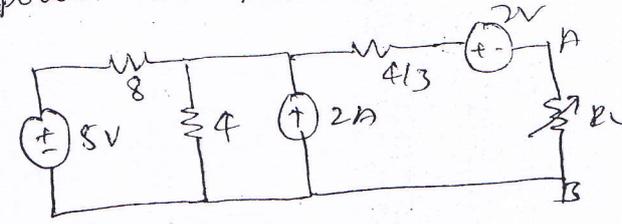Sem :	TI	Subject :	NA	Sub Code :	ISECS4	Date :	16/10/17
Q. No.	Bit	Description				Marks	Mapped CO's
3	a	Maximum value of resistance & maximum power transferred  <p> $V_{OC} = V_{TH} = 5V$ $R_{TH} = 4$ $P_{max} = 1.6W$ </p>				7	(204.2)
3	b)	Definition for the following 1) Resonance - 1.5M 3) selectivity - 1.5M 2) Q Factor - 4.5M 4) Bandwidth - 1.5M				6	(204.2)



THIRD INTERNAL ASSESSMENT

Sem: III
Date: 19/11/17

Sub: Network Analysis
Time: 3:00pm-4:00pm

Sub. Code: 15EC34
Max. Marks: 25

Note: Answer two full questions, draw sketches wherever necessary.

Q. No	Discription of Question	Marks	CO
1	a Calculate half power frequencies of series resonant circuit where the resonance frequency is 150KHz & Bandwidth is 75KHz.	7	C204.3
	b A series RLC circuit has $R=4\Omega$, $L=1mH$, & $C=10\mu F$ Calculate Q Factor, Bandwidth resonant frequencies & Half power frequencies f_1 & f_2 .	6	C204.3
OR			
2	a A 220V, 100Hz AC source supplies a series RLC ckt with a capacitor & a coil. If the coil has $50m\Omega$ resistance and $5mH$ inductance, Find the at a resonance frequency of 100Hz what is the value of capacitor. Also calculate the Q factor & half power frequencies of the ckt.	7	C204.3
	b Find the value of R_1 in the given ckt Fig.1 at resonant .	6	C204.3
3	a Obtain Relation between Y & H parameter.	6	C204.4
	b Determine Y parameter of 2 port n/w shown in Fig.2.	6	C204.4
OR			
4	a For the n/w shown below in Fig.3 Find the Z parameter.	6	C204.4
	b For the ckt shown below Fig.4 K is changed from position 1 to 2 at $t=0$ Find the values of $i, di/dt, d^2i/dt^2$ at $t=0+$	6	C204.5

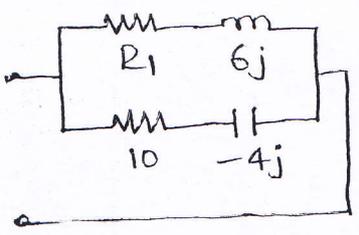


Fig.1

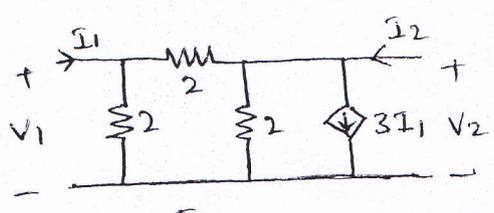


Fig. 2

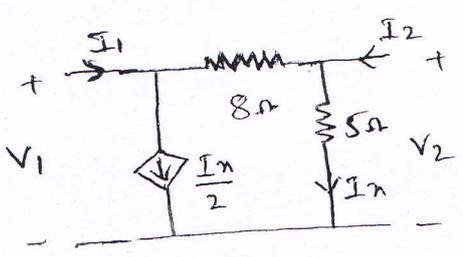


Fig. 3

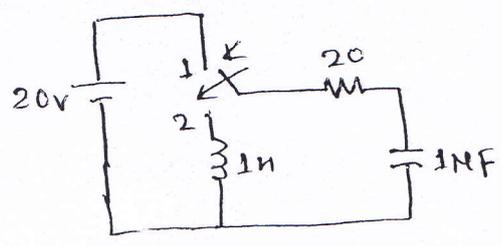


Fig. 4

[Signature]
Course Coordinator

[Signature]
Module Coordinator

[Signature]
HOD




III - IA SCHEME OF EVALUATION

Sem : II		Subject : MA	Sub Code : 15EC34	Date : 19/11/17	
Q. No.	Bit	Description	Marks	Mapped CO's	
1	a)	$f_r = 150 \text{ kHz} = \sqrt{f_1 f_2}$ $B_w = 75 \text{ kHz} = f_2 - f_1$ $f_1 f_2 = 22.5 \times 10^9$ $f_1 (75 \text{ kHz} + f_1) = 22.5 \times 10^9$ <div style="border: 1px solid black; padding: 5px; display: inline-block;"> $f_1 = 117.1 \text{ kHz}$ $f_2 = 192.16 \text{ kHz}$ </div>	7	C204-3	
1	b)	$R = 4 \text{ } \Omega, L = 1 \text{ mH}, C = 10 \text{ nF},$ $Q = \frac{1}{R} \sqrt{\frac{L}{C}} = 2.5$ <div style="border: 1px solid black; padding: 5px; display: inline-block;"> $B_w = 636.53 \text{ Hz}$ </div> $B_w = R / 2\pi L$ $f_r = \frac{1}{2\pi \sqrt{LC}} = 1.59 \text{ kHz}$ <div style="border: 1px solid black; padding: 5px; display: inline-block;"> $f_1 = 1.303 \text{ kHz}$ $f_2 = 1.940 \text{ kHz}$ </div>	6	C204-3	
2	a)	$f_0 = \frac{1}{2\pi \sqrt{LC}}, C = 0.506 \text{ nF}$ $Q = \frac{1}{R} \sqrt{\frac{L}{C}} = 62.83$ $B_w = f_2 - f_1 = \frac{R}{2\pi L} = 1.891$ $f_2 = 100.79$ $f_1 = 99.26$	7	C204-3	


 Course Coordinator


 Module Coordinator

III - IA SCHEME OF EVALUATION

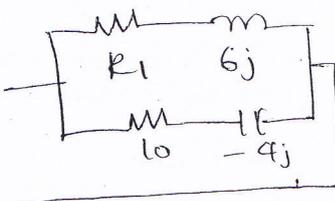Sem : III		Subject : NA	Sub Code : 15BC39	Date : 19/4/17	
Q. No.	Bit	Description	Marks	Mapped CO's	
2	b	 $Y_T = Y_L + Y_C$ $= \frac{1}{Z_L} + \frac{1}{Z_C}$ $= \frac{1}{R_1 + 6j} + \frac{1}{10 - 4j}$ $= \frac{R_1 - 6j}{R_1^2 + 36} + \frac{10 + 4j}{100 + 16}$ $= \left(\frac{R_1}{R_1^2 + 36} + \frac{10}{116} \right) + j \left(\frac{4}{116} - \frac{6}{R_1^2 + 36} \right)$ $\frac{4}{116} - \frac{6}{R_1^2 + 36} = 0$ $R_1 = 11.79 \Omega$	6	C204-3	
3	a	<p>Relation betn Y & H parameter</p> $\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} 1/h_{11} & -h_{12}/h_{11} \\ h_{21}/h_{11} & \Delta h/h_{11} \end{bmatrix}$	6	C204-4	
	b	<p>Y parameter</p> $Y_{11} = 1 \Omega, Y_{12} = -0.5 \Omega$ $Y_{21} = 2.5, Y_{22} = -0.5 \Omega$	6	C204-4	

Course Coordinator

Model Coordinator

100



III - IA SCHEME OF EVALUATION

Sem :	<u>III</u>	Subject :	NA	Sub Code :	15EC34	Date :	19/11/17
Q. No.	Bit	Description				Marks	Mapped CO's
4	a	<p>Z parameter for the circuit</p> $Z_{11} = \frac{2G}{3} = 8.66$ $Z_{12} = \frac{2}{3} = 0.66$ $Z_{21} = \frac{10}{3} = 3.33$ $Z_{22} = \frac{10}{3} = 3.33$				6	C204-f
	b	<p>$i(0^-) = i(0^+) = 1A$</p> <p>$\frac{di(t)}{dt} = -20A/sec$</p> <p>$\frac{d^2i(t)}{dt^2} = -0.99M A/sec^2$</p> <p>Steady state</p> <p>$i(0^-) = i(0^+) = 0$</p> <p>$\frac{di(t)}{dt} = -20A/sec$</p> <p>$\frac{d^2i(t)}{dt^2} = 4000A/sec^2$</p>				6	C204-f

Course Coordinator

Module Coordinator

POD