



- 3 b. Verify reciprocity theorem for the circuit shown in Fig.Q3(b). (06 Marks)

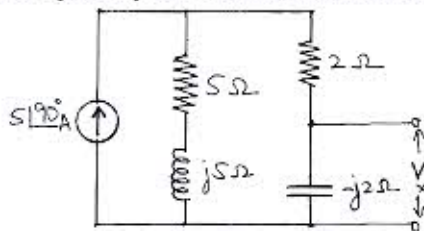


Fig.Q3(b)

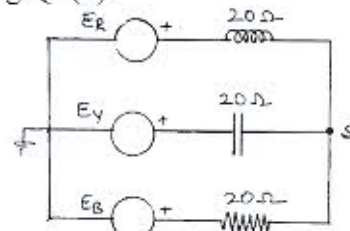


Fig.Q3(c)

- c. Use Millman's theorem to determine the voltage  $V_S$  of the network shown in Fig.Q3(c), given that  $E_R = 230 \angle 0^\circ$  V ;  $E_V = 230 \angle -120^\circ$  V and  $E_B = 230 \angle 120^\circ$  V. (06 Marks)
- 4 a. For the network shown in Fig.Q4(a), obtain the Thevenin's equivalent as seen from the terminals p and q. (08 Marks)

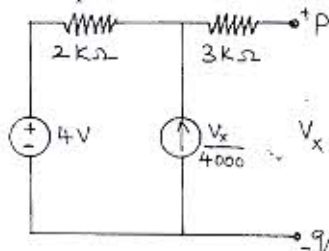


Fig.Q4(a)

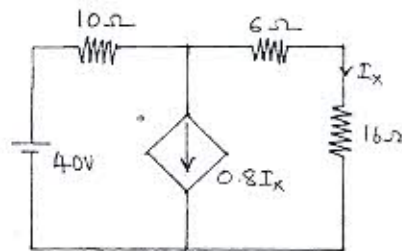


Fig.Q4(b)

- b. State Norton's theorem and find the current through  $16\Omega$  resistor using Norton's theorem in Fig.Q4(b). (06 Marks)
- c. For the network shown in Fig.Q4(c), determine the impedance  $Z_X$  such that maximum power is transferred from the source to the load of impedance  $Z_X$ .

Downloaded from [A-Z-Shiksha.com](http://www.A-Z-Shiksha.com)

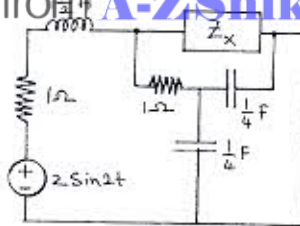


Fig.Q4(c)

(06 Marks)

### PART - B

- 5 a. Define the following terms with reference to resonant circuit:  
 i) Resonance    ii) Q-factor    iii) Selectivity    iv) Bandwidth (06 Marks)
- b. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.01\text{H}$  and  $C = 0.01\mu\text{F}$  and it is connected across 10 mV supply. Calculate: i)  $f_o$ ; ii)  $Q_o$ ; iii) Bandwidth; iv)  $f_1$  and  $f_2$ ; v)  $I_o$  (10 Marks)
- c. Determine  $R_L$  and  $R_C$  for which the circuit shown in Fig.Q5(c) resonates at all frequencies.

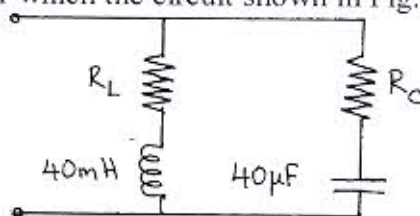


Fig.Q5(c)

(04 Marks)

- 6 a. Explain the transient behaviour of resistance, inductance and capacitance. Also explain the procedure for evaluating transient behaviour. (10 Marks)

- 6 b. In the network shown in Fig.Q6(b), 'K' is changed from position 'a' to 'b' at  $t = 0$ . Solve for  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ , if  $R = 1000 \Omega$ ,  $L = 1H$  and  $C = 0.1\mu F$  and  $V = 100V$ . Assume that the capacitor is initially uncharged. (10 Marks)

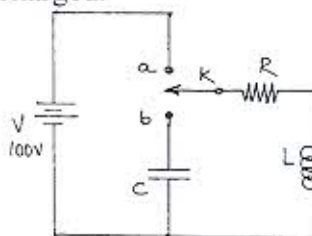


Fig.Q6(b)

- 7 a. Assuming that the staircase waveform of Fig.Q7(a) is not repeated, find its Laplace transform. If this voltage wave is applied to a RL series circuit with  $R = 1\Omega$  and  $L = 1H$ , find the current  $i(t)$ . (10 Marks)

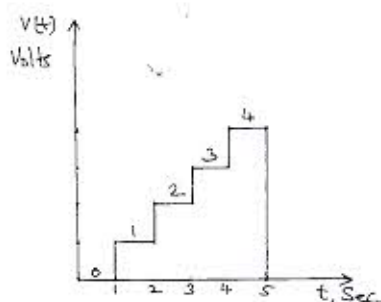


Fig.Q7(a)

- b. The network shown in Fig.Q7(b) was in steady state before  $t = 0$ . The switch is opened at  $t = 0$ . Find  $i(t)$  for  $t > 0$ , using Laplace transform. (10 Marks)

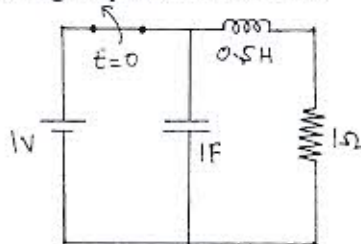


Fig.Q7(b)

- 8 a. Obtain the h-parameters for the network shown in Fig.Q8(a). (10 Marks)

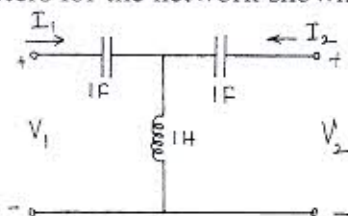


Fig.Q8(a)

- b. Obtain ABCD parameters in terms of z-parameters and hence show that  $AD - BC = 1$ . (10 Marks)

\*\*\*\*\*



**Third Semester B.E. Degree Examination, December 2012**  
**Network Analysis**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

**PART - A**

1. a. Define and distinguish the following network elements:  
 i) Linear and non-linear                      ii) Active and passive  
 iii) Lumped and distributed                      iv) Ideal and practical current sources                      (08 Marks)
- b. Write the mesh equation for the circuit shown in Fig.Q1(b) and determine mesh currents using mesh account analysis.                      (06 Marks)

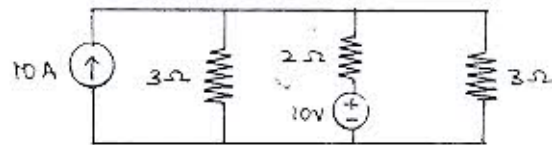


Fig.Q1(b)

- c. Reduce the network shown in Fig.Q1(c) to a single voltage source in series with a resistance using source shift and source transformations.                      (06 Marks)

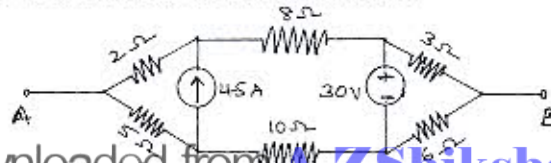


Fig.Q1(c)

Downloaded from [A-ZShiksha.com](http://A-ZShiksha.com)

2. a. Define the following terms with reference to network topology. Give examples.  
 i) Tree    ii) Graph    iii) Sub-graph    iv) Tie-set    v) Cut-set                      (10 Marks)
- b. Construct a tree for the network shown in Fig.Q2(b) so that all loop currents pass through 7Ω. Write the corresponding the set matrix.                      (06 Marks)

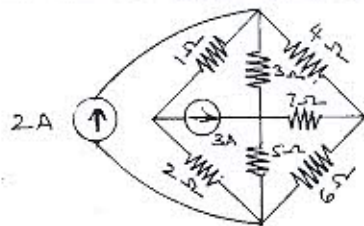


Fig.Q2(b)

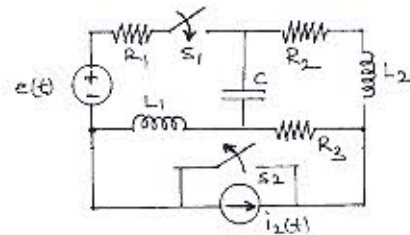


Fig.Q2(c)

- c. What are dual networks? Draw the dual of the circuit shown in Fig.Q2(c).                      (04 Marks)
3. a. Using superposition theorem, obtain the response I for the network shown in Fig.Q3(a).

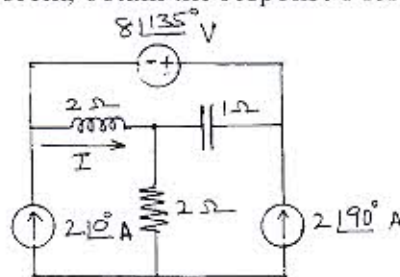


Fig.Q3(a)

(08 Marks)

- 3 b. Verify reciprocity theorem for the circuit shown in Fig.Q3(b). (06 Marks)

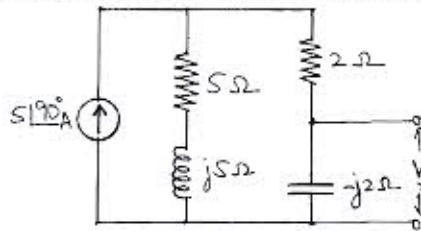


Fig.Q3(b)

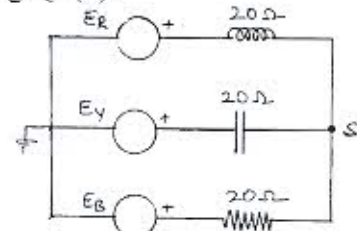


Fig.Q3(c)

- c. Use Millman's theorem to determine the voltage  $V_S$  of the network shown in Fig.Q3(c), given that  $E_R = 230 \angle 0^\circ$  V ;  $E_V = 230 \angle -120^\circ$  V and  $E_B = 230 \angle 120^\circ$  V. (06 Marks)
- 4 a. For the network shown in Fig.Q4(a), obtain the Thevenin's equivalent as seen from the terminals p and q. (08 Marks)

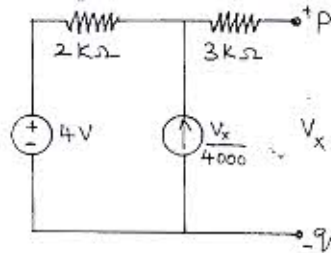


Fig.Q4(a)

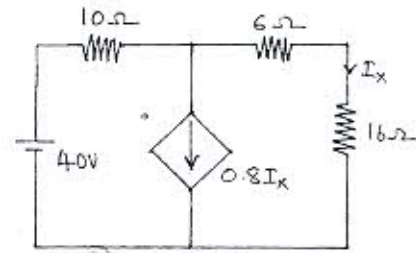


Fig.Q4(b)

- b. State Norton's theorem and find the current through 16Ω resistor using Norton's theorem in Fig.Q4(b). (06 Marks)
- c. For the network shown in Fig.Q4(c), determine the impedance  $Z_X$  such that maximum power is transferred from the source to the load of impedance  $Z_X$ .

Downloaded from [A-Z-Shiksha.com](http://www.A-Z-Shiksha.com)

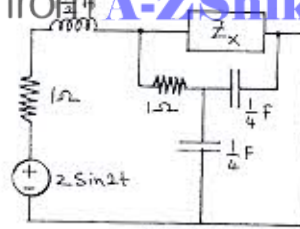


Fig.Q4(c)

(06 Marks)

**PART - B**

- 5 a. Define the following terms with reference to resonant circuit:  
 i) Resonance    ii) Q-factor    iii) Selectivity    iv) Bandwidth (06 Marks)
- b. A series RLC circuit has  $R = 10\Omega$ ,  $L = 0.01\text{H}$  and  $C = 0.01\mu\text{F}$  and it is connected across 10 mV supply. Calculate: i)  $f_o$ ; ii)  $Q_o$ ; iii) Bandwidth; iv)  $f_1$  and  $f_2$ ; v)  $I_o$  (10 Marks)
- c. Determine  $R_L$  and  $R_C$  for which the circuit shown in Fig.Q5(c) resonates at all frequencies.

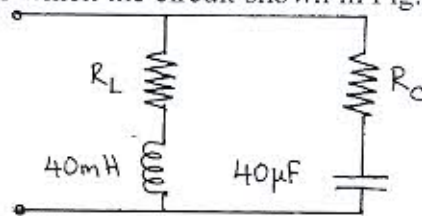


Fig.Q5(c)

(04 Marks)

- 6 a. Explain the transient behaviour of resistance, inductance and capacitance. Also explain the procedure for evaluating transient behaviour. (10 Marks)

- 6 b. In the network shown in Fig.Q6(b), 'K' is changed from position 'a' to 'b' at  $t = 0$ . Solve for  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t = 0^+$ , if  $R = 1000 \Omega$ ,  $L = 1H$  and  $C = 0.1\mu F$  and  $V = 100V$ . Assume that the capacitor is initially uncharged. (10 Marks)

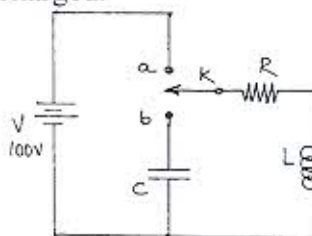


Fig.Q6(b)

- 7 a. Assuming that the staircase waveform of Fig.Q7(a) is not repeated, find its Laplace transform. If this voltage wave is applied to a RL series circuit with  $R = 1\Omega$  and  $L = 1H$ , find the current  $i(t)$ . (10 Marks)

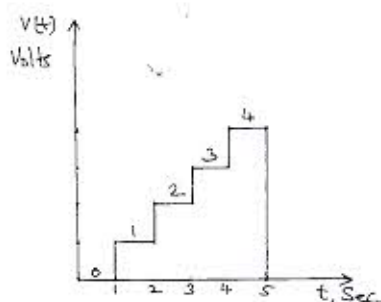


Fig.Q7(a)

- b. The network shown in Fig.Q7(b) was in steady state before  $t = 0$ . The switch is opened at  $t = 0$ . Find  $i(t)$  for  $t > 0$ , using Laplace transform. (10 Marks)

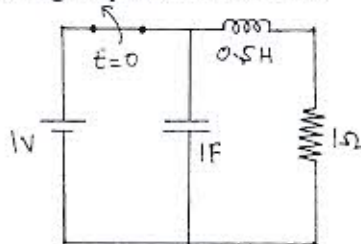


Fig.Q7(b)

- 8 a. Obtain the h-parameters for the network shown in Fig.Q8(a). (10 Marks)

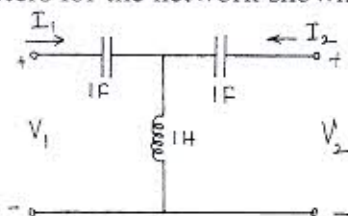


Fig.Q8(a)

- b. Obtain ABCD parameters in terms of z-parameters and hence show that  $AD - BC = 1$ . (10 Marks)

\*\*\*\*\*



--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, June 2012**  
**Network Analysis**

Time: 3 hrs.

Max. Marks:100

**Note: 1. Answer FIVE full questions, selecting atleast TWO questions from each part.**  
**2. Missing data, if any, may suitably be assumed.**

**PART - A**

- Find the equivalent resistance at AB using Y -  $\Delta$  transformation technique in Fig. Q1(a). (05 Marks)
  - Find the current I in 28  $\Omega$  resistor by Mesh analysis in Fig. Q1(b). (05 Marks)
  - Find the power dissipated in 10  $\Omega$  resistor by node voltage method in Fig. Q1(c). (10 Marks)

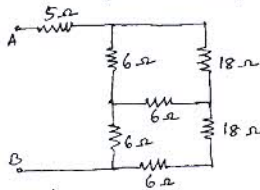


Fig. Q1(a)

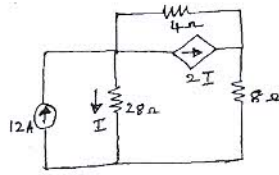


Fig. Q1(b)

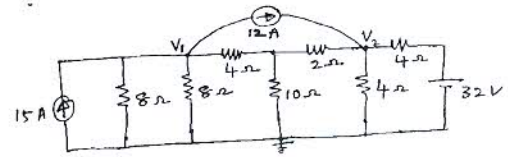


Fig. Q1(c)

- Write the oriented graph of the network shown in Fig. Q2(a). The numerical values of resistances also indicate the branch numbers. Select a tree with branches 1, 2, 3 as the tree branches with times and cites schedule. (10 Marks)
  - For the network shown in Fig. Q2(b), draw the dual network and write the node equations. (10 Marks)

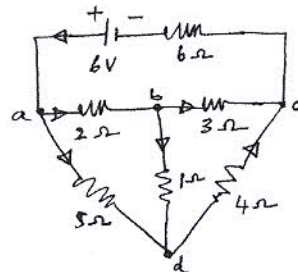


Fig. Q2(a)

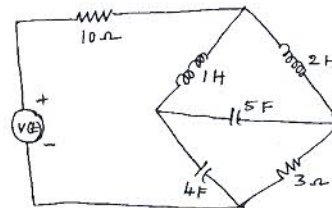


Fig. Q2(b)

- Determine the current through 10  $\Omega$  resistance of the network shown in Fig. Q3(a), using superposition theorem. (10 Marks)
  - State Milliman's theorem. Using Milliman's theorem, find  $I_L$  through  $R_L$  for the network shown in Fig. Q3(b). (10 Marks)

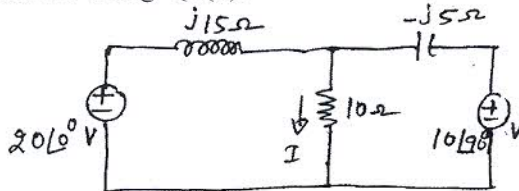


Fig. Q3(a)

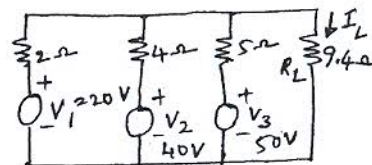


Fig. Q3(b)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

- 4 a. State Thevenin's theorem. For the circuit shown in Fig. Q4(a), find the current through  $R_L$  using Thevenin's theorem. (10 Marks)
- b. State maximum power transfer theorem. For the circuit shown in Fig. Q4(b), find the value of  $Z_L$  for which maximum power transfer occurs. Also find  $P_{max}$ . (10 Marks)

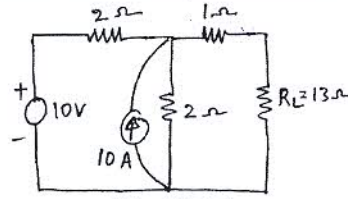


Fig. Q4(a)

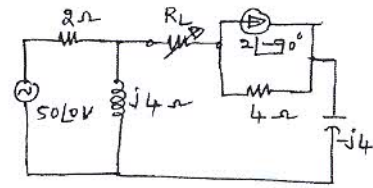


Fig. Q4(b)

PART - B

- 5 a. Define quality factor and bandwidth. Also establish the relationship between quality factor and bandwidth in a series resonance circuit and thereby prove that  $Q = \frac{f_0}{BW}$ , where  $f_0$  is the resonance frequency. (10 Marks)
- b. A series RLC circuit with  $R = 10 \Omega$ ,  $L = 10mH$  and  $C = 1\mu F$  has an applied voltage of 200 V at resonant frequency. Calculate the resonant frequency  $f_0$ , the current in the circuit at resonance, voltage across the elements at resonance. Also find quality factor and bandwidth. (10 Marks)

- 6 a. Determine  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t=0+$  when the switch is closed at  $t = 0$  in Fig. Q6(a). (10 Marks)
- b. Determine  $i$ ,  $\frac{di}{dt}$  and  $\frac{d^2i}{dt^2}$  at  $t=0+$  when the switch K is moved from position 1 to 2 at  $t = 0$  in the network shown in Fig. Q6(b), steady state having reached before switching. (10 Marks)

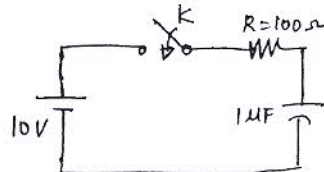


Fig. Q6(a)

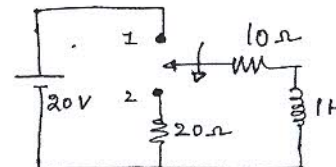


Fig. Q6(b)

- 7 a. Find the expression for the resultant current  $i(t)$  when switch K is closed at  $t = 0$  in Fig. Q7(a). (10 Marks)
- b. Find the Laplace transform of the given function  $f(t) = 5 + 4e^{-2t}$ . (04 Marks)
- c. Find the L.T of the saw tooth waveform in Fig. Q7(c). (06 Marks)

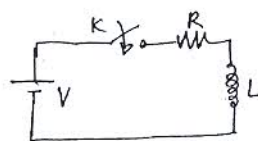


Fig. Q7(a)

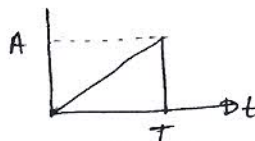


Fig. Q7(c)

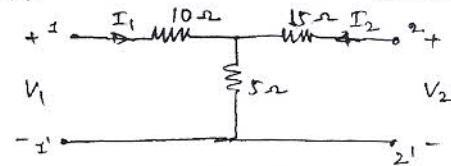


Fig. Q8(a)

- 8 a. Find the Z-parameters for the network shown in Fig. Q8(a). (10 Marks)
- b. The Z-parameters of a two port network are  $Z_{11} = 20 \Omega$ ,  $Z_{22} = 30 \Omega$ ,  $Z_{12} = Z_{21} = 10\Omega$ . Find Y and ABCD parameters of the network. (10 Marks)

\*\*\*\*\*