



S J P N Trust's

**Hirasugar Institute of Technology, Nidasoshi.**

*Inculcating Values, Promoting Prosperity*

Approved by AICTE, Recognized by Govt. of Karnataka and Affiliated to VTU Belagavi

**ECE Dept.**

**V.HDL**

**V Sem**

**2017-18**

**Department of Electronics & Communication Engg.**

**Course : Verilog HDL-15EC53.**

**Sem.: 5<sup>th</sup>**

**Course Coordinator:**

**Prof. Sachin S Patil**

# Verilog HDL -Introduction



Ref: Verilog – HDL by samir palnitkar 2<sup>nd</sup> Edition

# Module- Basic building block

```
module <module_name> (<module_terminal_list>);  
  
...  
<module internals>  
  
...  
  
...  
endmodule
```

**A module can be an element or collection of low level design blocks**


# Levels of Abstraction-1

- ❑ Switch Level: Module implemented with switches and interconnects. Lowest level of Abstraction
- ❑ Gate Level: Module implemented in terms of logic gates like (and ,or) and interconnection between gates

# Levels of Abstraction-2

- ❑ **Dataflow Level:** Module designed by specifying dataflow. The designer is aware of how data flows between hardware registers and how the data is processed in the design
- ❑ **Behavioral Level :**Module can be implemented in terms of the desired design algorithm without concern for the hardware implementation details. Very similar to C programming

# Hierrarchy

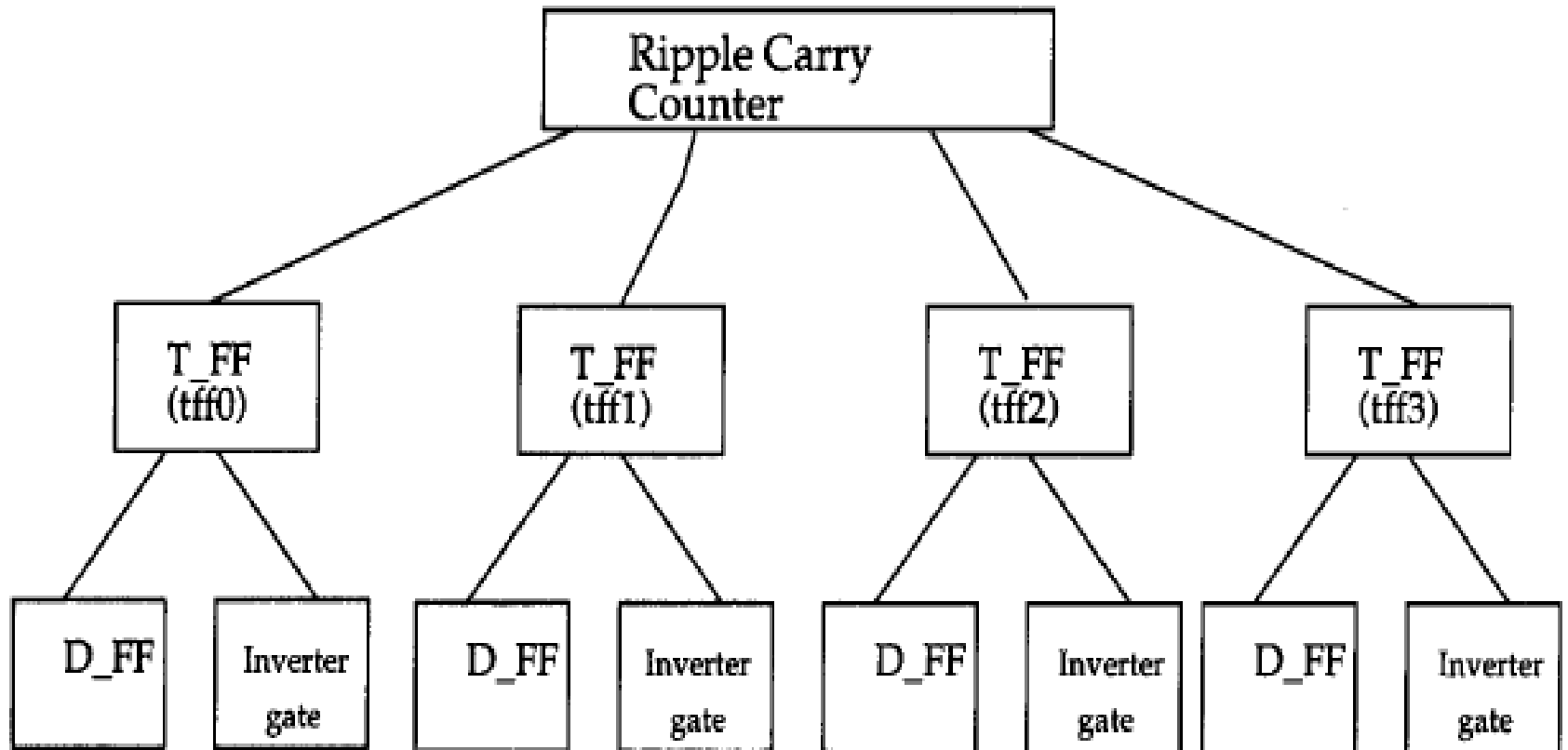

# Basic Concepts

□ Number is specified as

`<size>'<baseformat><number>`

```
4'b1111 // This is a 4-bit    binary number
12'habc  // This is a 12-bit   hexadecimal number
16'd255  // This is a 16-bit   decimal number.
```

```
23456 // This is a 32-bit    decimal number by default
'hc3  // This is a 32-bit    hexadecimal number
'o21  // This is a 32-bit    octal number
```

# Contd.

`-6'd3 // 8-bit` negative number stored as 2's complement of 3

<b>Value Level</b>	<b>Condition in Hardware Circuits</b>
0	Logic zero, false condition
1	Logic one, true condition
x	Unknown value
z	High impedance, floating state



# Nets



- Nets represent connections between hardware elements. Just as in real circuits, nets have values continuously driven on them by the outputs of devices that they are connected to.

```
wire a; // Declare net a for the above circuit  
wire b,c; // Declare two wires b,c for the above circuit
```

# Registers

- ❑ *Registers* represent data storage elements. Registers retain value until another value is placed onto them.
- ❑ In Verilog, the term *register* merely means a variable that can hold a value.
- ❑ Unlike a net, a register does not need a driver.

```
reg reset; // declare a variable reset that can hold its value
```

```
reset = 1'b1; //initialize reset to 1 to reset the digital circuit.
```

# Vectors

## □ Arrays of Regs and Nets

```
wire a; // scalar net variable, default
wire [7:0] bus; // 8-bit bus
wire [31:0] busA, busB, busC; // 3 buses of 32-bit width.
reg clock; // scalar register, default
reg [0:40] virtual_addr; // Vector register, virtual address 41 bits wide
```

# Integers and Parameters


```
integer counter; // general purpose variable used as a counter.  
initial  
    counter = -1; // A negative one is stored in the counter
```

```
parameter port_id = 5; // Defines a constant port_id  
parameter cache_line_width = 256; // Constant defines width of cache line
```
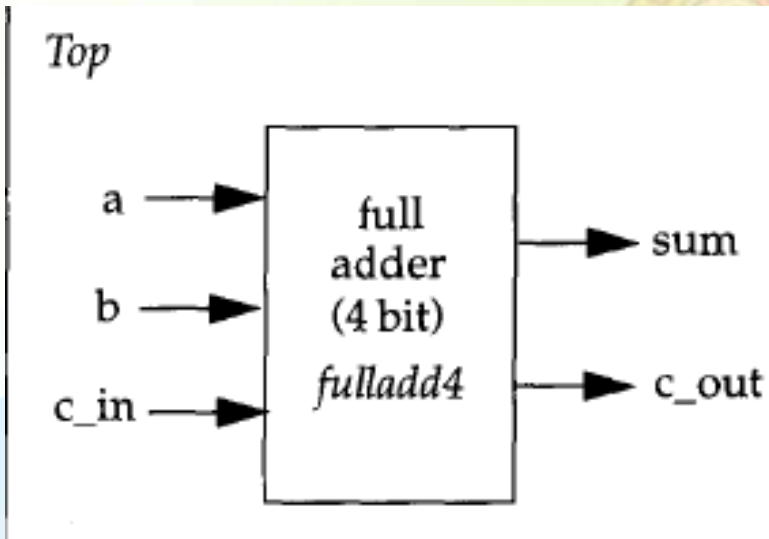
# Ports

- Ports provide interface for by which a module can communicate with its environment

```
module fulladd4(sum, c_out, a, b, c_in);
```



Verilog Keyword	Type of Port
<b>input</b>	Input port
<b>output</b>	Output port
<b>inout</b>	Bidirectional port

# Module

Module Name,  
Port List, Port Declarations (if ports present)  
Parameters(optional),

Declarations of **wires**,  
**regs** and other variables

Data flow statements  
(**assign**)


Instantiation of lower  
level modules

**always** and **initial** blocks.  
All behavioral statements  
go in these blocks.

Tasks and functions


endmodule statement

# Port connection rules

 
 
# Example

```
module DFF(q, d, clk, reset);  
output q;  
reg q; // Output port q holds value;  
input d, clk, reset;  
...  
...  
endmodule
```





# Connecting Ports

□ Suppose we have a module

```
module fulladd4(sum, c_out, a, b, c_in);
```

```
module Top;
```

```
//Declare connection variables
```

```
reg [3:0]A,B;
```

```
reg C_IN;
```

```
wire [3:0] SUM;
```

```
wire C_OUT;
```

```
//Instantiate fulladd4, call it fa_ordered.
```

```
//Signals are connected to ports in order (by position)
```

```
fulladd4 fa_ordered(SUM, C_OUT, A, B, C_IN);
```

```
fulladd4 fa0(SUM, , A, B, C_IN); // Output port c_out is unconnected
```

```
// Instantiate module fa_byname and connect signals to ports by name  
fulladd4 fa_byname(.sum(SUM), .b(B), .c_in(C_IN), .a(A),);
```

```
// Instantiate module fa_byname and connect signals to ports by name  
fulladd4 fa_byname(.c_out(C_OUT), .sum(SUM), .b(B), .c_in(C_IN),  
.a(A),);
```

# Gate Level Modeling

- ❑ A logic circuit can be designed by use of logic gates.
- ❑ Verilog supports basic logic gates as predefined *primitives*. These primitives are instantiated like modules except that they are predefined in Verilog and do not need a module definition.

`and`

`or`



`xor`

`nand`

`nor`

`xnor`

# Gate gate\_name(out,in1,in2...)

  

```
wire OUT, IN1, IN2;  
  
// basic gate instantiations.  
and a1(OUT, IN1, IN2);  
nand na1(OUT, IN1, IN2);  
or or1(OUT, IN1, IN2);  
nor nor1(OUT, IN1, IN2);  
xor x1(OUT, IN1, IN2);  
xnor nx1(OUT, IN1, IN2);
```

# Buf/not gates

- *Buf/not* gates have one scalar input and one or more scalar outputs.

```
// basic gate instantiations.
```

```
buf b1(OUT1, IN);
```

```
not n1(OUT1, IN);
```


```
// More than two outputs
```

```
buf b1_2out(OUT1, OUT2, IN);
```


```
// gate instantiation without instance name
```

```
not (OUT1, IN); // legal gate instantiation
```

# Bufif/notif

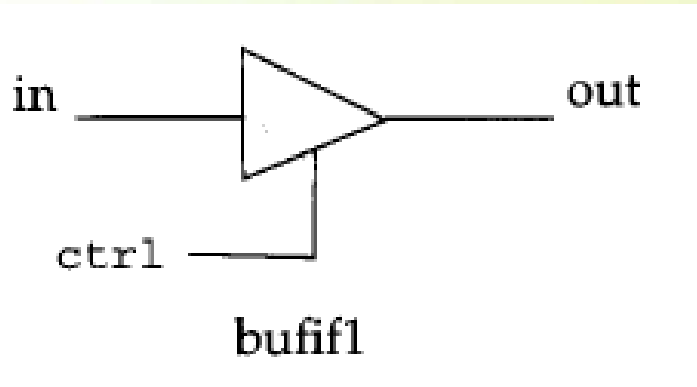

		ctrl			
		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	x	x	x

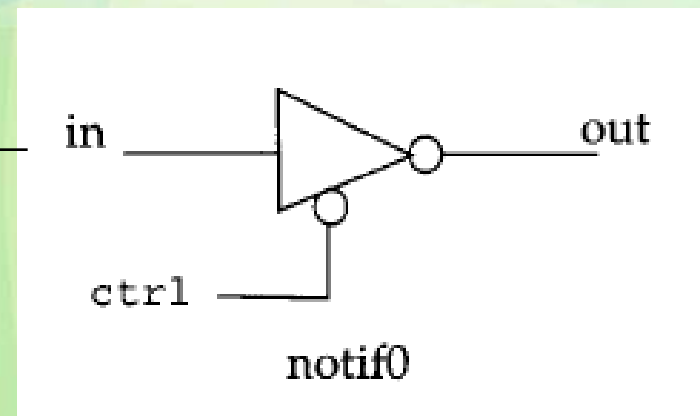


		ctrl			
		0	1	x	z
in	0	1	z	H	H
	1	0	z	L	L
	x	x	z	x	x
	z	x	z	x	x

# Instantiation of bufif gates

```
//Instantiation of bufif gates.  
bufif1 b1 (out, in, ctrl);  
bufif0 b0 (out, in, ctrl);  
  
//Instantiation of notif gates  
notif1 n1 (out, in, ctrl);  
notif0 n0 (out, in, ctrl);
```

# Design of 4:1 Multiplexer

 



# Contd..

```
// Module 4-to-1 multiplexer. Port list is taken exactly from
// the I/O diagram.
module mux4_to_1 (out, i0, i1, i2, i3, s1, s0);

// Port declarations from the I/O diagram
output out;
input i0, i1, i2, i3;
input s1, s0;
```

```
// Internal wire declarations
wire s1n, s0n;
wire y0, y1, y2, y3;

// Gate instantiations

// Create s1n and s0n signals.
not (s1n, s1);
not (s0n, s0);

// 3-input and gates instantiated
and (y0, i0, s1n, s0n);
and (y1, i1, s1n, s0);
and (y2, i2, s1, s0n);
and (y3, i3, s1, s0);

// 4-input or gate instantiated
or (out, y0, y1, y2, y3);

endmodule
```

# Stimulus

```
// Define the stimulus module (no ports)
module stimulus;

// Declare variables to be connected
// to inputs
reg IN0, IN1, IN2, IN3;
reg S1, S0;

// Declare output wire
wire OUTPUT;

// Instantiate the multiplexer
mux4_to_1 mymux(OUTPUT, IN0, IN1, IN2, IN3, S1, S0);
```

```
// Define the stimulus module (no ports)

// Stimulate the inputs
initial
begin
    // set input lines
    IN0 = 1; IN1 = 0; IN2 = 1; IN3 = 0;
    #1 $display("IN0= %b, IN1= %b, IN2= %b, IN3=
    %b\n", IN0, IN1, IN2, IN3);

    // choose IN0
    S1 = 0; S0 = 0;
    #1 $display("S1 = %b, S0 = %b, OUTPUT = %b \n", S1, S0, OUTPUT);


    // choose IN1
    S1 = 0; S0 = 1;
    #1 $display("S1 = %b, S0 = %b, OUTPUT = %b \n", S1, S0, OUTPUT);

    // choose IN2
    S1 = 1; S0 = 0;
    #1 $display("S1 = %b, S0 = %b, OUTPUT = %b \n", S1, S0, OUTPUT);

    // choose IN3
    S1 = 1; S0 = 1;
    #1 $display("S1 = %b, S0 = %b, OUTPUT = %b \n", S1, S0, OUTPUT);
end

endmodule
```

# 4 bit full adder

 

$$sum = (a \oplus b \oplus cin)$$

$$cout = (a \cdot b) + cin \cdot (a \oplus b)$$

# Declaration:

```
// Define a 1-bit full adder
module fulladd(sum, c_out, a, b, c_in);

// I/O port declarations
output sum, c_out;
input a, b, c_in;

// Internal nets
wire s1, c1, c2;
```

# Code contd..


```
// Instantiate logic gate primitives
xor (s1, a, b);
and (c1, a, b);

xor (sum, s1, c_in);
and (c2, s1, c_in);

or (c_out, c2, c1);

endmodule
```

# 4 bit adder using 1 bit adder

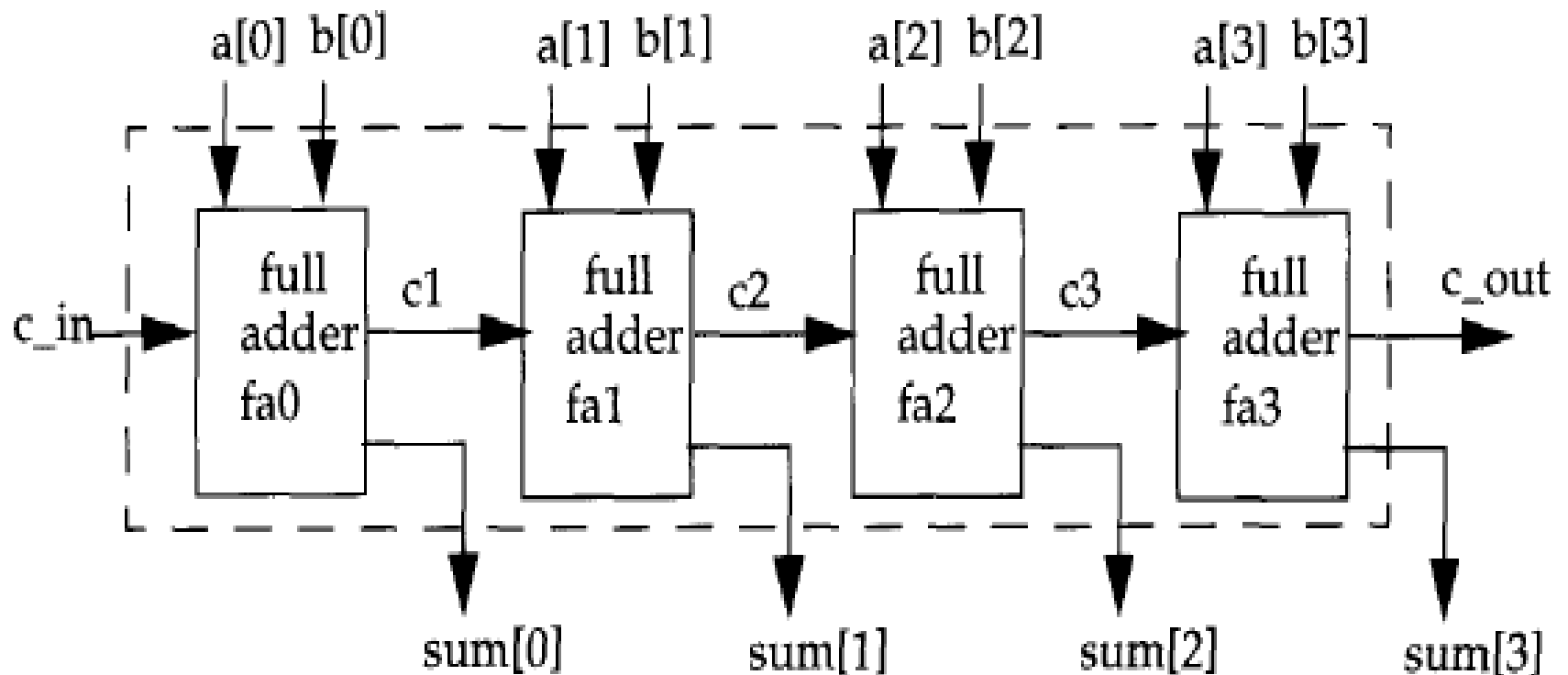



```
// Define a 4-bit full adder
module fulladd4(sum, c_out, a, b, c_in);

// I/O port declarations
output [3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;

// Internal nets
wire c1, c2, c3;

// Instantiate four 1-bit full adders.
fulladd fa0(sum[0], c1, a[0], b[0], c_in);
fulladd fa1(sum[1], c2, a[1], b[1], c1);
fulladd fa2(sum[2], c3, a[2], b[2], c2);
fulladd fa3(sum[3], c_out, a[3], b[3], c3);

endmodule
```

# Stimulus


```
// Define the stimulus (top level module)
module stimulus;

// Set up variables
reg [3:0] A, B;
reg C_IN;
wire [3:0] SUM;
wire C_OUT;

// Instantiate the 4-bit full adder. call it FA1_4
fulladd4 FA1_4(SUM, C_OUT, A, B, C_IN);
```

 
# Gate Delays:

□ Rise Delay: Delay associated with a o/p transition to 1 from any value.



Fall Delay: Delay associated with o/p transition to 0 from any value.

 
Turn off Delay: Delay associate with o/p transition to Z from another value.



$A = 1'b0$ ;  $B = 1'b0$ ;  $C = 1'b0$ ;

#10  $A = 1'b1$ ;  $B = 1'b1$ ;  $C = 1'b1$ ;
 
#10  $A = 1'b1$ ;  $B = 1'b0$ ;  $C = 1'b0$ ;



# Dataflow Modeling

- ❑ In complex designs the number of gates is very large
- ❑ Currently, automated tools are used to create a gate-level circuit from a dataflow design description. This process is called *logic synthesis*

# Continuous Assignment

```
//Syntax of assign statement in the simplest form  
<continuous_assign>  
    ::= assign <drive_strength>?<delay>? <list_of_assignments>;
```

```
// Continuous assign. out is a net. i1 and i2 are nets.  
assign out = i1 & i2;
```

```
// Continuous assign for vector nets. addr is a 16-bit vector net  
// addr1 and addr2 are 16-bit vector registers.  
assign addr[15:0] = addr1_bits[15:0] ^ addr2_bits[15:0];
```

```
// Concatenation. Left-hand side is a concatenation of a scalar  
// net and a vector net.  
assign {c_out, sum[3:0]} = a[3:0] + b[3:0] + c_in;
```


# Rules:

- The left hand side of an assignment must always be a scalar or vector net
- It cannot be a scalar or vector register.
- Continuous assignments are always active.
- The assignment expression is evaluated as soon as one of the right-hand-side operands changes and the value is assigned to the left-hand-side net.

- ❑ The operands on the right-hand side can be registers or nets.
- ❑ Delay values can be specified for assignments in terms of time units. Delay values are used to control the time when a net is assigned the evaluated value


 
```
assign #10 out = in1 & in2; // Delay in a continuous assign
```



# Operator Types

Operator Type	Operator Symbol	Operation Performed	Number of Operands
Arithmetic	*	multiply	two
	/	divide	two
	+	add	two
	-	subtract	two
	%	modulus	two
Logical	!	logical negation	one
	&&	logical and	two
		logical or	two
Relational	>	greater than	two
	<	less than	two
	>=	greater than or equal	two
	<=	less than or equal	two
Equality	==	equality	two
	!=	inequality	two
	===	case equality	two
	!==	case inequality	two
Bitwise	~	bitwise negation	one
	&	bitwise and	two
		bitwise or	two
	^	bitwise xor	two
	^~ or ~^	bitwise xnor	two

Operator Type	Operator Symbol	Operation Performed	Number of Operands
Shift	>>	Right shift	two
	<<	Left shift	two
Concatenation	{ }	Concatenation	any number
Replication	{ ( ) }	Replication	any number
Conditional	? :	Conditional	three

Reduction	&	reduction and	one
	~&	reduction nand	one
		reduction or	one
	~	reduction nor	one
	^	reduction xor	one
	^ ~ or ~ ^	reduction xnor	one

# Conditional Operator

*Usage: condition\_expr ? true\_expr : false\_expr ;*

```
//model functionality of a 2-to-1 mux  
assign out = control ? in1 : in0;
```

# 4:1 Multiplexer Example

```
// Module 4-to-1 multiplexer using data flow. logic equation
// Compare to gate-level model
module mux4_to_1 (out, i0, i1, i2, i3, s1, s0);

// Port declarations from the I/O diagram
output out;
input i0, i1, i2, i3;
input s1, s0;

//Logic equation for out
assign out = (~s1 & ~s0 & i0) |
             (~s1 & s0 & i1) |
             (s1 & ~s0 & i2) |
             (s1 & s0 & i3) ;

endmodule
```

# Queries ....?

