



S J P N Trust's

Hirasugar Institute of Technology, Nidasoshi.

Inculcating Values, Promoting Prosperity

Approved by AICTE, Recognized by Govt. of Karnataka and Affiliated to VTU Belagavi

ECE Dept.

DSDV

VI Sem

2017-18

Department of Electronics & Communication Engg.

Course : Digital System Design using Verilog.

Sem.: 6th (2017-18)

Course Coordinator:

Prof. D. M. Kumbhar

Digital System Design Using Verilog




Module 2 Memories

Portions of this work are from the book, *Digital Design: An Embedded Systems Approach Using Verilog*, by Peter J. Ashenden, published by Morgan Kaufmann Publishers, Copyright 2007 Elsevier Inc. All rights reserved.

General Concepts

 
- A memory is an array of storage locations
 - Each with a unique address
 - Like a collection of registers, but with optimized implementation
- Address is unsigned-binary encoded
 - n address bits $\Rightarrow 2^n$ locations
- All locations the same size
 - $2^n \times m$ bit memory



Memory Sizes

- Use power-of-2 multipliers
 - Kilo (K): $2^{10} = 1,024 \approx 10^3$
 - Mega (M): $2^{20} = 1,048,576 \approx 10^6$
 - Giga (G): $2^{30} = 1,073,741,824 \approx 10^9$
- Example
 - 32K × 32-bit memory
 - Capacity = 1,025K = 1Mbit
 - Requires 15 address bits
- Size is determined by application requirements


Basic Memory Operations

 


- a inputs: unsigned address
- d_in and d_out
 - Type depends on application
- Write operation
 - $en = 1$, $wr = 1$
 - d_in value stored in location given by address inputs
- Read operation
 - $en = 1$, $wr = 0$
 - d_out driven with value of location given by address inputs
- Idle: $en = 0$

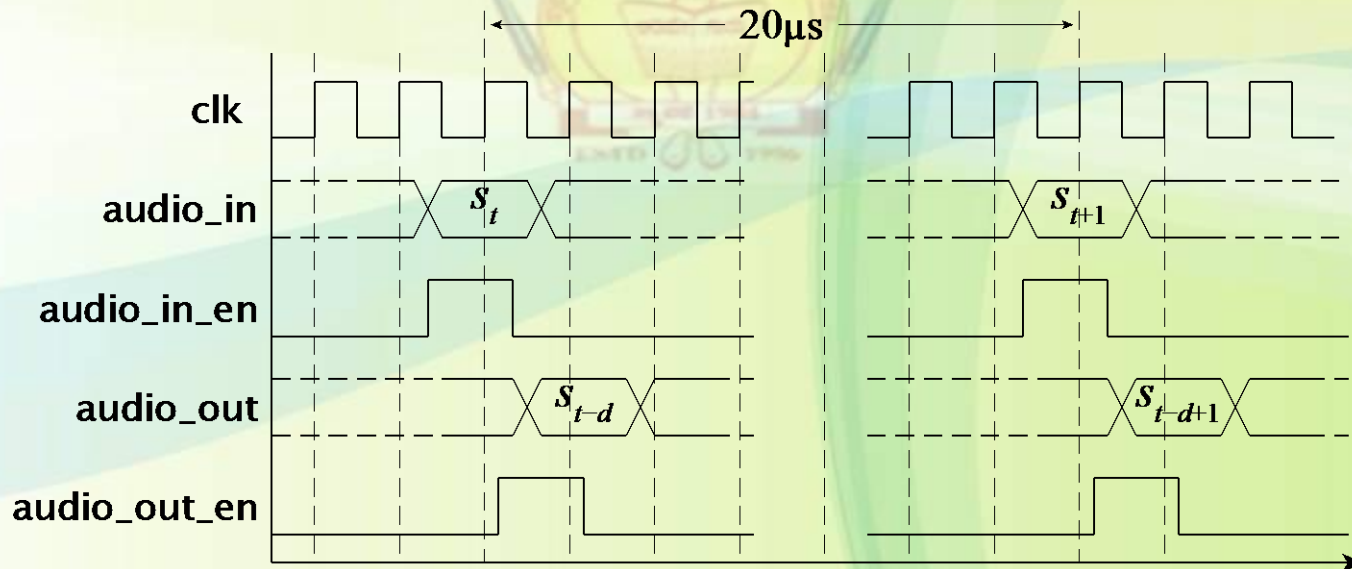Example: Audio Delay Unit

- System clock: 1MHz
- Audio samples: 8-bit signed, at 50kHz
 - New sample arrives when `audio_in_en = 1`
- Delay control: 8-bit unsigned \Rightarrow ms to delay
- Output: `audio_out_en = 1` when output ready



Audio Delay Datapath

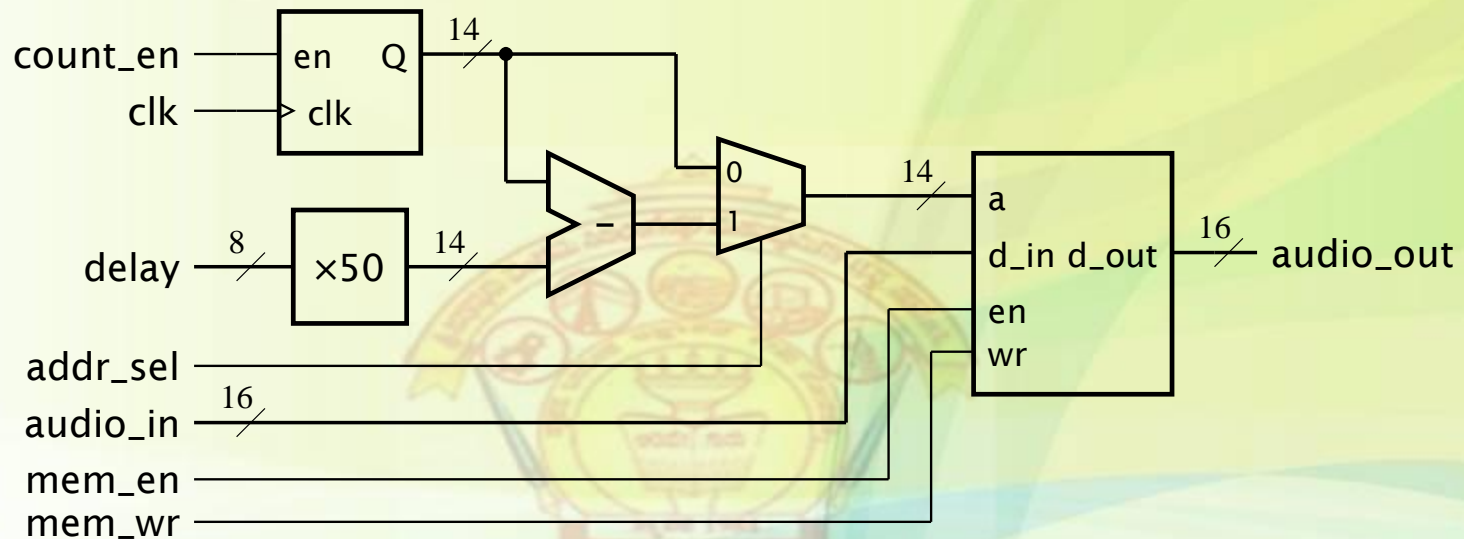

- Max delay = 255ms
 - Need to store $255 \times 50 = 12,750$ samples
 - Use a 16K \times 8-bit memory (14 address bits)

Audio Delay Control Section

Step 1: (idle state)

- audio_in_en = 0 \Rightarrow do nothing
- audio_in_en = 1 \Rightarrow write memory using counter value as address


- Step 2:

- Read memory using subtracter output as address, increment counter

State	audio_in_en	Next state	addr_sel	mem_en	mem_wr	count_en	audio_out_en
Step 1	0	Step 1	0	0	0	0	0
Step 1	1	Step 2	0	1	1	0	0
Step 2	–	Step 1	1	1	0	1	1


Wider Memories

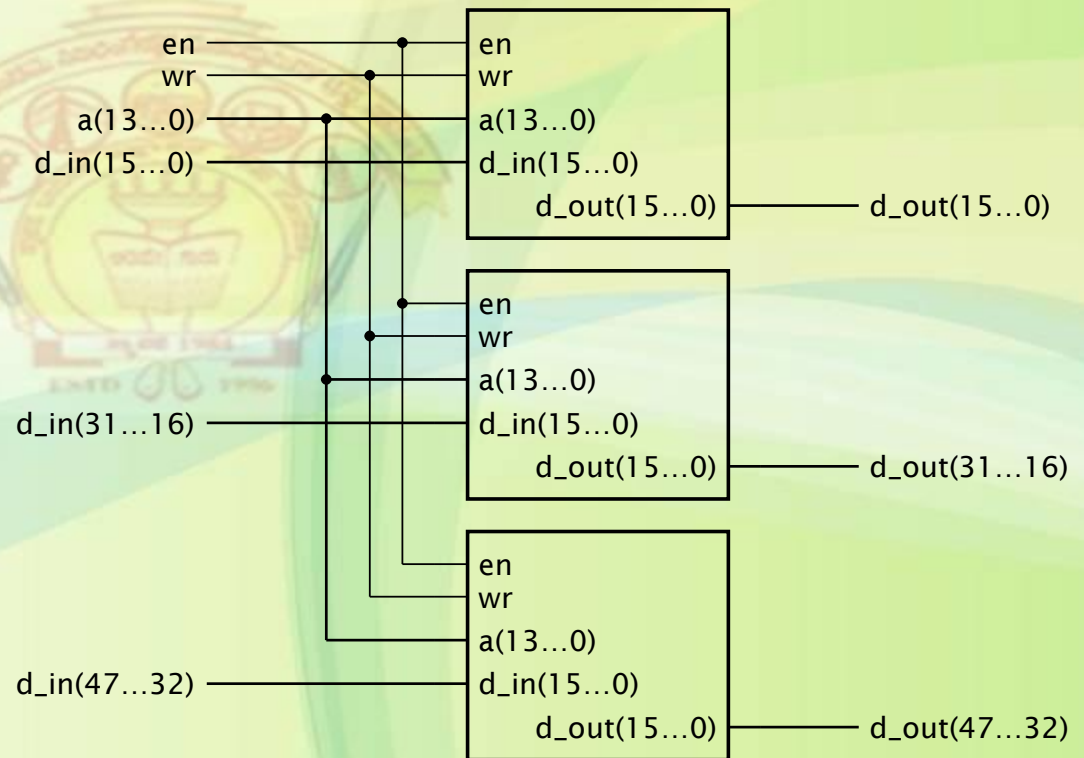- Memory components have a fixed width
 - E.g., $\times 1$, $\times 4$, $\times 8$, $\times 16$, ...
- Use memory components in parallel to make a wider memory
 - E.g, three $16\text{K}\times 16$ components for a $16\text{K}\times 48$ memory




More Locations

 - To provide 2^n locations with 2^k -location components
 - Use $2^{n/2^k}$ components
- Address A
 - at offset $A \bmod 2^k$
 - least-significant k bits of A
 - in component $\lfloor A/2^k \rfloor$
 - most-significant $n-k$ bits of A
 - decode to select component




More Locations

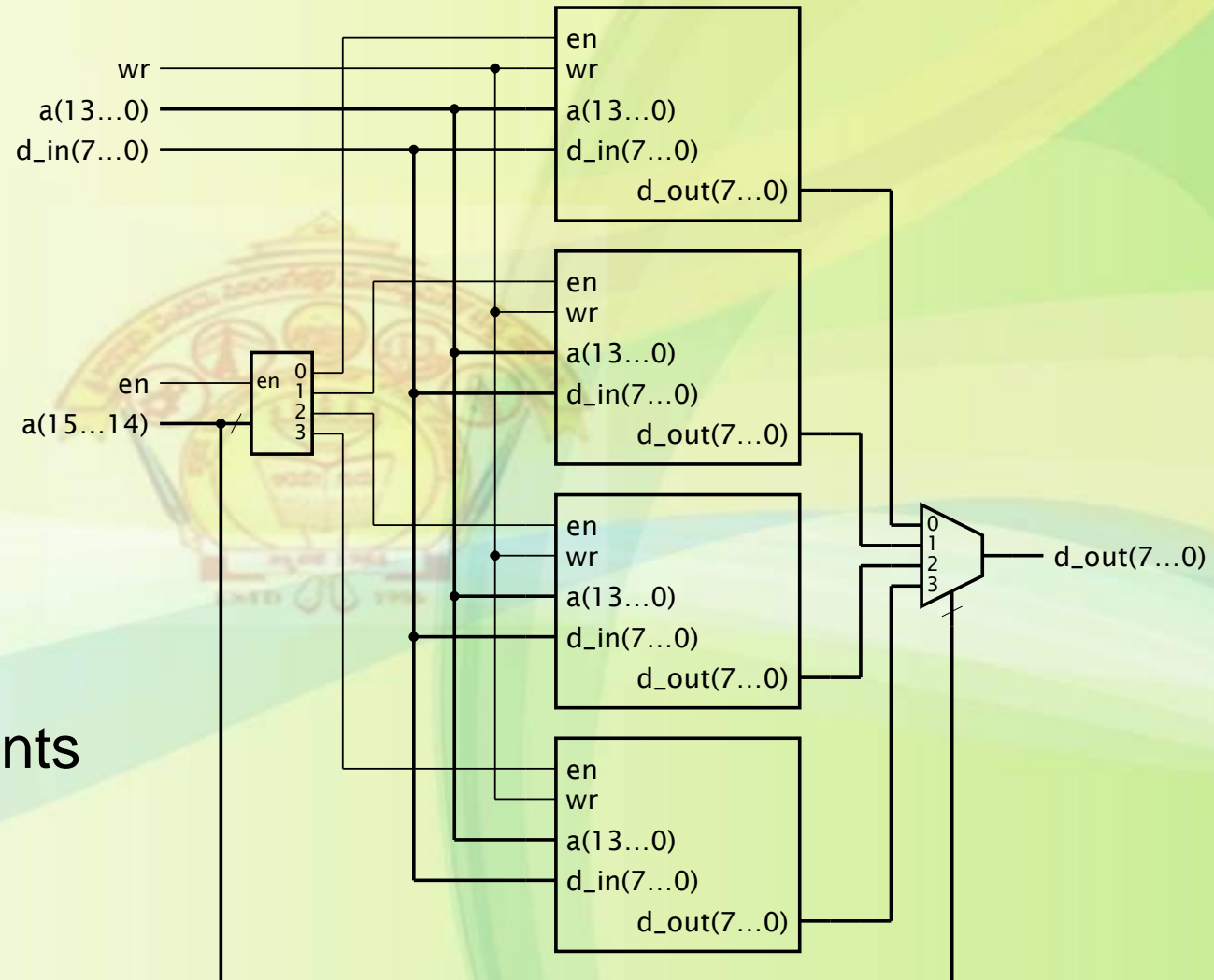- Example:
64K×8 memory
composed of
16K×8 components




Tristate Drivers

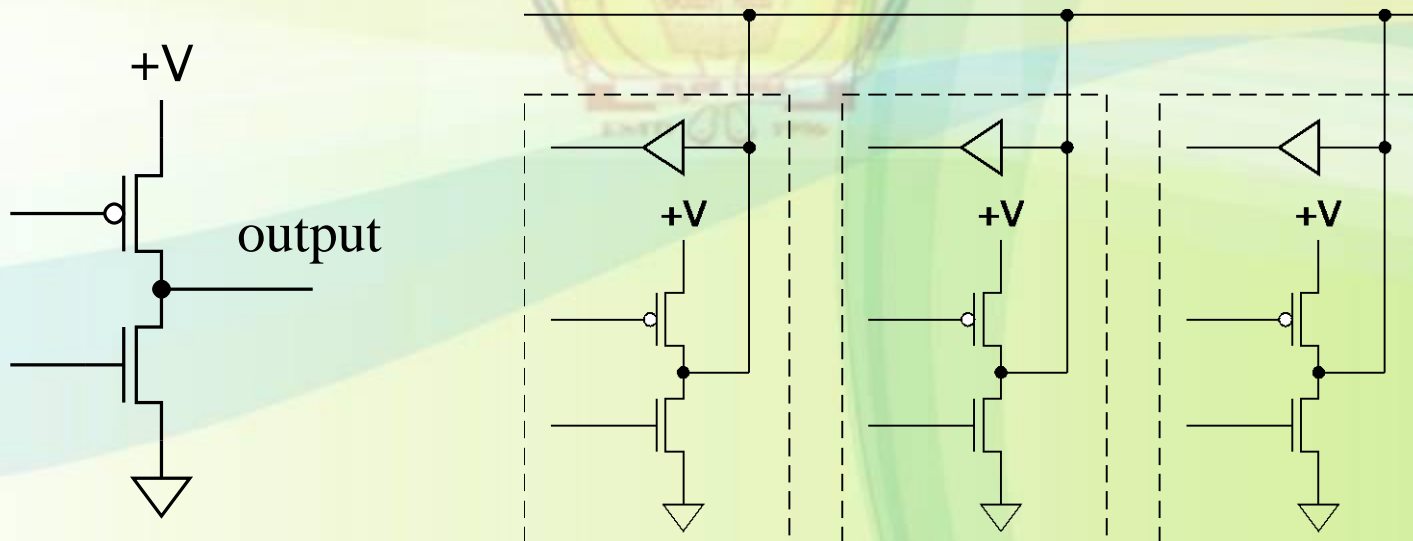- Allow multiple outputs to be connected together
 - Only one active at a time
 - Remaining outputs are high-impedance
 - Both output transistors turned off
- Allow bidirectional input/output ports



Memories with Tristate Ports

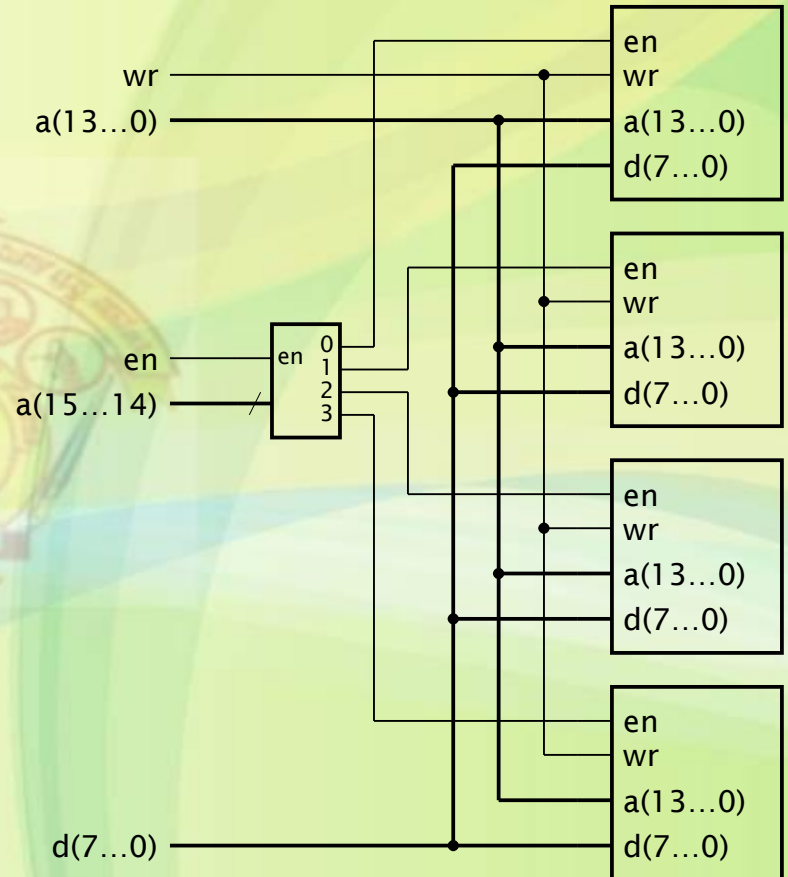- During write
 - memory d drivers hi-Z
 - memory senses d
- During read
 - selected memory drives d
- Fewer pins and wires
 - Reduced cost of PCB
- Usually not available within ASICs or FPGAs





Memory Types

- Random-Access Memory (RAM)
 - Can read and write
 - Static RAM (SRAM)
 - Stores data so long as power is supplied
 - Asynchronous SRAM: not clocked
 - Synchronous SRAM (SSRAM): clocked
 - Dynamic RAM (DRAM)
 - Needs to be periodically refreshed
- Read-Only Memory (ROM)
 - Combinational
 - Programmable and Flash rewritable
- Volatile and non-volatile

Asynchronous SRAM

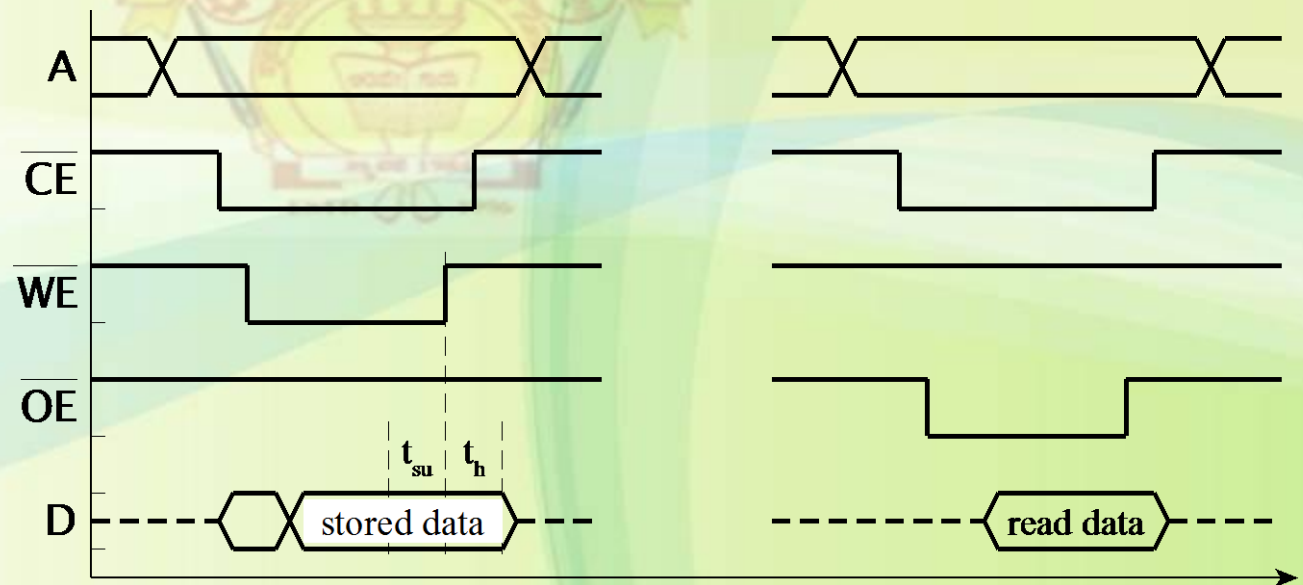 - Data stored in 1-bit latch cells
 - Address decoded to enable a given cell
- Usually use active-low control inputs
- Not available as components in ASICs or FPGAs



Asynch SRAM Timing

- Timing parameters published in data sheets
- Access time
 - From address/enable valid to data-out valid
- Cycle time
 - From start to end of access
- Data setup and hold
 - Before/after end of WE pulse
 - Makes asynch SRAMs hard to use in clocked synchronous designs

Example Data Sheet



CY7C1041BV33

Switching Characteristics^[4] Over the Operating Range


Parameter	Description	-12		-15		-17		Unit
		Min.	Max.	Min.	Max.	Min.	Max.	
READ CYCLE								
t _{RC}	Read Cycle Time	12		15		17		ns
t _{AA}	Address to Data Valid		12		15		17	ns
t _{OHA}	Data Hold from Address Change	3		3		3		ns
t _{ACE}	\overline{CE} LOW to Data Valid		12		15		17	ns
t _{DOE}	\overline{OE} LOW to Data Valid		6		7		8	ns
WRITE CYCLE^[7, 8]								
t _{WC}	Write Cycle Time	12		15		17		ns
t _{SCE}	\overline{CE} LOW to Write End	10		12		12		ns
t _{AW}	Address Set-Up to Write End	10		12		12		ns
t _{HA}	Address Hold from Write End	0		0		0		ns
t _{SA}	Address Set-Up to Write Start	0		0		0		ns
t _{PWE}	\overline{WE} Pulse Width	10		12		12		ns
t _{SD}	Data Set-Up to Write End	7		8		9		ns
t _{HD}	Data Hold from Write End	0		0		0		ns
t _{LZWE}	\overline{WE} HIGH to Low Z ^[6]	3		3		3		ns
t _{HZWE}	\overline{WE} LOW to High Z ^[5, 6]		6		7		8	ns
t _{BW}	Byte Enable to End of Write	10		12		12		ns

Synchronous SRAM (SSRAM)

- Clocked storage registers for inputs
 - address, data and control inputs
 - stored on a clock edge
 - held for read/write cycle

■ Flow-through SSRAM

- no register on data output

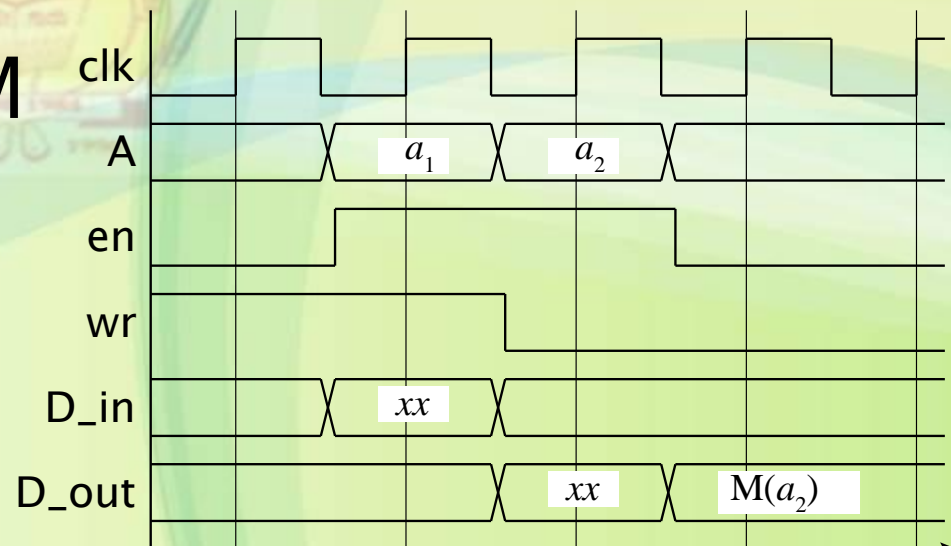


Example: Coefficient Multiplier


$$y = c_i \times x^2$$

- Compute function
 - Coefficient stored in flow-through SSRAM
 - 12-bit unsigned integer index for i
 - x, y, c_i 20-bit signed fixed-point
 - 8 pre- and 12 post-binary point bits
 - Use a single multiplier
 - Multiply $c_i \times x \times x$

Multiplier Datapath

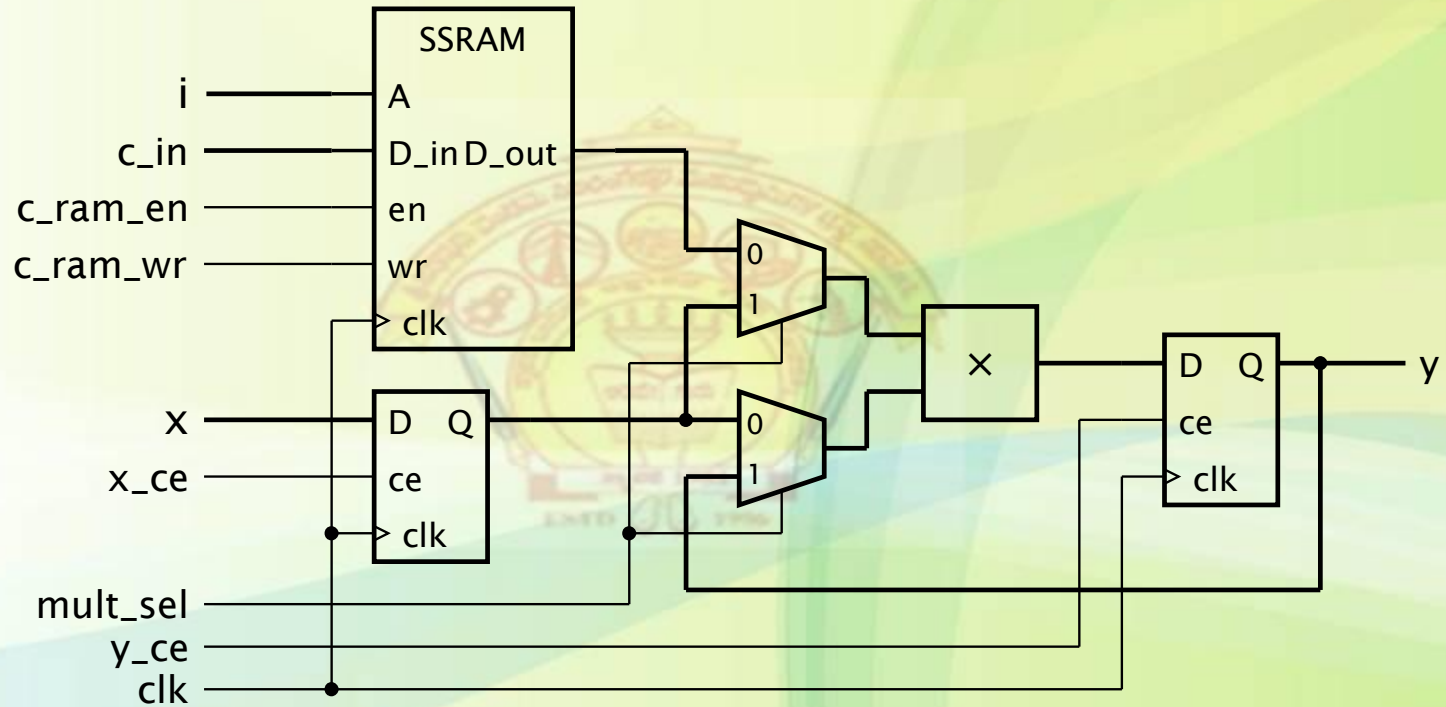


Multiplier Timing and Control

 

Pipelined SSRAM

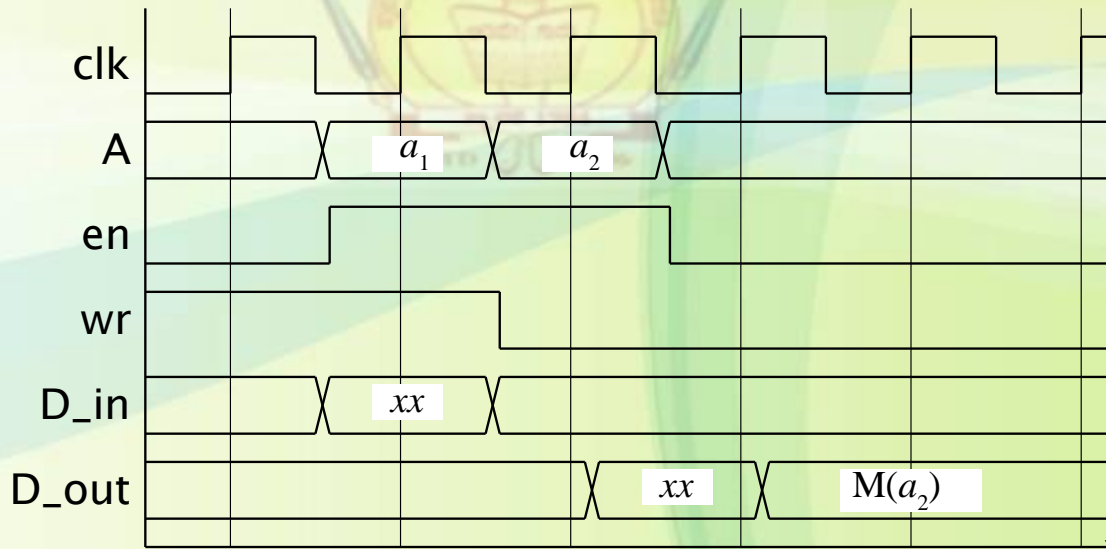- Data output also has a register
 - More suitable for high-speed systems
 - Access RAM in one cycle, use the data in the next cycle



Memories in Verilog

- RAM storage represented by an array variable

```
reg [15:0] data_RAM [0:4095];  
...  
always @(posedge clk)  
  if (en)  
    if (wr) begin  
      data_RAM[a] <= d_in;  d_out <= d_in;  
    end  
  else  
    d_out <= data_RAM[a];
```

Example: Coefficient Multiplier

```
module scaled_square ( output reg signed [7:-12] y,  
                      input      signed [7:-12] c_in, x,  
                      input      [11:0] i,  
                      input      start,  
                      input      clk, reset );  
  
wire      c_ram_wr;  
reg       c_ram_en, x_ce, mult_sel, y_ce;  
reg signed [7:-12] c_out, x_out;  
reg signed [7:-12] c_RAM [0:4095];  
reg signed [7:-12] operand1, operand2;  
parameter [1:0] step1 = 2'b00, step2 = 2'b01, step3 = 2'b10;  
reg       [1:0] current_state, next_state;  
assign c_ram_wr = 1'b0;
```


Example: Coefficient Multiplier

```
always @(posedge clk) // c RAM - flow through
  if (c_ram_en)
    if (c_ram_wr) begin
      c_RAM[i] <= c_in;
      c_out    <= c_in;
    end
    else
      c_out <= c_RAM[i];
always @(posedge clk) // y register
  if (y_ce) begin
    if (!mult_sel) begin
      operand1 = c_out;
      operand2 = x_out;
    end
    else begin
      operand1 = x_out;
      operand2 = y;
    end
    y <= operand1 * operand2;
  end
end
```

Example: Coefficient Multiplier

```
always @(posedge clk) // State register
...
always @* // Next-state logic
...
always @* begin // Output logic
...
endmodule
```

Pipelined SSRAM in Verilog

```
reg        pipelined_en;  
reg [15:0] pipelined_d_out;  
...
```

```
always @(posedge clk) begin  
    if (pipelined_en) d_out <= pipelined_d_out;  
    pipelined_en <= en;  
    if (en)  
        if (wr) begin  
            data_RAM([a] <= d_in;  pipelined_d_out <= d_in;  
        end  
        else  
            pipelined_d_out <= data_RAM[a];  
end
```

output
register

SSRAM

Multiport Memories


- Multiple address, data and control connections to the storage locations
- Allows concurrent accesses
 - Avoids multiplexing and sequencing
- Scenario
 - Data producer and data consumer
- What if two writes to a location occur concurrently?
 - Result may be unpredictable
 - Some multi-port memories include an arbiter

FIFO Memories


- First-In/First-Out buffer
 - Connecting producer and consumer
 - Decouples rates of production/consumption



 - Implementation using dual-port RAM
 - Circular buffer
 - Full: $\text{write-addr} = \text{read-addr}$
 - Empty: $\text{write-addr} = \text{read-addr}$




Example: FIFO Datapath

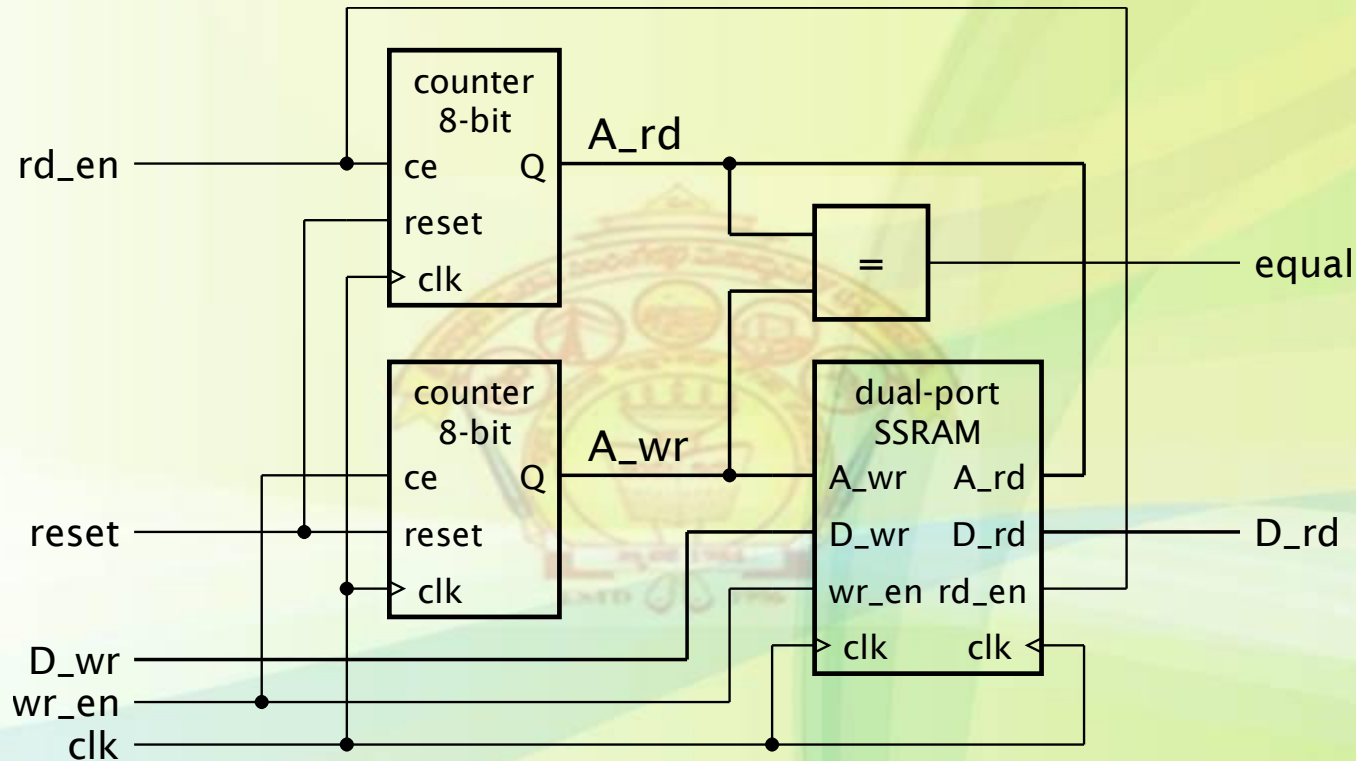

- Equal = full or empty
 - Need to distinguish between these states — How?

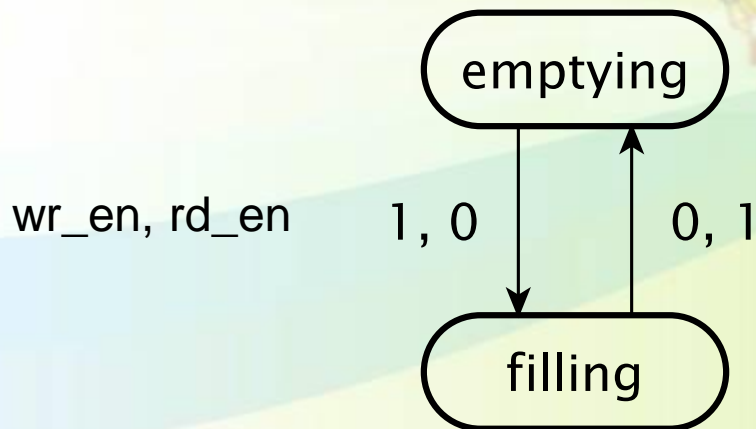Example: FIFO Control

- Control FSM
 - → filling when write without concurrent read
 - → emptying when without concurrent write
 - Unchanged when concurrent write and read



full = filling and equal


empty = emptying and equal

Multiple Clock Domains

- Need to resynchronize data that traverses clock domains
 - Use resynchronizing registers
- May overrun if sender's clock is faster than receiver's clock
- FIFO smooths out differences in data flow rates
 - Latch cells inside FIFO RAM written with sender's clock, read with receiver's clock

Dynamic RAM (DRAM)

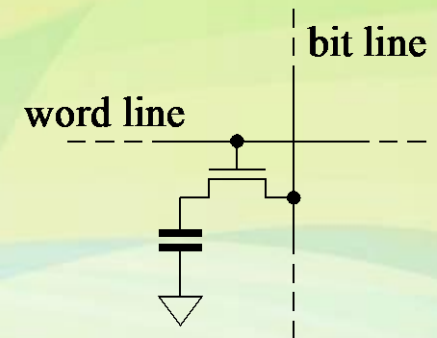- Data stored in a 1-transistor/1-capacitor cell
 - Smaller cell than SRAM, so more per chip
 - But longer access time
- Write operation
 - pull bit-line high or low (0 or 1)
 - activate word line
- Read operation
 - precharge bit-line to intermediate voltage
 - activate word line, and sense charge equalization
 - rewrite to restore charge



DRAM Refresh


- Charge on capacitor decays over time
 - Need to sense and rewrite periodically
 - Typically every cell every 64ms
 - *Refresh* each location
- DRAMs organized into banks of rows
 - Refresh whole row at a time
- Can't access while refreshing
 - Interleave refresh among accesses
 - Or burst refresh every 64ms

Read-Only Memory (ROM)

- For constant data, or CPU programs
- Masked ROM
 - Data manufactured into the ROM
- Programmable ROM (PROM)
 - Use a PROM programmer
- Erasable PROM (EPROM)
 - UV erasable
 - Electrically erasable (EEPROM)
 - Flash RAM

Combinational ROM

 - A ROM maps address input to data output
 - This is a combinational function!
 - Specify using a table
- Example: 7-segment decoder



Address	Content	Address	Content
0	0111111	6	1111101
1	0000110	7	0000111
2	1011011	8	1111111
3	1001111	9	1101111
4	1100110	10–15	1000000
5	1101101	16–31	0000000

Example: ROM in Verilog

```
module seven_seg_decoder ( output reg [7:1] seg,  
                          input          [3:0] bcd,  
                          input          blank );  
  
always @*  
  case ({blank, bcd})  
    5'b00000: seg = 7'b0111111; // 0  
    5'b00001: seg = 7'b0000110; // 1  
    5'b00010: seg = 7'b1011011; // 2  
    5'b00011: seg = 7'b1001111; // 3  
    5'b00100: seg = 7'b1100110; // 4  
    5'b00101: seg = 7'b1101101; // 5  
    5'b00110: seg = 7'b1111101; // 6  
    5'b00111: seg = 7'b0000111; // 7  
    5'b01000: seg = 7'b1111111; // 8  
    5'b01001: seg = 7'b1101111; // 9  
    5'b01010, 5'b01011, 5'b01100,  
    5'b01101, 5'b01110, 5'b01111:  
      seg = 7'b1000000; // "-" for invalid code  
    default: seg = 7'b0000000; // blank  
  endcase  
endmodule
```

Flash RAM

- Non-volatile, readable (relatively fast), writable (relatively slow)
- Storage partitioned into blocks
 - Erase a whole block at a time, then write/read
 - Once a location is written, can't rewrite until erased
- NOR Flash
 - Can write and read individual locations
 - Used for program storage, random-access data
- NAND Flash
 - Denser, but can only write and read block at a time
 - Used for bulk data, e.g., cameras, memory sticks

Memory Errors


- Bits in memory can be flipped
- Hard error
 - The chip is broken
 - E.g., manufacturing defect, wear (in Flash)
- Soft error
 - Stored data corrupted, but cell still works
 - E.g., from atmospheric neutrons
- Soft-error rate
 - frequency of occurrence

Error Detection using Parity


- Add a parity bit to each location
- On write access
 - compute data parity and store with data
- On read access
 - check parity, take exception on error
- If we could tell which bit flipped
 - correct by flipping it back, then write back to memory location
 - Can't do this with parity

Error-Correcting Codes (ECC)

 - Allow identification of the flipped bit
- Hamming Codes
 - E.g., for single-bit-error correction of N -bit word, need $\log_2 N + 1$ extra bits
- Example: 8-bit word, $d_1 \dots d_8$
 - 12-bit ECC code, $e_1 \dots e_{12}$
 - e_1, e_2, e_4, e_8 are check bits, the rest data



Hamming Code Example

 

e_1	0	0	0	1
e_2	0	0	1	0
e_4	0	1	0	0
e_8	1	0	0	0
e_3	0	0	1	1
e_5	0	1	0	1
e_6	0	1	1	0
e_7	0	1	1	1
e_9	1	0	0	1
e_{10}	1	0	1	0
e_{11}	1	0	1	1
e_{12}	1	1	0	0

$$e_1 = e_3 \oplus e_5 \oplus e_7 \oplus e_9 \oplus e_{11}$$

$$e_2 = e_3 \oplus e_6 \oplus e_7 \oplus e_{10} \oplus e_{11}$$

$$e_4 = e_5 \oplus e_6 \oplus e_7 \oplus e_{12}$$

$$e_8 = e_9 \oplus e_{10} \oplus e_{11} \oplus e_{12}$$

- Every data bit covered by two or more check bits
- On write: Compute check bits and store with data

Hamming Code Example

e_1	0	0	0	1
e_2	0	0	1	0
e_4	0	1	0	0
e_8	1	0	0	0
e_3	0	0	1	1
e_5	0	1	0	1
e_6	0	1	1	0
e_7	0	1	1	1
e_9	1	0	0	1
e_{10}	1	0	1	0
e_{11}	1	0	1	1
e_{12}	1	1	0	0

- On read: Recompute check bits and XOR with read check bits
 - result called the *syndrome*
- 0000 => no error
- If data bit flipped
 - covering bits of syndrome are 1
 - = binary code of flipped ECC bit
- If stored check bit flipped
 - that bit of syndrome is 1
- On error, unflip bit and rewrite memory location

Multiple-Error Detection

- What if two bits flip
 - syndrome identifies wrong bit, or is invalid
- One extra check bit allows
 - single-error correction, double-error detection

N	Single-bit correction		Double-bit detection	
	Check bits	Overhead	Check bits	Overhead
8	4	50%	5	63%
16	5	31%	6	38%
32	6	19%	7	22%
64	7	11%	8	13%
128	8	6.3%	9	7.0%
256	9	3.5%	10	3.9%

Summary

- Memory: addressable storage locations
- Read and Write operations
- Asynchronous RAM
- Synchronous RAM (SSRAM)
- Dynamic RAM (DRAM)
- Read-Only Memory (ROM) and Flash
- Multiport RAM and FIFOs
- Error Detection and Correction
 - Hamming Codes

Queries?

