



S J P N Trust's

Hirasugar Institute of Technology, Nidasoshi.

Inculcating Values, Promoting Prosperity

Approved by AICTE, Recognized by Govt. of Karnataka and Affiliated to VTU Belagavi

ECE Dept.

DSDV

VI Sem

2017-18

Department of Electronics & Communication Engg.

Course : Digital System Design using Verilog.

Sem.: 6th (2017-18)

Course Coordinator:

Prof. D. M. Kumbhar

Digital System Design Using Verilog



Module 1

Introduction and Methodology

Portions of this work are from the book, *Digital Design: An Embedded Systems Approach Using Verilog*, by Peter J. Ashenden, published by Morgan Kaufmann Publishers, Copyright 2007 Elsevier Inc. All rights reserved.

Digital Design

Digital: circuits that use two voltage levels to represent information

Logic: use truth values and logic to analyze circuits

Design: meeting functional requirements while satisfying constraints

History : Mechanical – electromechanical – analog

Use

Disadvantages : accuracy, speed, maintenance.

Early circuits - digital circuits.


Constraints: performance, size, power, cost, etc.

Design using Abstraction

- Circuits contain millions of transistors
 - How can we manage this complexity?
- Abstraction
 - Focus on aspects relevant aspects, ignoring other aspects
 - Don't break assumptions that allow aspect to be ignored!
- Examples:
 - Transistors are on or off
 - Voltages are low or high

Digital Systems

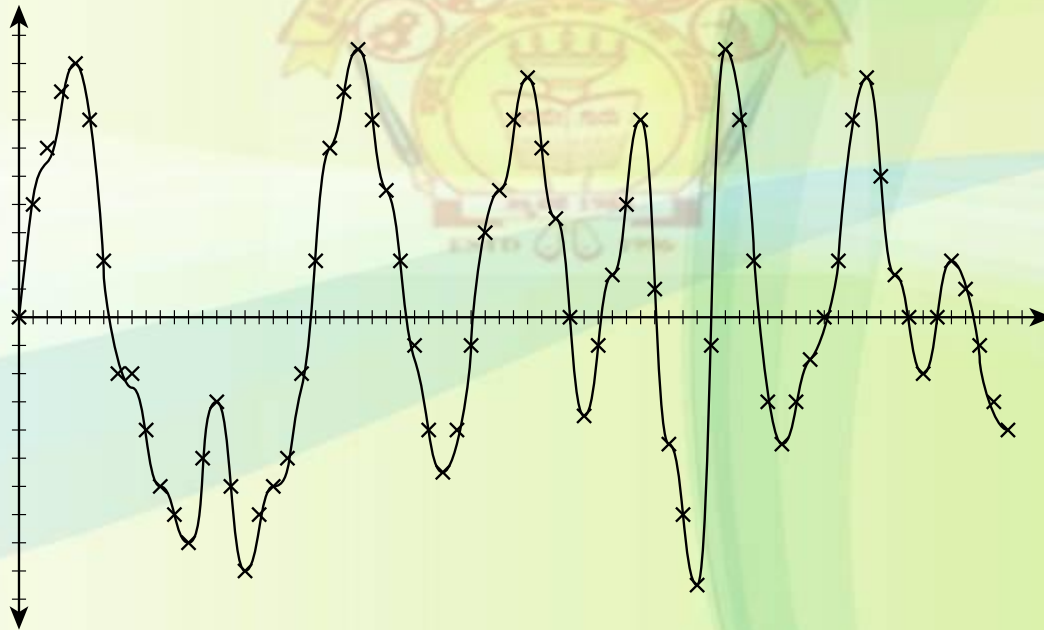- Electronic circuits that use discrete representations of information
 - Discrete in space and time



Embedded Systems

- Most real-world digital systems include embedded computers
 - Processor cores, memory, I/O
- Different functional requirements can be implemented
 - by the embedded software
 - by special-purpose attached circuits
- Trade-off among cost, performance, power, etc.

Binary Representation

- Basic representation for simplest form of information, with only two states
 - a switch: open or closed
 - a light: on or off
 - a microphone: active or muted
 - a logical proposition: false or true
 - a binary (base 2) digit, or bit: 0 or 1

Binary Representation: Example



- Signal represents the state of the switch
 - high-voltage => pressed,
 - low-voltage => not pressed
- Equally, it represents state of the lamp
 - lamp_lit = switch_pressed

Basic Gate Components

- Primitive components for logic design




AND gate



OR gate




inverter

 

multiplexer

Combinational Circuits

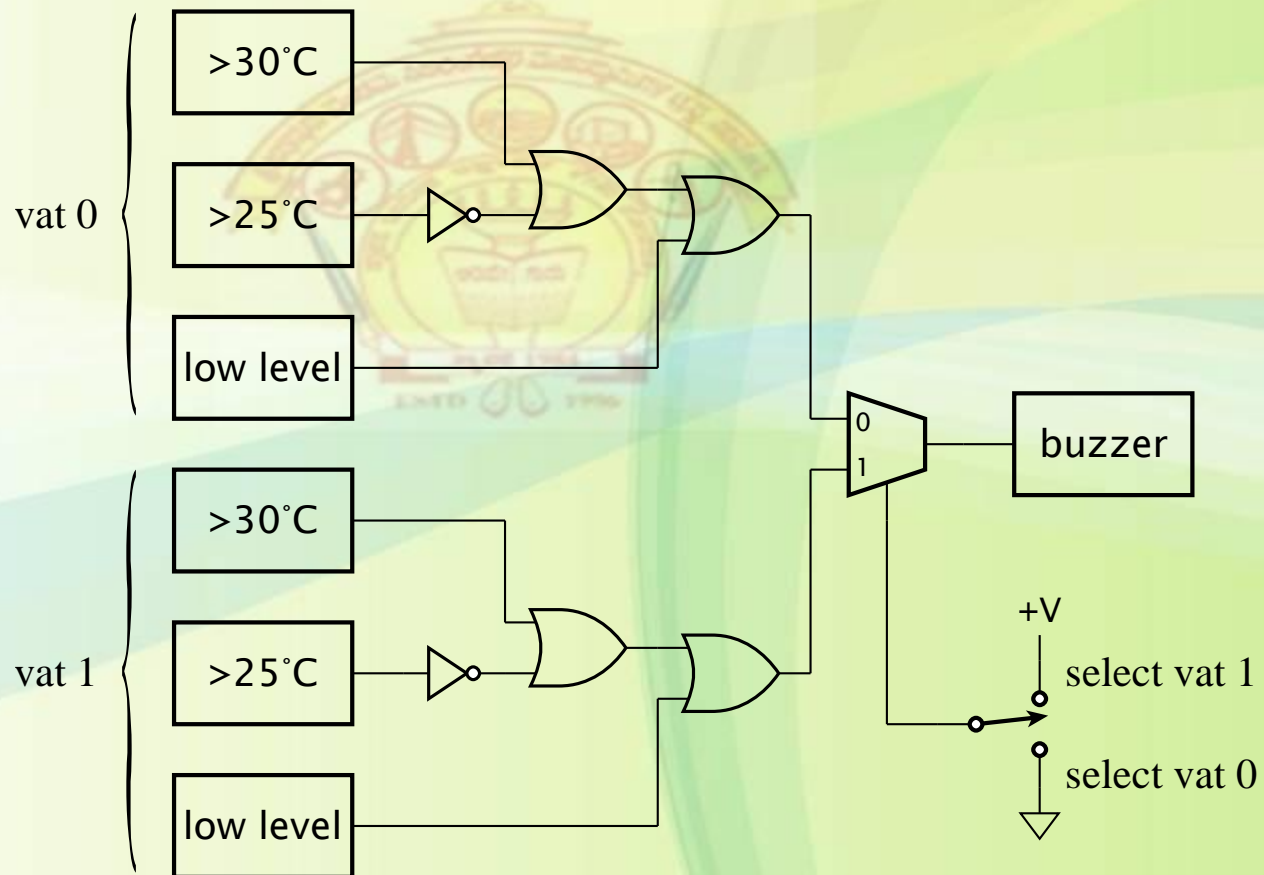- Circuit whose output values depend purely on current input values





Sequential Circuits

- Circuit whose output values depend on current *and previous* input values
 - Include some form of storage of values
- Nearly all digital systems are sequential
 - Mixture of gates and storage components
 - Combinational parts transform inputs and stored values

Flipflops and Clocks

  - Edge-triggered D-flipflop
 - stores one bit of information at a time






- Timing diagram
 - Graph of signal values versus time

Real-World Circuits

- Assumptions behind digital abstraction
 - ideal circuits, only two voltages, instantaneous transitions, no delay
- Greatly simplify functional design
- Constraints arise from real components and real-world physics
- Meeting constraints ensures circuits are “ideal enough” to support abstractions



Integrated Circuits (ICs)

   - Circuits formed on surface of silicon wafer
 - Minimum feature size reduced in each technology generation
 - Currently 90nm, 65nm
 - Moore's Law: increasing transistor count
 - CMOS: complementary MOSFET circuits




Logic Levels

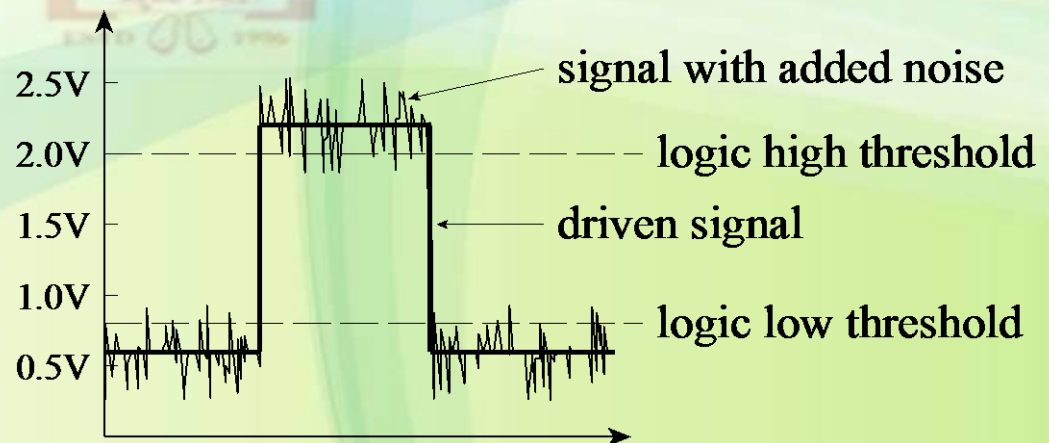 - Actual voltages for “low” and “high”
 - Example: 1.4V threshold for inputs



Logic Levels

- TTL logic levels with noise margins

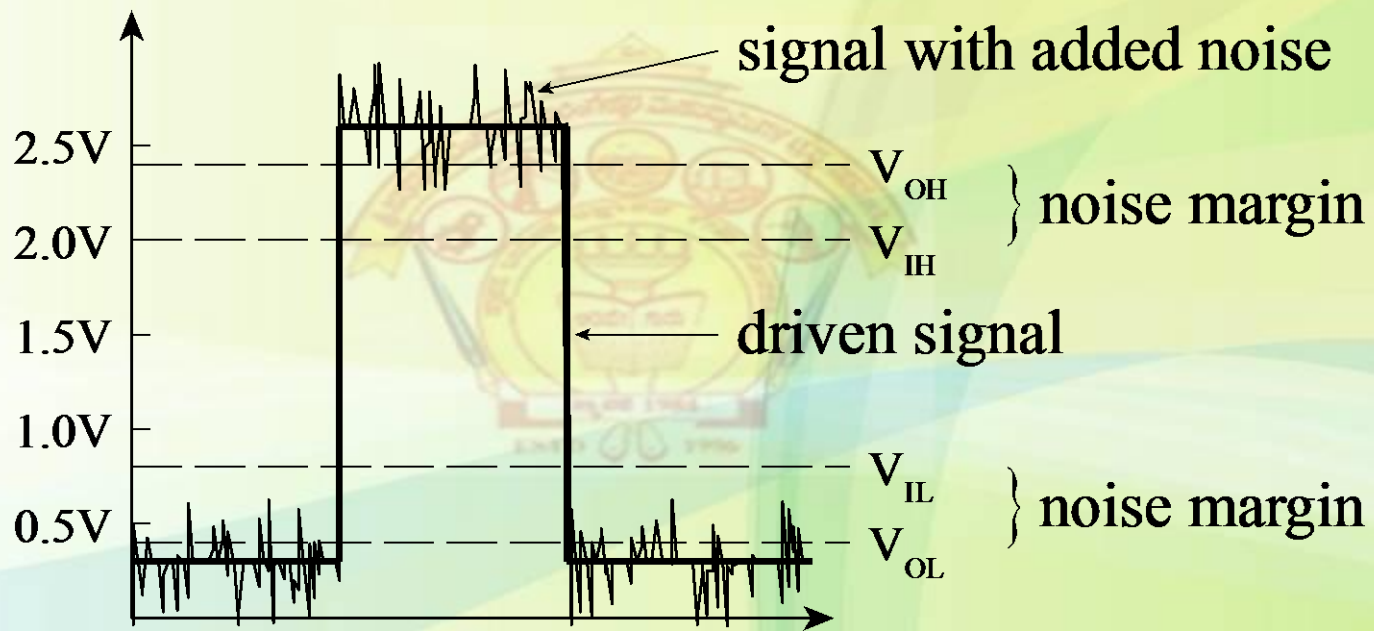

V_{OL} : output low voltage


V_{IL} : input low voltage

V_{OH} : output high voltage

V_{IH} : input high voltage

Static Load and Fanout

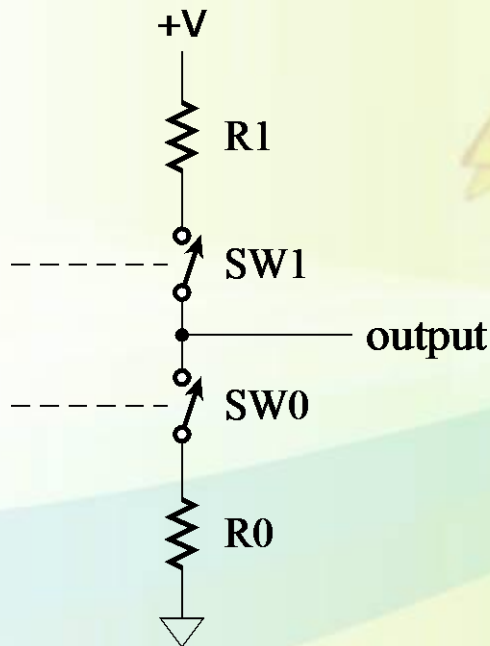
- Current flowing into or out of an output



- High: SW1 closed, SW0 open
 - Voltage drop across R1
 - Too much current: $V_O < V_{OH}$
- Low: SW0 closed, SW1 open
 - Voltage drop across R0
 - Too much current: $V_O > V_{OL}$
- Fanout: number of inputs connected to an output
 - determines static load

Static Load and Fanout

 
- Current flowing into or out of an output



- High: SW1 closed, SW0 open
 - Voltage drop across R1
 - Too much current: $V_O < V_{OH}$
- Low: SW0 closed, SW1 open
 - Voltage drop across R0
 - Too much current: $V_O > V_{OL}$
- Fanout: number of inputs connected to an output
 - determines static load

Capacitive Load and Prop Delay

- Inputs and wires act as capacitors

 

- t_r : rise time
- t_f : fall time
- t_{pd} : propagation delay
 - delay from input transition to output transition
 - $t_{pd} = \max(t_{pd01}, t_{pd10})$

Other Constraints

- Wire delay: delay for transition to traverse interconnecting wire
- Flipflop timing
 - delay from clk edge to Q output
 - D stable before and after clk edge
- Power
 - current through resistance => heat
 - must be dissipated, or circuit cooks!
 - Static & dynamic power consumption

Area and Packaging

- Circuits implemented on silicon chips
 - Larger circuit area => greater cost
- Chips in packages with connecting wires
 - More wires => greater cost
 - Package dissipates heat
- Packages interconnected on a printed circuit board (PCB)
 - Size, shape, cooling, etc, constrained by final product



Models


- **Model:** represents interested aspects omits other (abstraction of an object) Ex. House, train, plane.
- **Electronic model:** Prototype circuit
Abstract expression in some modeling language
- **Abstract representations of aspects of a system being designed**
 - Allow us to analyze the system before building it
- **Example: Ohm's Law**
 - $V = I \times R$
 - Represents electrical aspects of a resistor
 - Expressed as a mathematical equation
 - Ignores thermal, mechanical, materials aspects

Models

- **Model:** represents interested aspects omits other (abstraction of an object) Ex. House, train, plane.
- **Electronic model:** Prototype circuit
Abstract expression in some modeling language
- **Abstract representations of aspects of a system being designed**
 - Allow us to analyze the system before building it
- **Example: Ohm's Law**
 - $V = I \times R$
 - Represents electrical aspects of a resistor
 - Expressed as a mathematical equation
 - Ignores thermal, mechanical, materials aspects

Module Ports

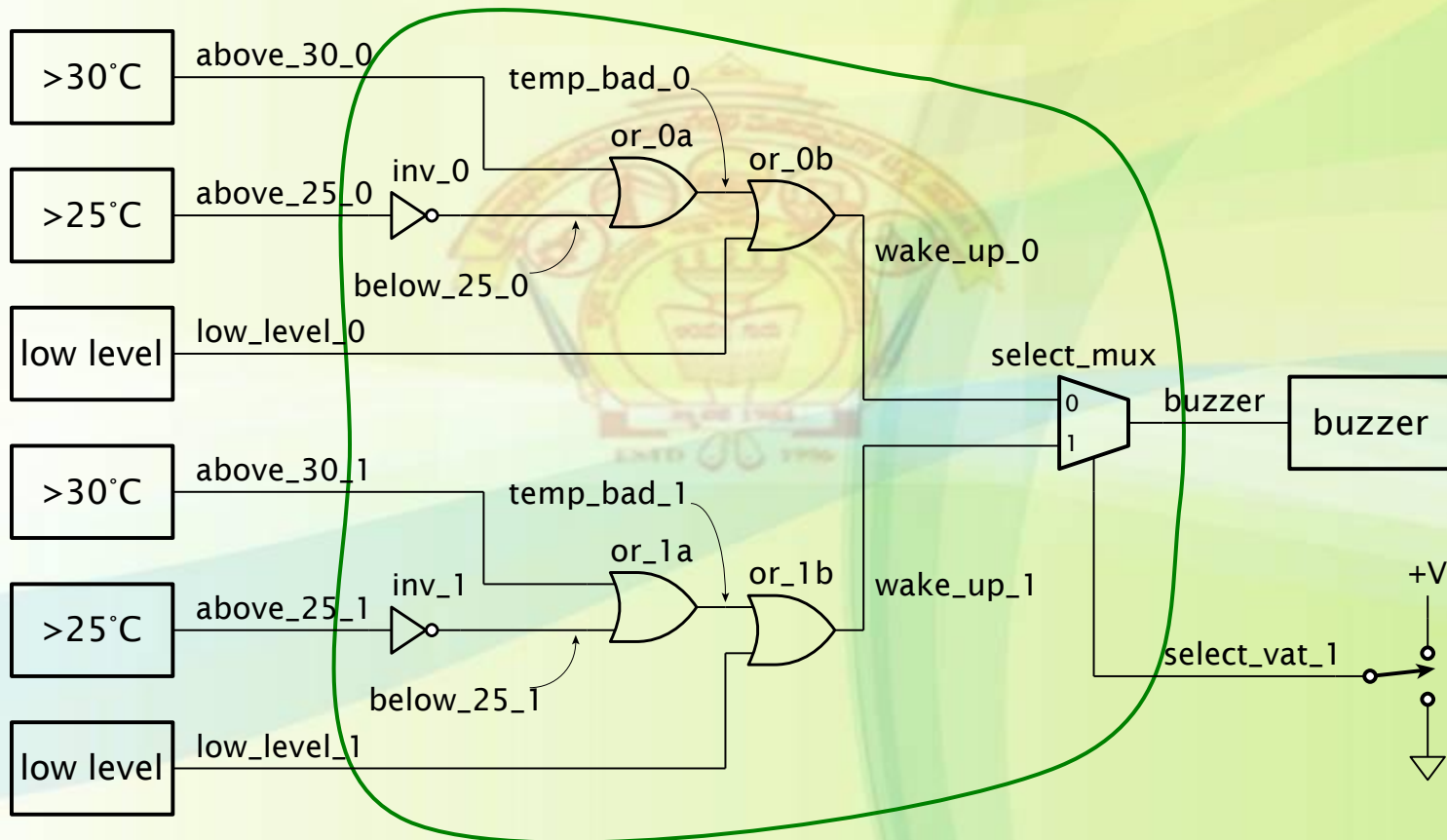- Describe input and outputs of a circuit



Structural Module Definition

```
module vat_buzzer_struct
  ( output buzzer,
    input above_25_0, above_30_0, low_level_0,
    input above_25_1, above_30_1, low_level_1,
    input select_vat_1 );

  wire below_25_0, temp_bad_0, wake_up_0;
  wire below_25_1, temp_bad_1, wake_up_1;

  // components for vat 0
  not inv_0 (below_25_0, above_25_0);
  or or_0a (temp_bad_0, above_30_0, below_25_0);
  or or_0b (wake_up_0, temp_bad_0, low_level_0);

  // components for vat 1
  not inv_1 (below_25_1, above_25_1);
  or or_1a (temp_bad_1, above_30_1, below_25_1);
  or or_1b (wake_up_1, temp_bad_1, low_level_1);

  mux2 select_mux (buzzer, select_vat_1, wake_up_0, wake_up_1);
endmodule
```

Behavioral Module Definition

```
module vat_buzzer_struct
  ( output buzzer,
    input above_25_0, above_30_0, low_level_0,
    input above_25_1, above_30_1, low_level_1,
    input select_vat_1 );

  assign buzzer =
    select_vat_1 ? low_level_1 | (above_30_1 | ~above_25_1)
      : low_level_0 | (above_30_0 | ~above_25_0);

endmodule
```


Design Methodology

- Design: complex, large no of undertakings & requirements.
Systematic approach of working out how to construct circuits that meets given requirements.
- Simple systems can be design by one person using *ad hoc* methods
- Real-world systems are design by teams
 - Require a systematic design methodology
 - Design methodology: systematic process of design, verification and preparation for manufacture a product.
- Specifies
 - Tasks to be undertaken
 - Information needed and produced
 - Relationships between tasks
 - dependencies, sequences
 - EDA tools used

Design Methodology

- A mature design methodology: schedule & budget, no of errors detected and missed, data from previous projects to improve new one
- Advantages:
 - Design process more reliable and predictable
 - Reducing risk and cost
 - Reducing scale


A Simple Design Methodology

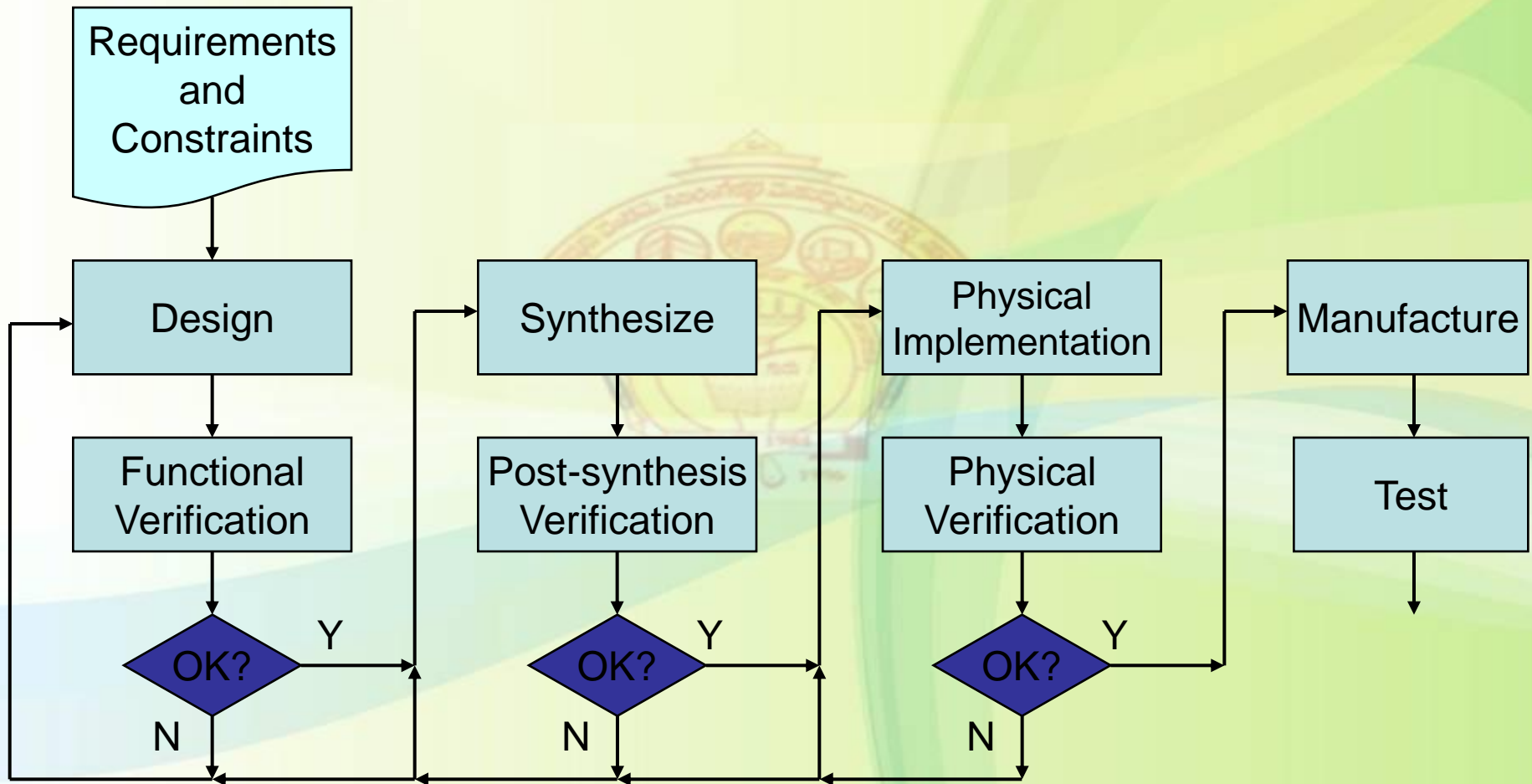

Hierarchical Design

- Circuits are too complex for us to design all the detail at once
- Design subsystems for simple functions
- Compose subsystems to form the system
 - Treating sub circuits as “black box” components
 - Ex. Display
 - Reuse-present, previous or third party project
 - Save – design effort & cost.
 - Verify independently, then verify the composition
- Top-down/bottom-up design

Hierarchical Design

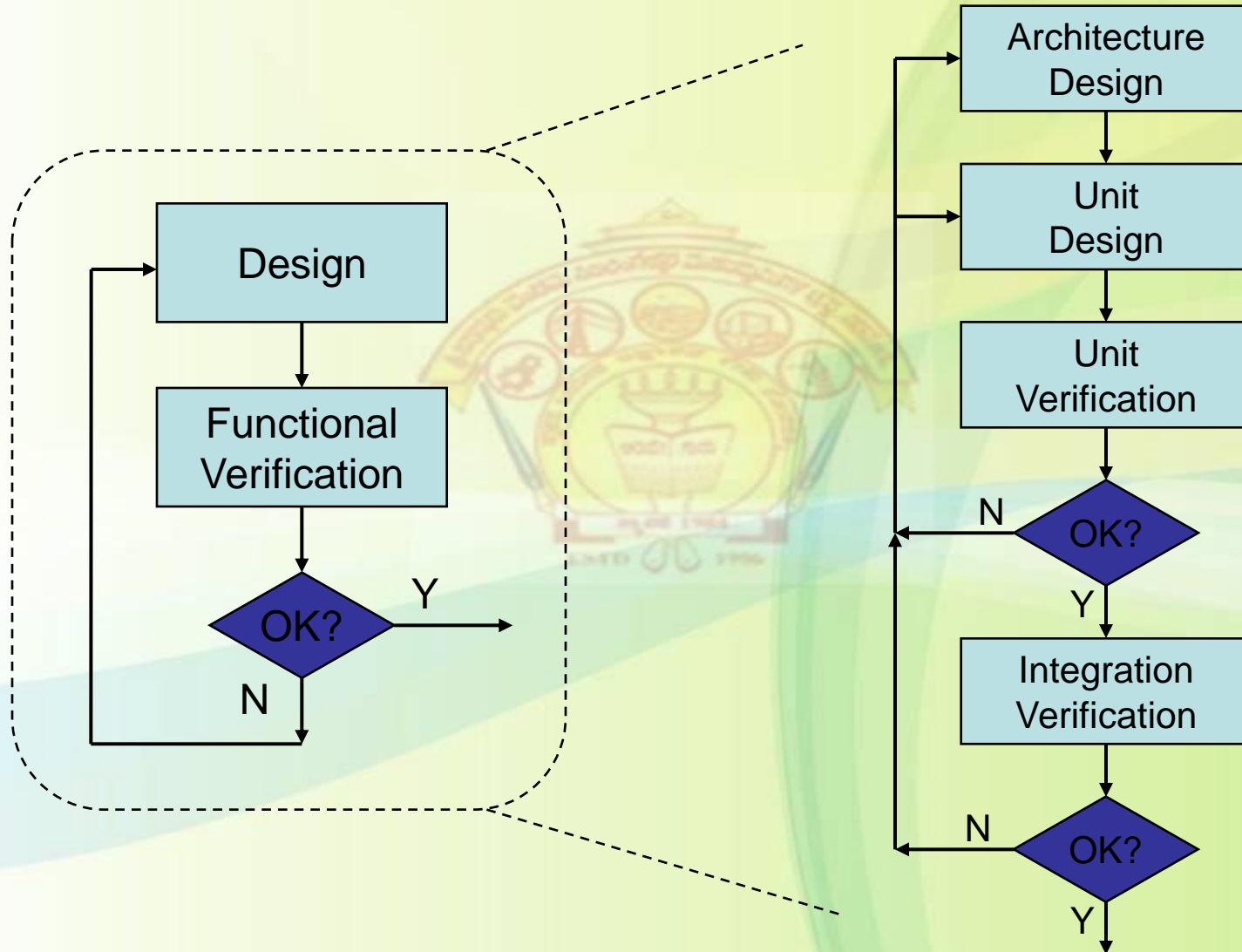


Synthesis

- We usually design using register-transfer-level (RTL) Verilog
 - Higher level of abstraction than gates
- Synthesis tool translates to a circuit of gates that performs the same function
- Specify to the tool
 - the target implementation fabric
 - Library – properties, timing, area, power
 - constraints on timing, area, etc.
- Post-synthesis verification
 - synthesized circuit meets constraints

Physical Implementation

- Implementation fabrics
 - Application-specific ICs (ASICs)
 - Field-programmable gate arrays (FPGAs)
- Floor-planning: arranging the subsystems
- Placement: arranging the gates within subsystems
- Routing: joining the gates with wires
- Physical verification
 - physical circuit still meets constraints
 - use better estimates of delays

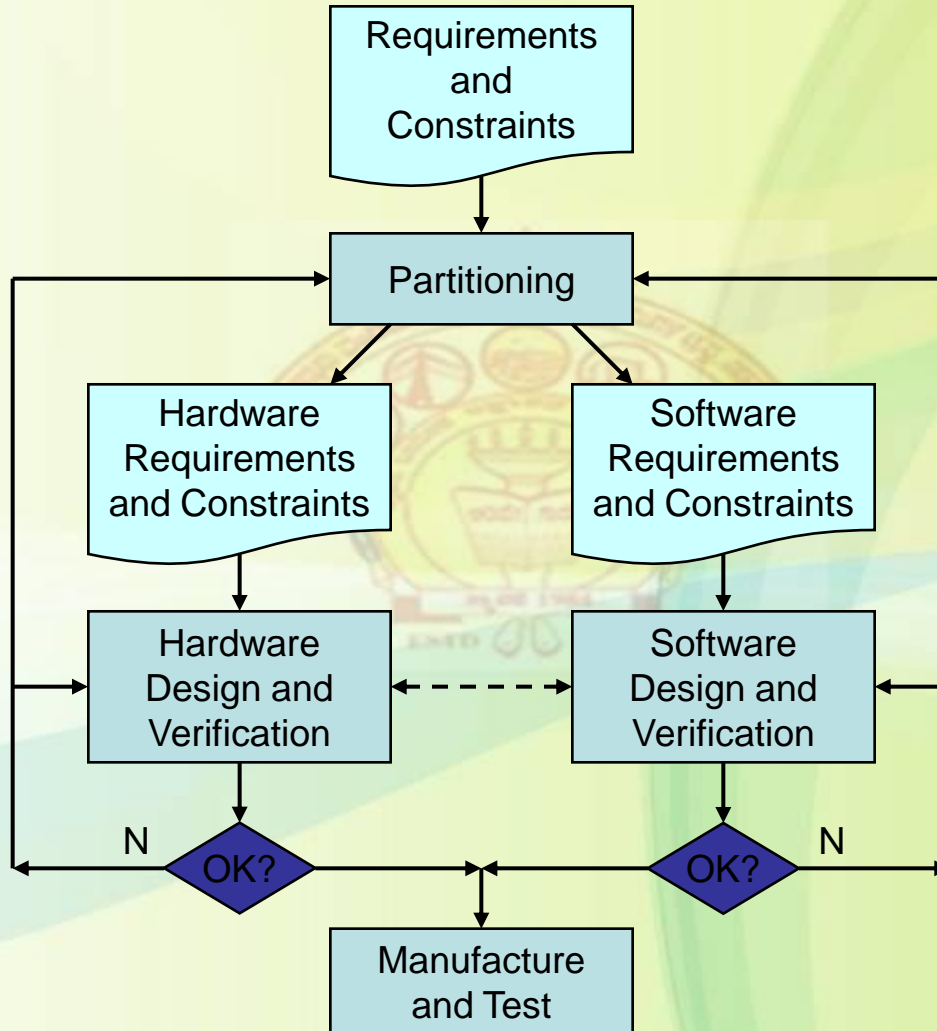Embedded system Design Codesign Methodology




Combinational Circuits

- Circuits whose outputs depend only on current input values
 - no storage of past input values
 - no *state*
- Can be analyzed using laws of logic
 - Boolean algebra, similar to propositional calculus

Combinational Components

- We can build complex combination components from gates
 - Decoders, encoders
 - Multiplexers
 - ...
- Use them as subcomponents of larger systems
 - Abstraction and reuse

Decoders

 

- A decoder derives control signals from a binary coded signal
 - One per code word
 - Control signal is 1 when input has the corresponding code word; 0 otherwise
- For an n -bit code input
 - Decoder has 2^n outputs
- Example: (a_3, a_2, a_1, a_0)
 - Output for $(1, 0, 1, 1)$: $y_{11} = a_3 \cdot \overline{a_2} \cdot a_1 \cdot a_0$

Decoder Example

Color	Codeword (c_2, c_1, c_0)
black	0, 0, 1
cyan	0, 1, 0
magenta	0, 1, 1
yellow	1, 0, 0
red	1, 0, 1
blue	1, 1, 0


Decoder Example

```
module ink_jet_decoder
  ( output black, cyan, magenta, yellow,
    light_cyan, light_magenta,
    input color2, color1, color0 );

  assign black      = ~color2 & ~color1 & color0;
  assign cyan       = ~color2 & color1 & ~color0;
  assign magenta    = ~color2 & color1 & color0;
  assign yellow     = color2 & ~color1 & ~color0;
  assign light_cyan = color2 & ~color1 & color0;
  assign light_magenta = color2 & color1 & ~color0;

endmodule
```

Encoders

 

- An encoder encodes which of several inputs is 1
 - Assuming (for now) at most one input is 1 at a time
- What if no input is 1?
 - Separate output to indicate this condition

Encoder Example

- Burglar alarm: encode which zone is active

Zone	Codeword
Zone 1	0, 0, 0
Zone 2	0, 0, 1
Zone 3	0, 1, 0
Zone 4	0, 1, 1
Zone 5	1, 0, 0
Zone 6	1, 0, 1
Zone 7	1, 1, 0
Zone 8	1, 1, 1

Encoder Example

```
module alarm_eqn ( output [2:0] intruder_zone,
                  output      valid,
                  input  [1:8] zone );

  assign intruder_zone[2] = zone[5] | zone[6] |
                             zone[7] | zone[8];
  assign intruder_zone[1] = zone[3] | zone[4] |
                             zone[7] | zone[8];
  assign intruder_zone[0] = zone[2] | zone[4] |
                             zone[6] | zone[8];

  assign valid = zone[1] | zone[2] | zone[3] | zone[4] |
                 zone[5] | zone[6] | zone[7] | zone[8];

endmodule
```

Priority Encoders

- If more than one input can be 1
 - Encode input that is 1 with highest priority

zone								intruder_zone			valid
(1)	(2)	(3)	(4)	(5)	(6)	(7)	(8)	(2)	(1)	(0)	
1	–	–	–	–	–	–	–	0	0	0	1
0	1	–	–	–	–	–	–	0	0	1	1
0	0	1	–	–	–	–	–	0	1	0	1
0	0	0	1	–	–	–	–	0	1	1	1
0	0	0	0	1	–	–	–	1	0	0	1
0	0	0	0	0	1	–	–	1	0	1	1
0	0	0	0	0	0	1	–	1	1	0	1
0	0	0	0	0	0	0	1	1	1	1	1
0	0	0	0	0	0	0	0	–	–	–	0

Priority Encoder Example

```
module alarm_priority_1 ( output [2:0] intruder_zone,
                        output      valid,
                        input  [1:8] zone );

  assign intruder_zone = zone[1] ? 3'b000 :
                        zone[2] ? 3'b001 :
                        zone[3] ? 3'b010 :
                        zone[4] ? 3'b011 :
                        zone[5] ? 3'b100 :
                        zone[6] ? 3'b101 :
                        zone[7] ? 3'b110 :
                        zone[8] ? 3'b111 :
                        3'b000;

  assign valid = zone[1] | zone[2] | zone[3] | zone[4] |
                zone[5] | zone[6] | zone[7] | zone[8];

endmodule
```


BCD Code

- Binary coded decimal
 - 4-bit code for decimal digits

0: 0000	1: 0001	2: 0010	3: 0011	4: 0100
5: 0101	6: 0110	7: 0111	8: 1000	9: 1001

Seven-Segment Decoder

 - Decodes BCD to drive a 7-segment LED or LCD display digit
 - Segments: (g, f, e, d, c, b, a)



0111111	0000110	1011011	1001111	1100110
1101101	1111101	0000111	1111111	1101111


Seven-Segment Decoder

```
module seven_seg_decoder ( output [7:1] seg,  
                           input  [3:0] bcd, input blank );  
  
    reg [7:1] seg_tmp;  
    always @*  
        case (bcd)  
            4'b0000: seg_tmp = 7'b0111111; // 0  
            4'b0001: seg_tmp = 7'b0000110; // 1  
            4'b0010: seg_tmp = 7'b1011011; // 2  
            4'b0011: seg_tmp = 7'b1001111; // 3  
            4'b0100: seg_tmp = 7'b1100110; // 4  
            4'b0101: seg_tmp = 7'b1101101; // 5  
            4'b0110: seg_tmp = 7'b1111101; // 6  
            4'b0111: seg_tmp = 7'b0000111; // 7  
            4'b1000: seg_tmp = 7'b1111111; // 8  
            4'b1001: seg_tmp = 7'b1101111; // 9  
            default: seg_tmp = 7'b1000000; // "-" for invalid code  
        endcase  
    assign seg = blank ? 7'b0000000 : seg_tmp;  
endmodule
```

Multiplexers


- Chooses between data inputs based on the select input

2-to-1 mux

 

sel	z
0	a_0
1	a_1

4-to-1 mux

 

two select bits

sel	z
00	a_0
01	a_1
10	a_2
11	a_3



- N -to-1 multiplexer needs $\lceil \log_2 N \rceil$ select bits

Multiplexer Example

```
module multiplexer_4_to_1 ( output reg      z,  
                           input          [3:0] a,  
                           input          sel );  
  
  always @*  
    case (sel)  
      2'b00: z = a[0];  
      2'b01: z = a[1];  
      2'b10: z = a[2];  
      2'b11: z = a[3];  
    endcase  
endmodule
```

Multi-bit Multiplexers

 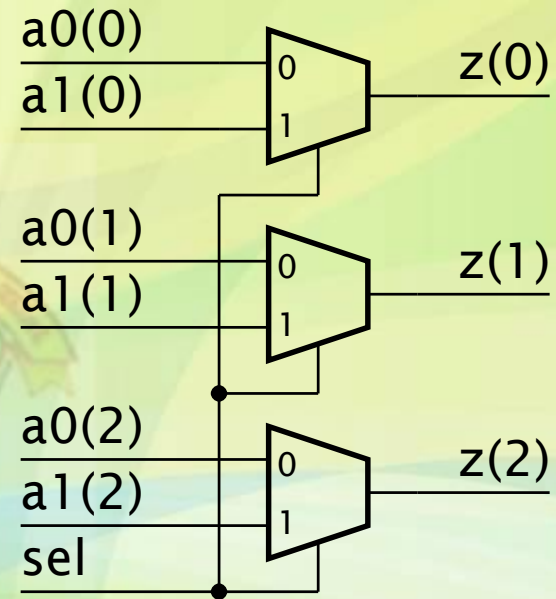- To select between N m -bit codeword inputs
 - Connect m N -input multiplexers in parallel
 - 3-bit 2 codewords requires 3, 2 input multiplexers
- Abstraction
 - Treat this as a component



Multi-bit Mux Example


```
module multiplexer_3bit_2_to_1 ( output [2:0] z,  
                                input  [2:0] a0, a1,  
                                input      sel );  
  
    assign z = sel ? a1 : a0;  
endmodule
```

Active-Low Logic

- We've been using active-high logic
 - 0 (low voltage): falsehood of a condition
 - 1 (high voltage): truth of a condition
- Active-low logic
 - 0 (low voltage): **truth** of a condition
 - 1 (high voltage): **falsehood** of a condition
 - reverses the representation, **not** negative voltage!
- In circuit schematics, label active-low signals with overbar notation
 - eg, $\overline{\text{lamp_lit}}$: low when lit, high when not lit


Active-Low Example

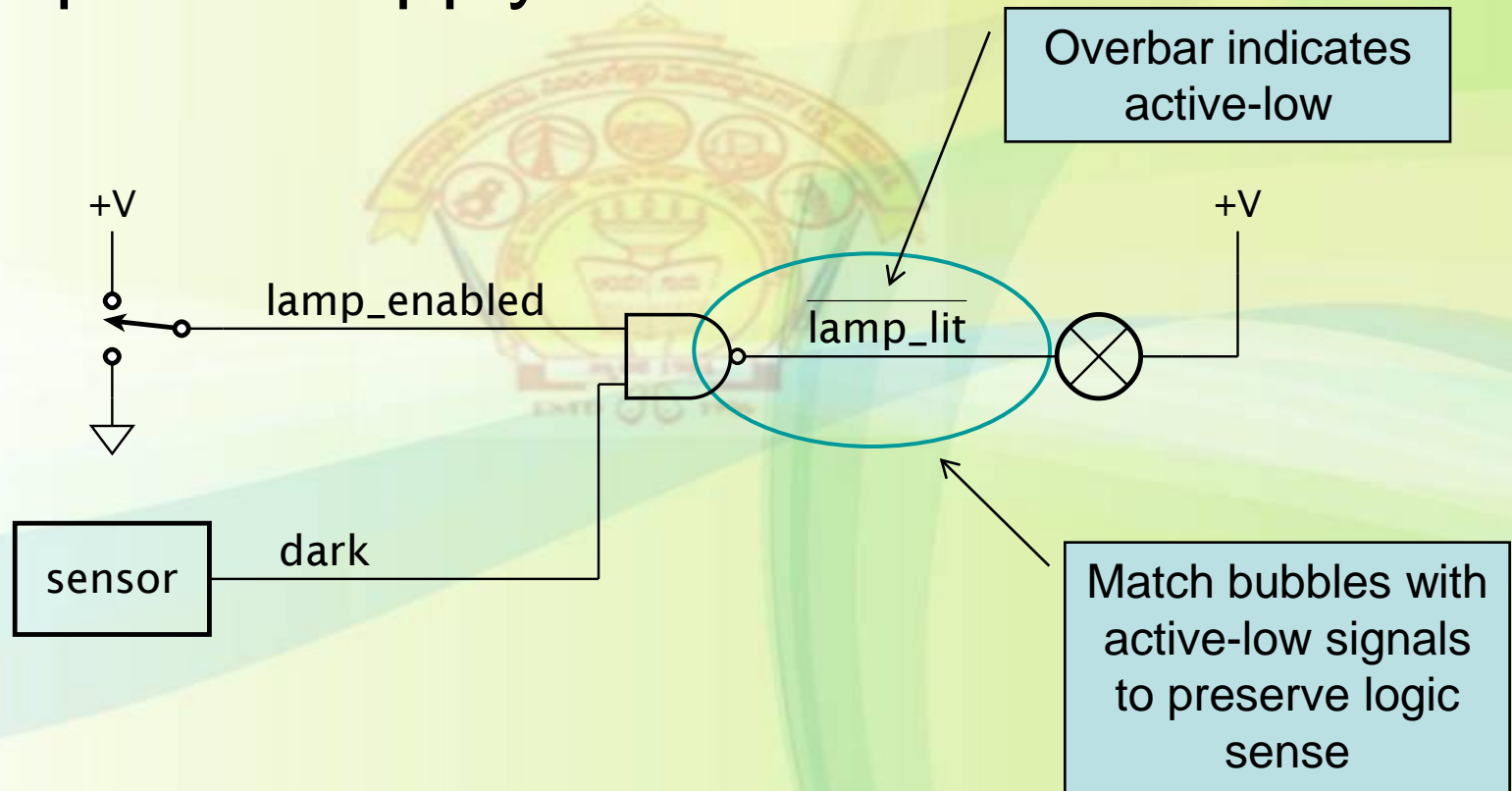- Night-light circuit, lamp connected to power supply



Implied Negation

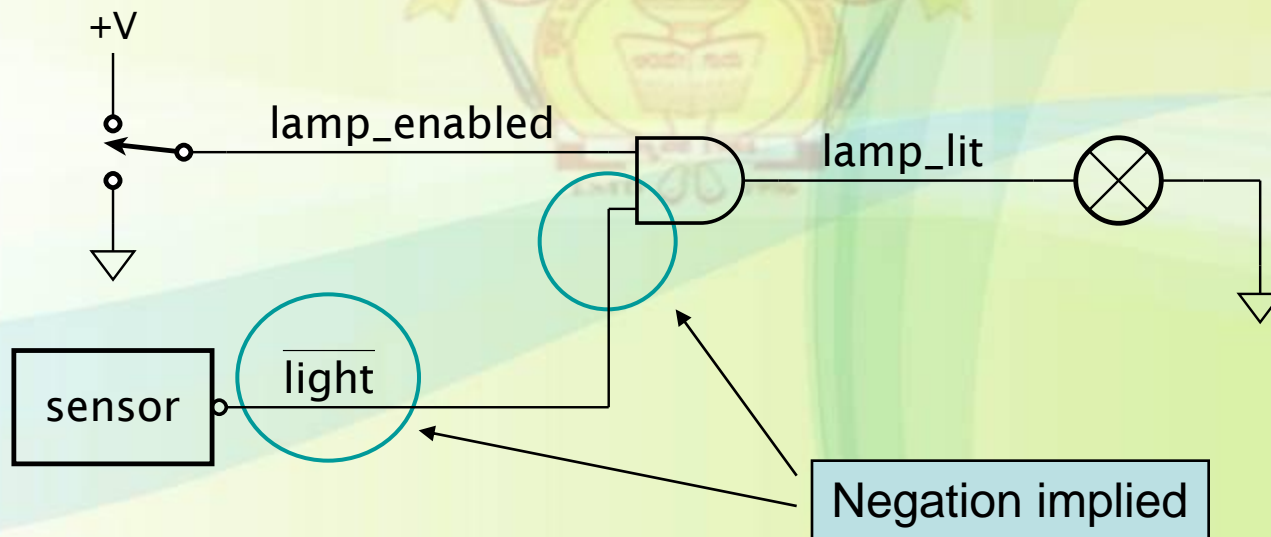- Negation implied by connecting
 - An active-low signal to an active-high input/output
 - An active-high signal to an active-low input/output



Active-Low Signals and Gates




- DeMorgan's laws suggest alternate views for gates
 - They're the same electrical circuit!
 - Use the view that best represents the logical function intended
 - Match the bubbles, unless implied negation is intended

Active-Low Logic in Verilog

- Can't draw an overbar in Verilog
 - Use `_N` suffix on signal or port name
- `1'b0` and `1'b1` in Verilog mean low and high
- For active-low logic
 - `1'b0` means the condition is true
 - `1'b1` means the condition is false
- Example
 - `assign lamp_lit_N = 1'b0;`
 - turns the lamp on

Combinational Verification

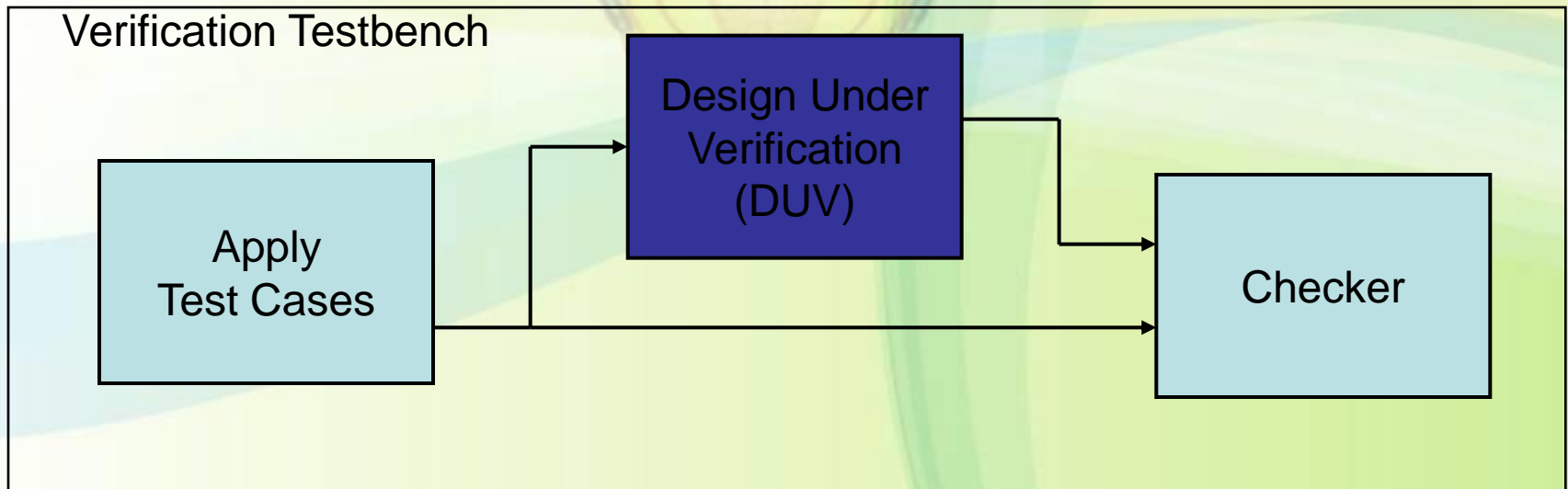- Design Methodology – requirements & constraints
- Combination circuits: outputs are a function of inputs
 - Functional verification: making sure it's the right function!
 - Testbench model
 - DUV /DUT



Verification Example

- Verify operation of traffic-light controller
- Property to check
 - $\text{enable} \Rightarrow \text{lights_out} == \text{lights_in}$
 - $\text{!enable} \Rightarrow$ all lights are inactive
- Represent this as an assertion in the checker

Testbench Module

```
`timescale 1ms/1ms
module light_testbench;
    wire [1:3] lights_out;
    reg  [1:3] lights_in;
    reg          enable;
    light_controller_and_enable duv ( .lights_out(lights_out),
                                     .lights_in(lights_in),
                                     .enable(enable) );
```

Applying Test Cases

```
initial begin  
    enable = 0; lights_in = 3'b000;  
    #1000 enable = 0; lights_in = 3'b001;  
    #1000 enable = 0; lights_in = 3'b010;  
    #1000 enable = 0; lights_in = 3'b100;  
    #1000 enable = 1; lights_in = 3'b001;  
    #1000 enable = 1; lights_in = 3'b010;  
    #1000 enable = 1; lights_in = 3'b100;  
    #1000 enable = 1; lights_in = 3'b000;  
    #1000 enable = 1; lights_in = 3'b111;  
    #1000 $finish;  
end
```

Checking Assertions

```
always @(enable or lights_in) begin
  #10
  if (!( ( enable && lights_out == lights_in) ||
        (!enable && lights_out == 3'b000) ))
    $display("Error in light controller output");
end
endmodule
```

Functional Coverage

- Did we test all possible input cases?
- For large designs, exhaustive testing is not tractable
 - N inputs: number of cases = 2^N
- Functional coverage
 - Proportion of test cases covered by a testbench
 - It can be hard to decide how much testing is enough

Sequential Basics

- Sequential circuits
 - Outputs depend on current inputs and previous inputs
 - Store *state*: an abstraction of the history of inputs
- Usually governed by a periodic clock signal
- Flip flop, registers, counters

Datapaths and Control

- Digital systems perform sequences of operations on encoded data
- *Datapath*
 - Combinational circuits for operations
 - Registers for storing intermediate results
- *Control section: control sequencing*
 - Generates *control signals*
 - Selecting operands
 - Selecting operations to perform
 - Enabling registers at the right times
 - Activate signal at right order & right time
 - Uses *status signals* from datapath
- *Challenging task: requirements & constraints*
 - Functional requirements – alternatives for implementation
 - Tradeoff – area, performance.

Example: Complex Multiplier

- Cartesian form, fixed-point
 - operands: 4 pre-, 12 post-binary-point bits
 - result: 8 pre-, 24 post-binary-point bits


- Subject to tight area constraints

$$a = a_r + ja_i \quad b = b_r + jb_i$$

$$p = ab = p_r + jp_i = (a_r b_r - a_i b_i) + j(a_r b_i + a_i b_r)$$

- 4 multiplies, 1 add, 1 subtract
 - Perform sequentially using 1 multiplier, 1 adder/subtracter

Complex Multiplier Datapath

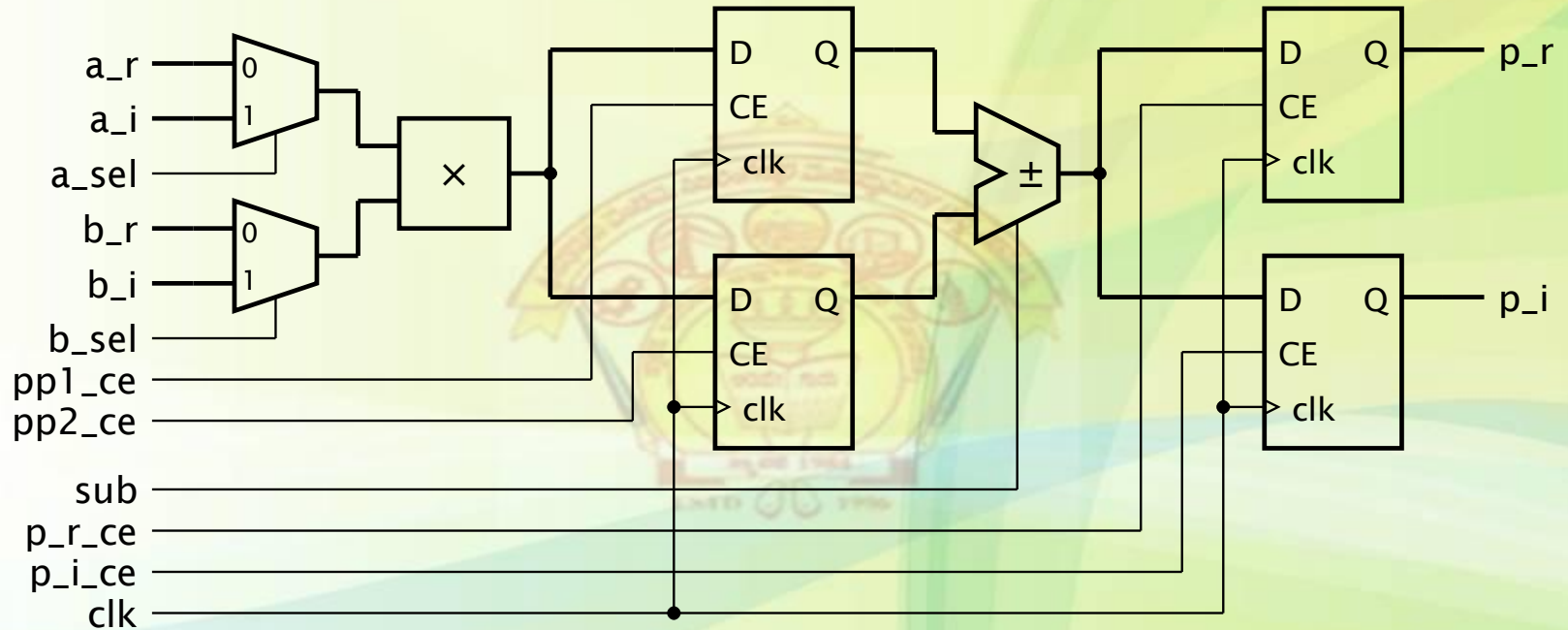

Complex Multiplier in Verilog

```
module multiplier
  ( output reg signed [7:-24] p_r, p_i,
    input  signed [3:-12] a_r, a_i, b_r, b_i,
    input  clk, reset, input_rdy );
  reg a_sel, b_sel, pp1_ce, pp2_ce, sub, p_r_ce, p_i_ce;
  wire signed [3:-12] a_operand, b_operand;
  wire signed [7:-24] pp, sum;
  reg signed [7:-24] pp1, pp2;
  ...

```

Complex Multiplier in Verilog

```
assign a_operand = ~a_sel ? a_r : a_i;
assign b_operand = ~b_sel ? b_r : b_i;
assign pp = {{4{a_operand[3]}}, a_operand, 12'b0} *
           {{4{b_operand[3]}}, b_operand, 12'b0};
always @(posedge clk) // Partial product 1 register
  if (pp1_ce) pp1 <= pp;
always @(posedge clk) // Partial product 2 register
  if (pp2_ce) pp2 <= pp;
assign sum = ~sub ? pp1 + pp2 : pp1 - pp2;
always @(posedge clk) // Product real-part register
  if (p_r_ce) p_r <= sum;
always @(posedge clk) // Product imaginary-part register
  if (p_i_ce) p_i <= sum;
...
endmodule
```

Multiplier Control Sequence

- Avoid resource conflict
- First attempt
 1. $a_r * b_r \rightarrow pp1_reg$
 2. $a_i * b_i \rightarrow pp2_reg$
 3. $pp1 - pp2 \rightarrow p_r_reg$
 4. $a_r * b_i \rightarrow pp1_reg$
 5. $a_i * b_r \rightarrow pp2_reg$
 6. $pp1 + pp2 \rightarrow p_i_reg$
- Takes 6 clock cycles

Multiplier Control Sequence

- Merge steps where no resource conflict
- Revised attempt
 1. $a_r * b_r \rightarrow pp1_reg$
 2. $a_i * b_i \rightarrow pp2_reg$
 3. $pp1 - pp2 \rightarrow p_r_reg$
 $a_r * b_i \rightarrow pp1_reg$
 4. $a_i * b_r \rightarrow pp2_reg$
 5. $pp1 + pp2 \rightarrow p_i_reg$
- Takes 5 clock cycles


Multiplier Control Signals

Step	a_sel	b_sel	pp1_ce	pp2_ce	sub	p_r_ce	p_i_ce
1	0	0	1	0	–	0	0
2	1	1	0	1	–	0	0
3	0	1	1	0	1	1	0
4	1	0	0	1	–	0	0
5	–	–	0	0	0	0	1

Finite-State Machines

- Used to implement control sequencing
 - Based on mathematical automaton theory
- A FSM is defined by
 - set of inputs: Σ
 - set of outputs: Γ
 - set of states: S
 - initial state: $s_0 \in S$
 - transition function: $\delta: S \times \Sigma \rightarrow S$
 - output function: $\omega: S \times \Sigma \rightarrow \Gamma$ or $\omega: S \rightarrow \Gamma$

FSM in Hardware

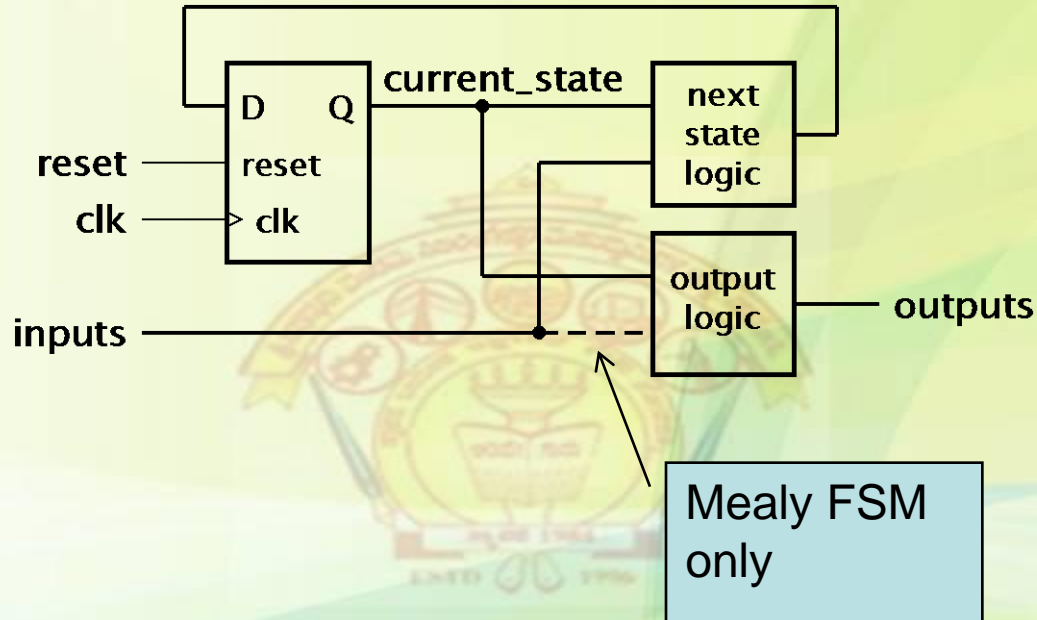

- Mealy FSM: $\omega: S \times \Sigma \rightarrow \Gamma$
- Moore FSM: $\omega: S \rightarrow \Gamma$

FSM Example: Multiplier Control

- One state per step
- Separate idle state?
 - Wait for `input_rdy = 1`
 - Then proceed to steps 1, 2, ...
 - But this wastes a cycle!
- Use step 1 as idle state
 - Repeat step 1 if `input_rdy ≠ 1`
 - Proceed to step 2 otherwise
- Output function
 - Defined by table on slide 43
 - Moore or Mealy?

Transition function

current_ state	input_ rdy	next_ state
step1	0	step1
step1	1	step2
step2	–	step3
step3	–	step4
step4	–	step5
step5	–	step1

State Encoding

- Encoded in binary
 - N states: use at least $\lceil \log_2 N \rceil$ bits
- Encoded value used in circuits for transition and output function
 - encoding affects circuit complexity
- Optimal encoding is hard to find
 - CAD tools can do this well
- One-hot works well in FPGAs
- Often use 000...0 for idle state
 - reset state register to idle

FSMs in Verilog

- Use parameters for state values
 - Synthesis tool can choose an alternative encoding

```
parameter [2:0] step1 = 3'b000, step2 = 3'b001,  
                step3 = 3'b010, step4 = 3'b011,  
                step5 = 3'b100;  
reg [2:0] current_state, next_state ;  
...
```

Multiplier Control in Verilog

```
always @(posedge clk or posedge reset) // State register
  if (reset) current_state <= step1;
  else      current_state <= next_state;
always @* // Next-state logic
  case (current_state)
    step1: if (!input_rdy) next_state = step1;
           else           next_state = step2;
    step2:                next_state = step3;
    step3:                next_state = step4;
    step4:                next_state = step5;
    step5:                next_state = step1;
  endcase
```

Multiplier Control in Verilog


```
always @* begin // Output_logic
  a_sel = 1'b0; b_sel = 1'b0; pp1_ce = 1'b0; pp2_ce = 1'b0;
  sub = 1'b0; p_r_ce = 1'b0; p_i_ce = 1'b0;
  case (current_state)
    step1: begin
      pp1_ce = 1'b1;
    end
    step2: begin
      a_sel = 1'b1; b_sel = 1'b1; pp2_ce = 1'b1;
    end
    step3: begin
      b_sel = 1'b1; pp1_ce = 1'b1;
      sub = 1'b1; p_r_ce = 1'b1;
    end
    step4: begin
      a_sel = 1'b1; pp2_ce = 1'b1;
    end
    step5: begin
      p_i_ce = 1'b1;
    end
  endcase
end
```

State Transition Diagrams

- Bubbles to represent states
- Arcs to represent transitions


■ Example

 - $S = \{s1, s2, s3\}$
- Inputs $(a1, a2)$:
 $\Sigma = \{(0,0), (0,1), (1,0), (1,1)\}$
- δ defined by diagram




State Transition Diagrams

 - Annotate diagram to define output function
 - Annotate states for Moore-style outputs
 - Annotate arcs for Mealy-style outputs
- Example
 - x_1, x_2 : Moore-style
 - y_1, y_2, y_3 : Mealy-style



Multiplier Control Diagram

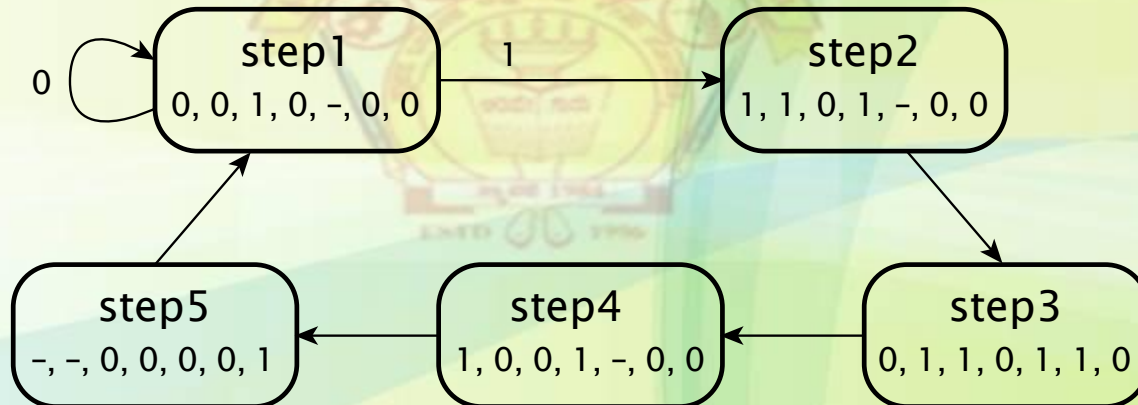- Input: input_rdy
- Outputs
 - a_sel, b_sel, pp1_ce, pp2_ce, sub, p_r_ce, p_i_ce




Bubble Diagrams or Verilog?

- Many CAD tools provide editors for bubble diagrams
 - Automatically generate Verilog for simulation and synthesis
- Diagrams are visually appealing
 - but can become unwieldy for complex FSMs
- Your choice...
 - or your manager's!


Register Transfer Level

 - RTL — a level of abstraction
 - data stored in registers
 - transferred via circuits that operate on data




Clocked Synchronous Timing

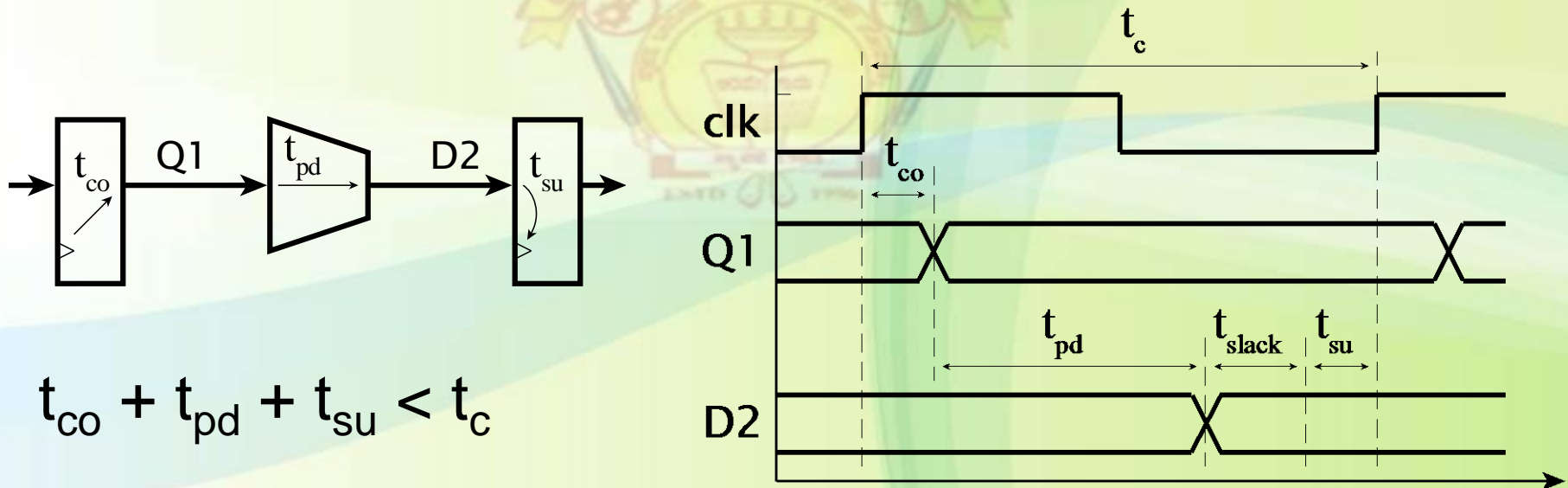- Registers driven by a common clock
 - Combinational circuits operate during clock cycles (between rising clock edges)



Control Path Timing

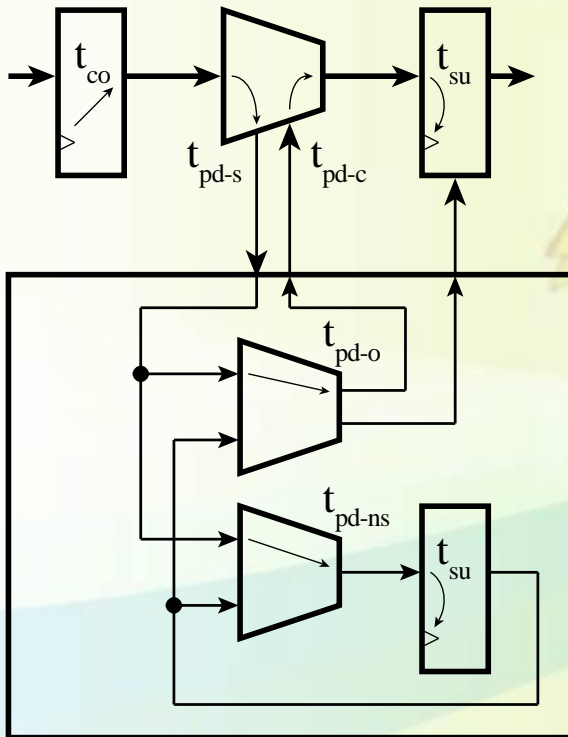

$$t_{co} + t_{pd-s} + t_{pd-o} + t_{pd-c} + t_{su} < t_c$$

$$t_{co} + t_{pd-s} + t_{pd-ns} + t_{su} < t_c$$

Ignore t_{pd-s} for a Moore FSM


Timing Constraints

- Inequalities must hold for all paths
- If t_{co} and t_{su} the same for all paths
 - Combinational delays make the difference
- *Critical path*
 - The combinational path between registers with the longest delay
 - Determines minimum clock period for the entire system
- Focus on it to improve performance
 - Reducing delay may make another path critical

Interpretation of Constraints

1. Clock period depends on delays
 - System can operate at any frequency up to a maximum
 - OK for systems where high performance is not the main requirement
2. Delays must fit within a target clock period
 - Optimize critical paths to reduce delays if necessary
 - May require revising RTL organization

Clock Skew

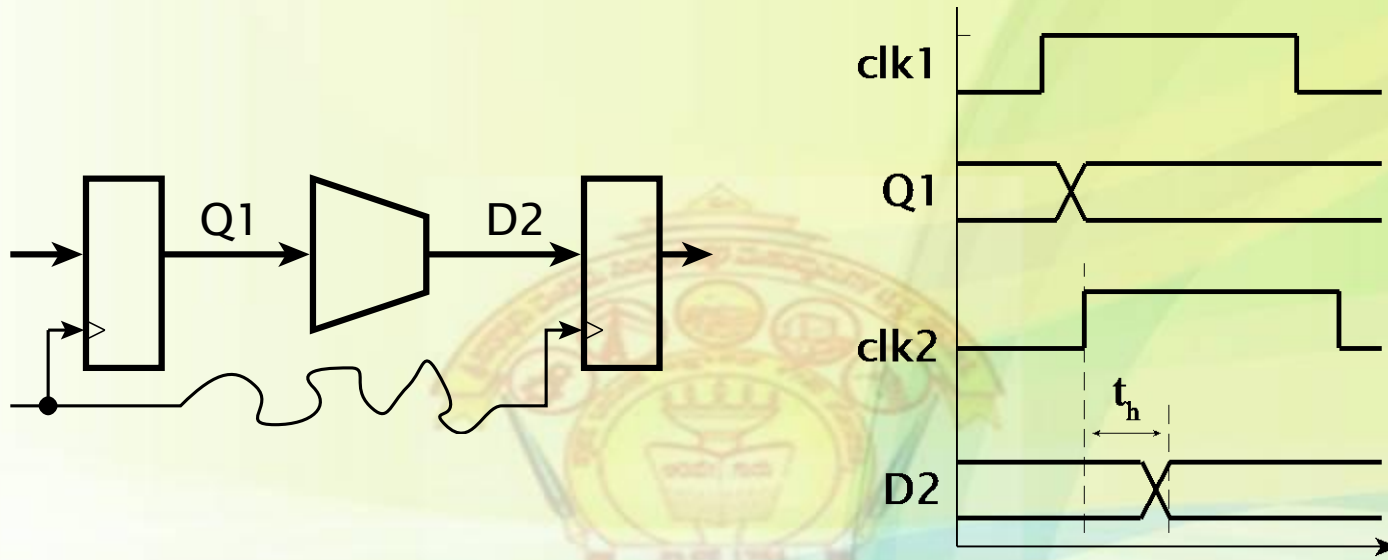

- Need to ensure clock edges arrive at all registers at the same time
 - Use CAD tools to insert clock buffers and route clock signal paths

Off-Chip Connections

- Delays going off-chip and inter-chip
 - Input and output pad delays, wire delays
- Same timing rules apply
 - Use input and output registers to avoid adding external delay to critical path



Asynchronous Inputs

- External inputs can change at any time
 - Might violate setup/hold time constraints
- Can induce *metastable state* in a flipflop




- Unbounded time to recover
 - May violate setup/hold time of subsequent flipflop

$$MTBF = \frac{e^{k_2 t}}{k_1 f_f f_2}$$

$$k_2 \gg 0$$


Synchronizers

 

- If input changes outside setup/hold window
 - Change is simply delayed by one cycle
- If input changes during setup/hold window
 - First flipflop has a whole cycle to resolve metastability
- See data sheets for metastability parameters

Switch Inputs and Debouncing

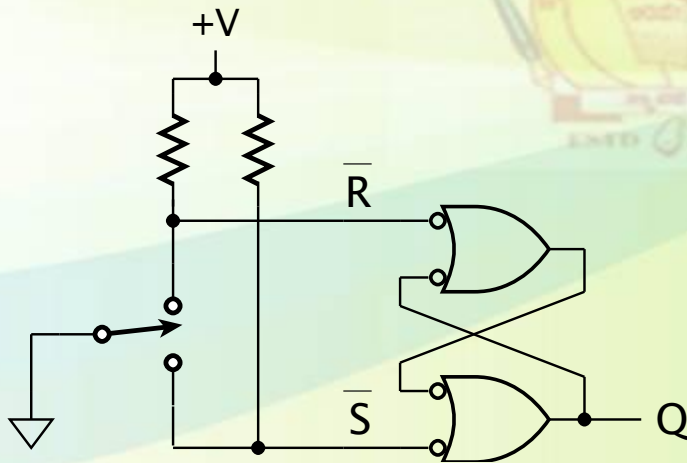
- Switches and push-buttons suffer from contact bounce
 - Takes up to 10ms to settle
- Need to *debounce* to avoid false triggering



- Requires two inputs and two resistors
- Must use a break-before-make double-throw switch

Switch Inputs and Debouncing

 - Alternative
 - Use a single-throw switch
 - Sample input at intervals longer than bounce time
 - Look for two successive samples with the same value



- Assumption

- Extra circuitry inside the chip is cheaper than extra components and connections outside

Queries?

