



S J P N Trust's

Hirasugar Institute of Technology, Nidasoshi.

Inculcating Values, Promoting Prosperity

Approved by AICTE, Recognized by Govt. of Karnataka and Affiliated to VTU Belagavi

ECE Dept.

DSDV

VI Sem

2017-18

Department of Electronics & Communication Engg.

Course : Digital System Design using Verilog.

Sem.: 6th (2017-18)

Course Coordinator:

Prof. D. M. Kumbhar

Digital System Design Using Verilog



Module 4 I/O Interfacing


Portions of this work are from the book, *Digital Design: An Embedded Systems Approach Using Verilog*, by Peter J. Ashenden, published by Morgan Kaufmann Publishers, Copyright 2007 Elsevier Inc. All rights reserved.

I/O Devices and Transducers

- Transducers convert between real-world effects and digital representation
 - Input transducers: sensors
 - May require analog-to-digital converter (ADC)
 - Output transducers: actuators
 - May require digital-to-analog converter (DAC)
- Human-interface devices
 - Buttons, switches, knobs, keypads, mouse
 - Indicators, displays, speakers

Keypads & Keyboards

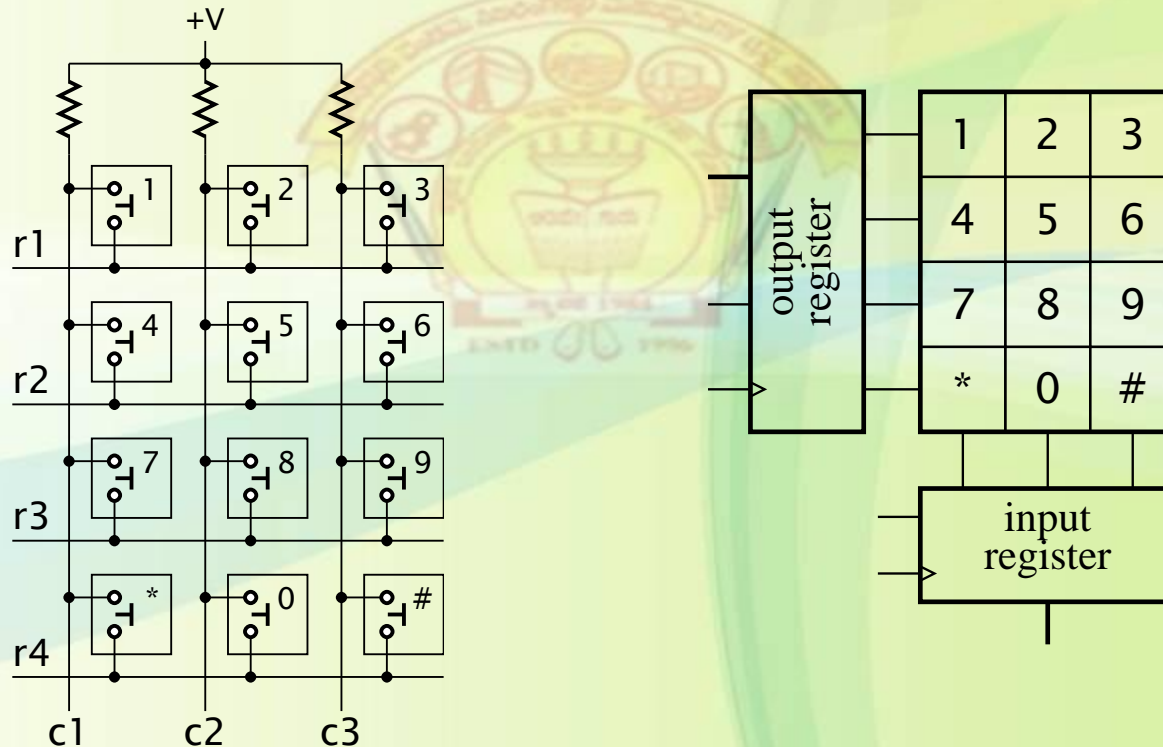- Recall switches and debouncing
- Keypad: array of push-button switches







Knobs & Position Encoders

- In analog circuits, use a variable resistor
- In digital circuits, could use pushbuttons
 - E.g., volume up/down
 - Not as easy to use as knobs or sliders
- Can use a position encoder attached to a knob
 - Recall Gray code encoder

Incremental Encoder

   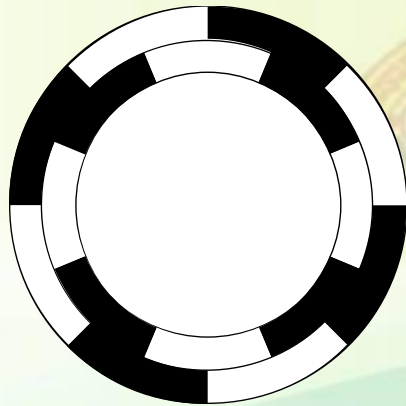- If absolute position is not important, incremental encoder is simpler




Analog Inputs


- Physical effect produces an analog voltage or current
- Microphone
 - In phones, cameras, voice recorders, ...
- Accelerometer
 - In airbag controllers
- Fluid-flow sensors
 - In industrial machines, coffee machines, ...
- Gas detectors
 - In safety equipment

Analog-to-Digital Converters

 - Basic element:
analog comparator
- Flash ADC
 - For n o/p $2^n - 1$ comparators
 - Simple, fast, but uses many comparators
- Resolution
 - Number of output bits




Successive Approximation ADC

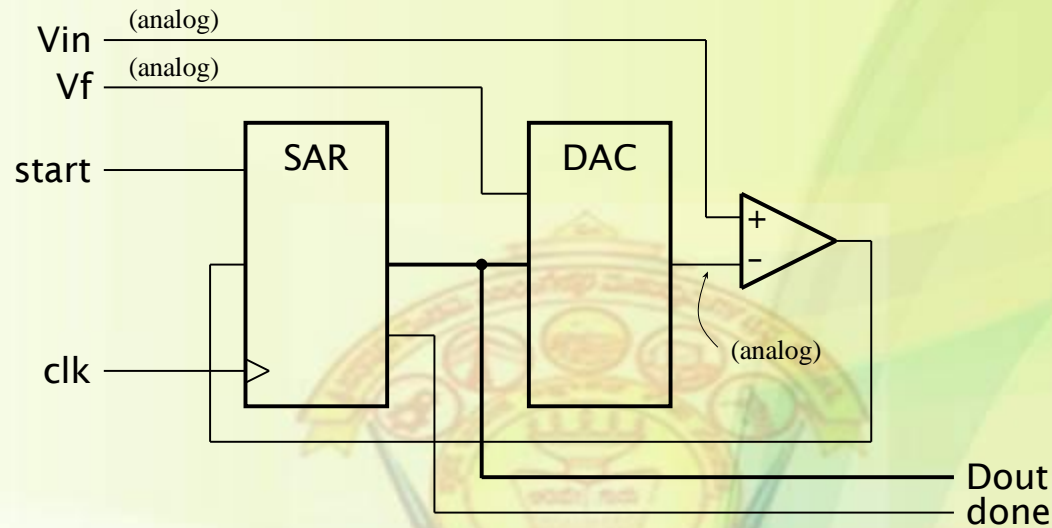

- Initial approximation: 01111111
 - Comparator output gives d_7
 - 1 if V_{in} is higher than 01111111, 0 otherwise
- Next approximation: d_7 01111111
 - Comparator output gives d_6
- Next approximation: d_7d_6 01111111, etc

LED Indicators

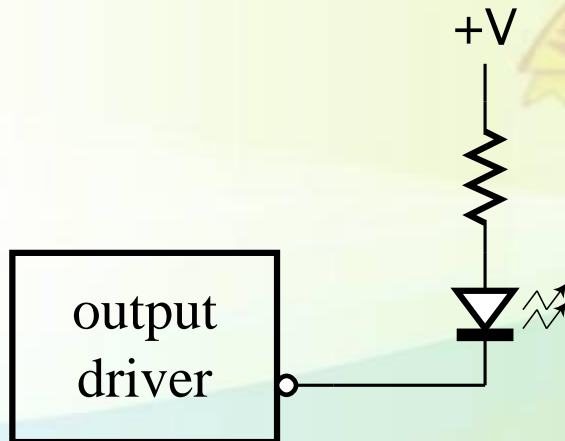
- Single LED shows 1-bit state
 - On/off, busy/ready, error/ok, ...



- Brightness depends on current
 - Determined by resistor
 - $I = (+V - V_{LED} - V_{OL}) / R$

7-Segment LED Displays

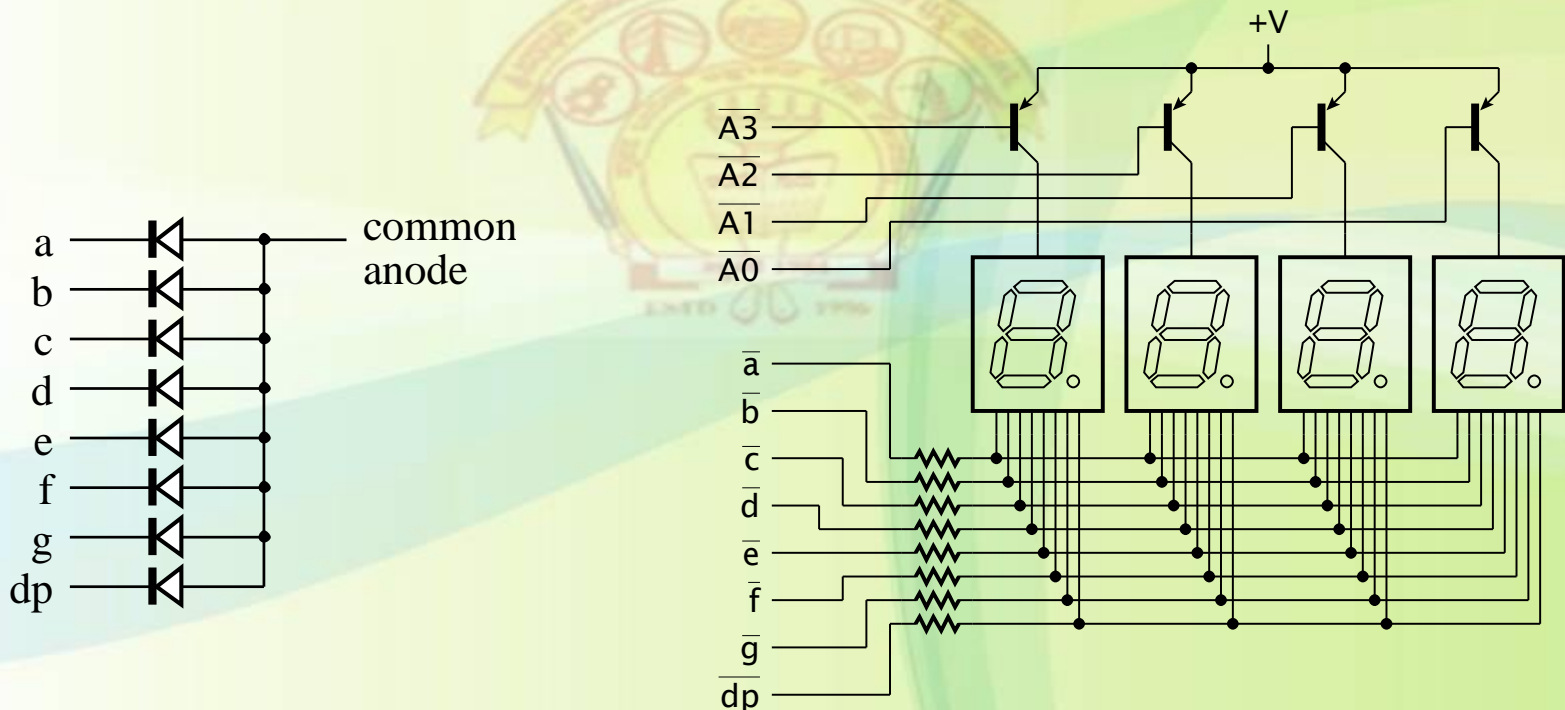- Each digit has common anodes or common cathodes
 - Scan: turn on one digit at a time



Example: Multiplexed Display

- Four BDC inputs, 10MHz clock
 - Turn on decimal point of leftmost digit only
 - 50Hz scan cycle (200Hz scan clock)

```
module display_mux ( output reg [3:0] anode_n,  
                    output [7:0] segment_n,  
                    input [3:0] bcd0, bcd1, bcd2, bcd3,  
                    input clk, reset );  
  
parameter clk_freq = 10000000;  
parameter scan_clk_freq = 200;  
parameter clk_divisor = clk_freq / scan_clk_freq;  
  
reg scan_clk;  
reg [1:0] digit_sel;  
reg [3:0] bcd;  
reg [7:0] segment;  
  
integer count;
```

Example: Multiplexed Display

```
// Divide master clock to get scan clock
always @(posedge clk)
  if (reset) begin
    count = 0;
    scan_clk <= 1'b0;
  end
  else if (count == clk_divisor - 1) begin
    count = 0;
    scan_clk <= 1'b1;
  end
  else begin
    count = count + 1;
    scan_clk <= 1'b0;
  end
end

// increment digit counter once per scan clock cycle
always @(posedge clk)
  if (reset) digit_sel <= 2'b00;
  else if (scan_clk) digit_sel <= digit_sel + 1;
```

Example: Multiplexed Display

```
// multiplexer to select a BCD digit
always @*
  case (digit_sel)
    2'b00: bcd = bcd0;
    2'b01: bcd = bcd1;
    2'b10: bcd = bcd2;
    2'b11: bcd = bcd3;
  endcase

// activate selected digit's anode
always @*
  case (digit_sel)
    2'b00: anode_n = 4'b1110;
    2'b01: anode_n = 4'b1101;
    2'b10: anode_n = 4'b1011;
    2'b11: anode_n = 4'b0111;
  endcase
```

Example: Multiplexed Display

```
// 7-segment decoder for selected digit
always @*
  case (bcd)
    4'b0000: segment[6:0] = 7'b0111111; // 0
    4'b0001: segment[6:0] = 7'b0000110; // 1
    4'b0010: segment[6:0] = 7'b1011011; // 2
    4'b0011: segment[6:0] = 7'b1001111; // 3
    4'b0100: segment[6:0] = 7'b1100110; // 4
    4'b0101: segment[6:0] = 7'b1101101; // 5
    4'b0110: segment[6:0] = 7'b1111101; // 6
    4'b0111: segment[6:0] = 7'b0000111; // 7
    4'b1000: segment[6:0] = 7'b1111111; // 8
    4'b1001: segment[6:0] = 7'b1101111; // 9
    default: segment[6:0] = 7'b1000000; // "-"
  endcase
```

Example: Multiplexed Display

```
// decimal point is only active for digit 3
always @* segment[7] = digit_sel == 2'b11;

// segment outputs are negative logic
assign segment_n = ~segment;

endmodule
```




Liquid Crystal Displays (LCDs)

- Advantages
 - Low power
 - Readable in bright ambient light conditions
 - Custom segment shapes
- Disadvantages
 - Require backlight for dark conditions
 - Not as robust as LEDs
- LCD panels
 - Rectangular array of pixels
 - Can be used for alphanumeric/graphical display
 - Controlled by a small microcontroller


Actuators & Valves

 - Actuators cause a mechanical effect
- Solenoid: current in coil moves armature
 - Can attach rods, levers, etc to translate the movement
- Solenoid valve
 - Armature controls fluid or gas valve
- Relay
 - Armature controls electrical contacts



Motors

 - Can provide angular position or speed
 - Use gears, screws, etc to convert to linear position or speed
- Stepper motors
 - Rotate in discrete steps




Motors

- Servo-motors
 - DC motor, speed controlled by varying the drive voltage
 - Use feedback to control the speed or to drive to a desired position
 - Requires a position sensor or tachometer
- Servo-controller
 - A digital circuit or an embedded processor
 - Compensates for non-ideal mechanical effects


Digital-to-Analog Converters

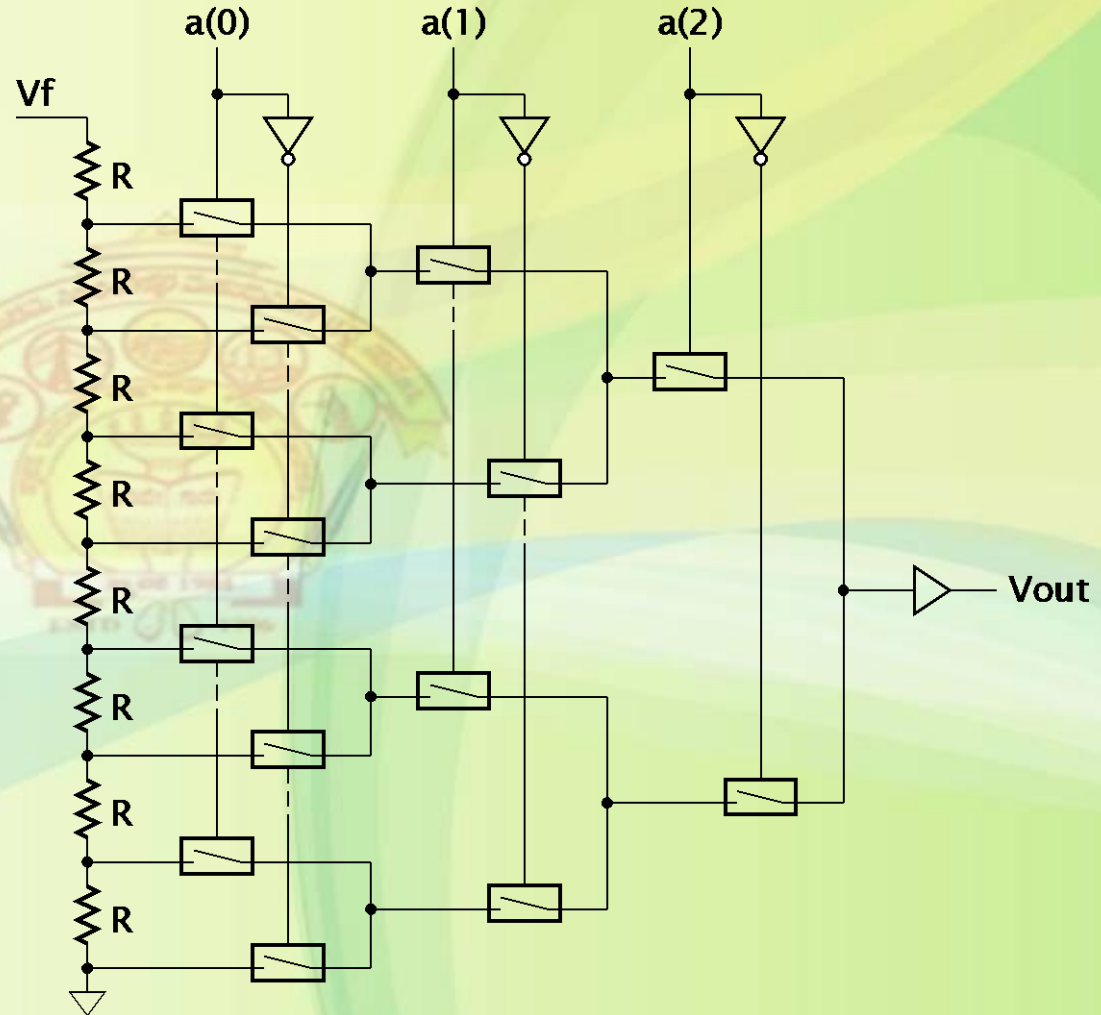- R-string DAC
 - Voltage divider and analog multiplexer
 - Requires 2^n precision resistors



Digital-to-Analog Converters

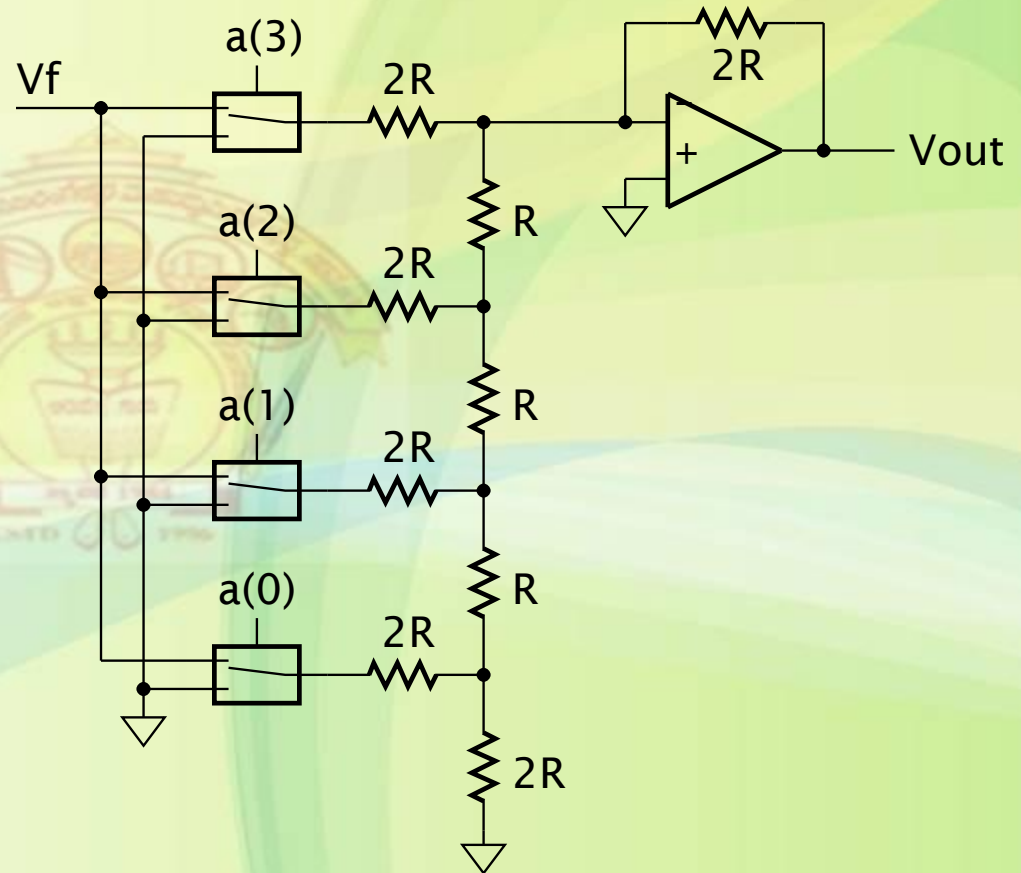- R-2R ladder DAC
 - Sums binary-weighted currents
 - Requires $2n$ matched resistors



I/O Controllers

- An embedded processor needs to access input/output data
- I/O controller
 - Circuit that connects I/O device to a processor
 - Includes control circuits
 - Input registers: for reading data
 - Output registers: for writing data
- I/O ports
 - Registers accessible to embedded software


Simple I/O Controller

- Just contains input and/or output registers
 - Select among them using a port address

```
module gumnut ( input      clk_i,  
                input      rst_i,  
                ...  
                output     port_cyc_o,  
                output     port_stb_o,  
                output     port_we_o,  
                input      port_ack_i,  
                output [7:0] port_adr_o,  
                output [7:0] port_dat_o,  
                input  [7:0] port_dat_i,  
                ... );  
  
endmodule
```

 
Example: Keypad Controller

- Output register for row drivers
- Input register for column sensing



Example: Keypad Controller

```
module keypad_controller ( input          clk_i,
                          input          cyc_i,
                          input          stb_i,
                          input          we_i,
                          output         ack_o,
                          input [7:0]    dat_i,
                          output reg [7:0] dat_o,
                          output reg [3:0] keypad_row,
                          input [2:0]    keypad_col );

    reg [2:0] col_synch;

    always @(posedge clk_i) // Row register
        if (cyc_i && stb_i && we_i) keypad_row <= dat_i[3:0];

    always @(posedge clk_i) begin // Column synchronizer
        dat_o      <= {5'b0, col_synch};
        col_synch <= keypad_col;
    end

    assign ack_o = cyc_i && stb_i;
endmodule
```


Control/Status Registers

- Control register
 - Contains bits that govern operation of the I/O device
 - Written by processor
- Status register
 - Contains bits that reflect status of device
 - Read by processor
- Either or both may be needed in an input or output controller

Example: ADC Controller

- Successive approximation ADC
 - 1 × analog input with sample/hold
 - 4 × analog reference voltages
- Control register
 - Selects reference voltage
 - Hold input voltage & start ADC
- Status register
 - Is conversion done?
- Input data register
 - Converted data

Example: ADC Controller

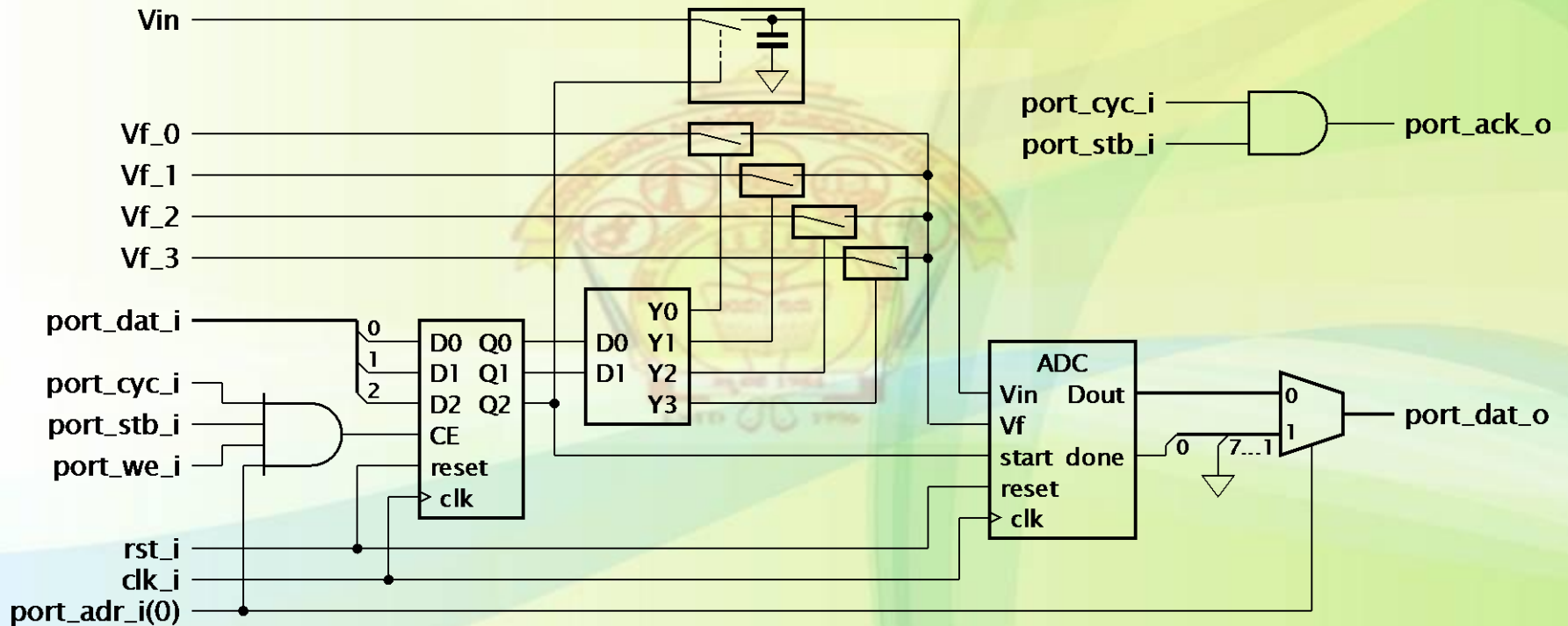

Autonomous I/O Controllers

- Independently sequence operation of a device
 - Processor initiates actions
 - Controller notifies processor of events, such as data availability, error condition, ...
- Processor can perform other operations concurrently
- Device operation not limited by processor performance or load

Example: LCD Module


- Rectangular array of pixels
 - Row and column connections
 - Controller scans rows, activates columns
- Image or character data stored in a small memory in the controller
 - Updated by an attached processor

Direct Memory Access (DMA)

- For high-speed input or output
 - Processor writes starting address to a control register
 - Controller transfers data to/from memory autonomously
 - Notifies processor on completion/error
- Reduces load on processor
- Common with accelerators



Parallel Buses

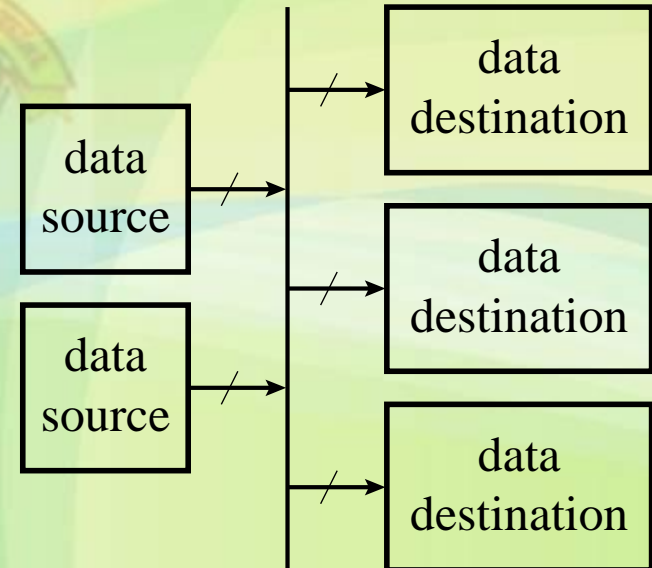- Interconnect components in a system
 - Transfer bits of data in parallel
- Conceptual structure
 - All inputs and output connected
- In practice
 - Can't tie multiple outputs together



Multiplexed Buses

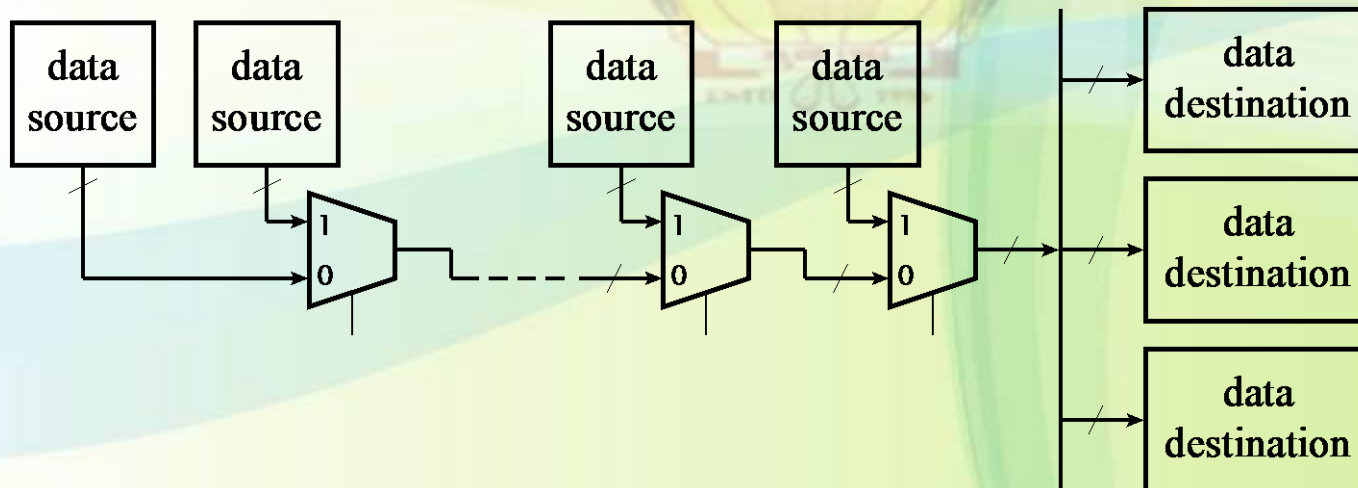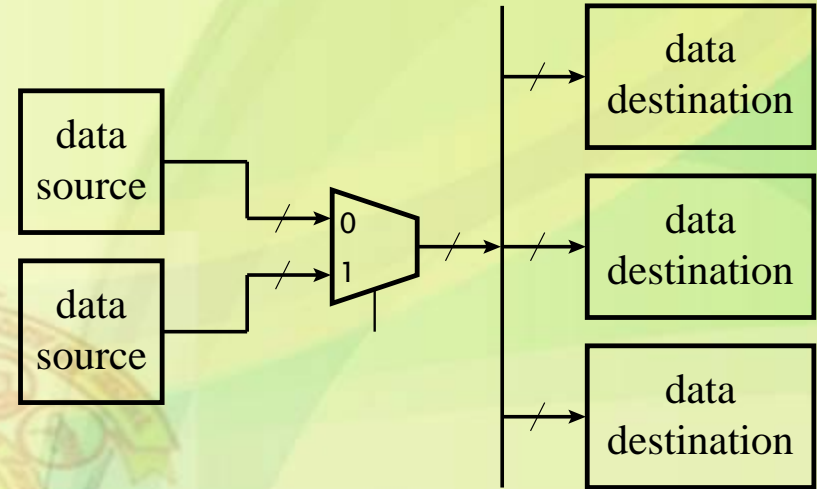
- Use multiplexer(s) to select among data sources
 - Can partition to aid placement on chip



Example: Wishbone Bus



- Non-proprietary bus spec
 - OpenCores Organization
- Gumnut uses simple form of Wishbone
 - One bus for each of instruction memory, data memory, and I/O ports
 - “..._o” denotes output
 - “..._i” denotes input

Example: Wishbone Bus

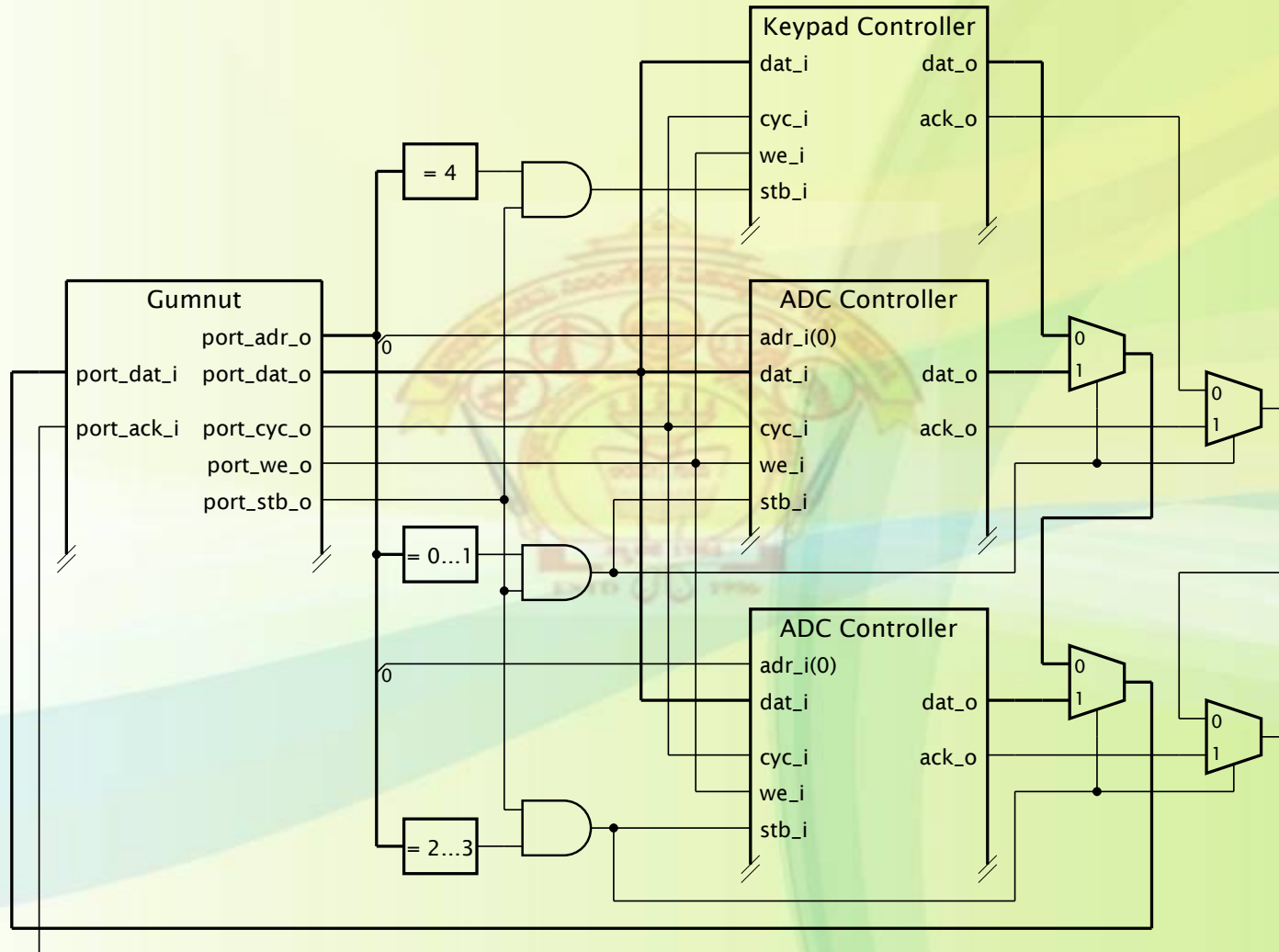



Tristate Buses

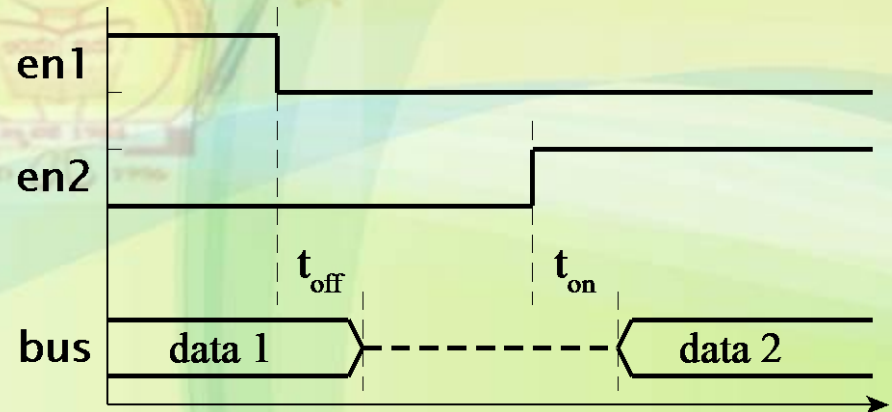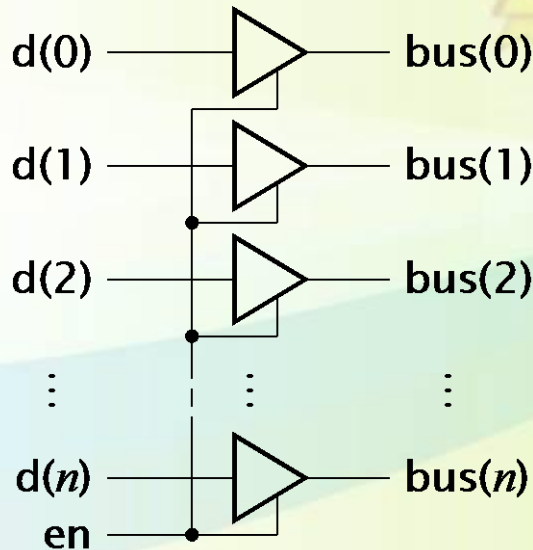- Use tristate drivers for data sources
 - Can “turn-off” (Hi-Z) when not supplying data
- Simplified bus wiring



Tristate Bus Issues

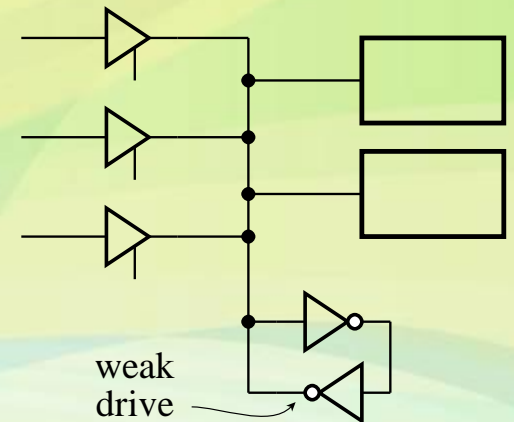 - Floating bus can cause spurious switching
 - Use pull-up resistors or weak keepers
- Need to avoid driver contention
 - Dead cycle between turn-off and turn-on
 - Or delayed enable




- Not all CAD tools and implementation fabrics support tristate buses

Tristate Drivers in Verilog

- Assign Z to an output to turn driver off
- Example: single-bit driver
 - `assign d_out = d_en ? d_in : 1'bZ;`
- Example: multi-bit driver
 - `assign bus_o = dat_en ? dat : 8'bZ;`
- Any other driver contributing 0 or 1 overrides Z value

Example: SN74x16541

 


Same as wire,
but indicates
tristate driver

```
module sn74x16541 ( output tri [7:0] y1, y2,  
                    input [7:0] a1, a2,  
                    input en1_1,  
                          en1_2,  
                          en2_1,  
                          en2_2 );  
    assign y1 = (~en1_1 & ~en1_2) ? a1 : 8'bz;  
    assign y2 = (~en2_1 & ~en2_2) ? a2 : 8'bz;  
endmodule
```



Unknown Values in Verilog

- What if two drivers are turned on?
 - One driving 0, the other driving 1
 - Resolved value is X — unknown
 - Can test for X during simulation
 - Use === and !== operators
 - C.f. == and !=, which are logical equivalence and inequivalence tests
- Z and X are not electrical logic levels
 - Notations for simulation and synthesis
 - Real logic levels are only 0 or 1

Open-Drain Buses

 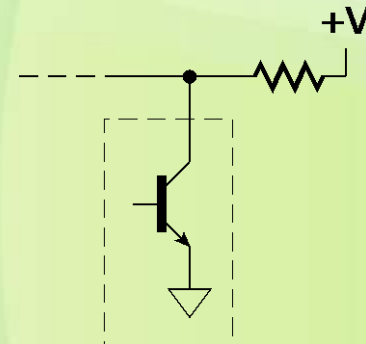

- Bus is 0 if any driver pulls it low
- If all drivers are off, bus is pulled high
 - Wired-AND
- Can also use open-collector drivers



Open-Drain Drivers in Verilog

- Assign 0 or 1 to model driver
- Model pull-up on open-drain bus using **wand** net
 - `wand bus_sig;`
 - Resolved value is logical AND of driver values


Bus Protocols

- Specification of signals, timing, and sequencing of bus operations
 - Allows independent design of components
 - Ensures interoperability
- Standard bus protocols
 - PCI, VXI, ...
 - For connecting boards in a system
 - AMBA (ARM), CoreConnect (IBM), Wishbone (Open Cores)
 - For connecting blocks within a chip


Example: Gumnut Wishbone

- Minimal 8-bit subset used for I/O ports
- Signals
 - port_cyc_o: “cycle” control for sequence of port operations
 - port_stb_o: “strobe” control for an operation
 - port_we_o: write enable
 - port_ack_i: acknowledge from addressed port
 - port_adr_o: 8-bit port address
 - port_dat_o: 8-bit data output from Gumnut
 - port_dat_i: 8-bit data input to Gumnut

Gumnut Wishbone Write

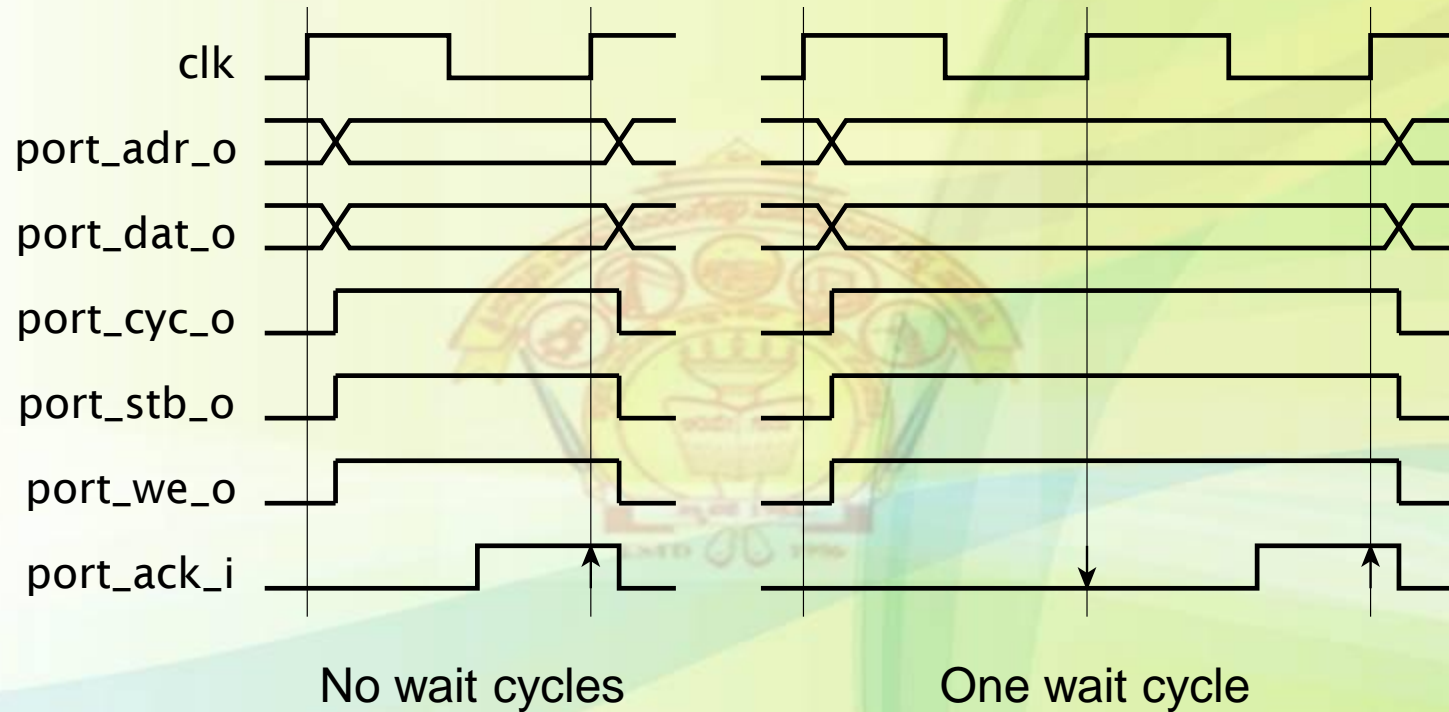



Gumnut Wishbone Read

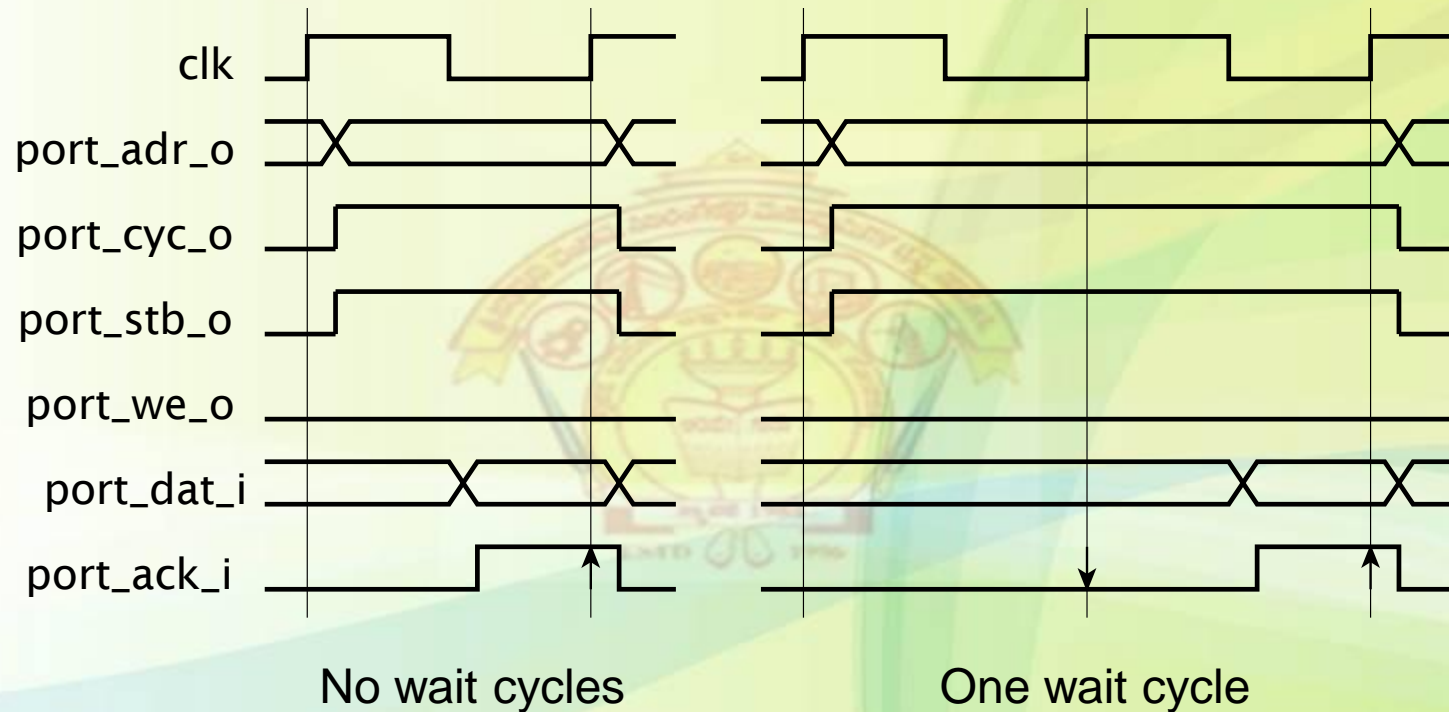

Serial Transmission

- Bits transmitted one after another on a single wire
 - Can afford to optimize the wire for speed
- C.f. parallel transmission, one wire per bit
 - Requires more wires
 - Cost per wire, greater area for wiring, complexity of place & route
 - Requires more pins
 - Cost of larger package
 - Other effects
 - Crosstalk, skew, delay due to increased area
- Serializer/deserializer (serdes)
 - Converts between parallel and serial form


Example: 64-bit Serdes

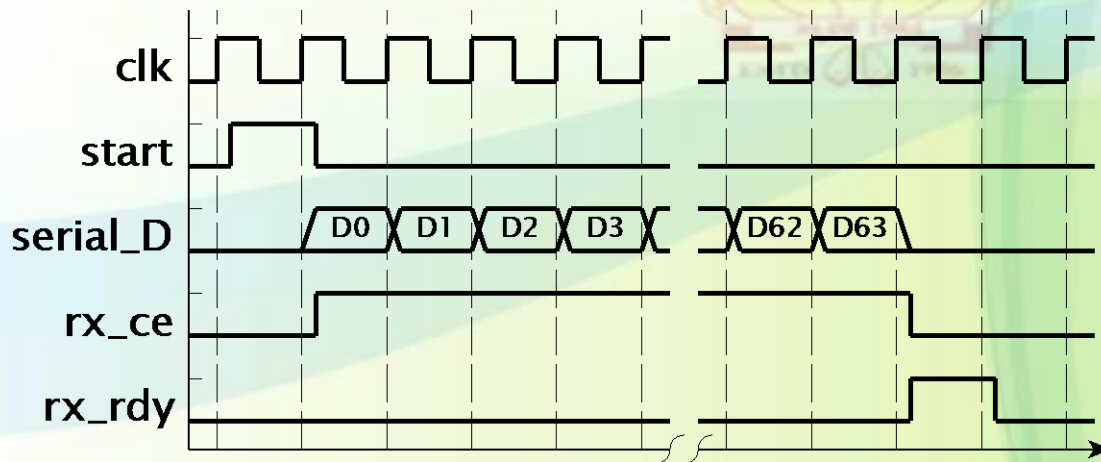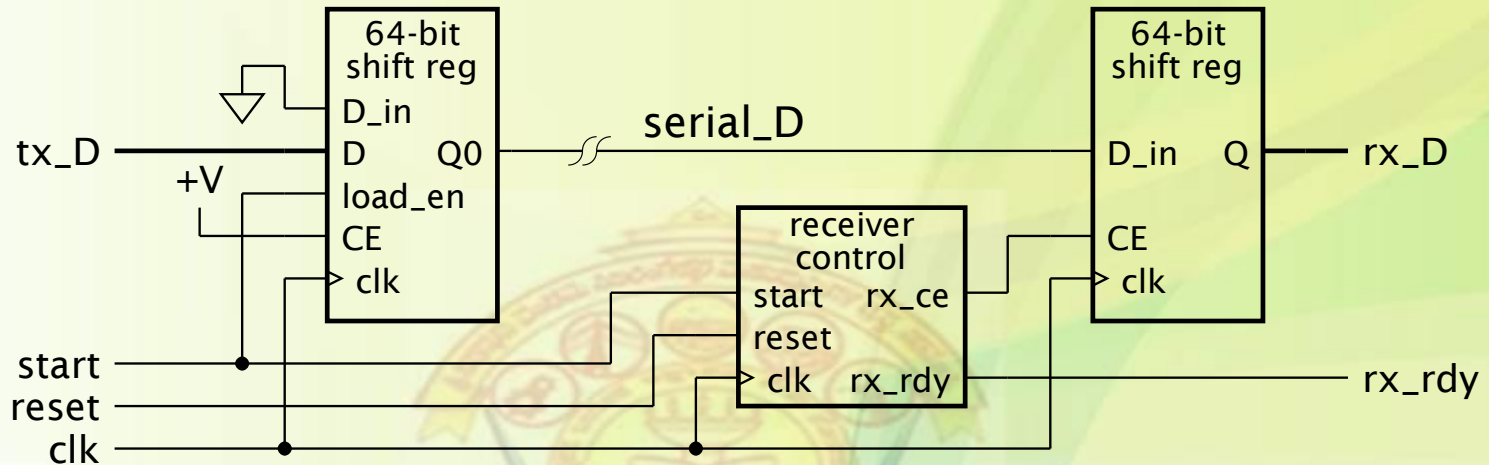

- Bit order is arbitrary, provided both ends agree
 - Often specified by standards⁴⁹


NRZ Transmission

 - Non-Return to Zero
 - Just set signal to high or low for each bit time
 - No indication of boundary between bit times
 - Need to synchronize transmitter and receiver separately
 - E.g., by a common clock and control signals, as in previous example




Start/Stop Bit Synchronization

 - Hold signal high when there is no data
- To transmit
 - Drive signal low for one bit time (start bit)
 - Then drive successive data bits
 - Then drive signal high for one bit time (stop bit)




UARTs

 - Universal Asynchronous Receiver/Transmitter
 - Common I/O controller for serial transmission using NRZ with start/stop bits
 - Relies on Tx and Rx clocks being approximately the same frequency




Manchester Encoding

 - Combine Tx clock with Tx data
 - Ensures regular edges in the serial signal
- Example: Manchester encoding
 - Transition in the middle of each bit time
 - 0: low-to-high transition
 - 1: high-to-low transition
 - May need a transition at the start of a bit time



Clock Recovery

 - Transmitter sends preamble before data
 - A sequence of encoded 1 bits
 - Serial signal then matches Tx clock
- Receiver uses a phase-locked loop (PLL) to match Rx clock to Tx clock



Serial Interface Standards


- Connection of I/O devices to computers
- Connection of computers in networks
- Use of standards reduces design effort
 - Reuse off-the-shelf components or IP
- RS-232: NRZ, start/stop bits
 - Originally for modems, now widely used for low-bandwidth I/O

Serial Interface Standards

- I²C: Inter-Integrated Circuit bus
 - 2 wires (NRZ data, clock), open drain
 - Simple protocol, low cost, 10kb/s–3.4Mb/s
- USB: Universal Serial Bus
 - For connecting I/O devices to computers
 - Differential signaling on 2 wires
 - 1.5Mb/s, 12Mb/s, 480Mb/s, ..., complex protocol
 - IP blocks available
- FireWire: IEEE Std 1394
 - 2 differential pairs (data, synch)
 - 400Mb/s, 3.2Gb/s, complex protocol

I²C Example: Temperature Sensor

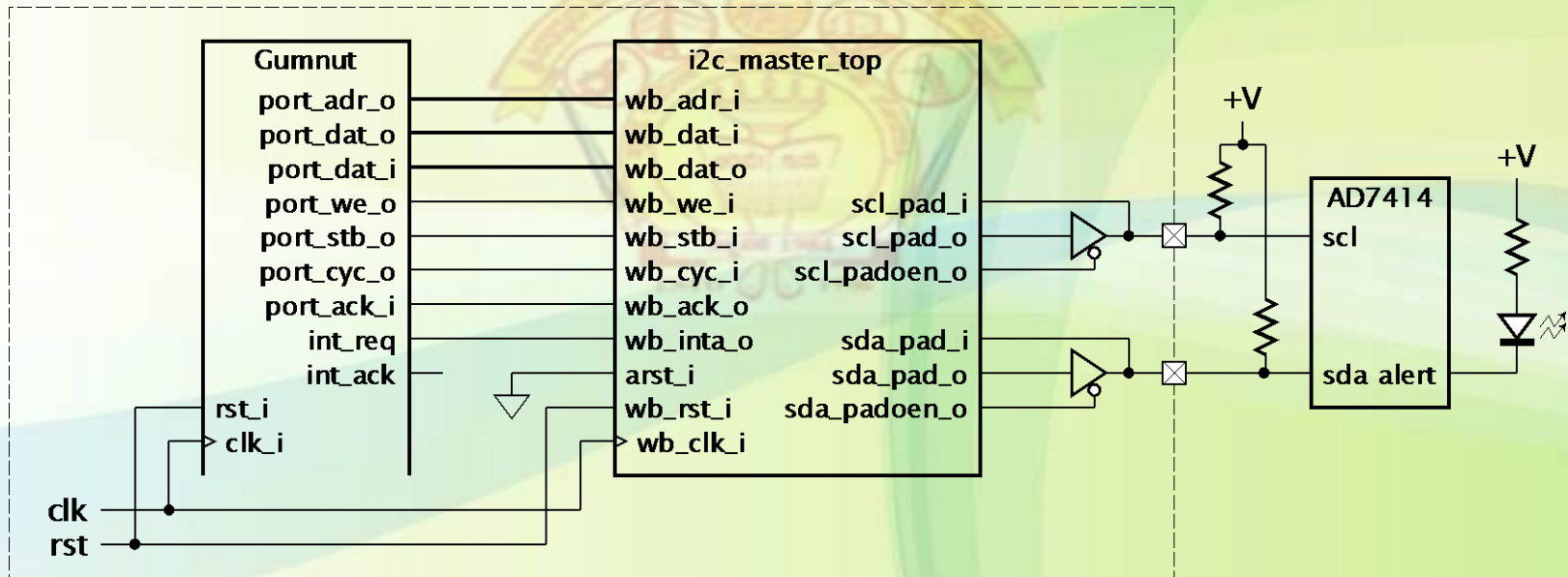- Gumnut, Analog Devices AD7414
 - I²C controller IP from OpenCores repository



I/O Software

- Use input and output instructions to access I/O controller registers
- I/O devices interact with the physical world
 - Software must respond to events when they occur
 - It must be able schedule activity at specific times or at regular intervals
 - *Real-time* behavior

Polling

- Software repeatedly reads I/O status to see if an event has occurred
 - If so, it performs the required action
- Multiple controllers
 - Software executes a polling loop, checking controllers in turn
- Advantage: simple I/O controllers
- Disadvantages
 - Processor is continually busy, consuming power
 - Delay in dealing with an event if processor is busy with another event

Polling Example

- Safety monitor in factory automation
 - Gumnut core
 - 16 alarm inputs
 - One per bit in registers at addresses 16 & 17
 - 0 \Rightarrow ok, 1 \Rightarrow abnormal condition
 - Temp sensor ADC at address 20
 - 8-bit binary code for $^{\circ}\text{C}$
 - Above 50°C is abnormal
 - Alarm output at address 40
 - 0 \Rightarrow ok, 1 \Rightarrow ring alarm bell

Polling Example

```
alarm_in_1: equ 16      ; address of alarm_in_1 input register
alarm_in_2: equ 17      ; address of alarm_in_2 input register
temp_in:    equ 20      ; address of temp_in input register
alarm_out:  equ 40      ; address of alarm_out output register
max_temp:   equ 50      ; maximum permissible temperature

poll_loop:  inp  r1, alarm_in_1
            sub  r0, r1, 0
            bnz  set_alarm ; one or more alarm_in_1 bits set
            inp  r1, alarm_in_2
            sub  r0, r1, 0
            bnz  set_alarm ; one or more alarm_in_2 bits set
            inp  r1, temp_in
            sub  r0, r1, max_temp
            bnc  set_alarm ; temp_in > max_temp
            out  r0, alarm_out ; clear alarm_out
            jmp  poll_loop

set_alarm:  add  r1, r0, 1
            out  r1, alarm_out ; set alarm_out bit 1 to 1
            jmp  poll_loop
```

Interrupts

- I/O controller notifies processor when an event occurs
 - Processor interrupts what it was doing
 - Executes interrupt service routine
 - A.k.a. interrupt handler
 - Then resumes interrupted task
 - May enter low-power standby
- Some systems prioritize interrupt requests
 - Allow higher priority events to interrupt service of lower priority events

Interrupt Mechanisms

- Interrupt request signal
- Means of disabling/enabling interrupts
 - So processor can execute *critical regions*
- Save processor state on an interrupt
 - So interrupted task can be resumed
- On interrupt, disable further interrupts
 - Until processor has saved state
- Find the handler code for the event
 - *Vector*: address of handler, or index into table of handler addresses
- Instruction to return from handler
 - Restoring saved state

Gumnut Interrupt Mechanisms


- `int_req` signal
- `disi` and `enai` instructions
- On interrupt, PC, Z, and C saved in special registers
- On interrupt, further interrupts are disabled
- Handler code starts at address 1
 - Gumnut sets PC to 1
- `reti` instruction
 - Restores PC, Z, and C from special registers, re-enables interrupts

Interrupt Acknowledgment

- Process may not respond immediately
 - But must tell controller when it does
 - Controller then deactivates request
 - To avoid multiple interrupts for one event
- Processor *acknowledges* the request
 - E.g., `int_ack` signal on Gumnut
 - Alternative: reading a status register

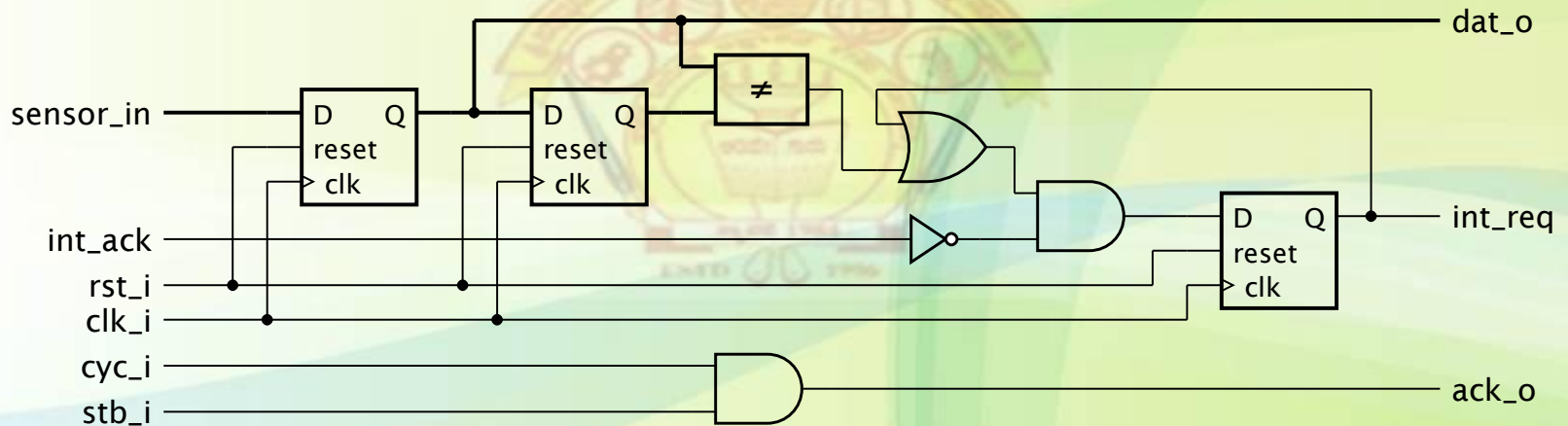Example: Sensor Controller

- 8-bit input from sensor
 - Interrupt request on change of value



Example: Sensor Handler

```
saved_r1:    data
             bss      1
             text
sensor_data: equ      0      ; address of sensor data
             ; input register


             org      1
             stm      r1, saved_r1
             inp      r1, sensor_data
             ...      ; process the data
             ldm      r1, saved_r1
             reti
```

Timers

- Real-time clock (RTC)
 - Generates periodic interrupts
 - Uses a counter to divide system clock
 - Control register for divisor
- Interrupt handler can perform periodic tasks
 - E.g., activate next digit of a scanned display

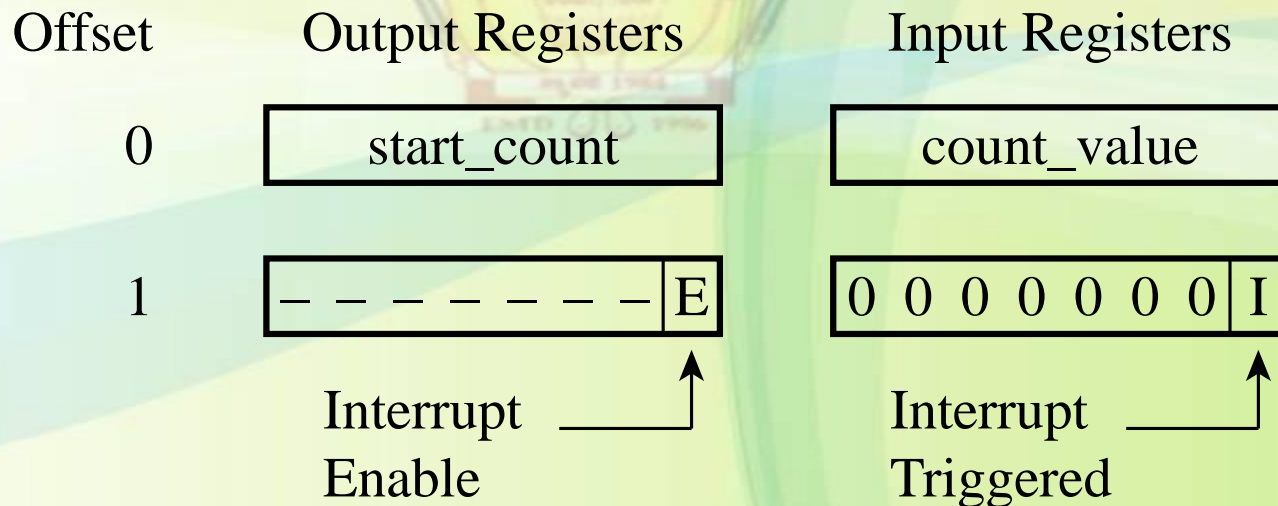Example: RTC for Gumnut

- 10 μ s timebase, divided by a down counter
 - Initial count loaded from a register
 - Interrupt triggered on count value = 0



Real-Time Executives

- Control program
 - A.k.a. real-time operating system (RTOS)
 - Timing based on a real-time clock
 - Schedules execution of tasks
 - In response to interrupts and timer events
- Can also manage other resources
 - Memory allocation
 - Storage (file system)
 - Use of I/O controllers
 - Use of accelerators

Example: Gumnut Executive

- RTC based at address 16
- Calls task_2ms every 2ms

```
;;; -----  
;;; Program reset: jump to main program  
                text  
                org    0  
                jmp    main  
;;; -----  
;;; Port addresses  
rtc_start_count:    equ    16 ; data output register  
rtc_count_value:   equ    16 ; data input register  
rtc_int_enable:    equ    17 ; control output register  
rtc_int_status:    equ    17 ; status input register
```

Example: Gumnut Executive

```
;;; -----  
;;; init_interrupts:    Initialize 2ms periodic interrupt, etc.  
                        data  
rtc_divisor:           equ    199        ; divide 100kHz down  
                        ; to 500Hz  
rtc_int_flag:         bss    1  
  
                        text  
init_interrupts:      add    r1, r0, rtc_divisor  
                        out   r1, rtc_start_count  
                        add   r1, r0, 1  
                        out   r1, rtc_int_enable  
                        stm   r0, rtc_int_flag  
                        ...    ; other initializations  
                        ret
```


Example: Gumnut Executive

```
;;; -----  
;;; Interrupt handler  
  
int_r1:          data  
                bss      1 ; save location for  
                    ; handler registers  
  
                text  
                org      1  
  
int_handler:    stm      r1, int_r1      ; save registers  
check_rtc:     inp      r1, rtc_status ; check for  
                    ; RTC interrupt  
  
                sub     r0, r1, 0  
                bz      check_next  
                add     r1, r0, 1  
                stm     r1, rtc_int_flag ; tell main  
                    ; program  
  
check_next:    ...  
  
int_end:       ldm      r1, int_r1 ; restore registers  
                reti
```

Example: Gumnut Executive

```
;;; -----  
;;; main program  
  
main:      text  
          jsb      init_interrupts  
          enai  
main_loop: stby  
          ldm      r1, rtc_int_flag  
          sub      r0, r1, 1  
          bnz     main_next  
          jsb     task_2ms  
          stm     r0, rtc_int_flag  
main_next: ...  
          jmp     main_loop
```

- Note: task_2ms not called as part of interrupt handler
 - Would slow down response to other interrupts

Summary

- Transducers: sensors and actuators
 - Analog-to-digital and digital-to-analog converters
- Input and output devices
- Controllers
 - Input, output, control, and status registers
 - Autonomous controllers
- Buses: multiplexed, tristate, open-drain
 - Bus protocols: signals, timing, operations

Summary

- **Serial transmission**
 - NRZ, embedded clock
- **Real-time software**
 - Reacting to I/O and timer events
 - Polling, interrupts
- **Real-time executives**

Queries?

